

# Chapter 2

## RTL Design with VHDL

# RTL Design with VHDL

## 2.1 Basic Structures of VHDL

- 2.1.1 Entities and Architectures
- 2.1.2 Entity-Architecture Outline
- 2.1.3 Entity Ports
- 2.1.4 Signals and Variables
- 2.1.5 Logic Value System
- 2.1.6 Resolutions

## 2.2 Combinational Circuits

- 2.2.1 Gate Level Combinational Circuits
- 2.2.2 Gate Level Synthesis
- 2.2.3 Descriptions by Use of Equations
- 2.2.4 Instantiating Other Modules
- 2.2.5 Synthesis of Assignment Statements
- 2.2.6 Descriptions with Sequential Flow
- 2.2.7 Combinational Rules

# RTL Design with VHDL

2.2.8 Bussing

2.2.9 Synthesizing Procedural Blocks

## 2.3 Sequential Circuits

2.3.1 Basic Memory Elements at the Gate Level

2.3.2 Memory Elements Using Procedural Statements

2.3.3 Flip-flop Synthesis

2.3.4 Registers, Shifters and Counters

2.3.5 Synthesis of Shifters and Counters

2.3.6 State Machine Coding

2.3.7 State Machine Synthesis

2.3.8 Memories

## 2.4 Writing Testbenches

## 2.5 Synthesis Issues

February 2019

VHDL: Modular Design and  
Synthesis of Cores and Systems  
Copyright Z. Navabi, 2007

# RTL Design with VHDL

## 2.6 VHDL Essential Terminologies

2.6.1 Design

2.6.2 Analysis

2.6.3 Library

2.6.4 Standard Packages

2.6.5 Elaboration

2.6.6 Event Driven Simulation

2.6.7 Concurrency

2.6.8 Concurrent Bodies

2.6.9 Sequentiality

2.6.10 Sequential Bodies

2.6.11 VHDL Objects and Classes

2.6.12 Real Time

2.6.13 Delta Delay

2.6.14 Scheduling


2.6.15 Resolution

2.6.16 Code Formal

## 2.7 Summary


VHDL: Modular Design and  
Synthesis of Cores and Systems  
Copyright Z. Navabi, 2007

# Basic Structures of VHDL

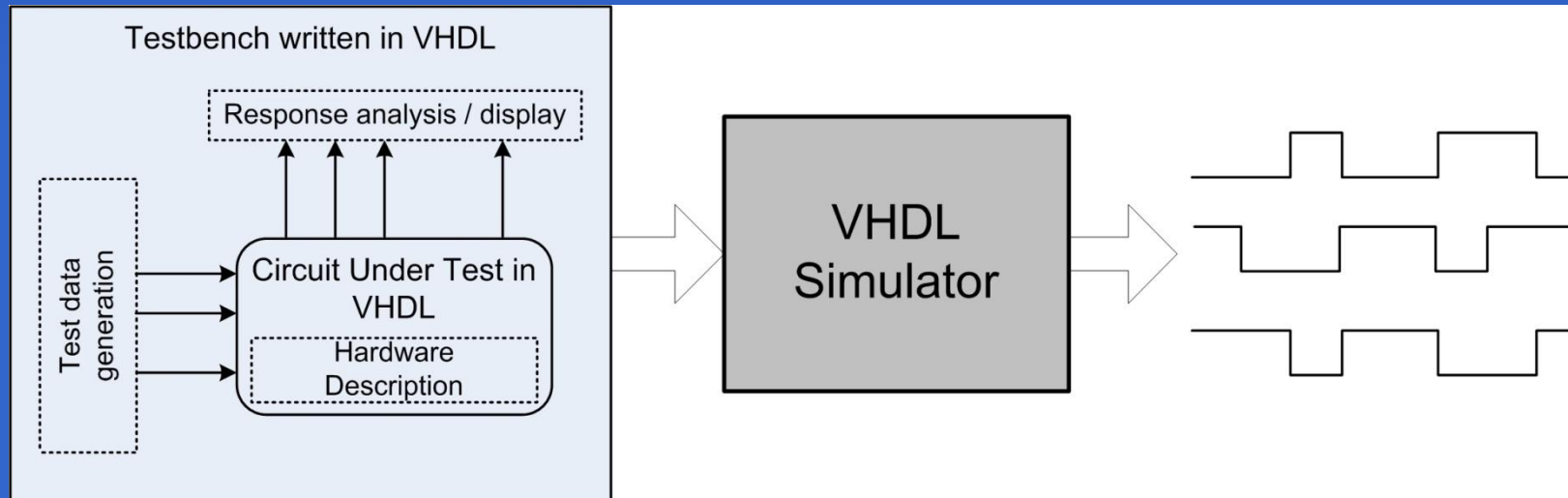


- **Simulation in VHDL**

# Basic Structures of VHDL

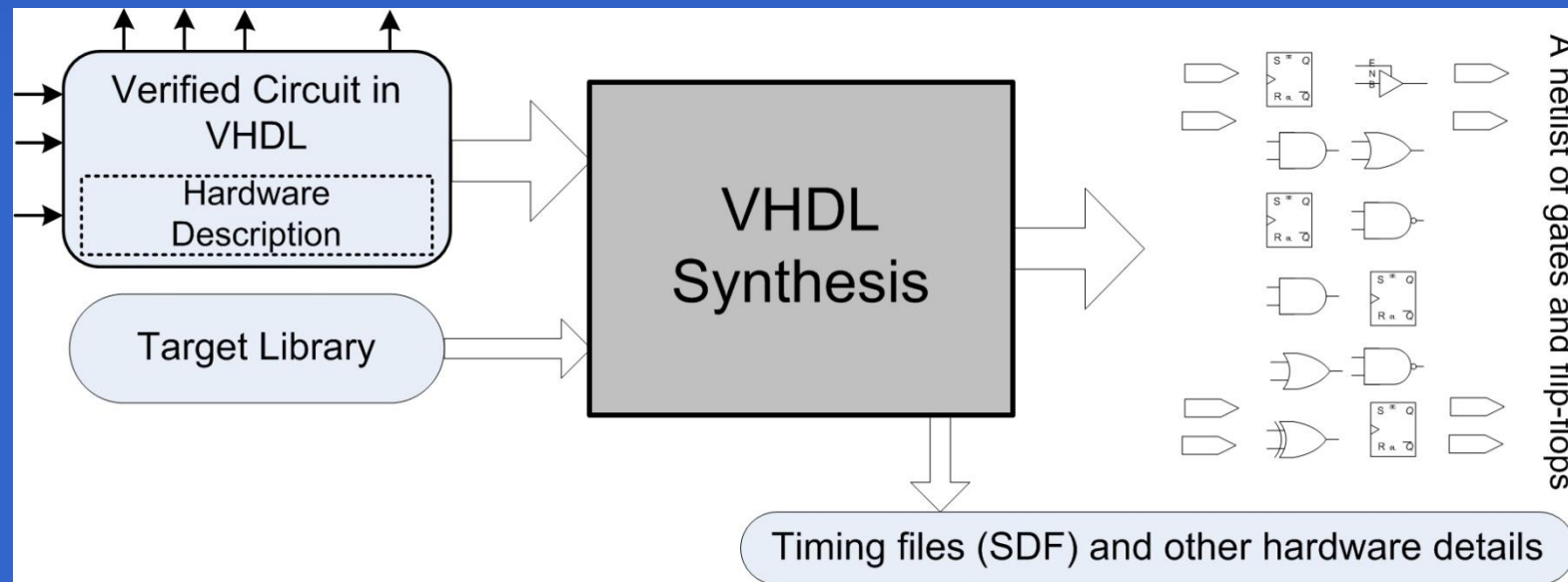

## ■ Synthesis of a VHDL Design

# Basic Structures of VHDL

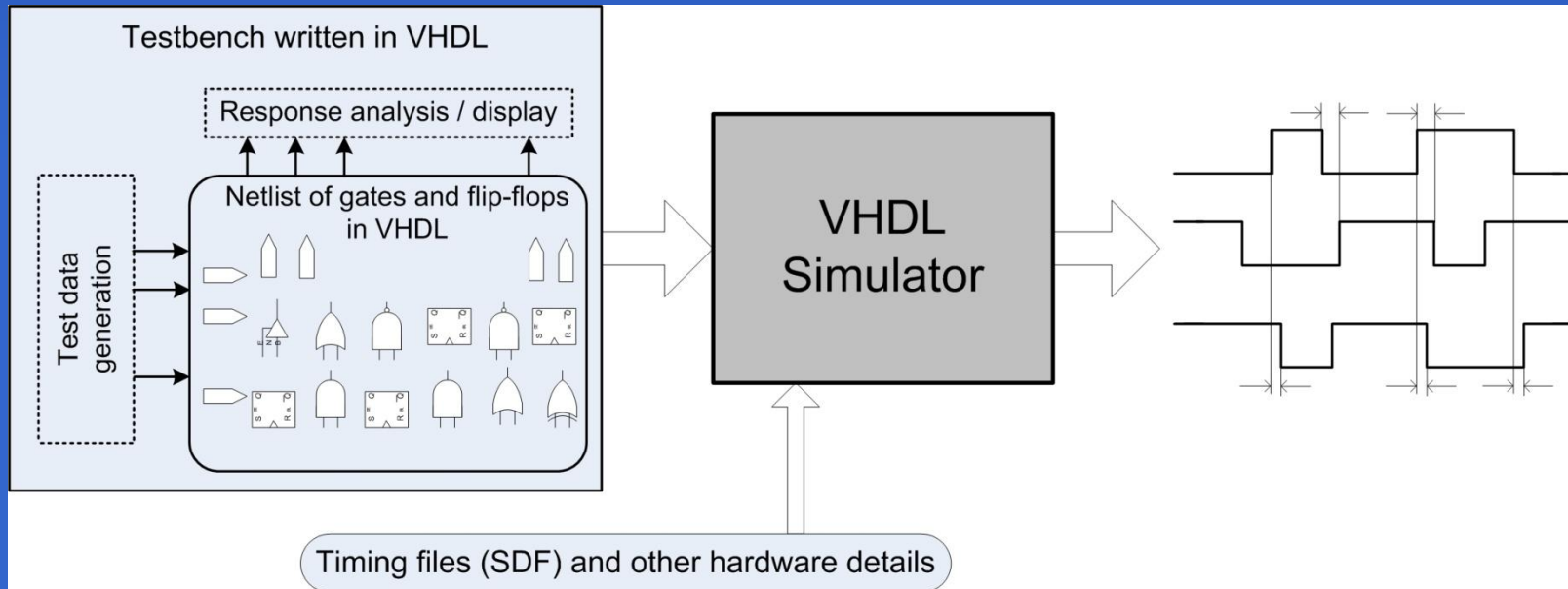


## ■ Post-synthesis Simulation in VHDL

# Entities and Architectures

```
ENTITY entity_name IS
    input and output ports
END ENTITY entity_name;
ARCHITECTURE identifier OF entity_name IS
    declarative part
BEGIN
    statement part
END ARCHITECTURE identifier;
```



# Entities and Architectures

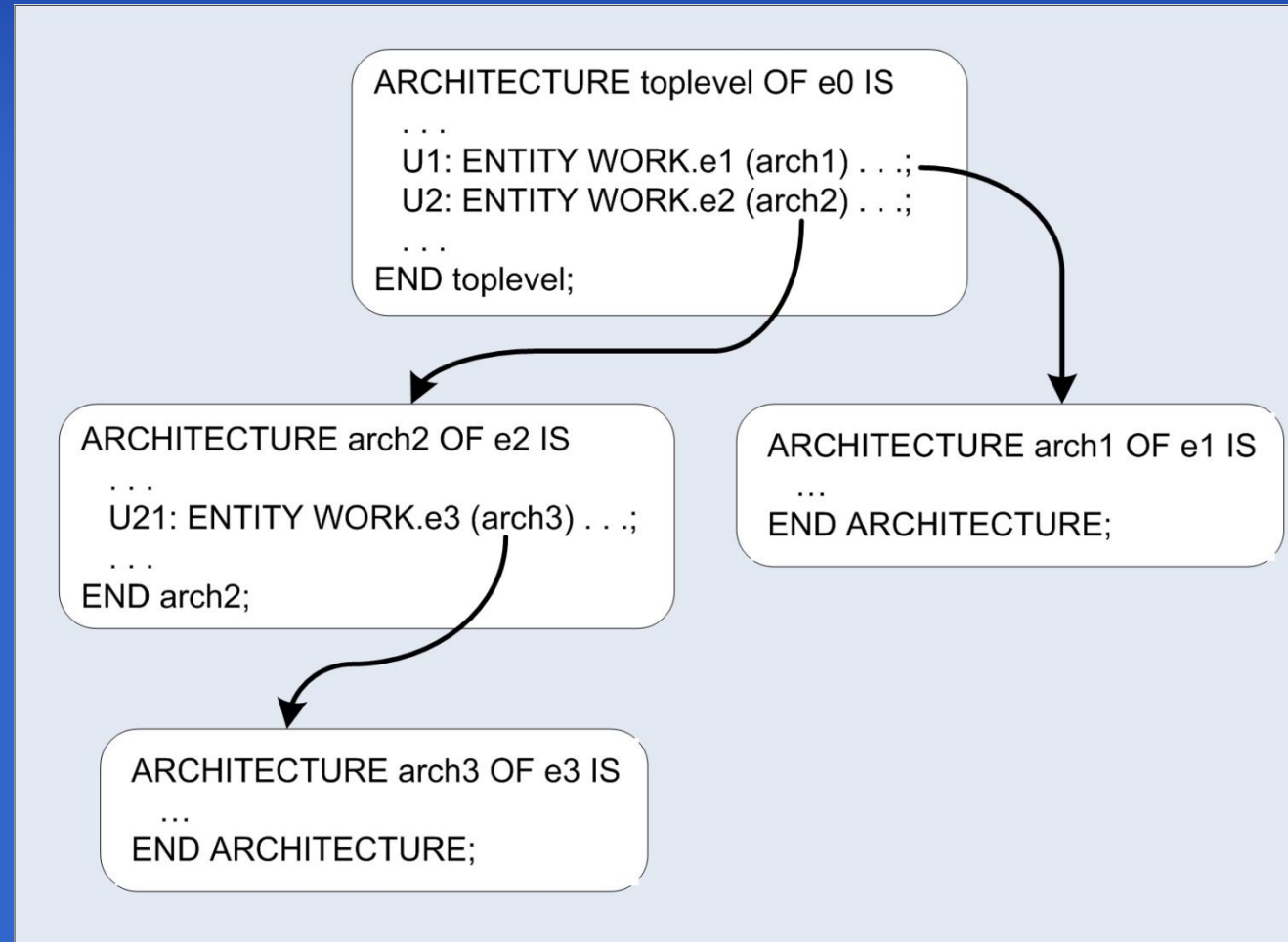

# Entity-Architecture Outline

```
ENTITY entity1 IS PORT (i1, i2 : IN BIT; w1 : OUT
BIT);
END ENTITY entity1;
ARCHITECTURE simple1 OF entity1 IS
    SIGNAL s1 : BIT;
BEGIN
    statement1;
    statement2;
    statement3;
END ARCHITECTURE simple1;
```

# Entity-Architecture Outline

```
ENTITY simple IS PORT (i1, i2, i3 : IN BIT; w1, w2 : OUT BIT); END ENTITY simple;
```

```
ARCHITECTURE simple_1a OF simple IS  
  SIGNAL c1 : BIT;  
BEGIN  
  U1: ENTITY WORK.nor2 PORT MAP (i1, i2, c1);  
  U2: ENTITY WORK.and2 PORT MAP (c1, i3, w1);  
  U3: ENTITY WORK.xor2 PORT MAP (c1, i3, w2);  
END ARCHITECTURE simple_1a;
```

```
ARCHITECTURE simple_1b OF simple IS  
BEGIN  
  w1 <= (i1 NOR i2) AND i3;  
  w2 <= (i1 NOR i2) XOR i3;  
END ARCHITECTURE simple_1b;
```

```
ARCHITECTURE simple_1c OF simple IS  
BEGIN  
  PROCESS (i1, i2, i3)  
    VARIABLE c1 : BIT;  
  BEGIN  
    c1 := i1 NOR i2;  
    IF (c1 = '1') THEN w1 <= i3; ELSE w1 <= '0';  
    IF (c1 = i3 ) THEN w2 <= '0'; ELSE w2 <= '1';  
  END PROCESS;  
END ARCHITECTURE simple_1c;
```

## Architecture Definition Alternatives

VHDL: Modular Design and  
Synthesis of Cores and Systems  
Copyright Z. Navabi, 2007

# Entity Ports

```
ENTITY aCircuit IS
  PORT (a, b : IN BIT;
        c : INOUT BIT;
        av, bv : IN BIT_VECTOR (7 DOWNTO 0);
        cv : INOUT BIT_VECTOR (7 DOWNTO 0);
        w : OUT BIT;
        wv : OUT BIT_VECTOR (7 DOWNTO 0));
END ENTITY aCircuit;
```

# Signals and Variables

```
ARCHITECTURE two_processes OF aCircuit IS
    SIGNAL d : BIT;
    SIGNAL dv : BIT_VECTOR (7 DOWNTO 0);
BEGIN
    p1: PROCESS (a, b, cv)
        VARIABLE e : BIT;
        VARIABLE ev : BIT_VECTOR (7 DOWNTO 0);
    BEGIN
        -- Can see all of aCircuit, plus d, dv, e, and ev.
        . . .
    END PROCESS;
    p2: PROCESS (av, bv, c)
        VARIABLE f : BIT;
        VARIABLE fv : BIT_VECTOR (7 DOWNTO 0);
    BEGIN
        -- Can see all of aCircuit, plus d, dv, f, and fv.
        . . .
    END PROCESS;
END ARCHITECTURE two_processes;
```

- **Signal and Variable Declaration**

VHDL: Modular Design and  
Synthesis of Cores and Systems  
Copyright Z. Navabi, 2007

# Data Part

```
ARCHITECTURE four_assignments OF aCircuit IS
    SIGNAL d : BIT;
    SIGNAL iv, jv, kv : BIT_VECTOR (7 DOWNTO 0);
BEGIN
    iv <= av AND cv;
    jv <= bv AND cv;
    kv <= av NOR bv;
    wv <= iv XOR jv WHEN c = '1' ELSE iv NAND kv;
END ARCHITECTURE four_assignments;
```

- Using Signals

# Data Part

```
ARCHITECTURE mixed_processes_assignments OF aCircuit IS
    SIGNAL d : BIT;
    SIGNAL dv : BIT_VECTOR (7 DOWNTO 0);
BEGIN
    p1: PROCESS (a, b, cv)
        VARIABLE e : BIT;
        VARIABLE ev : BIT_VECTOR (7 DOWNTO 0);
    BEGIN
        IF (a = b) THEN ev := av; ELSE ev := bv;
        IF (a = '1') THEN wv <= av; ELSE wv <= "1000111";
        d <= e;
    END PROCESS;

    dv <= av XOR bv;
    w <= d AND a;
END ARCHITECTURE mixed_processes_assignments;
```

- Using Signals and Variables

# Data Part

```
ARCHITECTURE indexing_slicing OF aCircuit IS
    SIGNAL d : BIT;
    SIGNAL dv : BIT_VECTOR (7 DOWNTO 0);
BEGIN
    wv (3 DOWNTO 0) <= av (7 DOWNTO 4) AND
                                     cv (7 DOWNTO 4);

    w <= cv (4);
    cv (7) <= av (0);
END ARCHITECTURE indexing_slicing;
```

- Using Indexing and Slicing



# Logic Value System

<b>Value</b>	<b>Representing</b>
'U'	Uninitialized
'X'	Forcing Unknown
'0'	Forcing 0
'1'	Forcing 1
'Z'	High Impedance
'W'	Weak Unknown
'L'	Weak 0
'H'	Weak 1
'-'	Don't care

# Resolutions

```
LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
ENTITY selector IS
    PORT (av, bv: IN std_logic_vector (7 DOWNTO 0),
          as, bs: IN std_logic;
          yv: OUT std_logic_vector (7 DOWNTO 0));
END ENTITY selector;
ARCHITECTURE multiple_drivers OF selector IS
BEGIN
    yv <= av WHEN as = '1' ELSE "ZZZZZZZZ";
    yv <= bv WHEN bs = '1' ELSE "ZZZZZZZZ";
END ARCHITECTURE multiple_drivers;
```

- Multiple Assignments to a Resolved Signal

# Resolutions

U	U	X	0	1	Z
U	U	U	U	U	U
X	U	X	X	X	X
0	U	X	0	X	0
1	U	X	X	1	1
Z	U	X	0	1	Z

- *Partial std\_logic resolved* Function

# Gate Level Combinational Circuits

```
ENTITY AND2 IS PORT (i1, i2 : IN std_logic; o1: OUT std_logic);
END ENTITY AND2;

ARCHITECTURE example OF AND2 IS
BEGIN
    o1 <= i1 AND i2 AFTER 3 NS;
END example;

ENTITY OR3 IS PORT (i1, i2, i3 : IN std_logic; o1: OUT std_logic);
END ENTITY OR3;

ARCHITECTURE example OF OR3 IS
BEGIN
    o1 <= i1 OR i2 OR i3 AFTER 6 NS;
END example;

ENTITY BUFIF1 IS PORT (i1, en : IN std_logic; o1: OUT std_logic);
END ENTITY BUFIF1;


ARCHITECTURE example OF BUFIF1 IS
BEGIN
    o1 <= i1 AFTER 4 NS WHEN en = '1' ELSE 'Z' AFTER 3 NS;
END example;

ENTITY BUFIF0 IS PORT (i1, en : IN std_logic; o1: OUT std_logic);
END ENTITY BUFIF0;

ARCHITECTURE example OF BUFIF0 IS
BEGIN
    o1 <= i1 AFTER 4 NS WHEN en = '0' ELSE 'Z' AFTER 3 NS;
END example;
```

- Basic Primitives Described in VHDL

# Majority Example

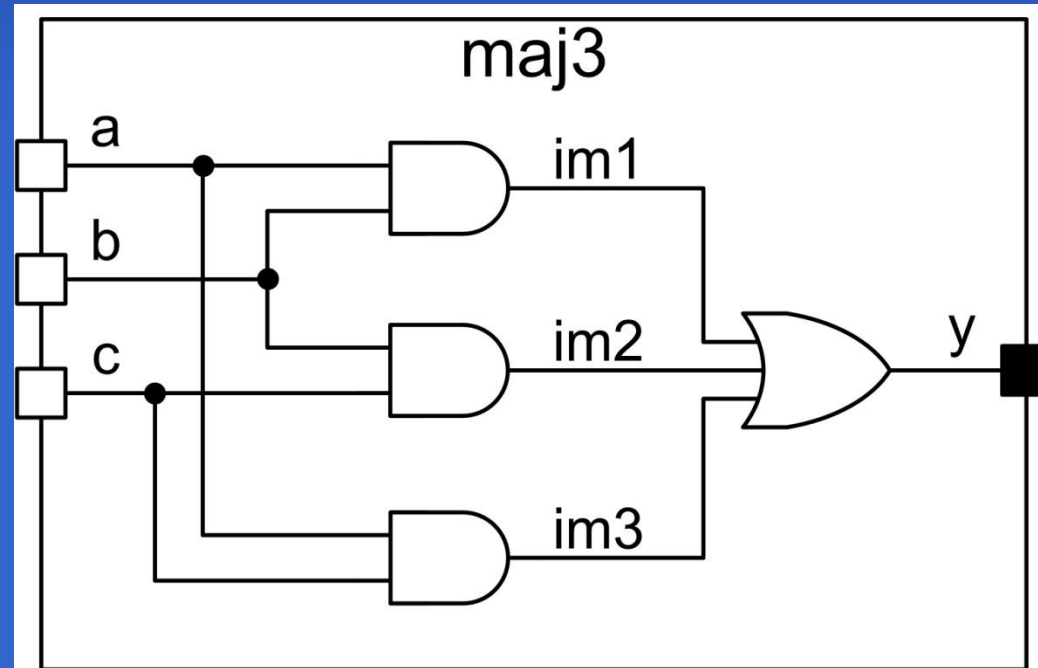


- A Majority Circuit

# Majority Example

```
LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
ENTITY maj3 IS
    PORT (a, b, c : IN std_logic;      y : OUT
          std_logic);
END maj3;

ARCHITECTURE gate_level OF maj3 IS
    SIGNAL im1, im2, im3 : std_logic;
BEGIN
    ANDa: ENTITY WORK.AND2 PORT MAP (a, b, im1);
    ANDb: ENTITY WORK.AND2 PORT MAP (b, c, im2);
    ANDc: ENTITY WORK.AND2 PORT MAP (a, c, im3);
    ORa : ENTITY WORK.OR3  PORT MAP (im1, im2, im3, y);
END ARCHITECTURE gate_level;
```

# Multiplexer Example

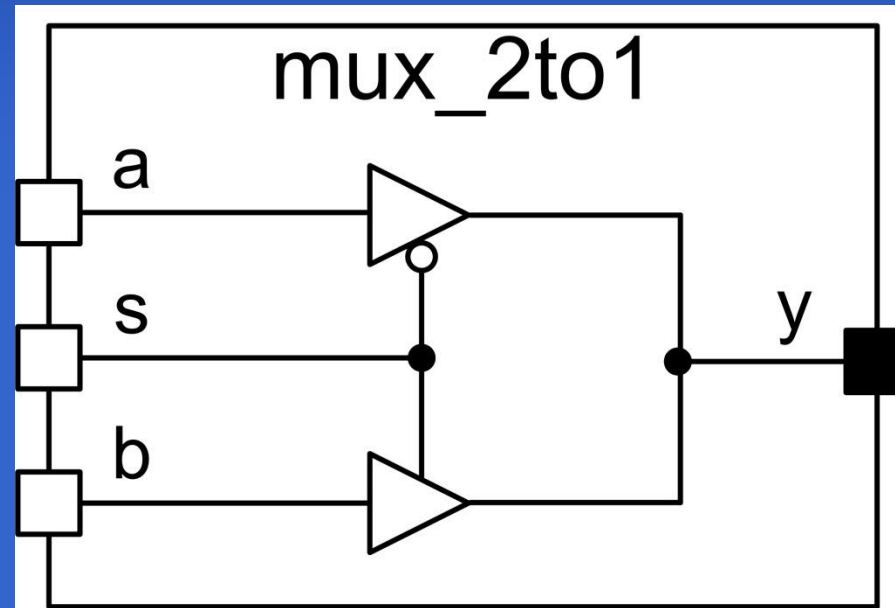


- Multiplexer Using Three-state Gates

# Multiplexer Example

```
ENTITY mux_2to1 IS
    PORT (a, b, s: IN std_logic; y: OUT std_logic);
END ENTITY mux_2to1;
ARCHITECTURE gate_level OF mux_2to1 IS BEGIN
    BUFIF1a: ENTITY WORK.BUFIF1(example) PORT MAP (b, s, y);
    BUFIF1b: ENTITY WORK.BUFIF0(example) PORT MAP (a, s, y);
END ARCHITECTURE gate_level;
```




# Gate Level Synthesis

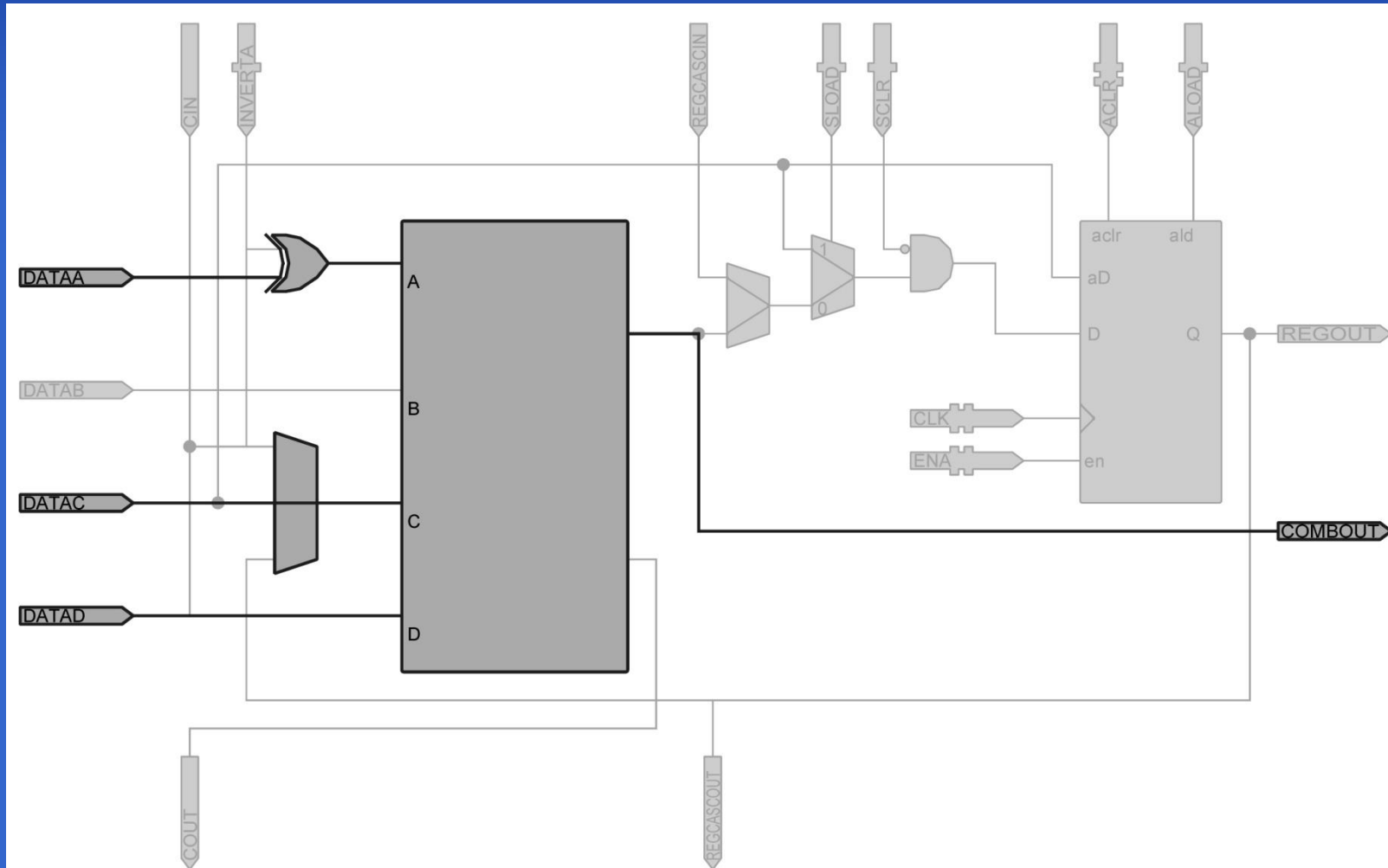

VHDL: Modular Design and  
Synthesis of Cores and Systems  
Copyright Z. Navabi, 2007

# Gate Level Synthesis

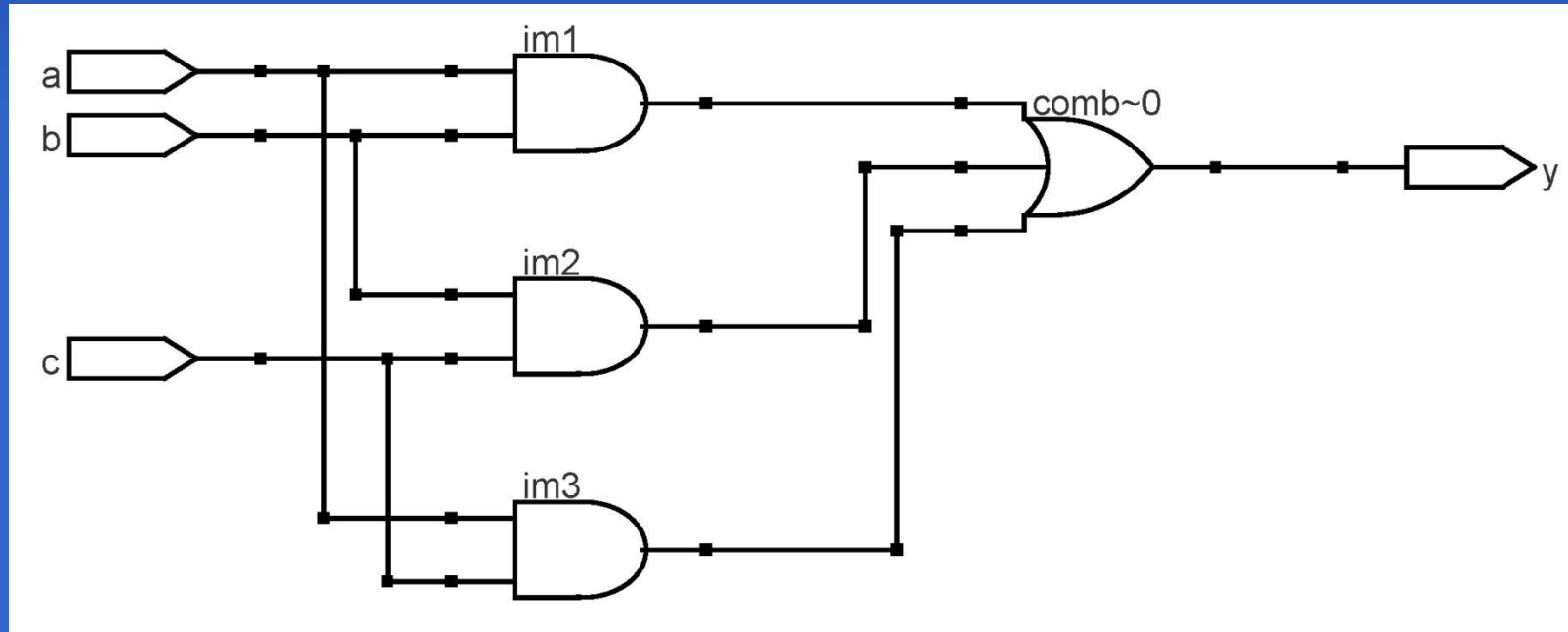

- RTL (logical) View of Synthesized *maj3*

# Descriptions by Use of Equations

<b>Boolean Operators</b>	<b>NOT</b>	<b>AND</b>	<b>OR</b>	<b>NAND</b>	<b>NOR</b>	<b>XOR</b>	<b>XNOR</b>	
<b>Comparison Operators</b>	<b>=</b>	<b>/=</b>	<b>&lt;</b>	<b>&lt;=</b>	<b>&gt;</b>	<b>&gt;=</b>		
<b>Arithmetic Operators</b>	<b>+</b>	<b>-</b>	<b>ABS</b>	<b>MOD</b>	<b>REM</b>	<b>*</b>	<b>/</b>	<b>**</b>
<b>Concat. Operators</b>	<b>&amp;</b>							

- **VHDL Operators**

# XOR Example

```
ENTITY xor2 IS
    PORT (i1, i2: IN std_logic; o1: OUT std_logic);
END ENTITY xor2;
--
ARCHITECTURE expression OF xor2 IS
BEGIN
    o1 <= i1 XOR i2 AFTER 3 NS;
END ARCHITECTURE expression;
```

# Full-Adder Example

```
ENTITY full_adder IS
    PORT (a, b, cin : IN std_logic;
          sum, cout : OUT std_logic);
END ENTITY full_adder;
--
ARCHITECTURE expression OF full_adder IS
BEGIN
    sum <= a XOR b XOR cin AFTER 0.3 NS;
    cout <= (a AND b) OR (a AND cin) OR (b AND cin) AFTER 0.2
NS;
END ARCHITECTURE expression;
```

- Assign Statement and Boolean

# Comparator Example

```
ENTITY comp_4bit IS PORT (  
  in1, in2 : IN std_logic_vector (3 DOWNTO 0);  
  eq       : OUT std_logic );  
END comp_4bit;  
  
ARCHITECTURE functional OF comp_4bit IS  
  SIGNAL im : std_logic_vector (3 DOWNTO 0);  
  FUNCTION nor_reduce  
    (in1: IN std_logic_vector (3 DOWNTO 0))  
    RETURN std_logic  
  IS  
    VARIABLE result : std_logic ;  
  BEGIN  
    result:= NOT (in1(3) OR in1(2) OR in1(1) OR  
in1(0)) ;  
    RETURN result;  
  END;  
  BEGIN  
    im <= in1 XOR in2;  
    eq <= nor_reduce(im);  
  END functional;
```

# Multiplexer Example

```
ENTITY multiplexer IS
    PORT (a, b : IN std_logic_vector; s : IN
std_logic;
        w : OUT std_logic_vector);
END ENTITY;
ARCHITECTURE expression OF multiplexer IS
BEGIN
    w <= a WHEN s = '0' ELSE b;
END ARCHITECTURE expression;
```

- An Unconstrained 2-to-1 Mux using Condition Operator

# Decoder Example

```
ENTITY dcd2to4 IS
    PORT (sel: IN std_logic_vector (1 DOWNTO 0);
          y: OUT std_logic_vector (3 DOWNTO 0) );
END dcd2to4;
ARCHITECTURE structural OF dcd2to4 IS
BEGIN
    WITH sel SELECT
        y <= "0001" WHEN "00",
            "0010" WHEN "01",
            "0100" WHEN "10",
            "1000" WHEN "11",
            "0000" WHEN OTHERS;
END ARCHITECTURE structural;
```



# Adder Example

```
LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
USE IEEE.std_logic_unsigned.ALL;
ENTITY adder8 IS PORT (
    a      : IN  std_logic_vector (7 DOWNTO 0);
    b      : IN  std_logic_vector (7 DOWNTO 0);
    ci     : IN  std_logic;
    s      : OUT std_logic_vector (7 DOWNTO 0);
    co     : OUT std_logic);
END ENTITY adder8;
--
ARCHITECTURE equation OF adder8 IS
    SIGNAL mid : std_logic_vector (8 DOWNTO 0);
BEGIN
    mid <= ('0'&a) + ('0'&b) + ci;
    co <= mid (8);
    s  <= mid (7 DOWNTO 0);
END equation;
```

- Adder with Carry-in and Carry-out

# ALU Example

```
ENTITY alu8 IS PORT (  
    a, b      : IN  std_logic_vector (7 DOWNT0 0);  
    addsub    : IN  std_logic;  
    gt, zero, co : OUT std_logic;  
    r         : OUT std_logic_vector (7 DOWNT0 0));  
END ENTITY alu8;  
ARCHITECTURE assigns OF alu8 IS  
    SIGNAL mid : std_logic_vector (8 DOWNT0 0);  
BEGIN  
    mid <= ('0' & a) + ('0' & b) WHEN addsub = '1' ELSE ('0' & a)  
- ('0' & b);  
    co <= mid (8);  
    r  <= mid (7 DOWNT0 0);  
    gt <= '1' WHEN a > b ELSE '0';  
    zero <= '1' WHEN mid (7 DOWNT0 0) = "00000000" ELSE '0';  
END assigns;
```


# ALU Example Using Adder

```
ENTITY alu8add IS PORT (  
  a, b : IN std_logic_vector (7 DOWNT0 0);  
  gt, zero, co : OUT std_logic;  
  r : OUT std_logic_vector (7 DOWNT0 0));  
END ENTITY alu8add;  
ARCHITECTURE assigns OF alu8add IS  
  SIGNAL mid8 : std_logic_vector (7 DOWNT0 0);  
  SIGNAL mid1 : std_logic;  
BEGIN  
  AD: ENTITY WORK.adder8 PORT MAP (a, b, '0', mid8, OPEN);  
  -- AD: ENTITY WORK.adder8 PORT MAP  
  -- (a => a, b => b, ci => '0', s => mid8);  
  r <= mid8;  
  gt <= '1' WHEN a > b ELSE '0';  
  zero <= '1' WHEN mid8 = "00000000" ELSE '0';  
END assigns;
```

## ALU VHDL Code Using Instantiating an Adder


VHDL: Modular Design and  
Synthesis of Cores and Systems  
Copyright Z. Navabi, 2007

# Synthesis of Assignment Statements

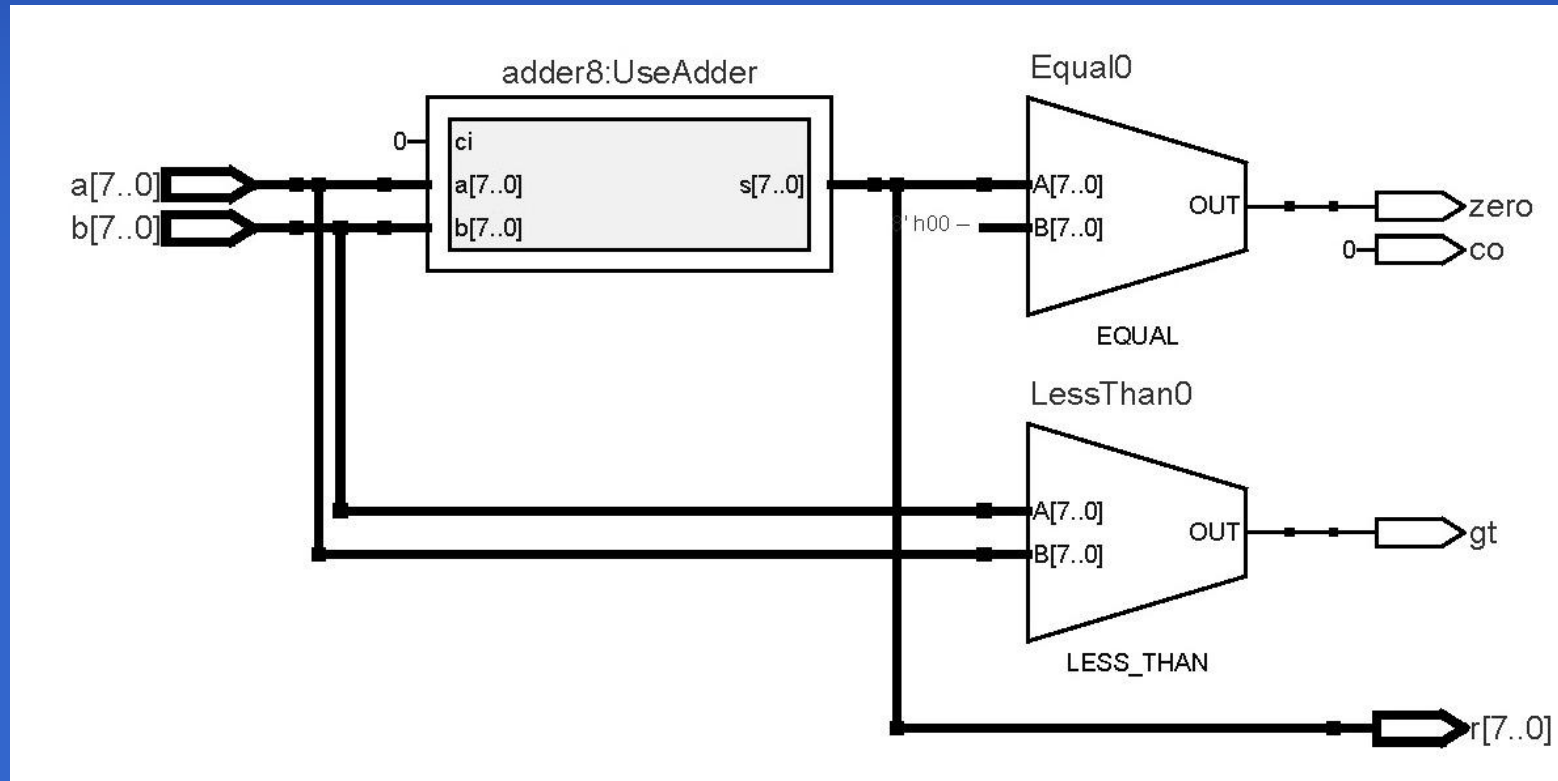

- *ALU\_Adder* RTL View after Synthesis

# Synthesis of Assignment Statements

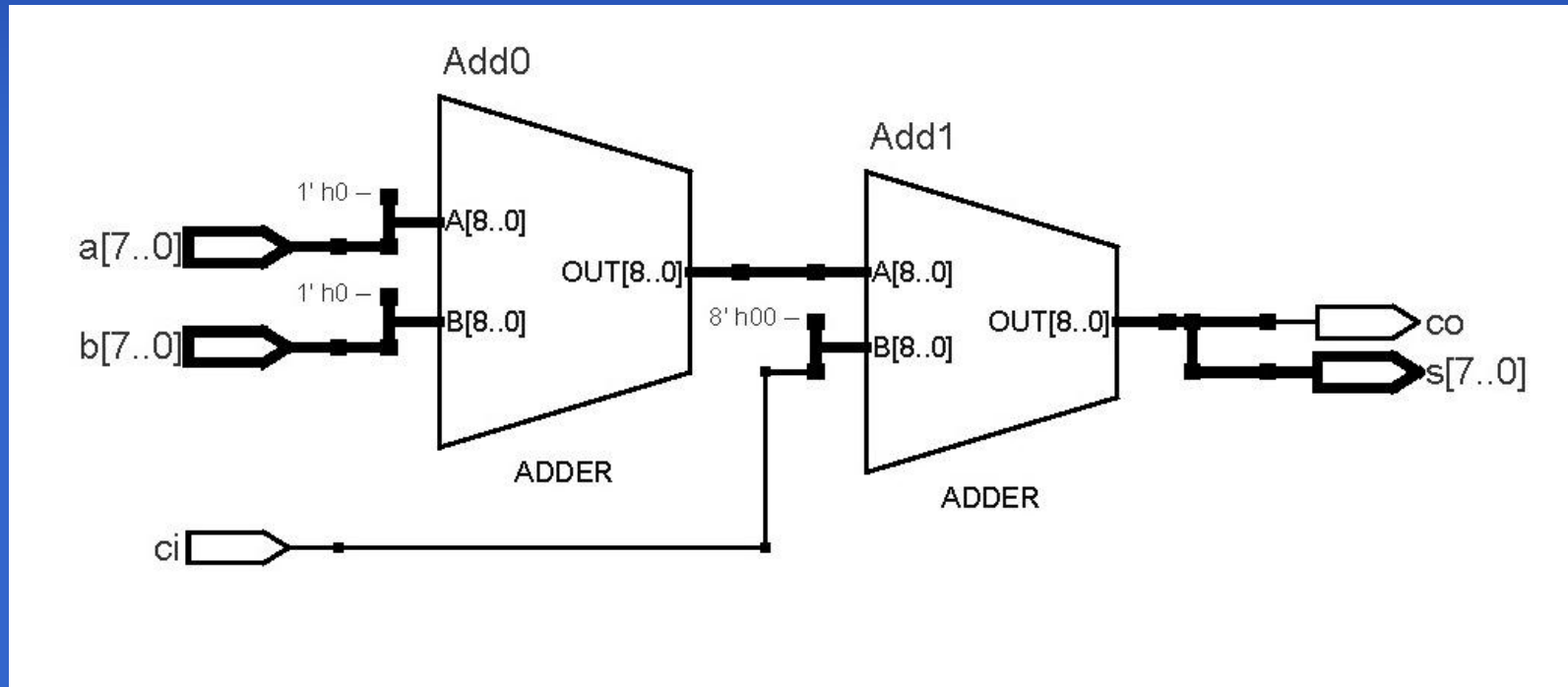

- *ALU\_Adder* RTL View after Synthesis

# Descriptions with Sequential Flow

```
ENTITY maj3 IS
    PORT (a, b, c : IN std_logic;
          y       : OUT std_logic);
END maj3;
ARCHITECTURE sequential OF maj3 IS
BEGIN
    PROCESS (a, b, c)
    BEGIN
        y <= (a AND b) OR (b AND c) OR (a AND c);
    END PROCESS;
END ARCHITECTURE sequential;
```

- Procedural Block Describing a Majority Circuit

# Majority Example with Delay

```
ARCHITECTURE sequential_delay OF maj3 IS
BEGIN
    PROCESS (a, b, c)
    BEGIN
        y <= (a AND b) OR (b AND c) OR (a AND c) AFTER 5
    NS;
    END PROCESS;
END ARCHITECTURE sequential_delay;
```

# Procedural Multiplexer Example

```
ENTITY multiplexer IS
    PORT (a, b, s : IN BIT; w : OUT BIT);
END ENTITY;
--
ARCHITECTURE procedural OF multiplexer IS BEGIN
    PROCESS (a, b, s) BEGIN
        IF (s = '0') THEN w <= a;
        ELSE w <= b;
        END IF;
    END PROCESS;
END ARCHITECTURE procedural;
```

- Sequential Flow Multiplexer



# Procedural ALU Example


```
ENTITY alu8 IS
    PORT (left_i, right_i: IN std_logic_vector (7 DOWNTO 0);
          mode : IN std_logic_vector (1 DOWNTO 0);
          aluout : OUT std_logic_vector (7 DOWNTO 0));
END ENTITY;
--
ARCHITECTURE procedural OF alu8 IS BEGIN
    PROCESS (left_i, right_i, mode) BEGIN
        CASE mode IS
            WHEN "00" => aluout <= left_i + right_i;
            WHEN "01" => aluout <= left_i - right_i;
            WHEN "10" => aluout <= left_i AND right_i;
            WHEN "11" => aluout <= left_i OR right_i;
            WHEN OTHERS => aluout <= "XXXXXXXX";
        END CASE;
    END PROCESS;
END ARCHITECTURE procedural;
```

# Bussing

```
ENTITY bussing IS
  PORT (
    busin1: IN std_logic_vector (3 DOWNTO 0);
    busin2: IN std_logic_vector (3 DOWNTO 0);
    busin3: IN std_logic_vector (3 DOWNTO 0);
    en1: IN  std_logic;
    en2: IN  std_logic;
    en3: IN  std_logic;
    busout: OUT std_logic_vector(3 DOWNTO 0) );
END bussing;
--
ARCHITECTURE structural OF bussing IS
BEGIN
  busout <= busin1 WHEN en1 = '1' ELSE (OTHERS => 'Z');
  busout <= busin2 WHEN en2 = '1' ELSE (OTHERS => 'Z');
  busout <= busin3 WHEN en3 = '1' ELSE (OTHERS => 'Z');
END structural;
```


- Three-state Bussing

# Synthesizing Procedural Blocks

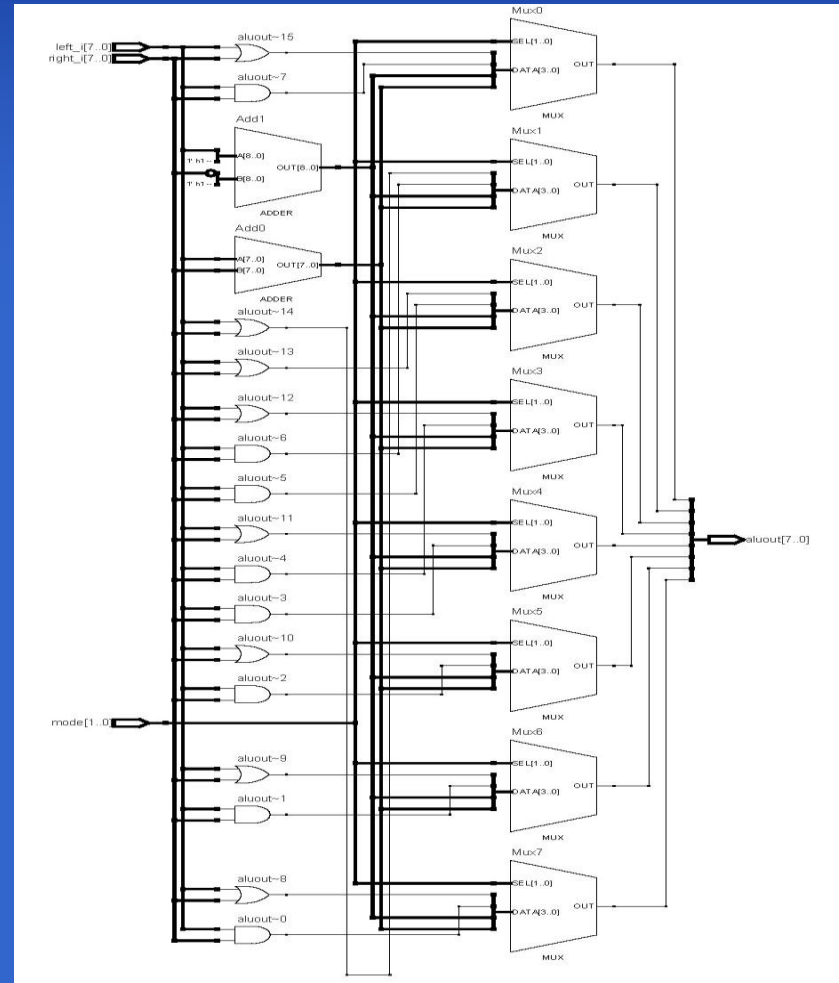

- Synthesis of Sequential Flow ALU
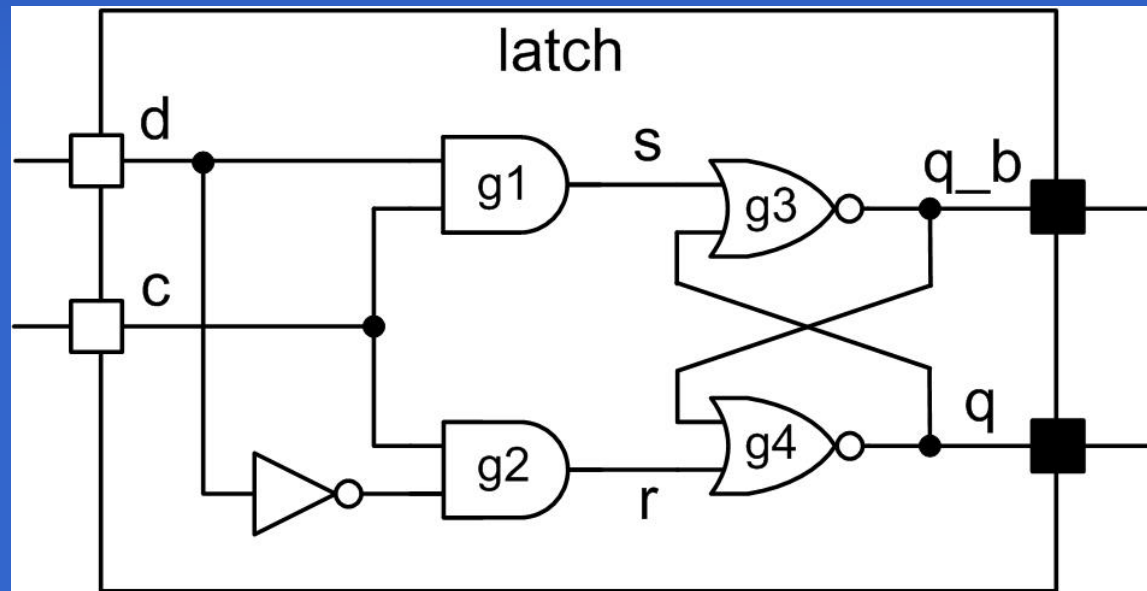
# Basic Memory Elements at the Gate Level



- Clocked D-latch

# Basic Memory Elements at the Gate Level

```
ENTITY latch IS
  PORT (d, c: IN std_logic;
        q, q_b : BUFFER std_logic);
END latch;
ARCHITECTURE structural OF latch IS
  SIGNAL s, r : std_logic;
BEGIN
  s   <= c AND d      AFTER 6 ns;
  r   <= c AND (NOT d) AFTER 6 ns;
  q_b <= s NOR q     AFTER 4 ns;
  q   <= r NOR q_b   AFTER 4 ns;
END structural;
```

- 37 VHDL Code for a Clocked D-latch

# Basic Memory Elements at the Gate Level

```
ENTITY master_slave IS
    PORT (d, c: IN std_logic;
          q : OUT std_logic);
END master_slave;
ARCHITECTURE dual OF master_slave IS
    SIGNAL qm : std_logic;
BEGIN
    qm <= d WHEN c = '1';
    q  <= qm WHEN c = '0';
END dual;
```

- Master-Slave Flip-Flop

# Memory Elements Using Procedural Statements

```
ENTITY latch1 IS
    PORT (d, c: IN std_logic; q: OUT std_logic);
END latch1;
ARCHITECTURE behavioral OF latch1 IS
BEGIN
    PROCESS (d, c)
    BEGIN
        IF c = '1' THEN
            q <= d;
        END IF;
    END PROCESS;
END ARCHITECTURE behavioral;
```

- **Procedural Latch**

# D Flip-Flop

```
ENTITY DFF1 IS
    PORT (d, clk: IN std_logic; q : OUT std_logic);
END DFF1;
--
ARCHITECTURE behavioral OF DFF1 IS
BEGIN
    PROCESS (clk)
    BEGIN
        IF clk = '1' AND clk'EVENT THEN
            q <= d;
        END IF;
    END PROCESS;
END ARCHITECTURE behavioral;
```


- A Positive-Edge D Flip-Flop



# Synchronous Control

```
ENTITY DFF1sr IS
    PORT (d, clk, s, r: IN std_logic; q : OUT std_logic);
END DFF1sr;
--
ARCHITECTURE behavioral OF DFF1sr IS
BEGIN
    PROCESS (clk)
    BEGIN
        IF clk = '1' AND clk'EVENT THEN
            IF s = '1' THEN
                q <= '1';
            ELSIF r = '1' THEN
                q <= '0';
            ELSE
                q <= d;
            END IF;
        END IF;
    END PROCESS;
END ARCHITECTURE behavioral;
```


# Synchronous Control

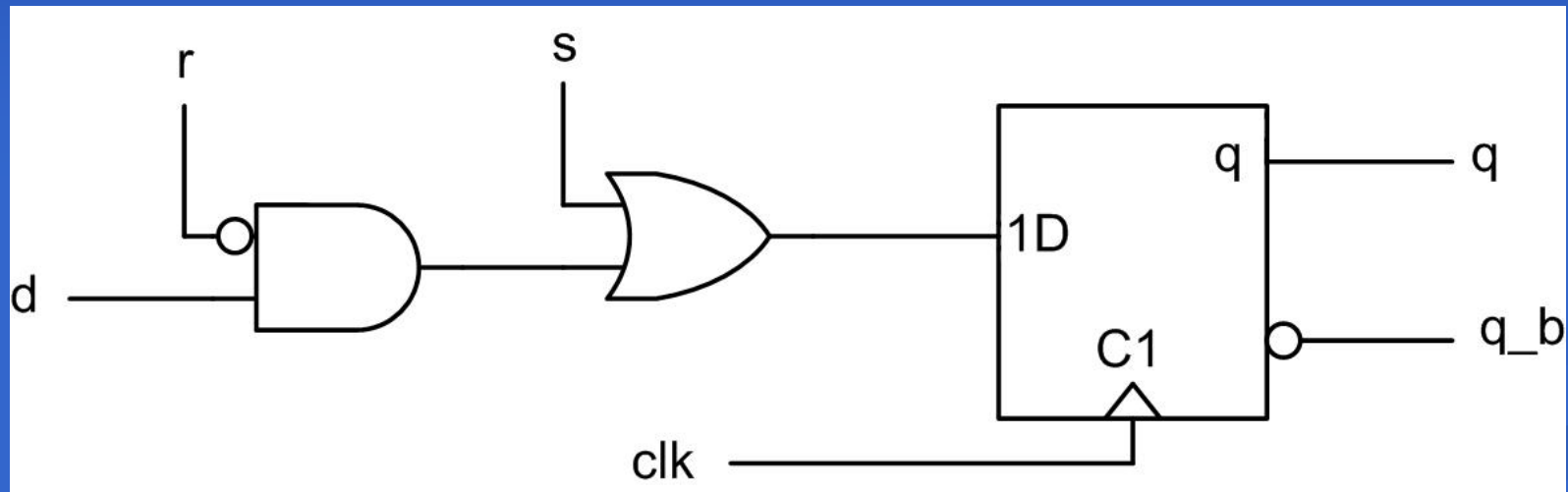


# Asynchronous Control

```
ARCHITECTURE asynchronous OF DFF1sr IS
BEGIN
  PROCESS (clk, s, r) BEGIN
    IF s = '1' THEN
      q <= '1';
    ELSIF r = '1' THEN
      q <= '0';
    ELSIF clk = '1' AND clk'EVENT THEN
      q <= d;
    END IF;
  END PROCESS;
END ARCHITECTURE asynchronous;
```

# Asynchronous Control

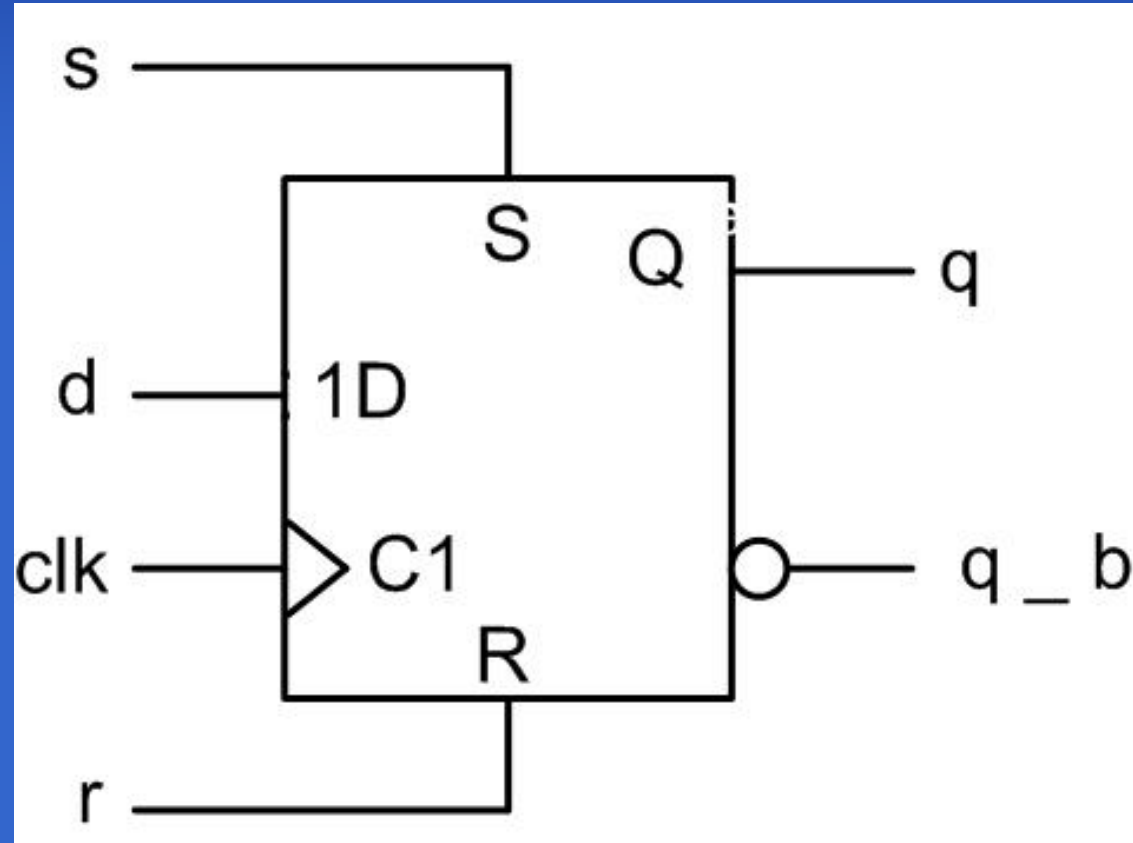


# Flip-flop Synthesis

 

- Synchronous Flip-Flop Synthesis

VHDL: Modular Design and  
Synthesis of Cores and Systems  
Copyright Z. Navabi, 2007


# Flip-flop Synthesis

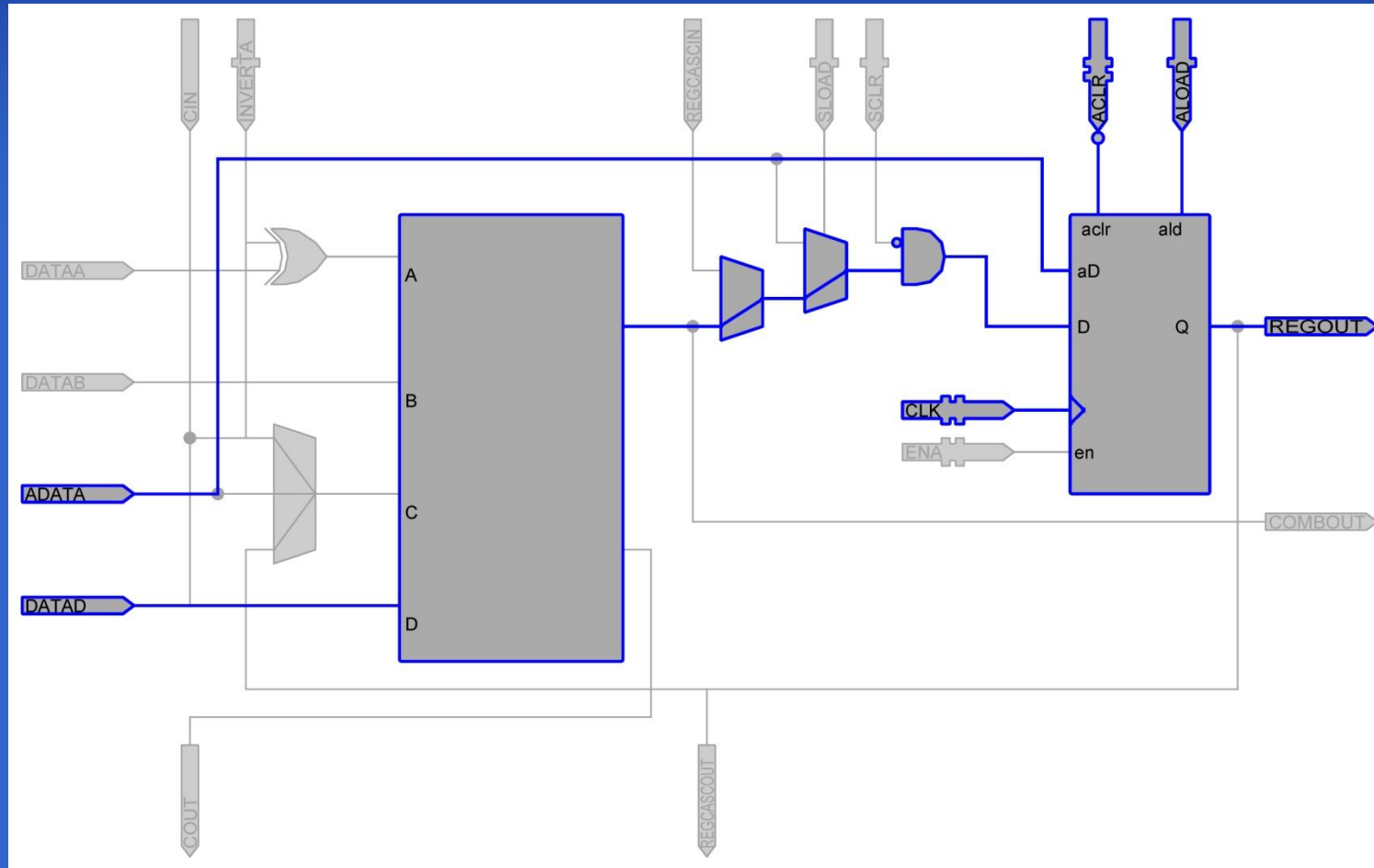


- **Asynchronous Flip-Flop Synthesis**

VHDL: Modular Design and  
Synthesis of Cores and Systems  
Copyright Z. Navabi, 2007

# Flip-flop Synthesis

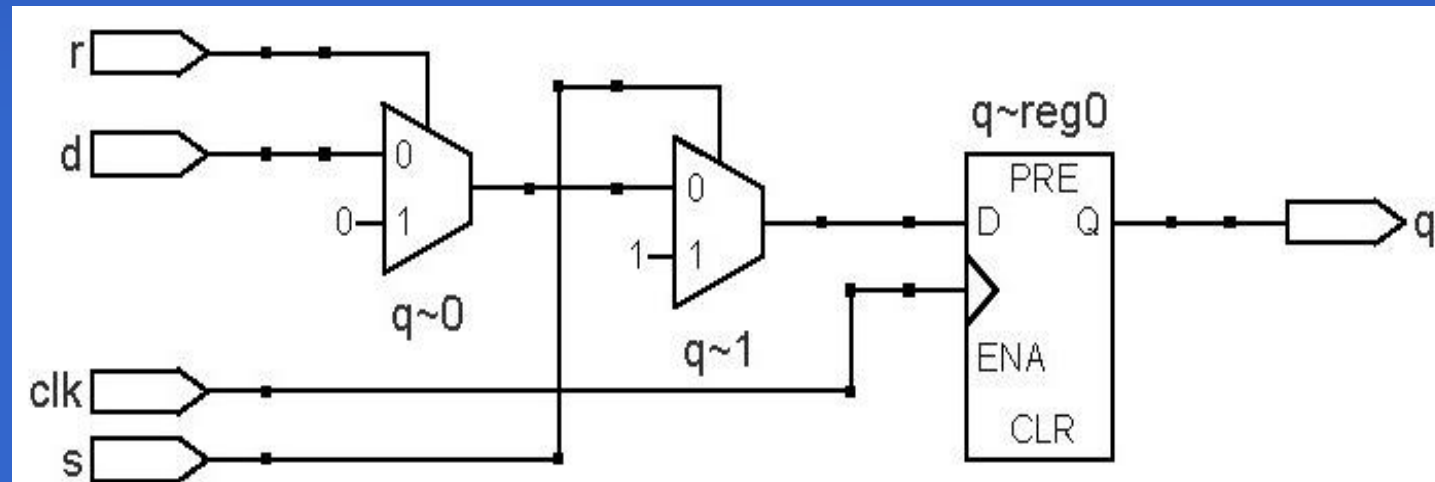

# Flip-flop Synthesis

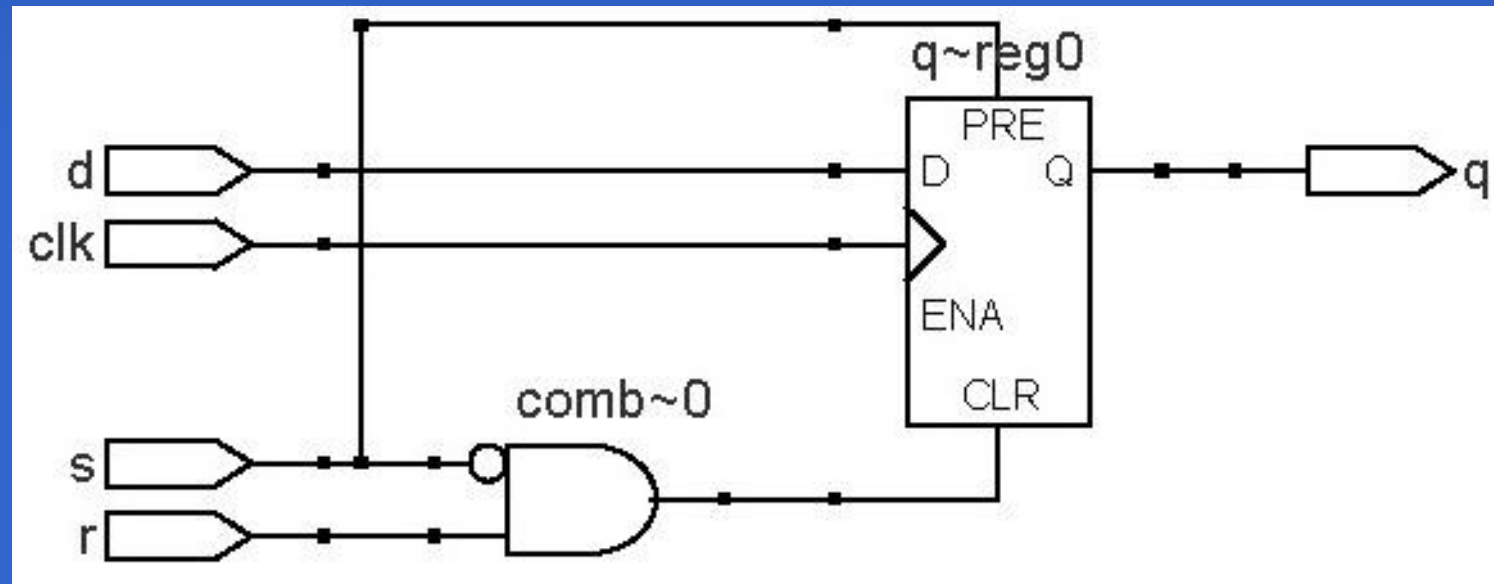



# Registers

```
ENTITY register8 IS
  PORT (
    : IN std_logic_vector (7 DOWNTO 0);           d
    : IN std_logic;           clk, s, r
    : OUT std_logic_vector ( 7 DOWNTO 0));       q
END register8;
--
ARCHITECTURE behavioral OF register8 IS
BEGIN
  PROCESS (clk)
  BEGIN
    IF clk = '1' AND clk'event THEN
      IF s= '1' THEN
        q <= (OTHERS => '1');
      ELSIF r = '1' THEN
        q <= (OTHERS => '0');
      ELSE
        q <= d;
      END IF;
    END IF;
  END PROCESS;
END behavioral;
```


# Shift-Registers

```
ENTITY shift_reg4 IS
  PORT (
    d      : IN std_logic_vector (3 DOWNTO 0);
    clk, ld, rst, l_r, s_in : IN std_logic;
    q      : OUT std_logic_vector (3 DOWNTO 0));
END shift_reg4;
ARCHITECTURE behavioral OF shift_reg4 IS
BEGIN
  PROCESS (clk)
    VARIABLE q_t: std_logic_vector (3 DOWNTO 0);
  BEGIN
    IF rising_edge (clk) THEN
      IF rst= '1' THEN
        q_t := (OTHERS => '0');
      ELSIF ld = '1' THEN
        q_t := d;
      ELSIF l_r = '1' THEN
        q_t := q_t (2 DOWNTO 0) & s_in ;
      ELSE
        q_t := s_in & q_t (3 DOWNTO 1);
      END IF;
    END IF;
    q <= q_t;
  END PROCESS;
END behavioral;
```

# Counters

```
ENTITY counter4 IS
    PORT (reset, clk : IN std_logic;
          count : OUT std_logic_vector (3 DOWNTO 0));
END ENTITY;
--
ARCHITECTURE procedural OF counter4 IS
    SIGNAL cnt_reg : std_logic_vector (3 DOWNTO 0);
BEGIN
    PROCESS (clk)
    BEGIN
        IF (clk = '0' AND clk'EVENT) THEN
            IF (reset='1') THEN
                cnt_reg <="0000" AFTER 1.2 NS;
            ELSE
                cnt_reg <= cnt_reg + 1 AFTER 1.2 NS;
            END IF;
        END IF;
    END PROCESS;
    count <= cnt_reg;
END ARCHITECTURE procedural;
```


# Synthesis of Shifters and Counters

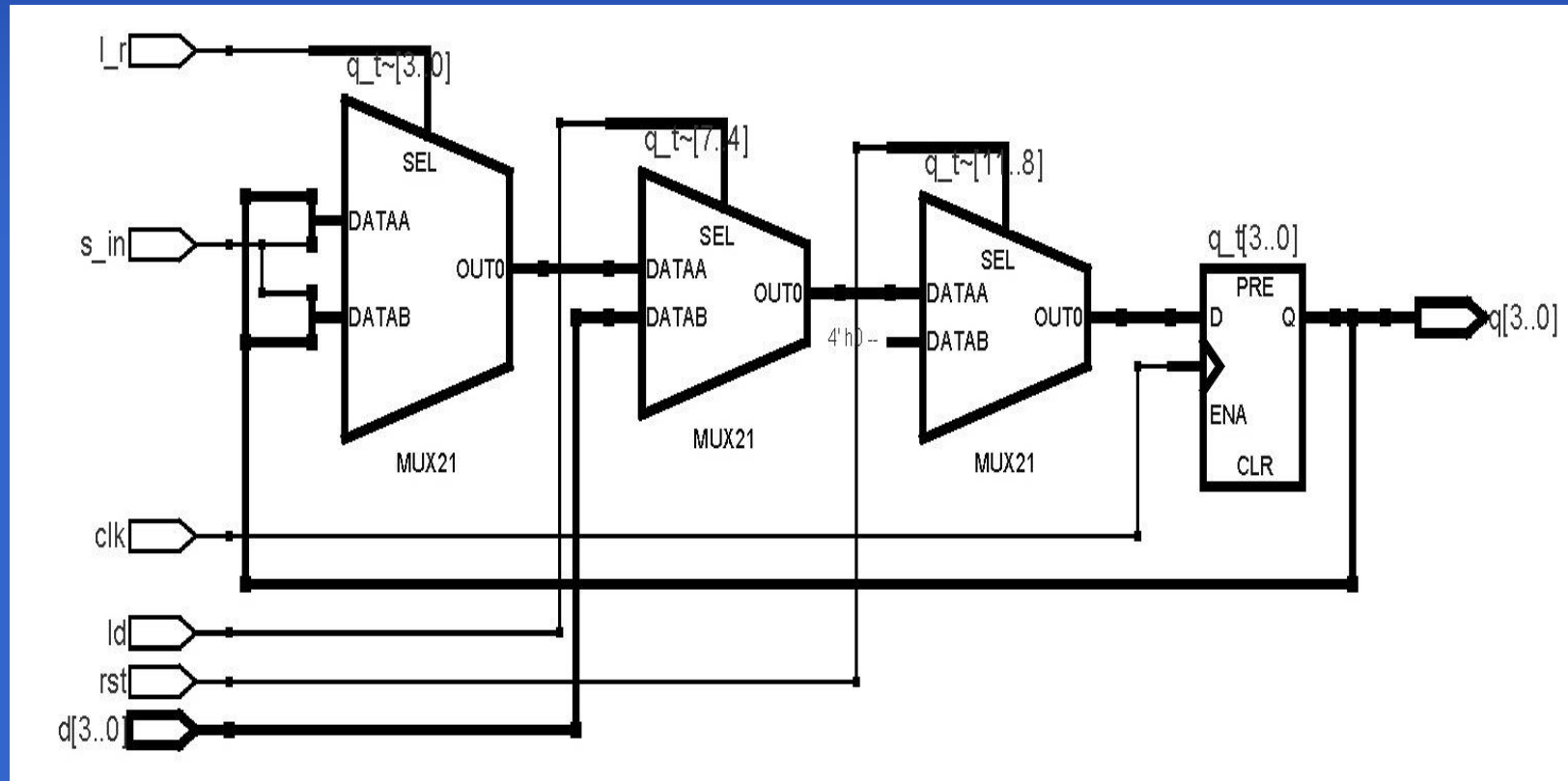

- **Shift Register Synthesis RTL View**

VHDL: Modular Design and  
Synthesis of Cores and Systems  
Copyright Z. Navabi, 2007

# State Machine Coding

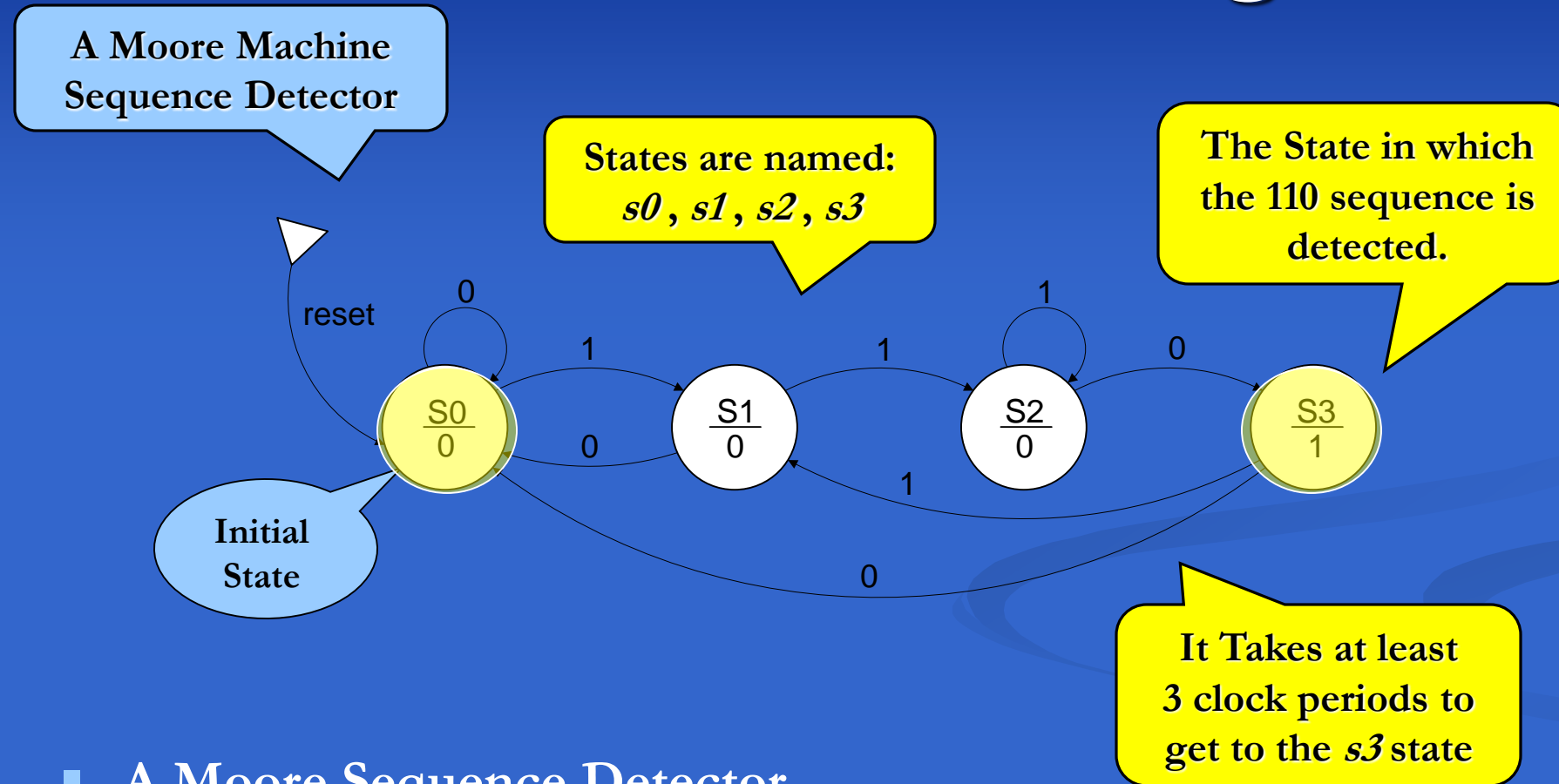

- A Moore Sequence Detector

# Moore Machine VHDL Code

```
ENTITY detector110 IS
    PORT (a, clk, reset : IN std_logic; w : OUT
std_logic);
END ENTITY;
--
ARCHITECTURE procedural OF detector110 IS
    TYPE state IS (S0, S1, S2, S3);
    SIGNAL current : state := S0;
BEGIN
    PROCESS (clk) BEGIN
        IF (clk = '0' AND clk'EVENT) THEN
            IF reset = '1' THEN current <= S0;
            ELSE
                CASE current IS
                    WHEN S0 =>
                        IF a='1' THEN current <= S1;
                        ELSE current <= S0; END IF;
```


```
                    WHEN S1 =>
                        IF a='1' THEN current <= S2;
                        ELSE current <= S0; END IF;
                    WHEN S2 =>
                        IF a='1' THEN current <= S2;
                        ELSE current <= S3; END IF;
                    WHEN S3 =>
                        IF a='1' THEN current <= S1;
                        ELSE current <= S0; END IF;
                    WHEN OTHERS => current <= S0;
                END CASE;
            END IF;
        END IF;
    END PROCESS;
    w <= '1' WHEN current = S3 ELSE '0';
END ARCHITECTURE procedural;
```

# Pulse Synchronizer

```
ENTITY synchronizer IS
    PORT (clk, adata : IN std_logic;
          synched : OUT std_logic);
END ENTITY;
--
ARCHITECTURE procedural OF synchronizer IS
    TYPE state IS (S0, S1);
    SIGNAL current : state;
BEGIN
    PROCESS (clk) BEGIN
        IF (rising_edge(clk)) THEN
            IF current = S0 THEN
                IF adata = '0' THEN
                    current <= S0;
                ELSE
                    current <= S1;
                END IF;
            ELSE -- current = S1
                current <= S0;
            END IF;
        END IF;
    END PROCESS;
    synched <= '1' WHEN current = S1 ELSE '0';
END ARCHITECTURE procedural;
```


VHDL: Modular Design and  
Synthesis of Cores and Systems  
Copyright Z. Navabi, 2007

# State Machine Synthesis

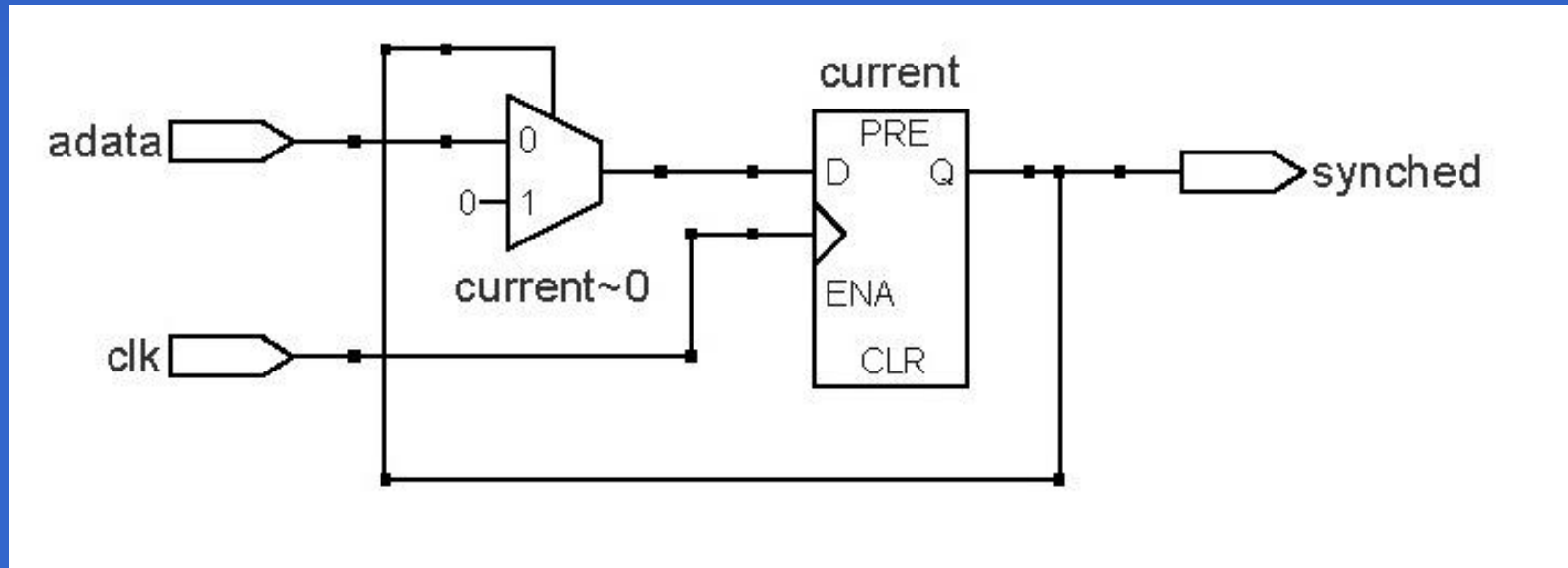



# State Machine Synthesis

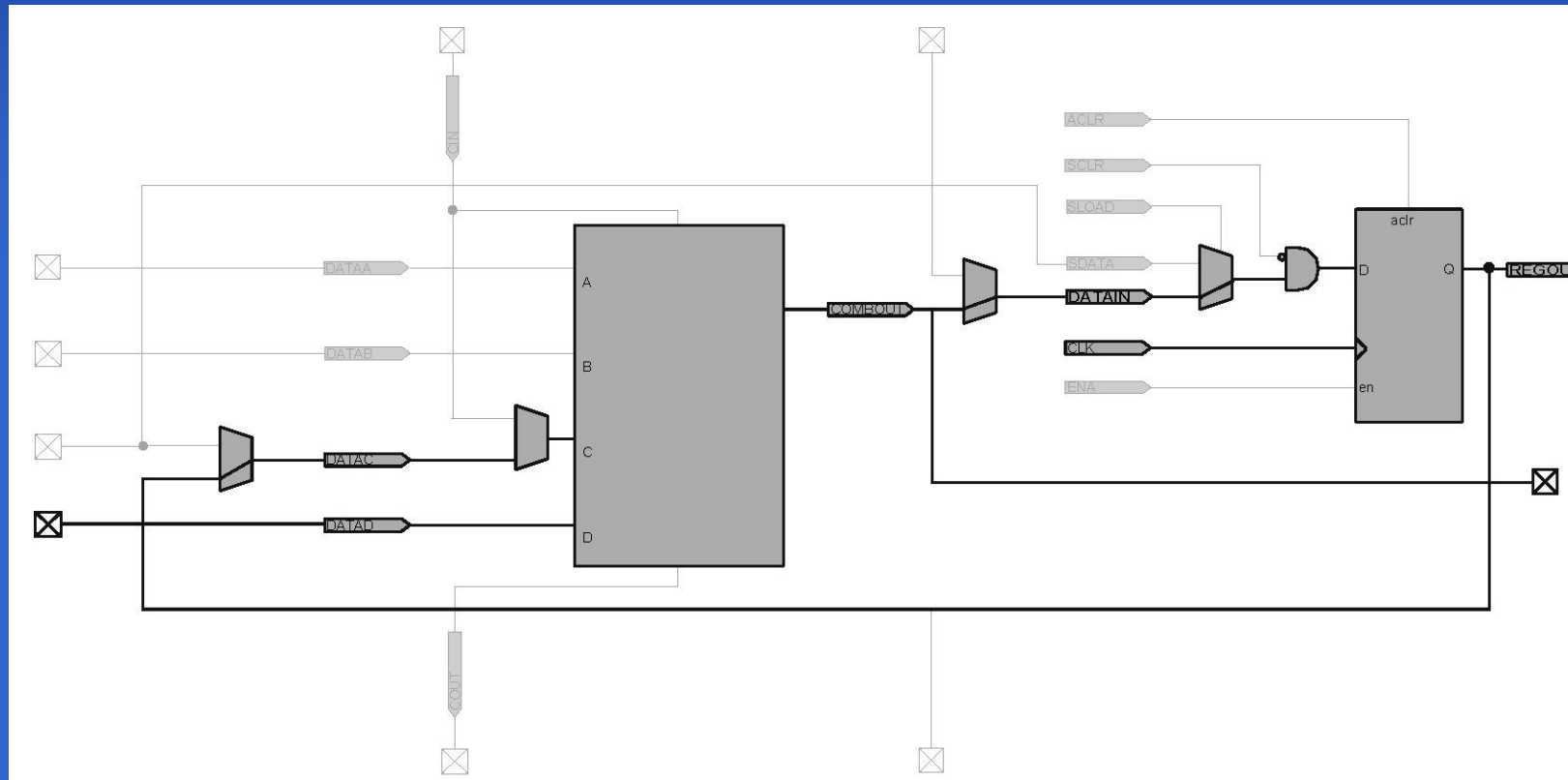

# Writing Testbenches

```
ARCHITECTURE . . .
  TYPE memory IS
    ARRAY (INTEGER RANGE <>) OF
      std_logic_vector (7 DOWNTO 0);
  SIGNAL mem: memory(0 to 1023);
BEGIN
  PROCESS (mem)
    VARIABLE memv: memory(0 to 15);
    VARIABLE data: std_logic_vector(7 DOWNTO 0);
    VARIABLE short_data: std_logic_vector(3 DOWNTO 0);
  BEGIN
    . . .
    data := mem(956);
    short_data := mem(931) (6 downto 3);
    memv (12) := mem(189);
    mem (932) <= data ;
    mem (321) (5 DOWNTO 2) <= short_data;
    mem (940) <= "0000" & short_data ;
  END PROCESS;
  . . .
END ARCHITECTURE;
```


VHDL: Modular Design and  
Synthesis of Cores and Systems  
Copyright Z. Navabi, 2007

# Writing Testbenches

```
ENTITY detector110_tester IS END ENTITY;
--
ARCHITECTURE timed OF detector110_tester IS
    SIGNAL aa, clock, rst, ww : std_logic := '0';
BEGIN
    UUT1: ENTITY WORK.detector110 (procedural)
        PORT MAP (aa, clock, rst, ww);
    rst <= '1' AFTER 31 NS, '0' AFTER 54 NS;
    clock <= NOT clock AFTER 7 NS WHEN NOW<=165 NS ELSE '0';
    PROCESS BEGIN
        WAIT FOR 23 NS; aa <= '1';
        WAIT FOR 21 NS; aa <= '0';
        WAIT FOR 19 NS; aa <= '1';
        WAIT FOR 31 NS; aa <= '0';
        WAIT;
    END PROCESS;
    PROCESS (ww) BEGIN
        REPORT "Signal w changed to:" & std_logic'IMAGE(ww) &
            " at " & TIME'IMAGE(NOW)
            SEVERITY NOTE;
    END PROCESS;
END ARCHITECTURE timed;
```

VHDL: Modular Design and  
Synthesis of Cores and Systems  
Copyright Z. Navabi, 2007

# Writing Testbenches

 

- **Testbench Waveform Results**

# Summary

- This chapter presented:
  - RT level description in the VHDL HDL language
  - examples of synthesizable one-to-one hardware correspondence
  - introducing some VHDL terminologies that are needed for understanding the linguistics of VHDL
  - How testbenches could be developed in VHDL and new constructs of it in this part