

# Chapter 3

## VHDL Constructs for Structure and Hierarchy Descriptions

# VHDL Constructs for Structure and Hierarchy Descriptions

## 3.1 Basic Components

### 3.1.1 Basic Model

## 3.2 Component Instantiations

### 3.2.1 Direct Instantiation

### 3.2.2 Component Instantiation

## 3.3 Iterative Networks

### 3.3.1 Multi-bit Vectors

### 3.3.2 Multi-instance Generations

### 3.3.3 Simplified Generations

## 3.4 Binding Alternatives

## 3.5 Association Methods

# VHDL Constructs for Structure and Hierarchy Descriptions

## 3.6 Generic Parameters

3.6.1 Using Generic Default Values

3.6.2 Generic Map Aspect

3.6.3 Generic Association List

## 3.7 Design Configuration

3.7.1 Basic Configuration Declaration

3.7.2 Incremental Configuration

3.7.3 Configuring Nested Components


3.7.4 Indexing Block Configurations

3.7.5 Instantiating a Design Unit

## 3.8 Design Simulation


## 3.9 Summary

# Basic Model

 


```
ENTITY inv IS
    PORT (i1 : IN BIT; y : OUT BIT);
END ENTITY;
--
ARCHITECTURE delay1 OF inv IS
BEGIN
    y <= NOT i1 AFTER 3 NS;
END ARCHITECTURE delay1;
```

# Basic Model

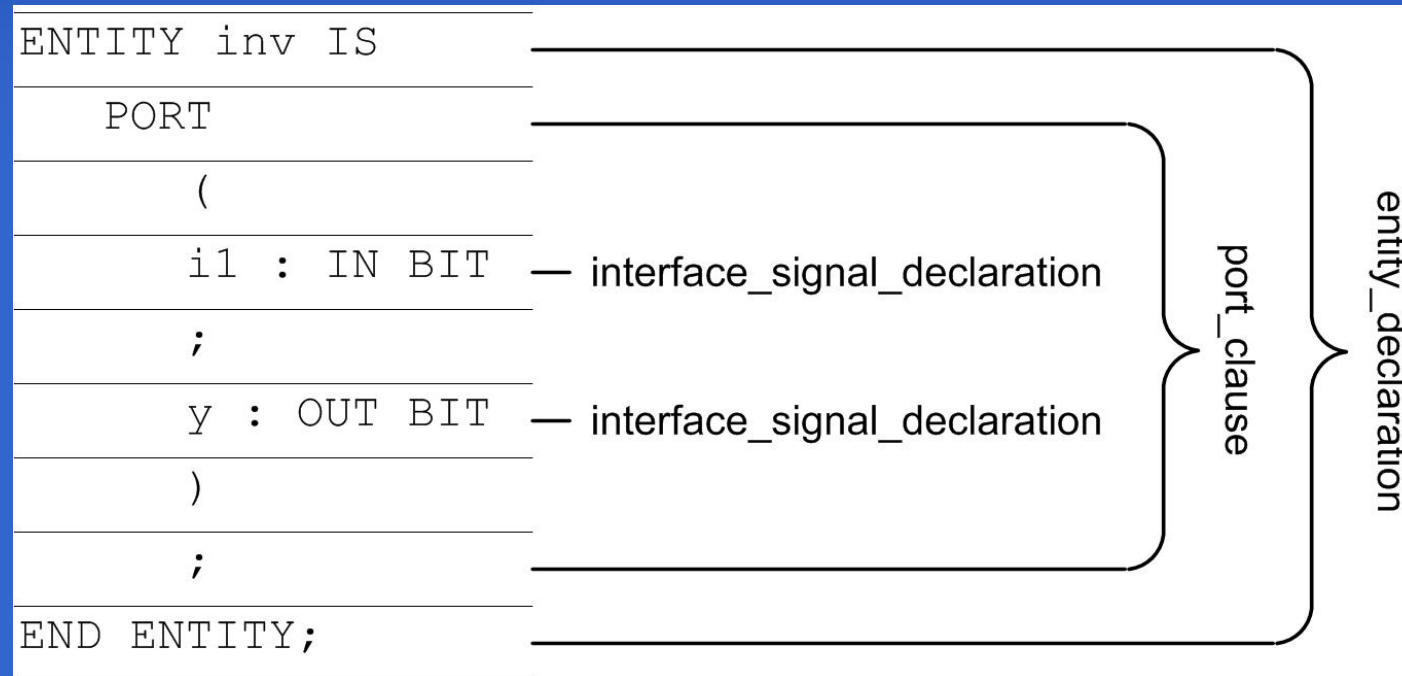


- Details of the Entity Declaration of the Inverter


# Basic Model

 


IN

 

OUT

 


INOUT

 

BUFFER


- Entity Parts, (a) Inputs, (b) Outputs, (c) Bidirectional, (d) Buffers

# Basic Model

 

```
ENTITY nand2 IS
    PORT (i1, i2 : IN BIT; y : OUT BIT);
END ENTITY;
--
ARCHITECTURE delay1 OF nand2 IS
BEGIN
    y <= i1 NAND i2 AFTER 5 NS;
END ARCHITECTURE delay1;
```


# Basic Model

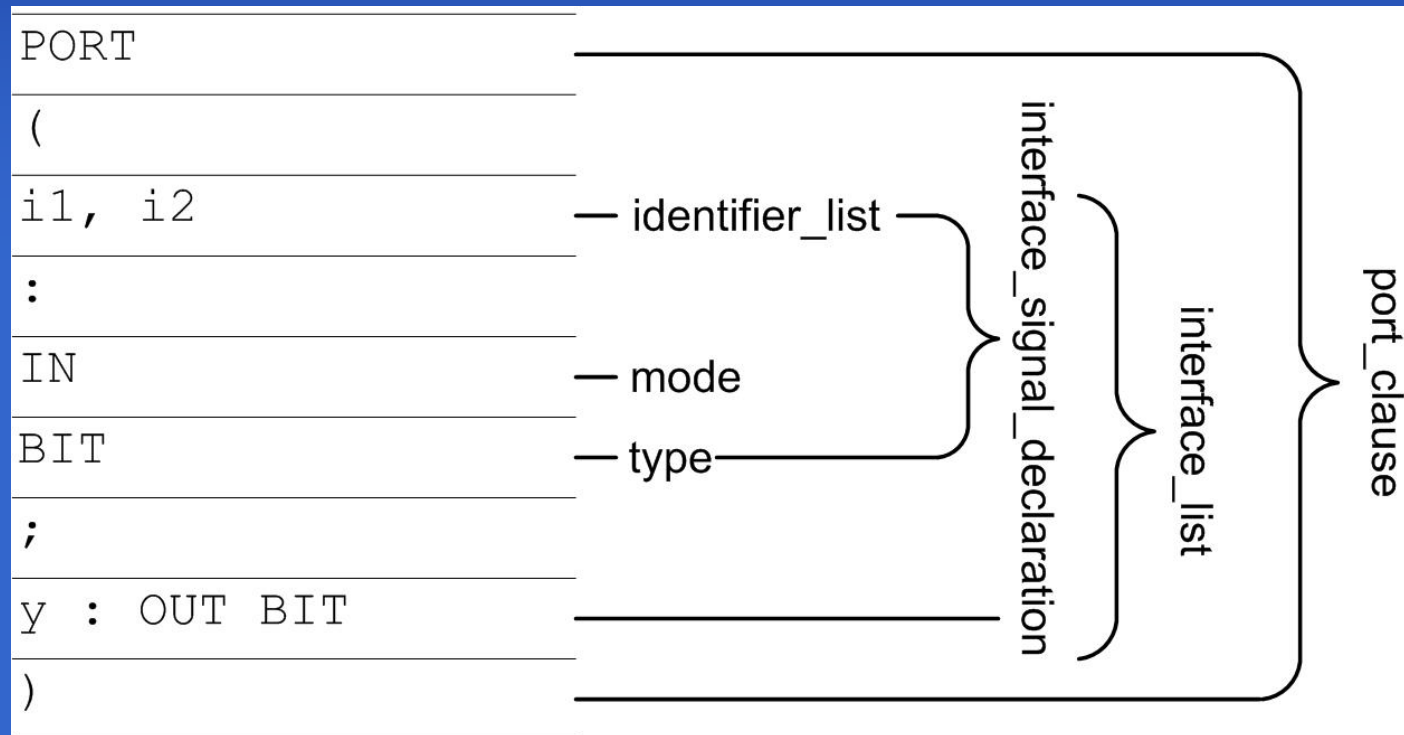

- Port Clause Details for *nand2*



# Component Instantiations

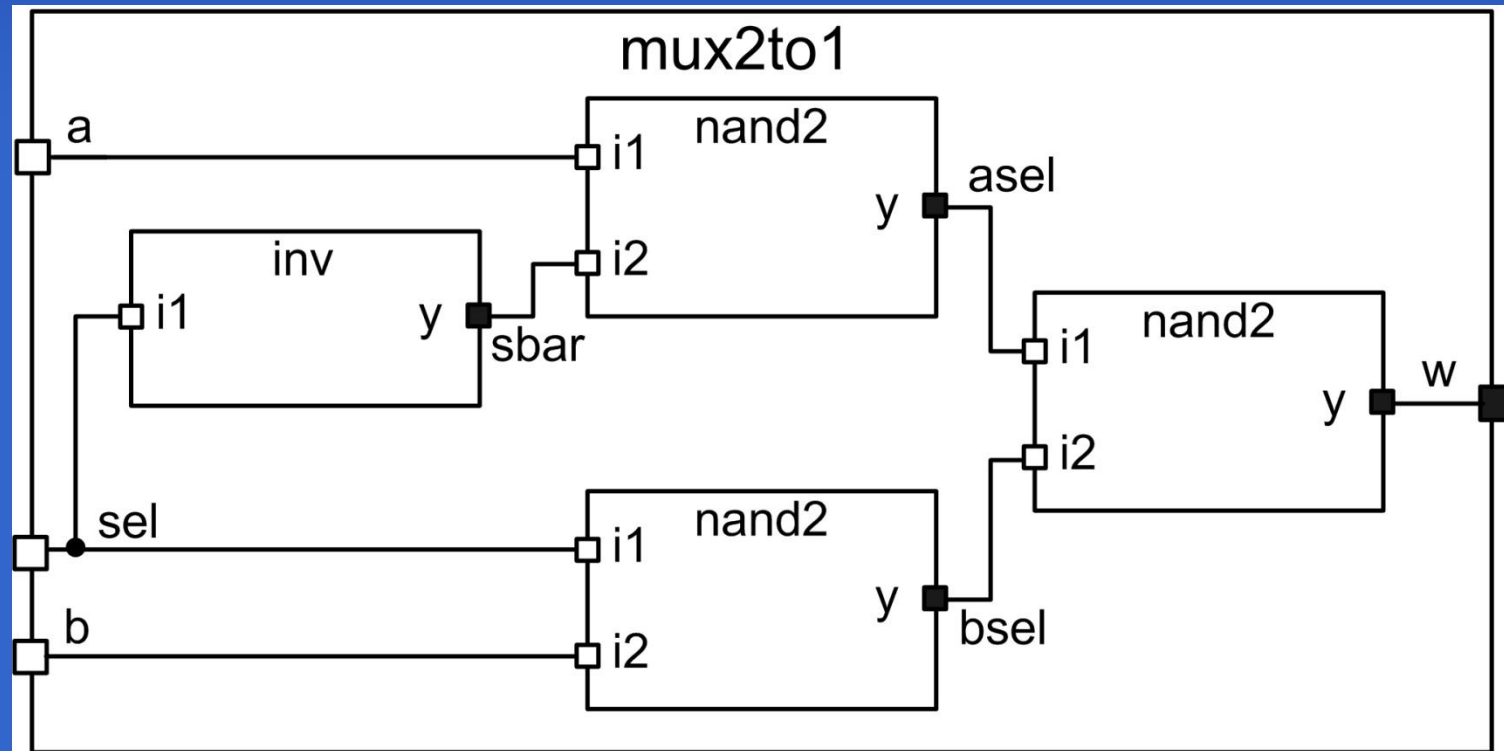

# Direct Instantiation


```
ENTITY multiplexer IS
  PORT (a, b, s : IN BIT;
         w : OUT BIT);
END ENTITY;
--
ARCHITECTURE direct OF multiplexer IS
  SIGNAL sbar, asel, bsel : BIT;
BEGIN
  U1: ENTITY WORK.inv (delay1) PORT MAP (s, sbar);
  U2: ENTITY WORK.nand2 (delay1) PORT MAP (a, sbar, asel);
  U3: ENTITY WORK.nand2 (delay1) PORT MAP (b, s, bsel);
  U4: ENTITY WORK.nand2 (delay1) PORT MAP (asel, bsel, w);
END ARCHITECTURE direct;
```

- Using Direct Instantiations

# Component Instantiation


```
ARCHITECTURE gates OF multiplexer IS
  COMPONENT n1
    PORT (i1: IN BIT; y: OUT BIT);
  END COMPONENT;
  COMPONENT n2
    PORT (i1, i2: IN BIT; y: OUT BIT);
  END COMPONENT;
  FOR ALL : n1 USE ENTITY WORK.inv (delay1);
  FOR ALL : n2 USE ENTITY WORK.nand2 (delay1);
  SIGNAL sbar, asel, bsel : BIT;
BEGIN
  U1: n1 PORT MAP (s, sbar);
  U2: n2 PORT MAP (a, sbar, asel);
  U3: n2 PORT MAP (b, s, bsel);
  U4: n2 PORT MAP (asel, bsel, w);
END ARCHITECTURE gates;
```

# Component Instantiation

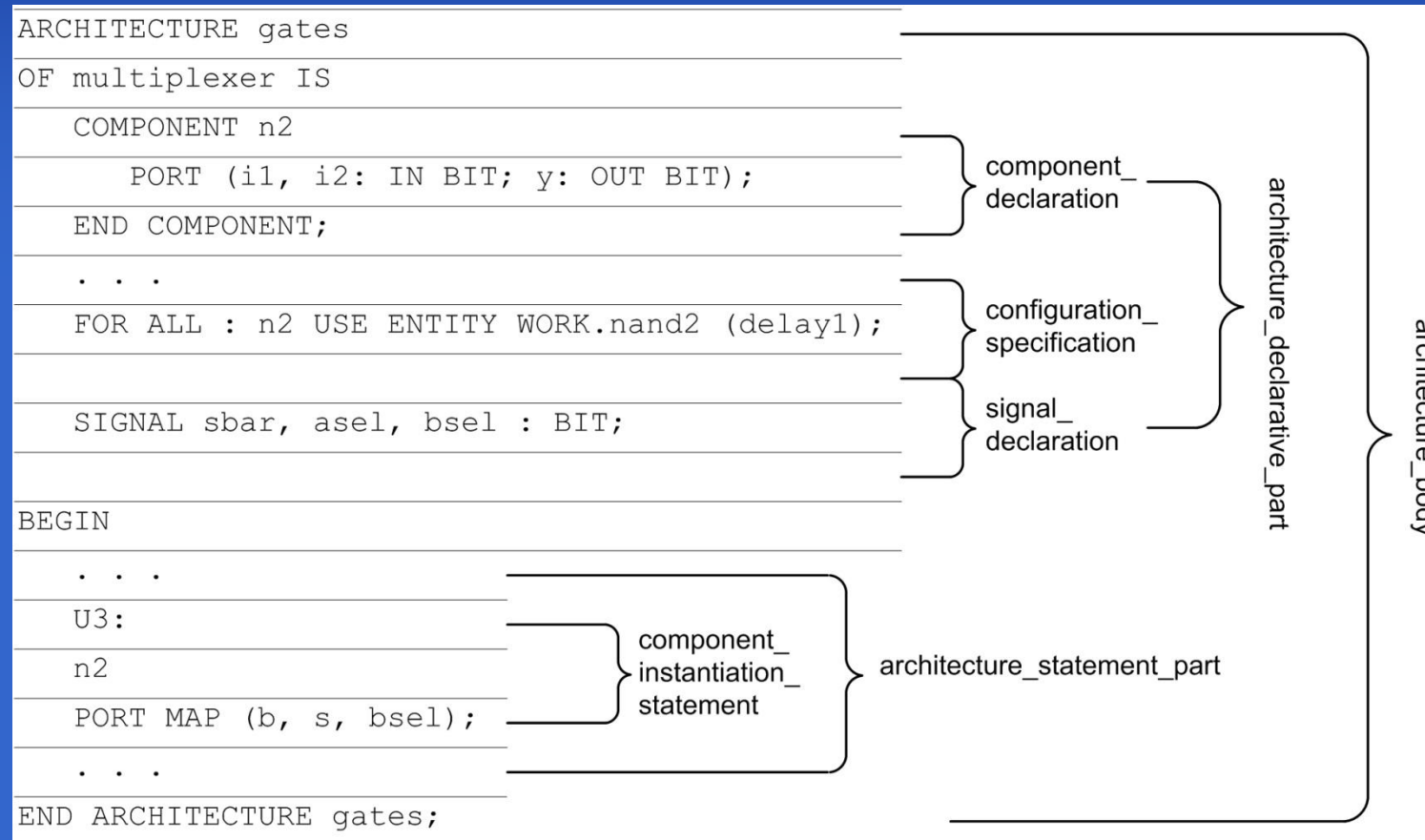


- Syntax Details of the Architecture Body of *multiplexer(gates)*

# Component Instantiation

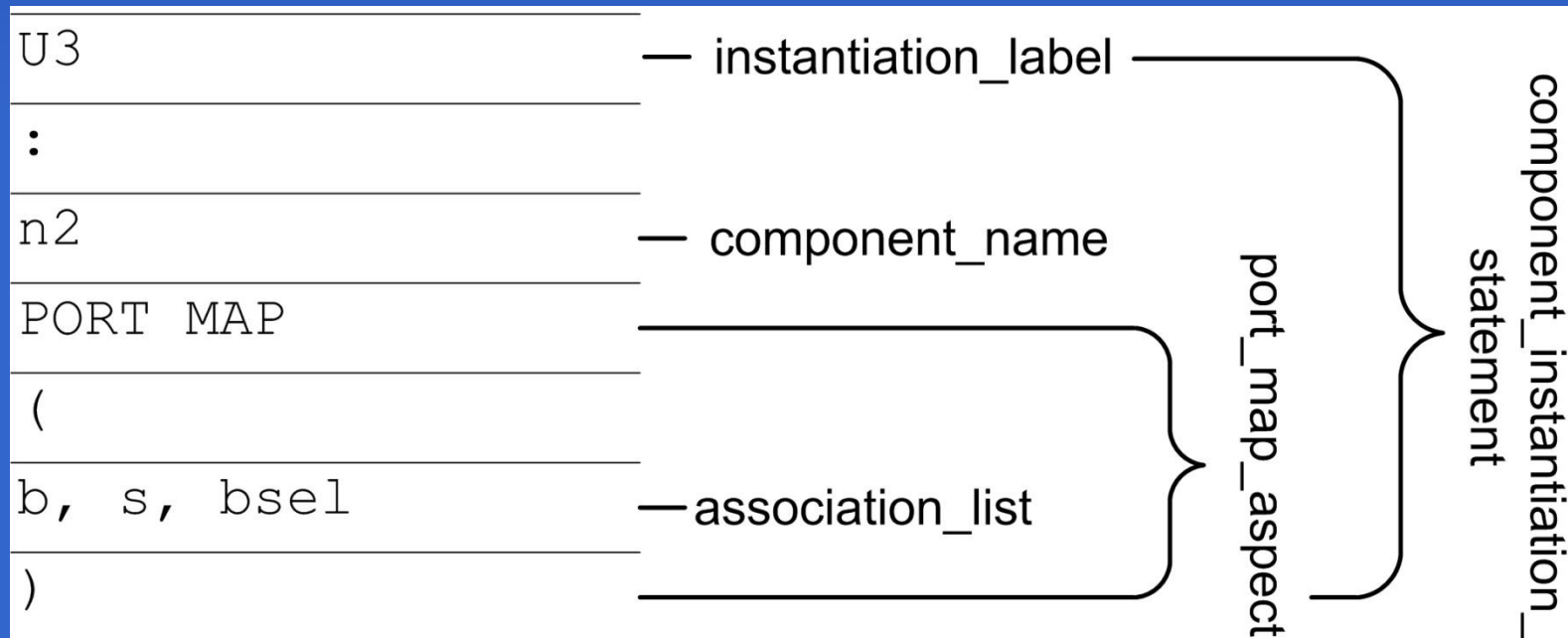

- **Component Instantiation Statement Syntax Details**


# Multi-bit Vectors

 

```
ENTITY multiplexer8 IS
    PORT (
        a, b : IN BIT_VECTOR (7 DOWNTO 0);
        s : IN BIT;
        w : OUT BIT_VECTOR (7 DOWNTO 0) );
END ENTITY;
```

- Interface Description *multiplexer8*

# Multi-instance Generations

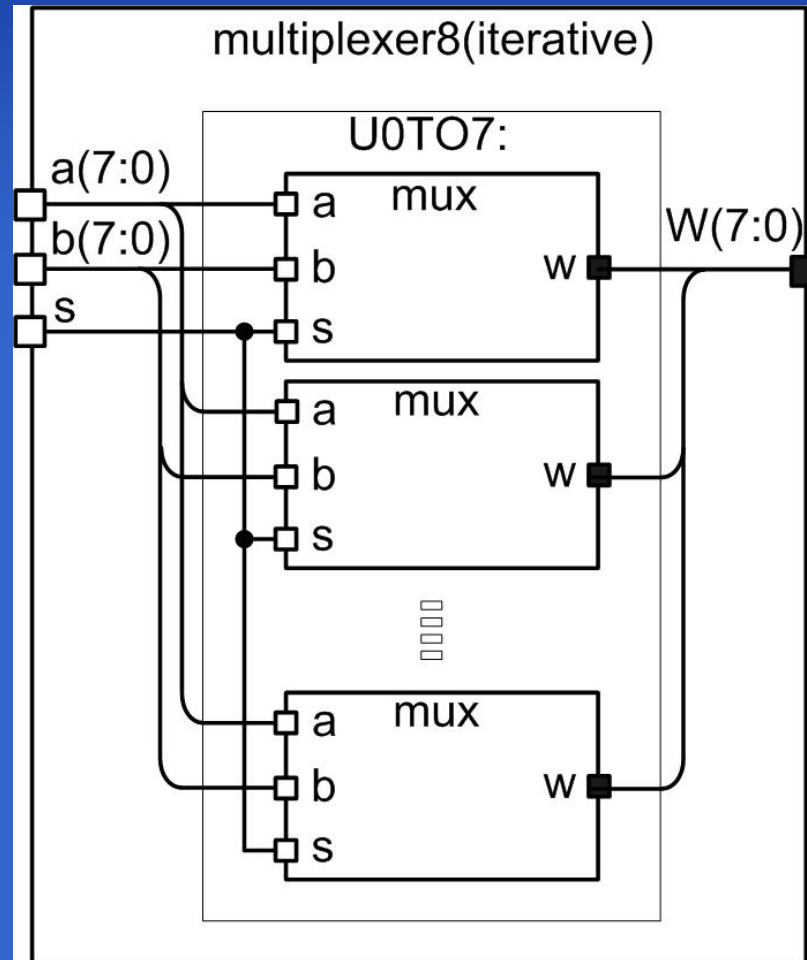

- *multiplexer8* Hierarchical Structure


# Multi-instance Generations

```
ARCHITECTURE iterative OF multiplexer8 IS
    COMPONENT mux PORT (a, b, s : IN BIT; w : OUT BIT);
    END COMPONENT;
BEGIN
    U0TO7: FOR i IN 0 TO 7 GENERATE
        FOR ALL : mux USE ENTITY WORK.multiplexer (gates);
        BEGIN
            Ui: mux PORT MAP (a(i), b(i), s, w(i));
        END GENERATE;
    END ARCHITECTURE iterative;
```

- Iterative Architecture of *multiplexer8*



# Multi-instance Generations

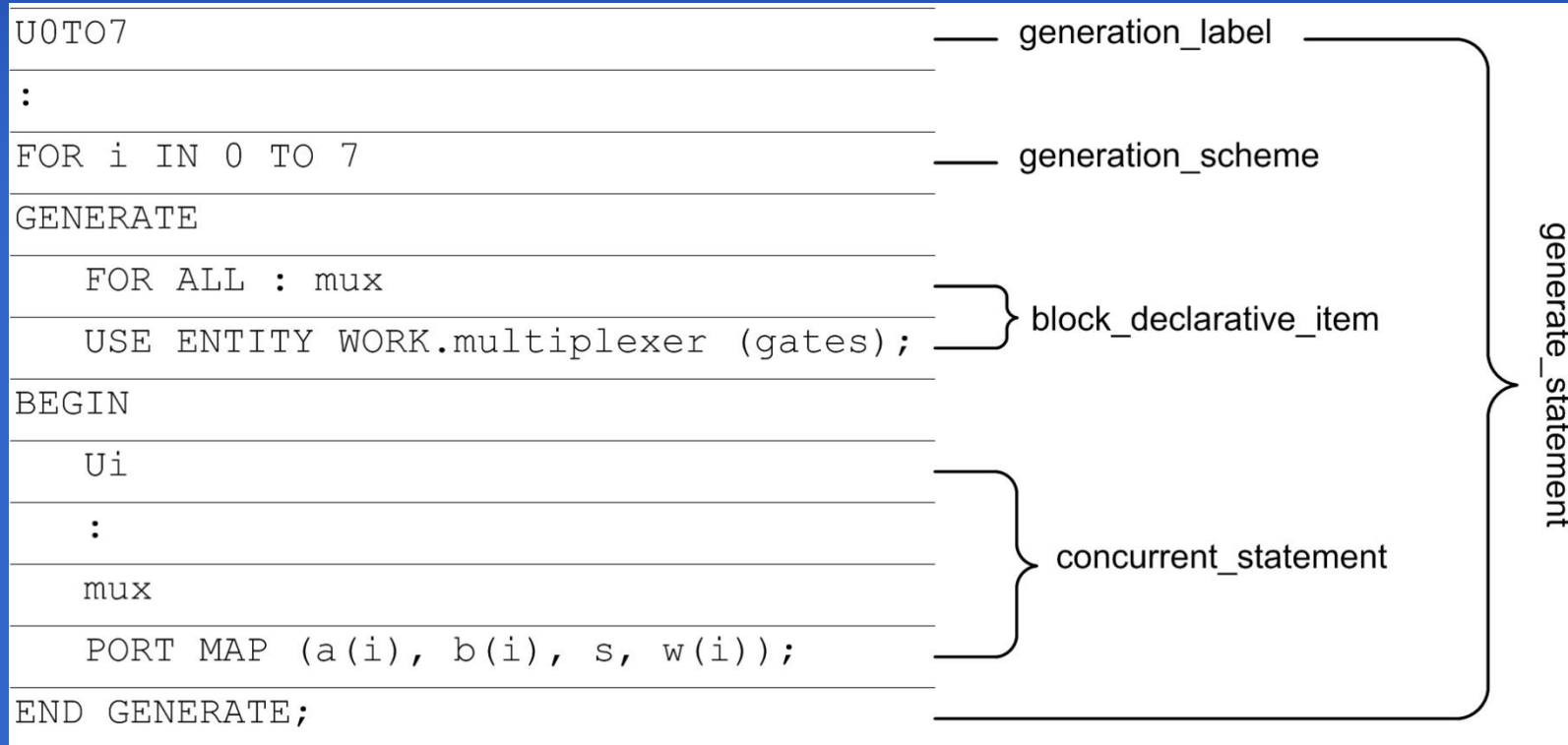

## ■ Generate Statement Syntax Details

# Simplified Generations

```
ARCHITECTURE direct OF multiplexer8 IS
BEGIN
    U0TO7: FOR i IN 0 TO 7 GENERATE
        Ui: ENTITY WORK.multiplexer
            PORT MAP (a(i), b(i), s, w(i));
        END GENERATE;
    END ARCHITECTURE direct;
```


- **Generating Direct Instantiation**

# Binding Alternatives

```
ARCHITECTURE alter OF multiplexer IS
  COMPONENT n1
    PORT (i1: IN BIT; y: OUT BIT);
  END COMPONENT;
  COMPONENT n2
    PORT (i1, i2: IN BIT; y: OUT BIT);
  END COMPONENT;
  FOR U1 : n1
    USE ENTITY WORK.nand2 (delay1) PORT MAP (i1, i1, y);
  FOR ALL : n2 USE ENTITY WORK.nand2 (delay1);
  SIGNAL sbar, asel, bsel : BIT;
BEGIN
  U1: n1 PORT MAP (s, sbar);
  U2: n2 PORT MAP (a, sbar, asel);
  U3: n2 PORT MAP (b, s, bsel);
  U4: n2 PORT MAP (asel, bsel, w);
END ARCHITECTURE alter;
```

- Configuration Specification Port Map

# Binding Alternatives

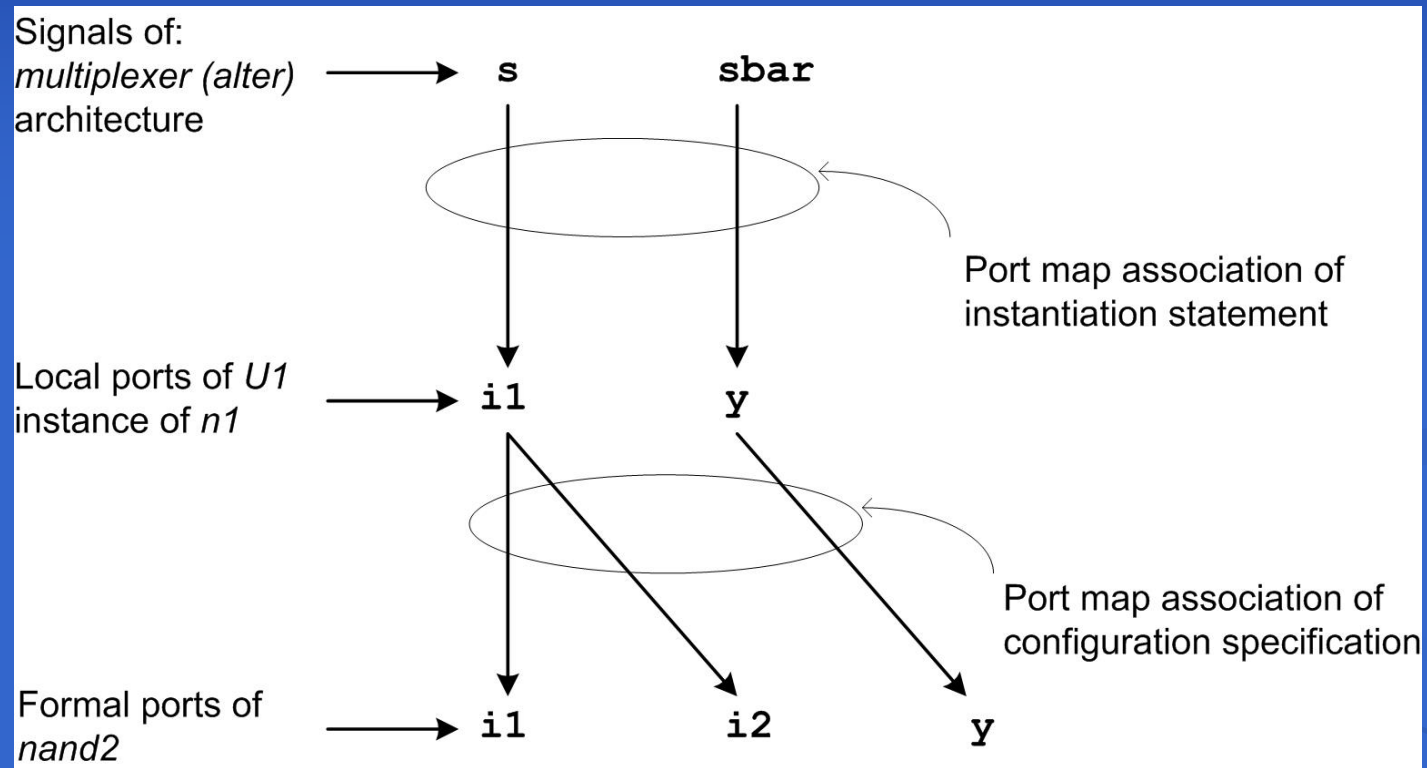

- **Two-step Associations**

# Generic Parameters

```
ENTITY inv_t IS
    GENERIC (tphl : TIME := 5 NS; tphl : TIME := 3 NS);
    PORT (i1 : IN BIT; y : OUT BIT);
END ENTITY;
--
ARCHITECTURE delay2 OF inv_t IS
BEGIN
    y <= '1' AFTER tphl WHEN (NOT i1) = '1' ELSE
        '0' AFTER tphl;
END ARCHITECTURE delay2;
-- --
```

# Generic Parameters

```
ENTITY nand2_t IS  
    GENERIC (tplh: TIME := 6 NS; tphl : TIME := 4 NS);  
    PORT (i1, i2 : IN BIT;  
          y : OUT BIT);  
END ENTITY;  
--  
ARCHITECTURE delay2 OF nand2_t IS  
BEGIN  
    y <= '1' AFTER tplh WHEN (i1 NAND i2) = '1' ELSE  
        '0' AFTER tphl;  
END ARCHITECTURE delay2;
```

# Generic Parameters

```
ENTITY SWITCH IS
```

```
GENERIC (Psize : INTEGER := 16);
```

```
PORT (CLK : IN STD_LOGIC;
```


```
Start_Worm_Hole_E, Start_Worm_Hole_W,
```

```
Start_Worm_Hole_N, Start_Worm_Hole_S : IN STD_LOGIC;
```


```
East, West, North, South : INOUT STD_LOGIC_VECTOR(Psize-1 downto 0);
```

```
Busy_H, Busy_V : OUT STD_LOGIC);
```

```
END ENTITY;
```

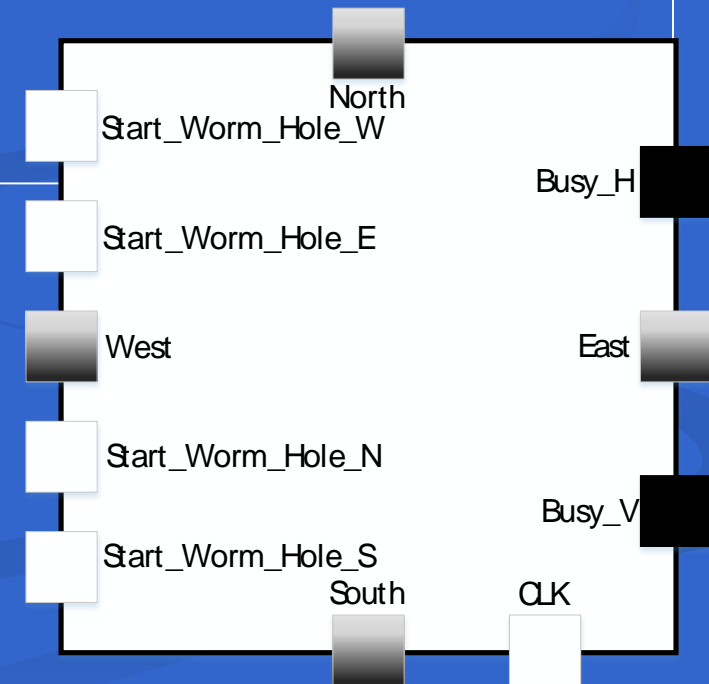

# Generic Parameters

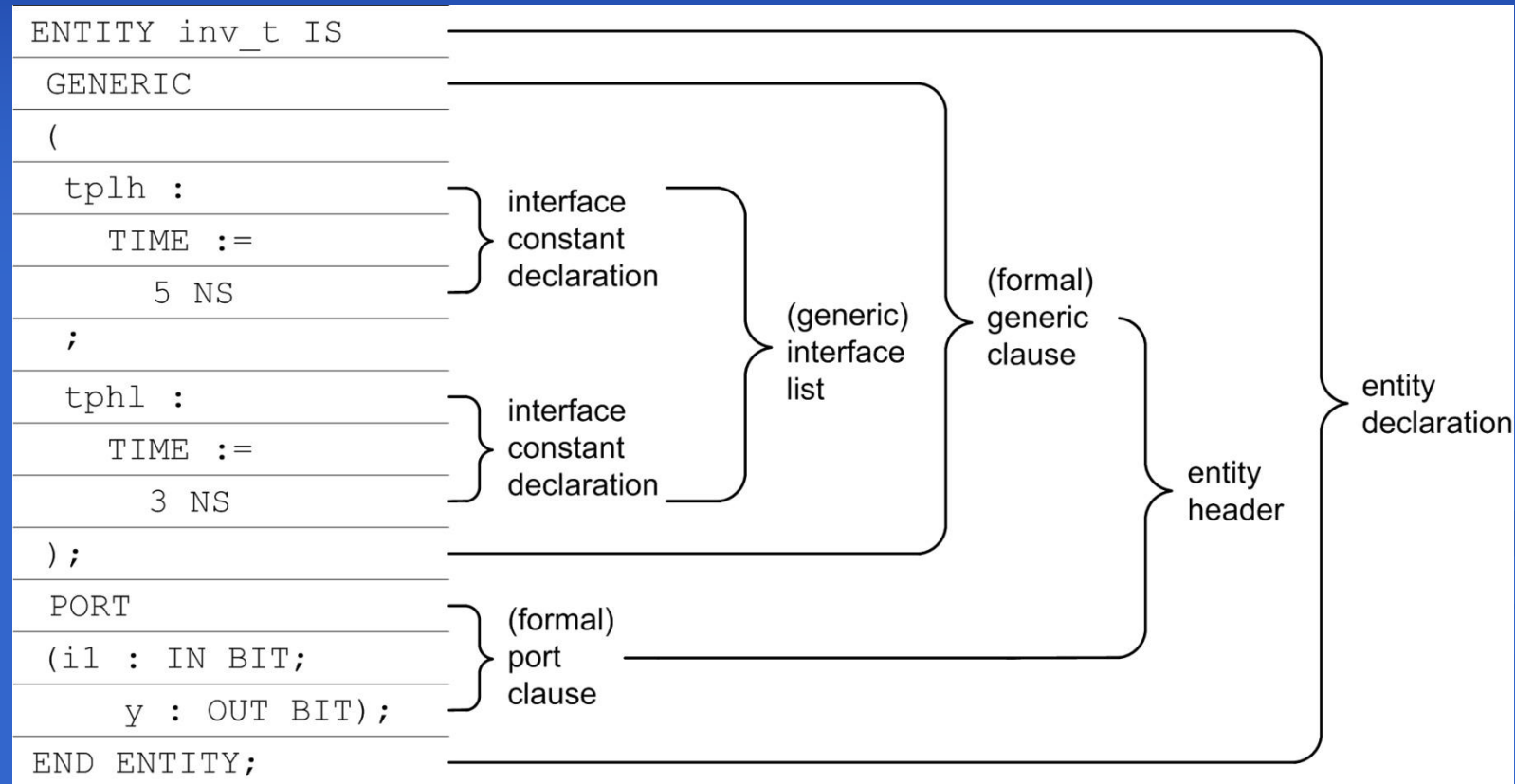

- **Details of the Entity Declaration of the Inverter with Generics**



# Using Generic Default Values

```
ARCHITECTURE default OF multiplexer IS
  COMPONENT n2
    PORT (i1, i2: IN BIT; y: OUT BIT);
  END COMPONENT;
  FOR ALL : n2 USE ENTITY WORK.nand2_t (delay2);
  SIGNAL sbar, asel, bsel : BIT;
BEGIN
  U1: n2 PORT MAP (s, s, sbar);
  U2: n2 PORT MAP (a, sbar, asel);
  U3: n2 PORT MAP (b, s, bsel);
  U4: n2 PORT MAP (asel, bsel, w);
END ARCHITECTURE default;
```


- Default Values for Generic Parameters

# Generic Map Aspect

```
ARCHITECTURE fixed OF multiplexer IS
  COMPONENT n2
    GENERIC (tplh, tphl : TIME);
    PORT (i1, i2: IN BIT; y: OUT BIT);
  END COMPONENT;
  FOR ALL : n2 USE ENTITY WORK.nand2_t (delay2);
  SIGNAL sbar, asel, bsel : BIT;
BEGIN
  U1:n2 GENERIC MAP (5 NS, 3 NS) PORT MAP (s, s, sbar);
  U2:n2 GENERIC MAP (5 NS, 3 NS) PORT MAP (a, sbar, asel);
  U3:n2 GENERIC MAP (5 NS, 3 NS) PORT MAP (b, s, bsel);
  U4:n2 GENERIC MAP (5 NS, 3 NS) PORT MAP (asel, bsel, w);
END ARCHITECTURE fixed;
```

- Using Generic Map Aspect

# Generic Map Aspect

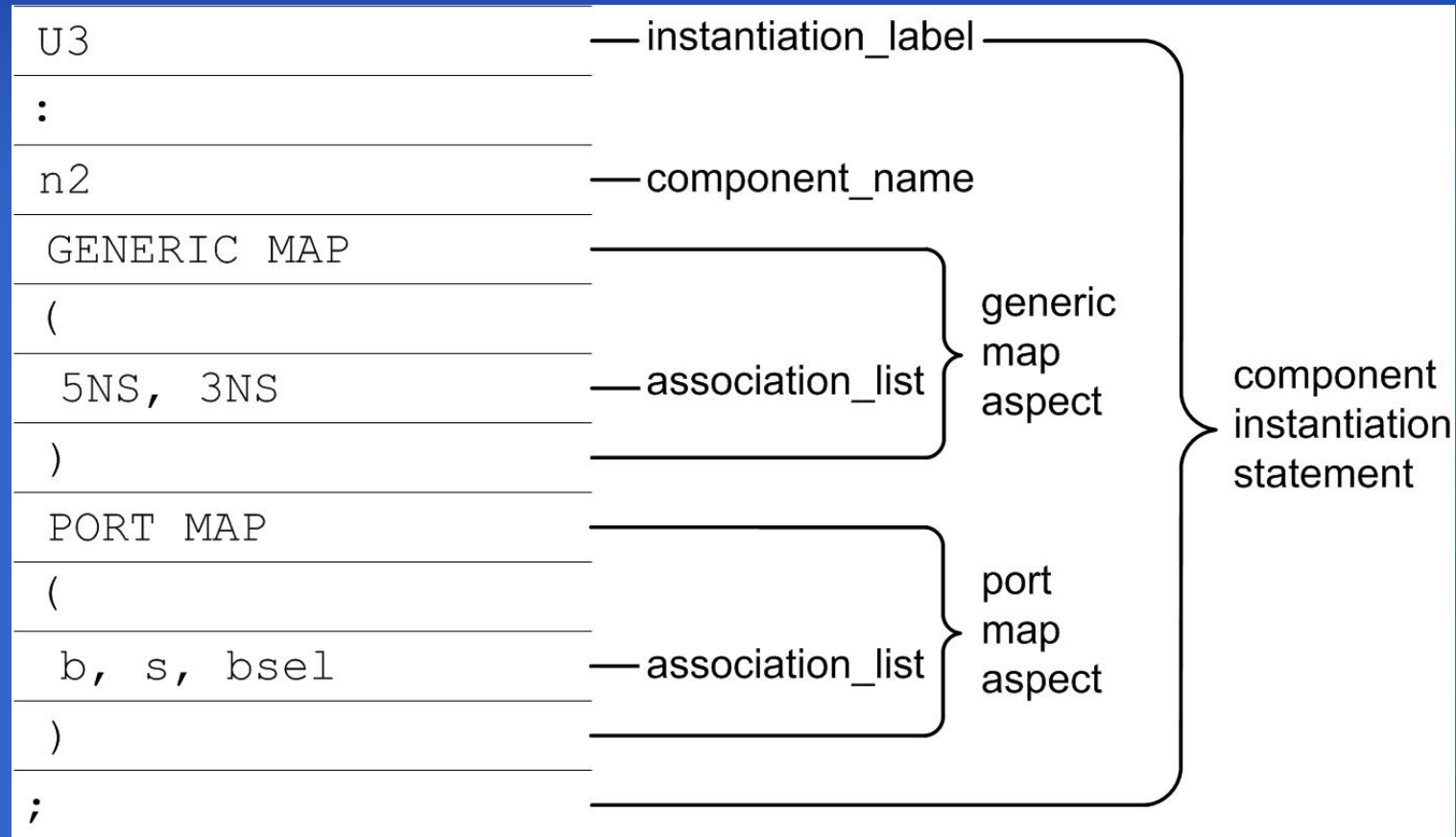

- **Component Instantiation Statement with a Generic Map Aspect**

# Basic Configuration Declaration

```
ARCHITECTURE configurable OF multiplexer IS
  COMPONENT n2
    GENERIC (tplh, tphl : TIME := 4 NS);
    PORT (i1, i2: IN BIT; y: OUT BIT);
  END COMPONENT;
  SIGNAL sbar, asel, bsel : BIT;

BEGIN
  U1: n2 PORT MAP (s, s, sbar);
  U2: n2 PORT MAP (a, sbar, asel);
  U3: n2 PORT MAP (b, s, bsel);
  U4: n2 PORT MAP (asel, bsel, w);
END ARCHITECTURE configurable;
```

# Basic Configuration Declaration

```
CONFIGURATION configured OF multiplexer IS
  FOR configurable
    FOR ALL : n2
      USE ENTITY WORK.nand2_t (delay2)
      GENERIC MAP (5 NS, 3 NS);
    END FOR;
  END FOR;
END CONFIGURATION configured;
```


- Basic Configuration Declaration

# Basic Configuration Declaration

```
CONFIGURATION another_configured OF multiplexer IS
  FOR configurable
    FOR ALL : n2
      USE ENTITY WORK.nand2_t (delay2);
    END FOR;
  END FOR;
END CONFIGURATION another_configured;
```

- Another Configuration Declaration for Multiplexer

# Basic Configuration Declaration

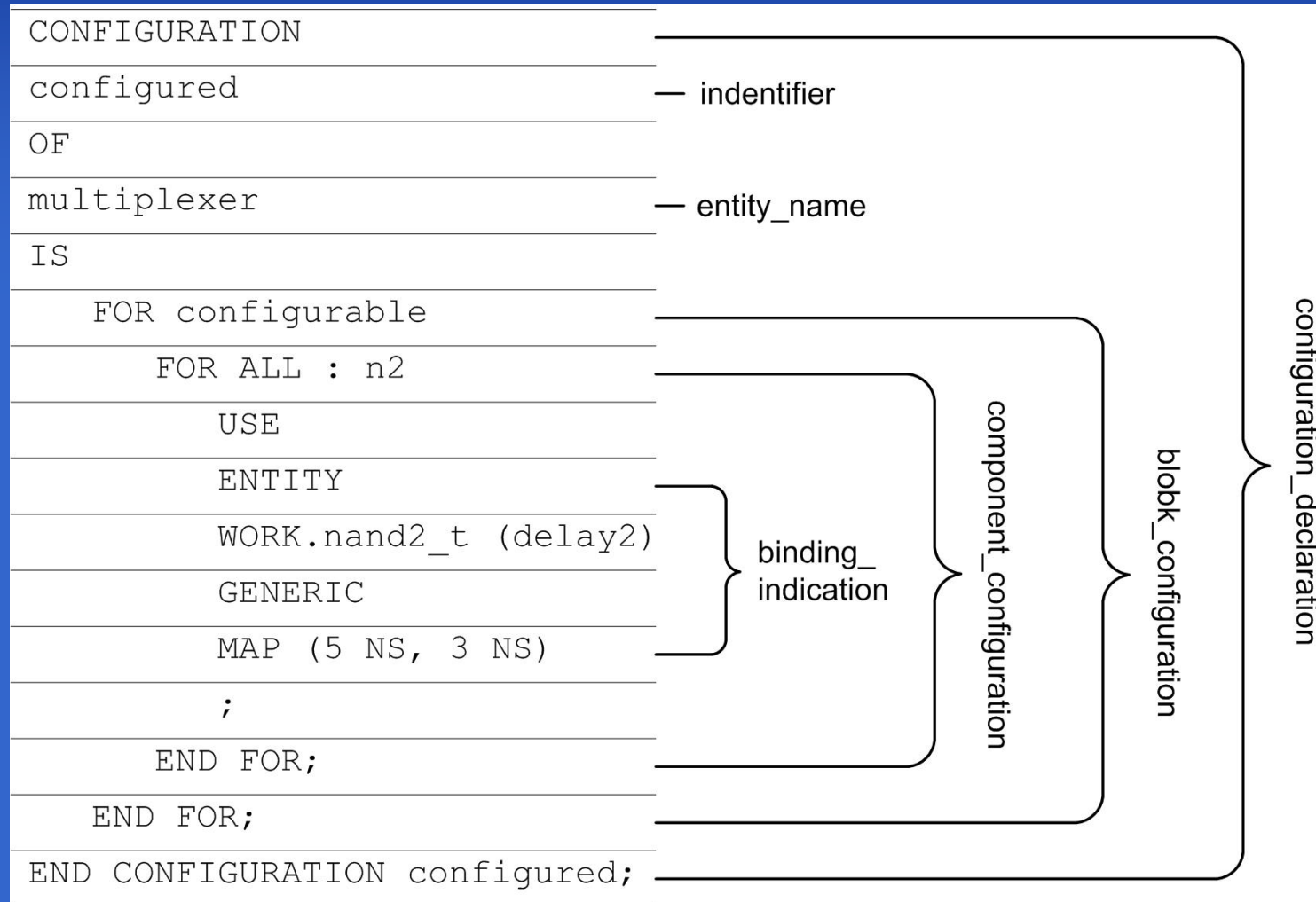

# Incremental Configuration

```
ARCHITECTURE reconfigurable OF multiplexer IS
  COMPONENT n2
    GENERIC (tplh, tphl : TIME := 4 NS);
    PORT (i1, i2: IN BIT; y: OUT BIT);
  END COMPONENT;
  --Primary Binding:
  FOR ALL : n2 USE ENTITY WORK.nand2_t (delay2);
  SIGNAL sbar, asel, bsel : BIT;
BEGIN
  U1: n2 PORT MAP (s, s, sbar);
  U2: n2 PORT MAP (a, sbar, asel);
  U3: n2 PORT MAP (b, s, bsel);
  U4: n2 PORT MAP (asel, bsel, w);
END ARCHITECTURE reconfigurable;
```

```
CONFIGURATION reconfigured OF multiplexer IS
  FOR reconfigurable
    FOR ALL : n2
      GENERIC MAP (5 NS, 3 NS);
    END FOR;
  END FOR;
END CONFIGURATION reconfigured;
```

- Incremental Binding



# Configuring Nested Components

```
ARCHITECTURE multiconfig OF multiplexer8 IS
  COMPONENT mux
    PORT (a, b, s : IN BIT; w : OUT BIT);
  END COMPONENT;
BEGIN
  U0TO7: FOR i IN 0 TO 7 GENERATE
    Ui: mux PORT MAP (a(i), b(i), s, w(i));
  END GENERATE;
END ARCHITECTURE multiconfig;
```

- Unspecified Components and Sub-components

# Configuring Nested Components

```
01:  CONFIGURATION multiconfiged OF multiplexer8 IS
02:      FOR multiconfig
03:          FOR U0TO7
04:              FOR ALL : mux
05:                  : USE ENTITY WORK.multiplexer (configurable);
06:                      FOR configurable
07:                          FOR ALL : n2
08:                              USE ENTITY WORK.nand2_t (delay2)
09:                                  GENERIC MAP (5 NS, 3 NS);
10:                                      END FOR;
11:                                          END FOR;
12:                                              END FOR;
13:                                                  END FOR;
14:  END CONFIGURATION multiconfiged;
```

- **Multi-level Configuration Declaration**

# Configuring Nested Components

Starts and Ends in Line	Language Structure	Visibility to:	Binding to:
1-14	Configuration Declaration	-	-
2-13	Block Configuration	<i>multiplexer8</i> ( <i>multiconfig</i> ) Architecture	-
3-12	Block Configuration	<i>U0T07:</i> Generate	-
4-11	Component Configuration	-	<i>multiplexer</i> ( <i>configurable</i> )
5-10	Block Configuration	<i>multiplexer8</i> ( <i>multiconfig</i> ) Architecture	
6-9	Component Configuration	-	<i>nand2_t</i> ( <i>delay2</i> )

# Indexing Block Configurations

```
CONFIGURATION differentlyconfiged OF multiplexer8 IS
  FOR multiconfig
    FOR U0TO7 (0)
      FOR Ui : mux
        USE ENTITY WORK.multiplexer (configurable);
        FOR configurable
          FOR U3 : n2
            USE ENTITY WORK.nand2_t (delay2)
            GENERIC MAP (3 NS, 2 NS);
          END FOR;
          FOR OTHERS : n2
            USE ENTITY WORK.nand2_t (delay2)
            GENERIC MAP (4 NS, 6 NS);
          END FOR;
        END FOR;
      END FOR;
    END FOR;
  END FOR;
```

```
    FOR U0TO7 (1 TO 7)
      FOR Ui : mux
        USE ENTITY WORK.multiplexer (configurable);
        FOR configurable
          FOR ALL : n2
            USE ENTITY WORK.nand2_t (delay2)
            GENERIC MAP (8 NS, 5 NS);
          END FOR;
        END FOR;
      END FOR;
    END FOR;
  END FOR;
END CONFIGURATION differentlyconfiged;
```


- Indexing Configurations for Generate Statements

# Instantiating a Design Unit

```
ENTITY multiplexer_tester IS
END ENTITY;
--
ARCHITECTURE timed OF multiplexer_tester IS
    SIGNAL a, b, s, w1, w2, w3, w4, w5, w6, w7 : BIT;
BEGIN
    UUT1:ENTITY WORK.multiplexer(direct) PORT MAP (a,b,s,w1);
    UUT2:ENTITY WORK.multiplexer(gates) PORT MAP (a,b,s,w2);
    UUT3:ENTITY WORK.multiplexer(alter) PORT MAP (a,b,s,w3);
    UUT4:ENTITY WORK.multiplexer(default) PORT MAP (a,b,s,w4);
    UUT5:ENTITY WORK.multiplexer(fixed) PORT MAP (a,b,s,w5);
    UUT6:CONFIGURATION WORK.configured PORT MAP (a,b,s,w6);
    UUT7:CONFIGURATION WORK.reconfigured PORT MAP (a,b,s,w7);
    a <= '0', '1' AFTER 020 NS, '0' AFTER 065 NS, '1' AFTER 179 NS;
    b <= '1', '0' AFTER 045 NS, '1' AFTER 105 NS, '0' AFTER 215 NS;
    s <= '0', '1' AFTER 129 NS, '0' AFTER 211 NS, '1' AFTER 245 NS;
END ARCHITECTURE timed;
```

- Instantiating Design Units

# Design Simulation

 

- Multiplexer Simulation Report

# Summary

- This chapter presented:
  - Formation and configuration of upper level structures based on lower level design units
  - Illustrating various forms of component specifications, configurations, and delay parameter specifications
  - Simple examples to avoid discussion of more complex language constructs and focus only on the structural descriptions
  - Using lower level design example (NAND gate), and forming a multiplexer based on that.

# Acknowledgment

Slides developed by:

Nadereh Hatami

First revision 2019 by

Saba Yousefzadeh