

# Chapter 4

## Concurrent Constructs for RT Level Descriptions

# Concurrent Constructs for RT Level Descriptions

## 4.1 Concurrent Signal Assignments

### 4.1.1 Simple Assignments

### 4.1.2 Conditional Signal Assignment

### 4.1.3 Selected Signal Assignment

## 4.2 Guarded Signal Assignments

### 4.2.1 GUARD Signal and Expression

### 4.2.2 Block Statement

### 4.2.3 Block Statement Ports


### 4.2.4 Nested Block Statements

### 4.2.5 Guarded Signals


### 4.2.6 Timing Disconnections

## 4.3 Summary

# Concurrent Signal Assignments

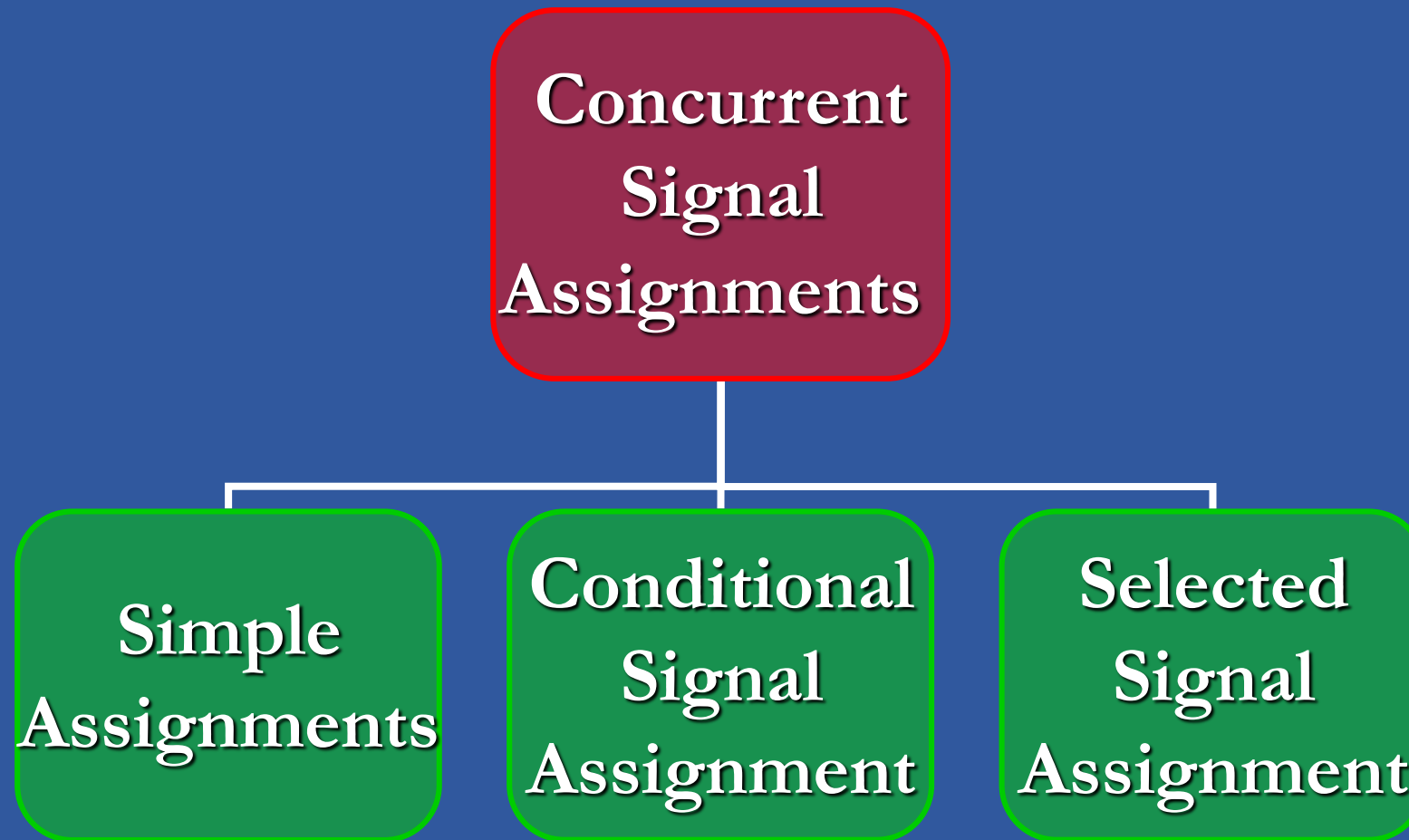

# Simple Assignments

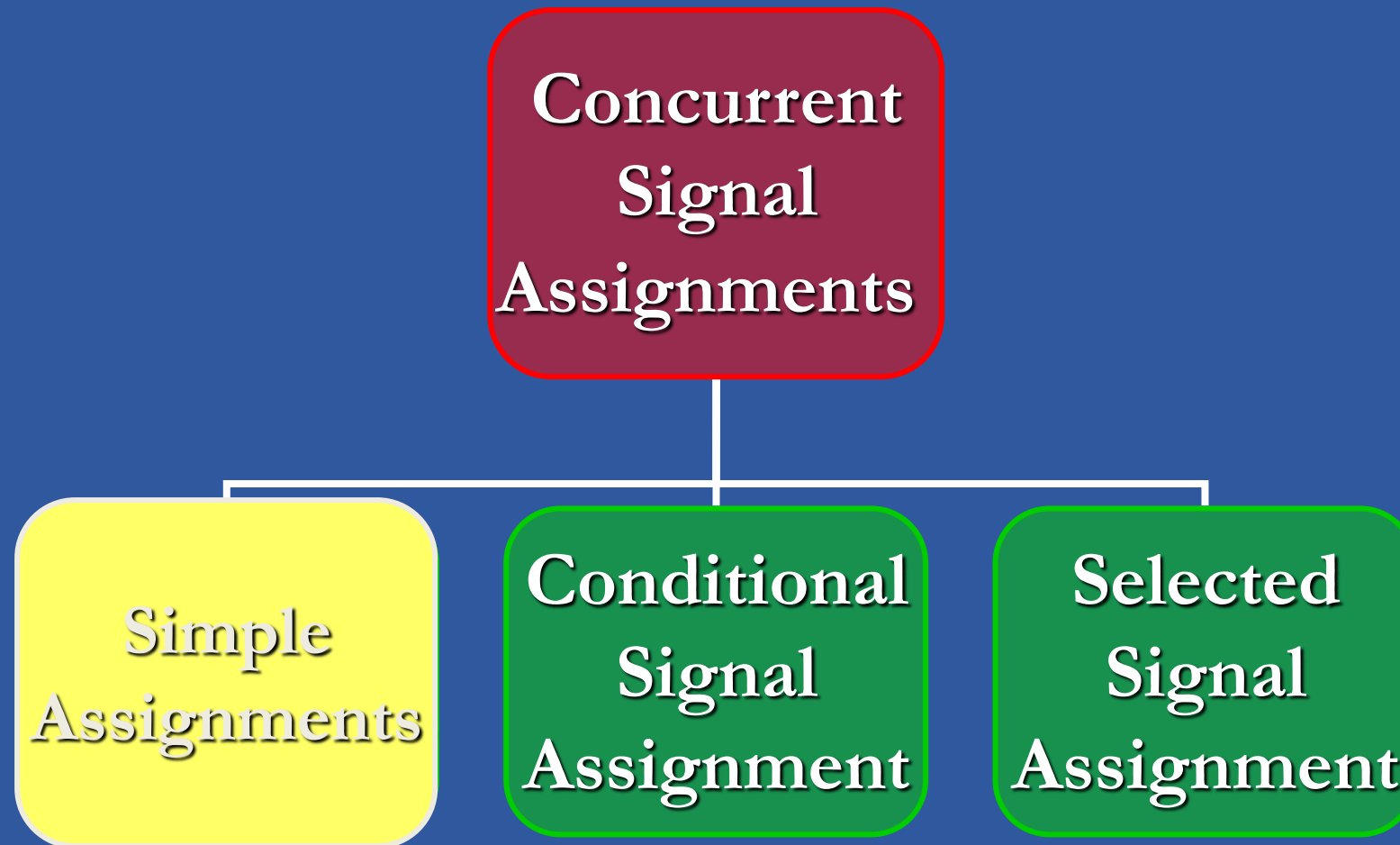


# Simple Assignments

```
ENTITY multiplexer IS
    PORT (a, b, s : IN BIT; w : OUT BIT);
END ENTITY;
--
ARCHITECTURE expression OF multiplexer IS
BEGIN
    w <= (a AND NOT s) OR (b AND s) AFTER 7 NS;
END ARCHITECTURE expression;
```


- Concurrent Signal Assignment

# Simple Assignments

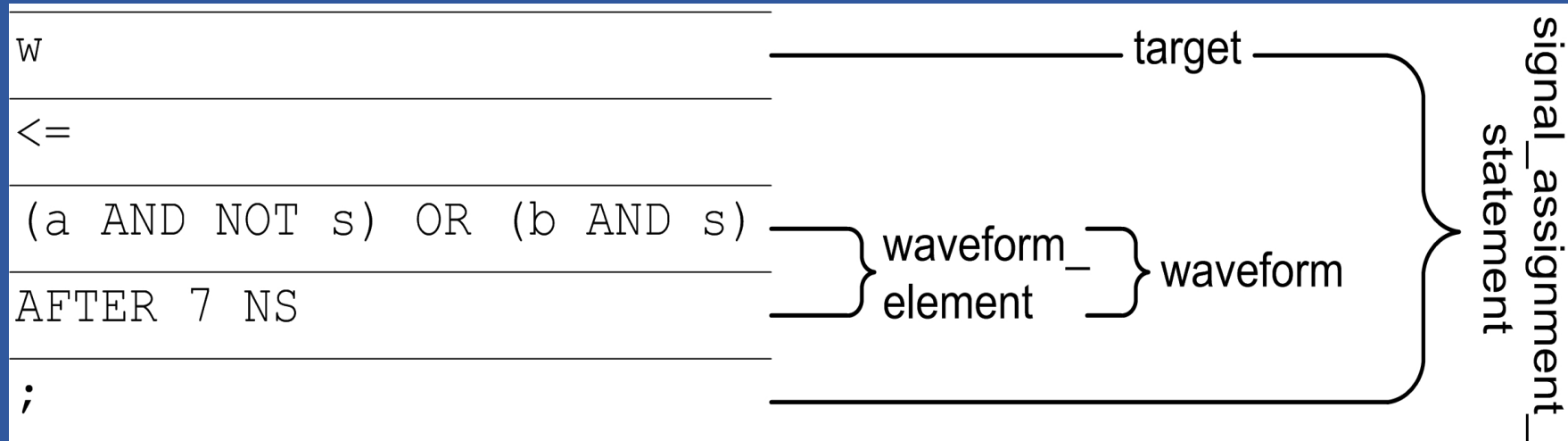

- **Signal Assignment Syntax Structure**

# Conditional Signal Assignment

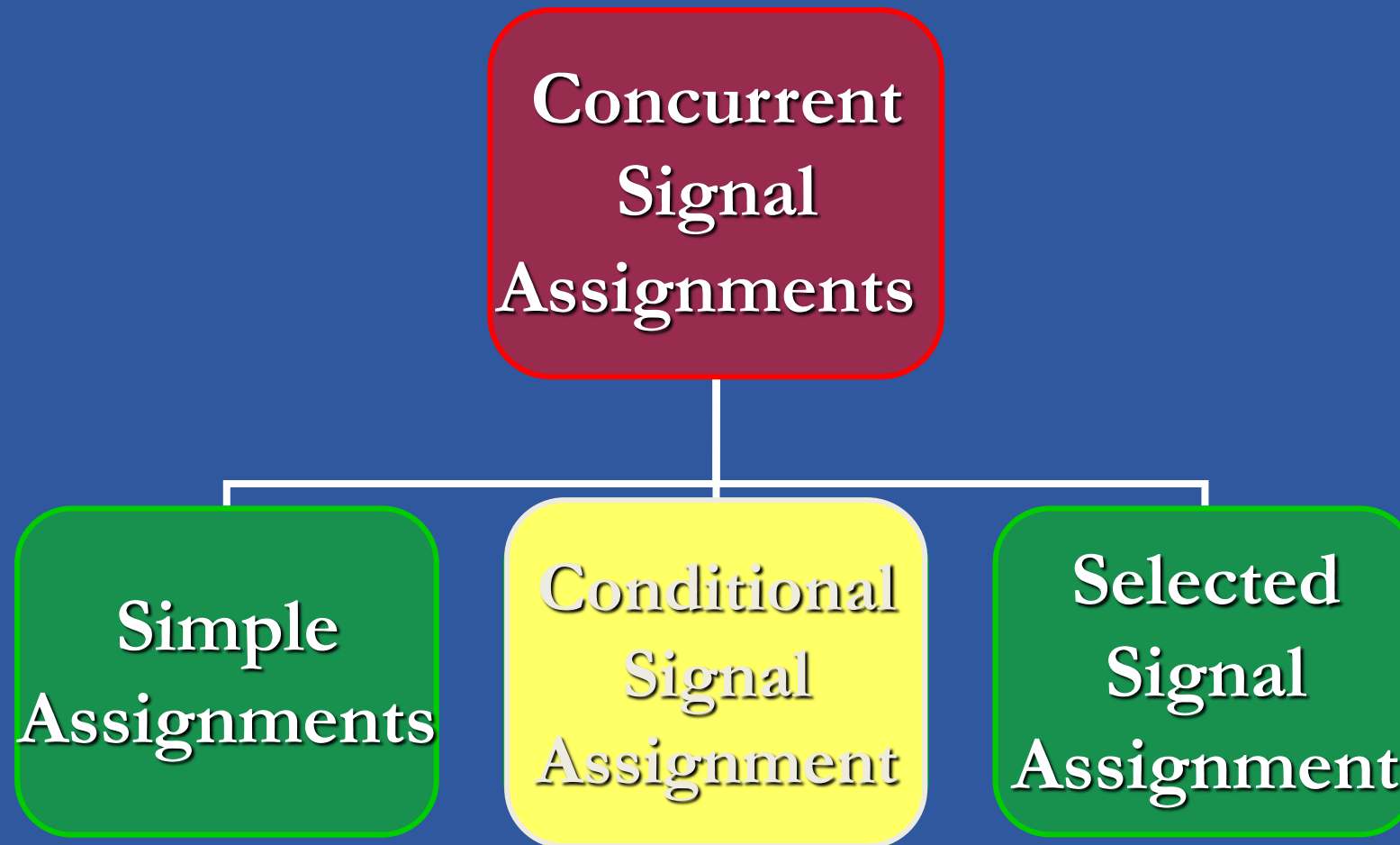


# Conditional Signal Assignment

```
ARCHITECTURE conditional OF multiplexer IS
BEGIN
    w <= a AFTER 7 NS WHEN s='0' ELSE
        b AFTER 8 NS;
END ARCHITECTURE conditional;
```

- Using Conditional Signal Assignment



# Conditional Signal Assignment

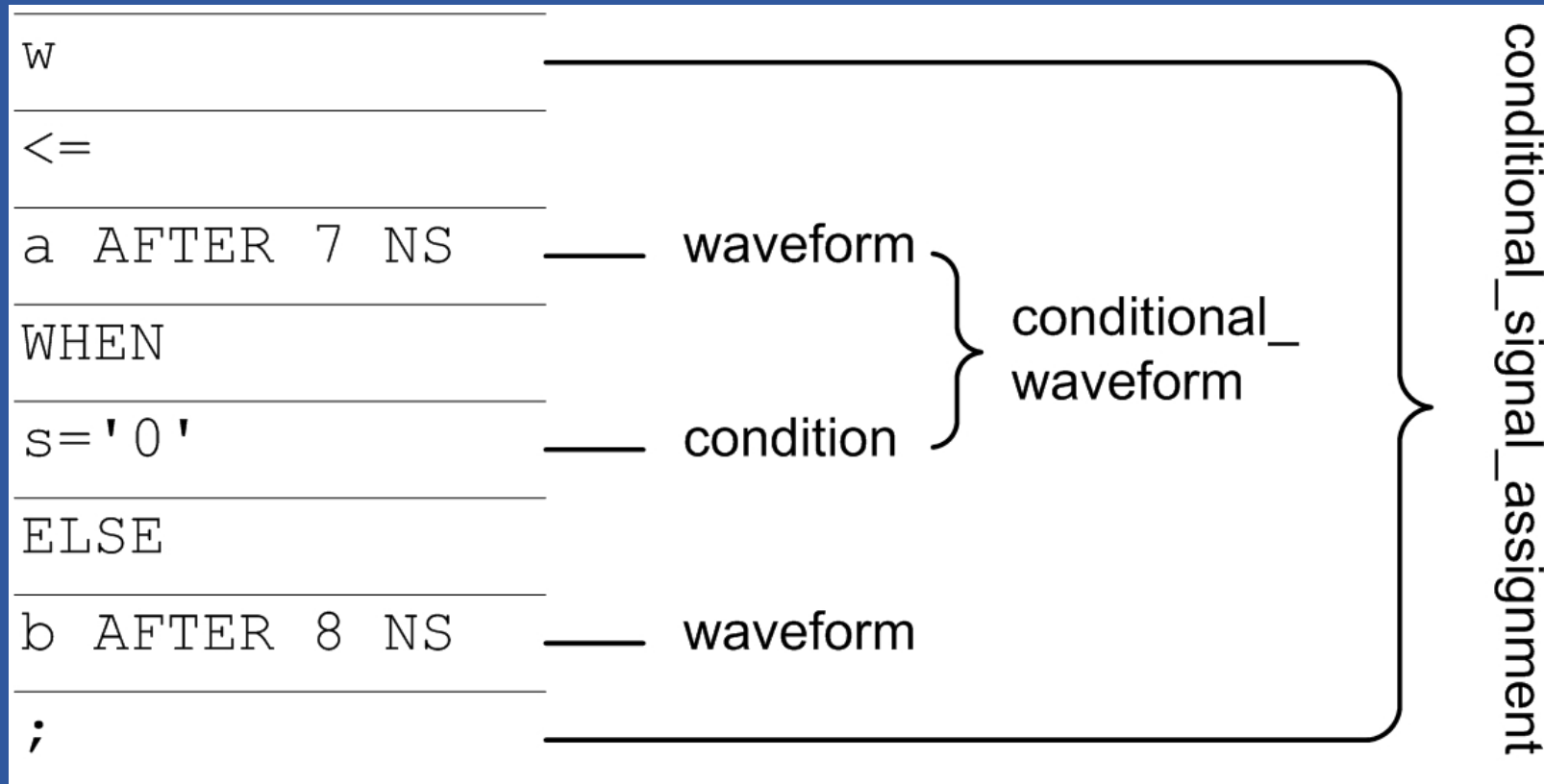

- **Syntax Structure of Conditional Signal Assignments**

# Conditional Signal Assignment

```
ENTITY flipflop IS
    PORT (reset, din, clk : IN BIT; qout : OUT BIT);
END ENTITY;
--
ARCHITECTURE async_reset OF flipflop IS
BEGIN
    qout <= '0' WHEN reset = '1' ELSE
           din WHEN clk'EVENT AND clk = '1';
END ARCHITECTURE async_reset;
```


- Flip-Flop Using Conditional Signal Assignment

# Conditional Signal Assignment

```
ENTITY latch IS
    PORT (din, clk : IN BIT; qout : OUT BIT);
END ENTITY;
--
ARCHITECTURE assign OF latch IS
BEGIN
    qout <= din WHEN clk = '1';
END ARCHITECTURE assign;
--
ARCHITECTURE unafect OF latch IS
BEGIN
    qout <= din WHEN clk='1' ELSE UNAFFECTED;
END ARCHITECTURE unafect;
```

- Conditional Signal Assignment Used in Latch Description

# Selected Signal Assignment

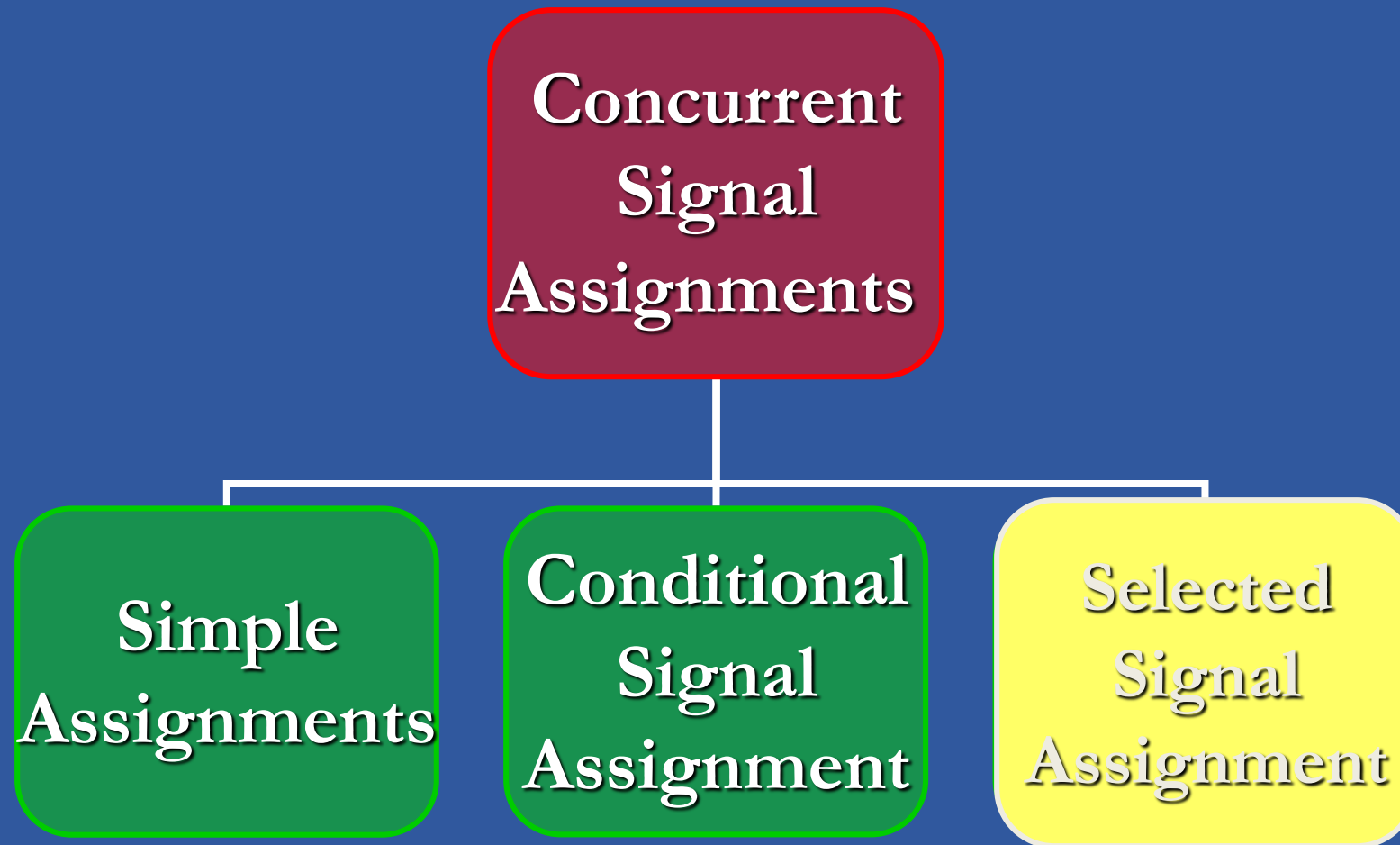

# Selected Signal Assignment

```
ENTITY binary3to8decoder IS
    PORT (bin_in : IN BIT_VECTOR (2 DOWNTO 0);
          en : IN BIT;
          dcd_ou : OUT BIT_VECTOR (0 TO 7));
END ENTITY binary3to8decoder;
--
ARCHITECTURE selected OF binary3to8decoder IS
    SIGNAL tmp : BIT_VECTOR(dcd_ou'RANGE);
    .....
    .....
    .....
```

- Using a Selected Signal Assignment

# Selected Signal Assignment

```
.....  
BEGIN
```

```
  WITH bin_in SELECT
```


```
    tmp <= "10000000" WHEN "000",  
          "01000000" WHEN "001",  
          "00100000" WHEN "010",  
          "00010000" WHEN "011",  
          "00001000" WHEN "100",  
          "00000100" WHEN "101",  
          "00000010" WHEN "110",  
          "00000001" WHEN "111";
```

```
    dcd_ou <= tmp WHEN en = '1' ELSE (OTHERS =>  
'0');
```

```
END ARCHITECTURE selected;
```

- Using a Selected Signal Assignment (Continued)

# Selected Signal Assignment

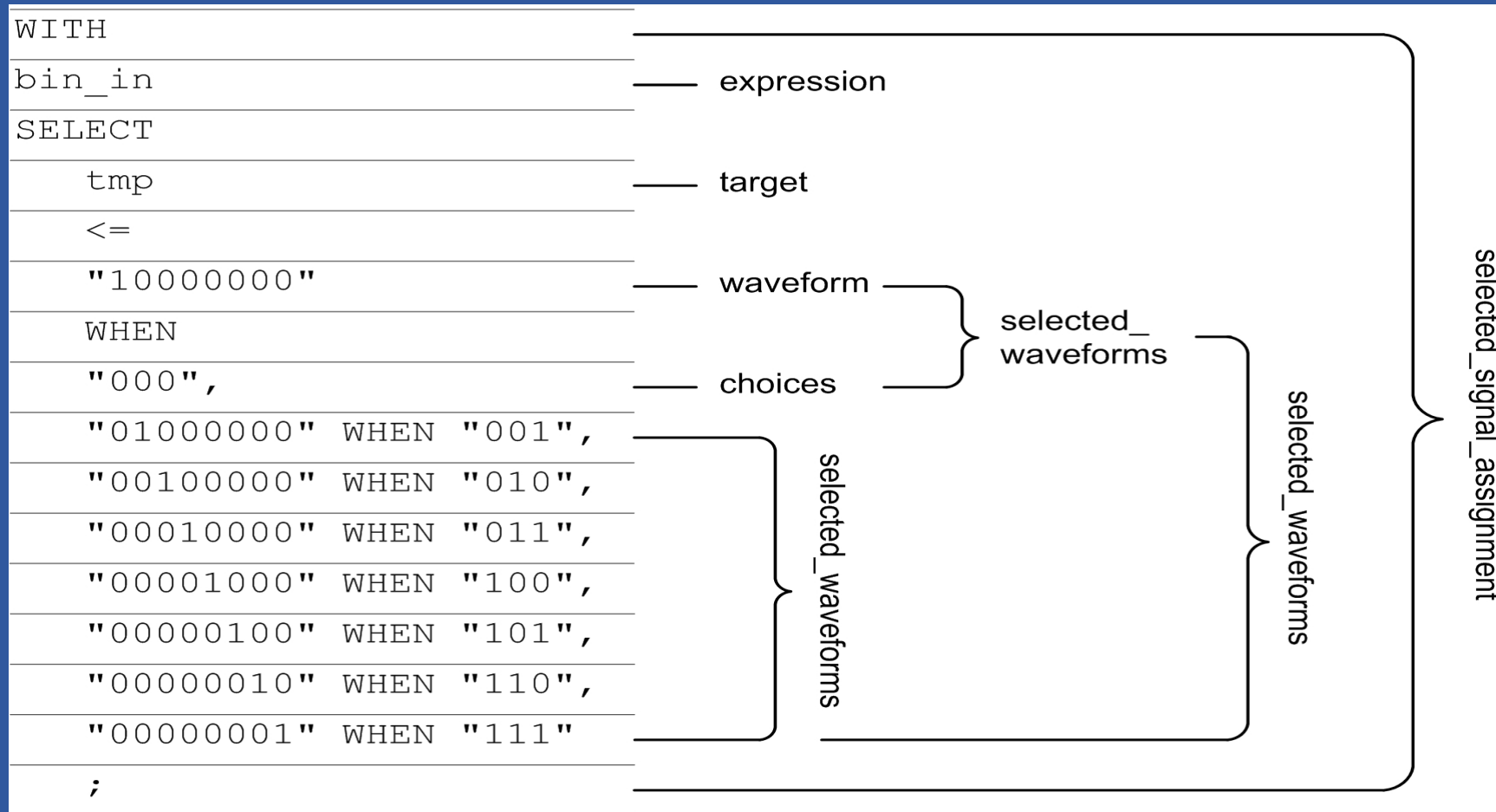

- **Syntax of Selected Signal Assignment**

# Selected Signal Assignment

```
ENTITY ssd IS
    PORT (bcd : IN BIT_VECTOR (3 DOWNTO 0);
          display : OUT BIT_VECTOR (1 TO 7));
END ENTITY;
--
.....
.....
.....
```

- Selected Signal Assignment with Others




# Selected Signal Assignment


```
ARCHITECTURE selected OF ssd IS
BEGIN
  WITH bcd SELECT
    display <= "1111110" WHEN "0000",
               "0110000" WHEN "0001",
               "1101101" WHEN "0010",
               "1111001" WHEN "0011",
               "0110011" WHEN "0100",
               "1101101" WHEN "0101",
               "1011111" WHEN "0110",
               "1110000" WHEN "0111",
               "1111111" WHEN "1000",
               "1111101" WHEN "1001",
               "1001111" WHEN OTHERS;
END ARCHITECTURE selected;
```

- Selected Signal Assignment with Others (Continued)

# Guarded Signal Assignments

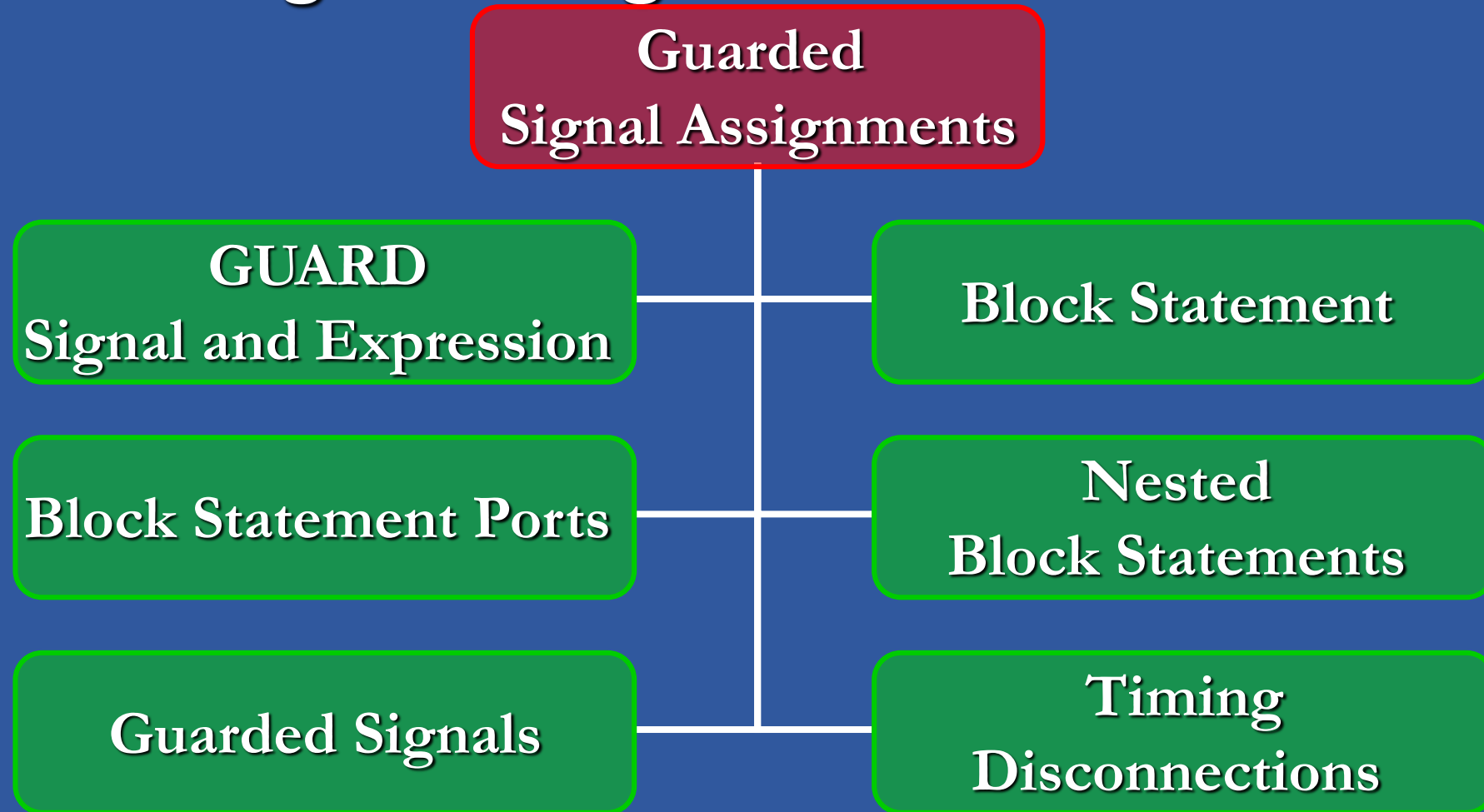

# GUARD Signal and Expression

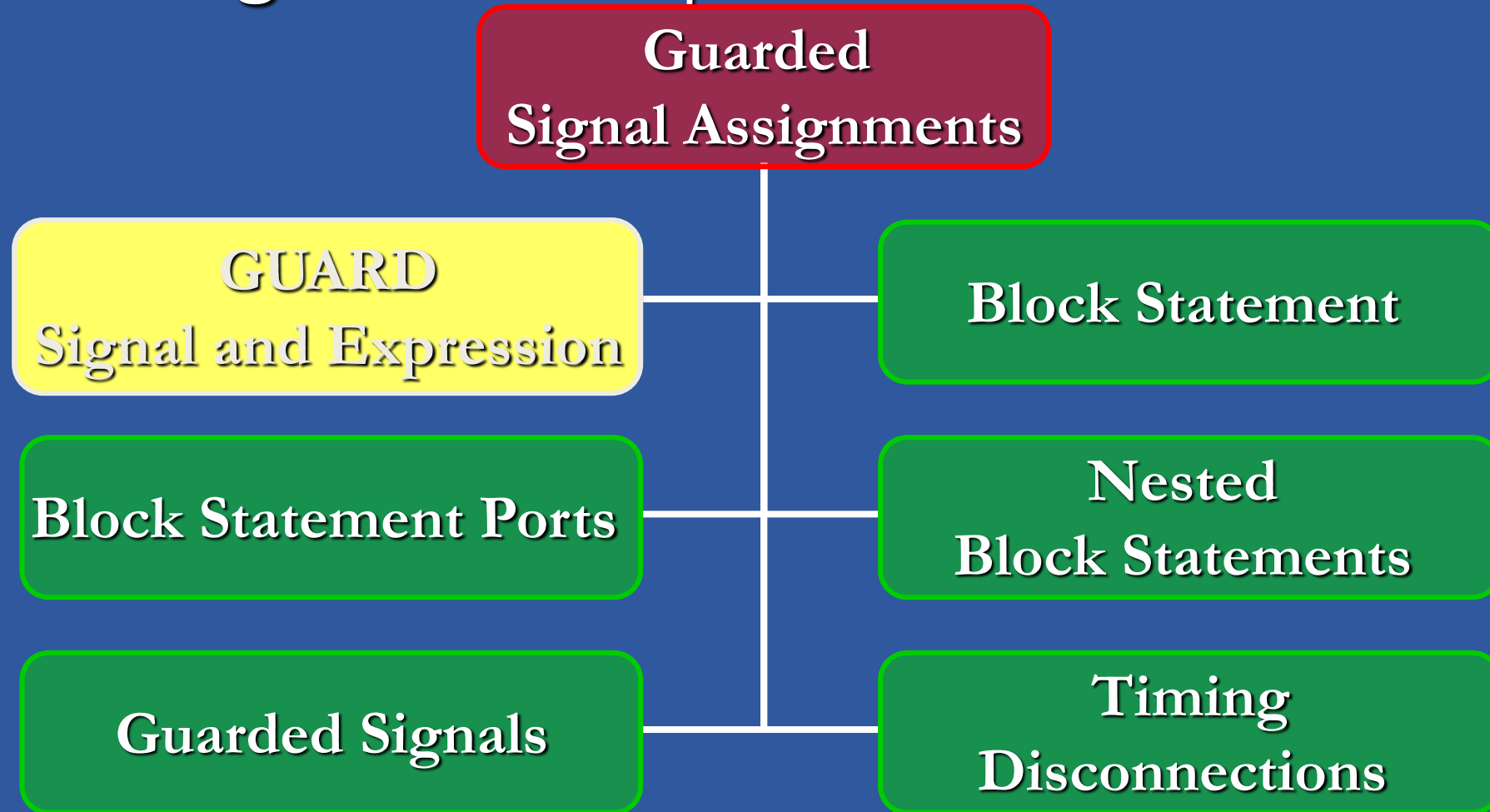


# GUARD Signal and Expression

```
ARCHITECTURE explicit OF flipflop IS
    SIGNAL GUARD : BOOLEAN;
BEGIN
    GUARD <= clk = '1' AND NOT clk'STABLE;
    qout <= GUARDED '0' WHEN reset = '1' ELSE din;
END ARCHITECTURE explicit;
```

- Explicit GUARD Signal

# Block Statement

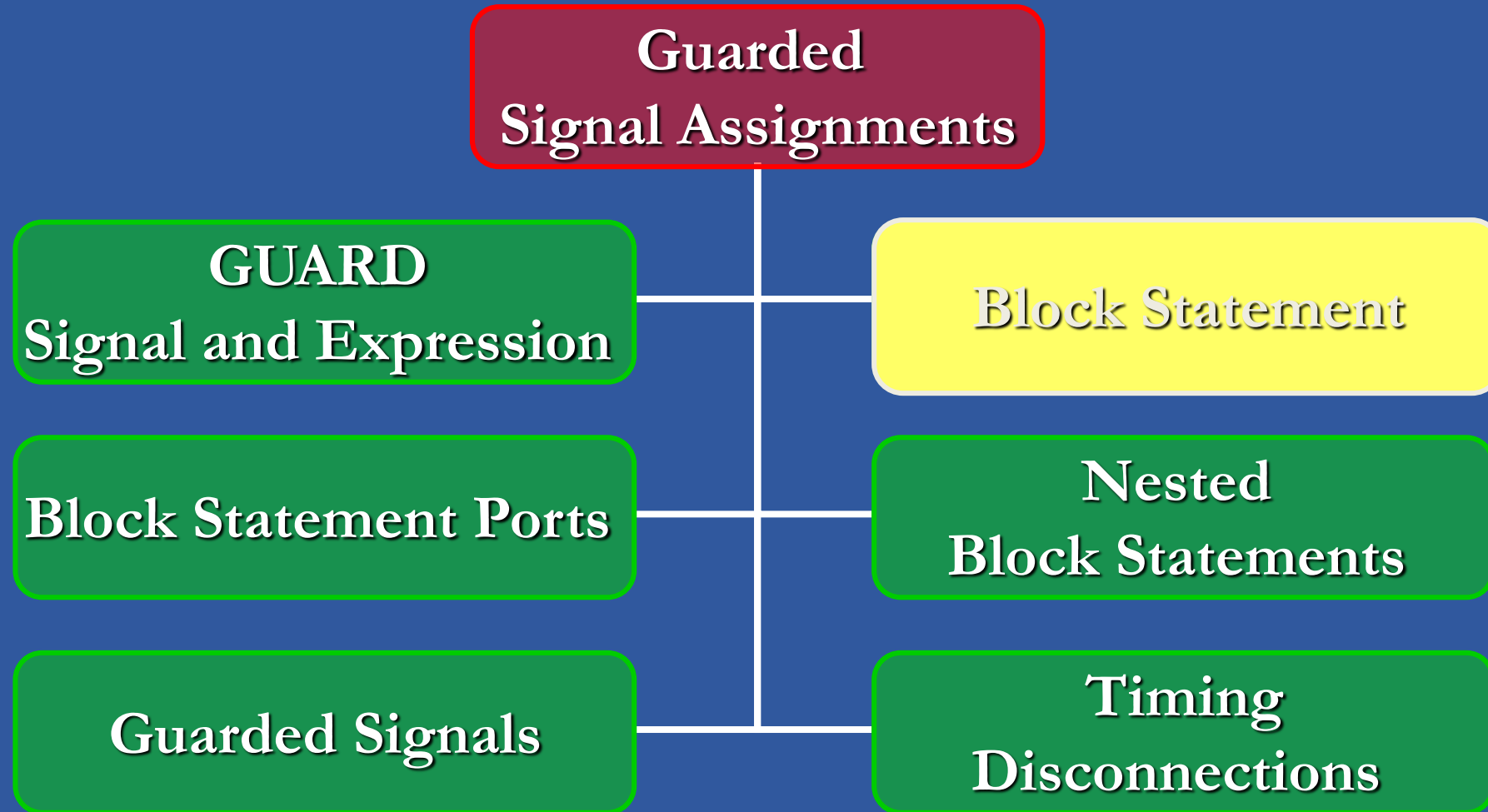


# Block Statement

```
ARCHITECTURE blocking OF flipflop IS
BEGIN
    reg: BLOCK (clk = '1' AND NOT clk'STABLE) BEGIN
        qout <= GUARDED '0' WHEN reset = '1'
            ELSE din;
    END BLOCK reg;
END ARCHITECTURE blocking;
```


- Block Statement with Guard Expression

# Block Statement

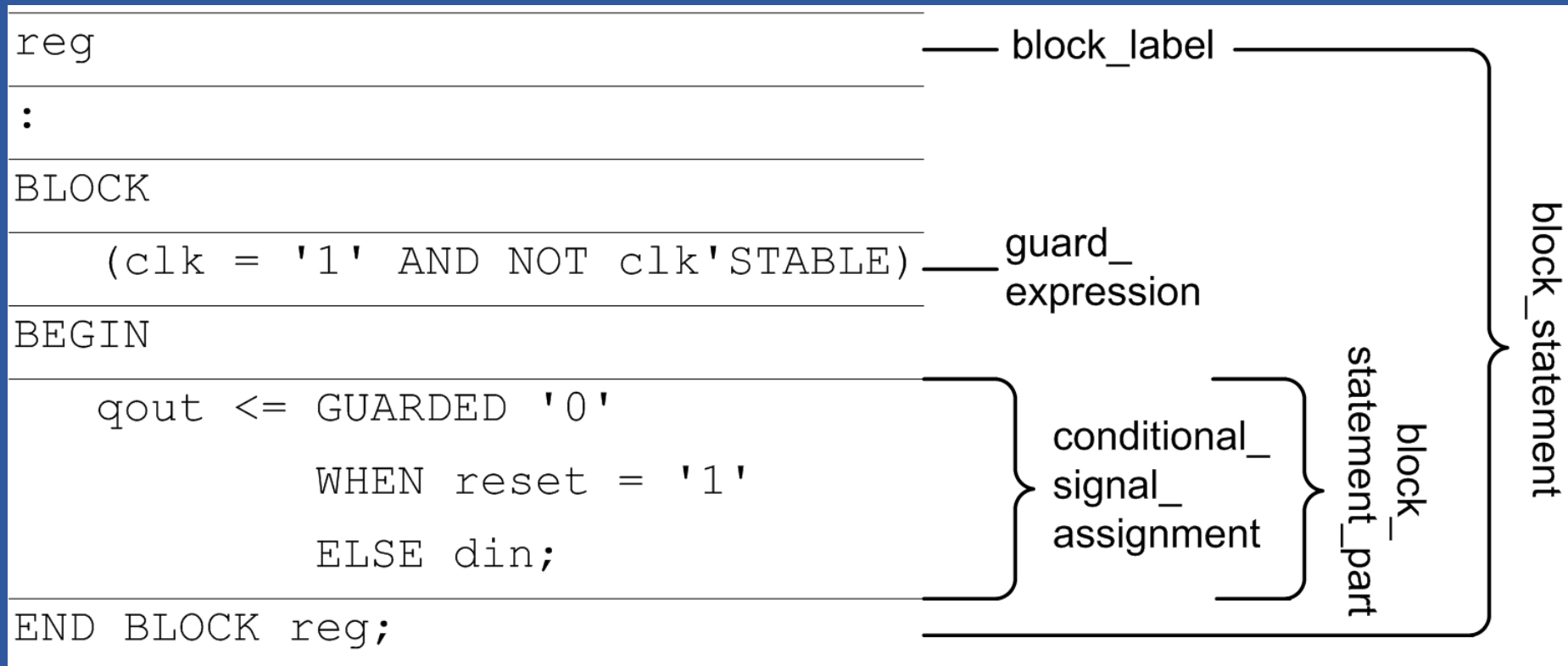

- **Block Statement Syntax**

# Block Statement Ports

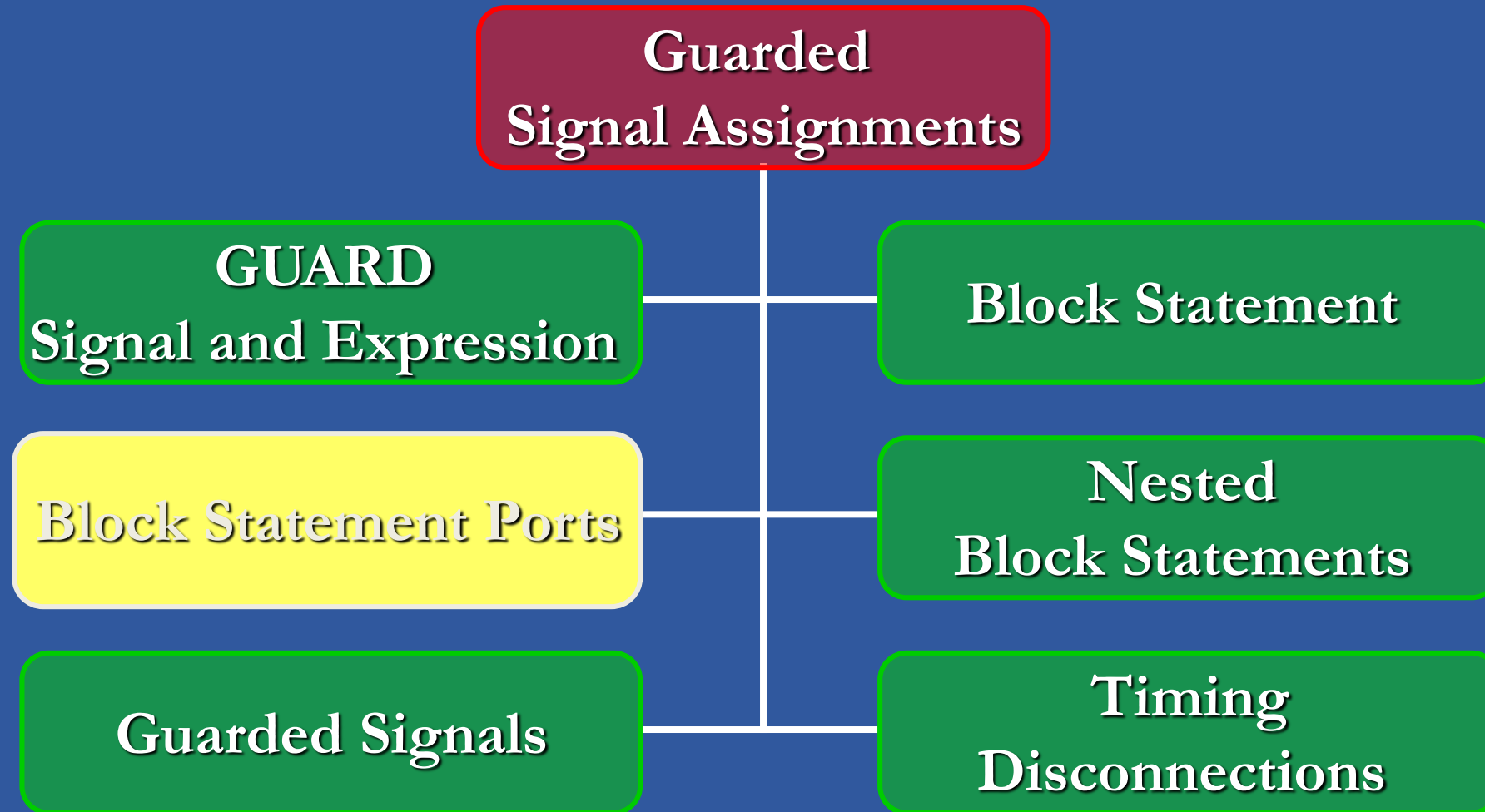




# Block Statement Ports

```
ARCHITECTURE blockport OF flipflop IS
BEGIN
  reg: BLOCK (clk = '1' AND NOT clk'STABLE) IS
    PORT (r, d, c : IN BIT; q : OUT BIT);
    PORT MAP (reset, din, clk, qout);
  BEGIN
    q <= GUARDED '0' WHEN r = '1' ELSE d;
  END BLOCK reg;
END ARCHITECTURE blockport;
```

- Block Statement with Ports

# Nested Block Statements

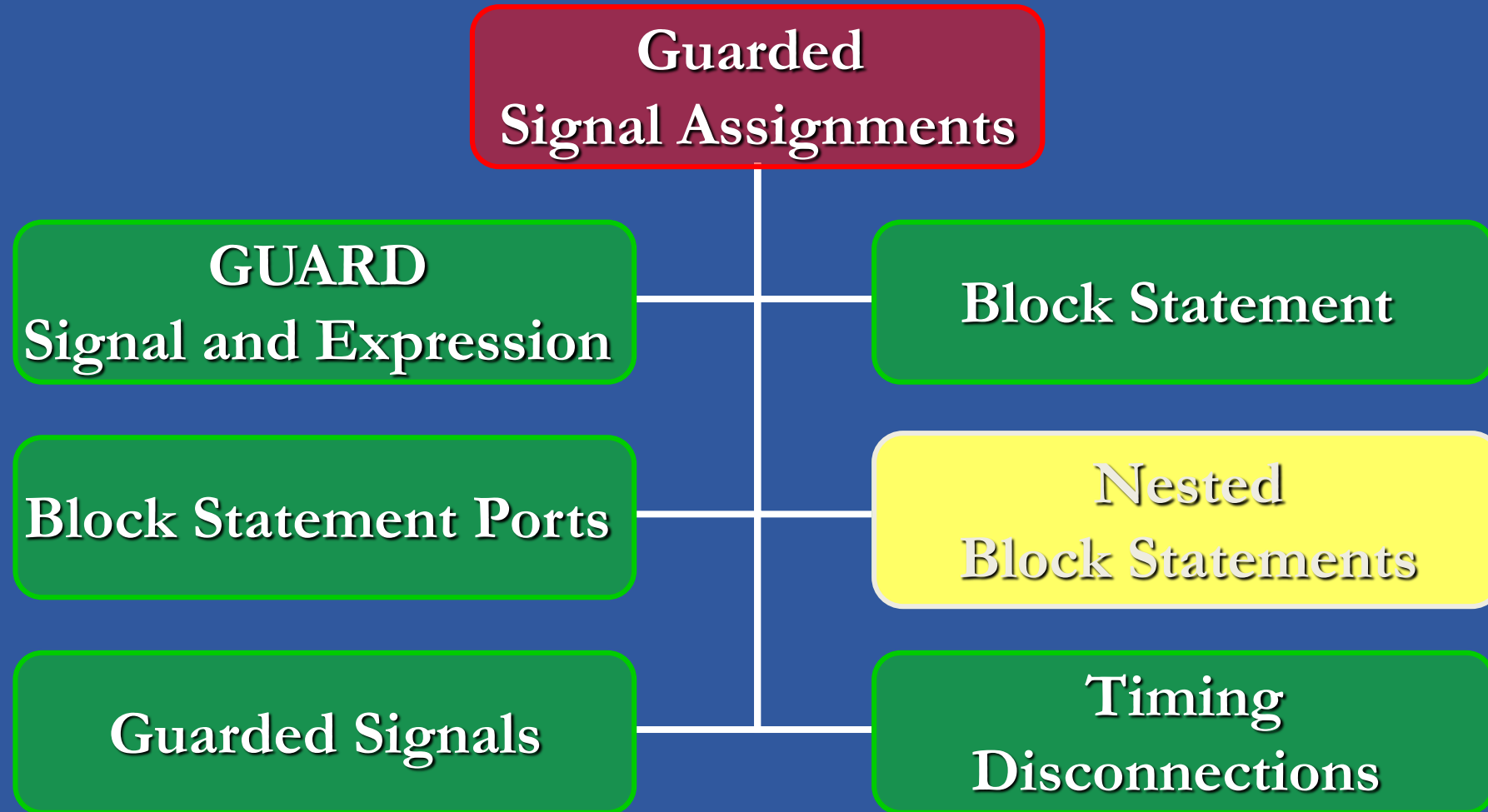


# Nested Block Statements


```
ENTITY latchflop IS
    PORT (din, clk : IN BIT; ql, qf : OUT BIT);
END ENTITY;
--
ARCHITECTURE nested OF latchflop IS
BEGIN
    lat: BLOCK (clk = '1') BEGIN
        ql <= GUARDED din;
        reg: BLOCK (GUARD AND NOT clk'STABLE) BEGIN
            qf <= GUARDED din;
        END BLOCK reg;
    END BLOCK lat;
END ARCHITECTURE nested;
```

- Nested Block Statements


# Guarded Signals

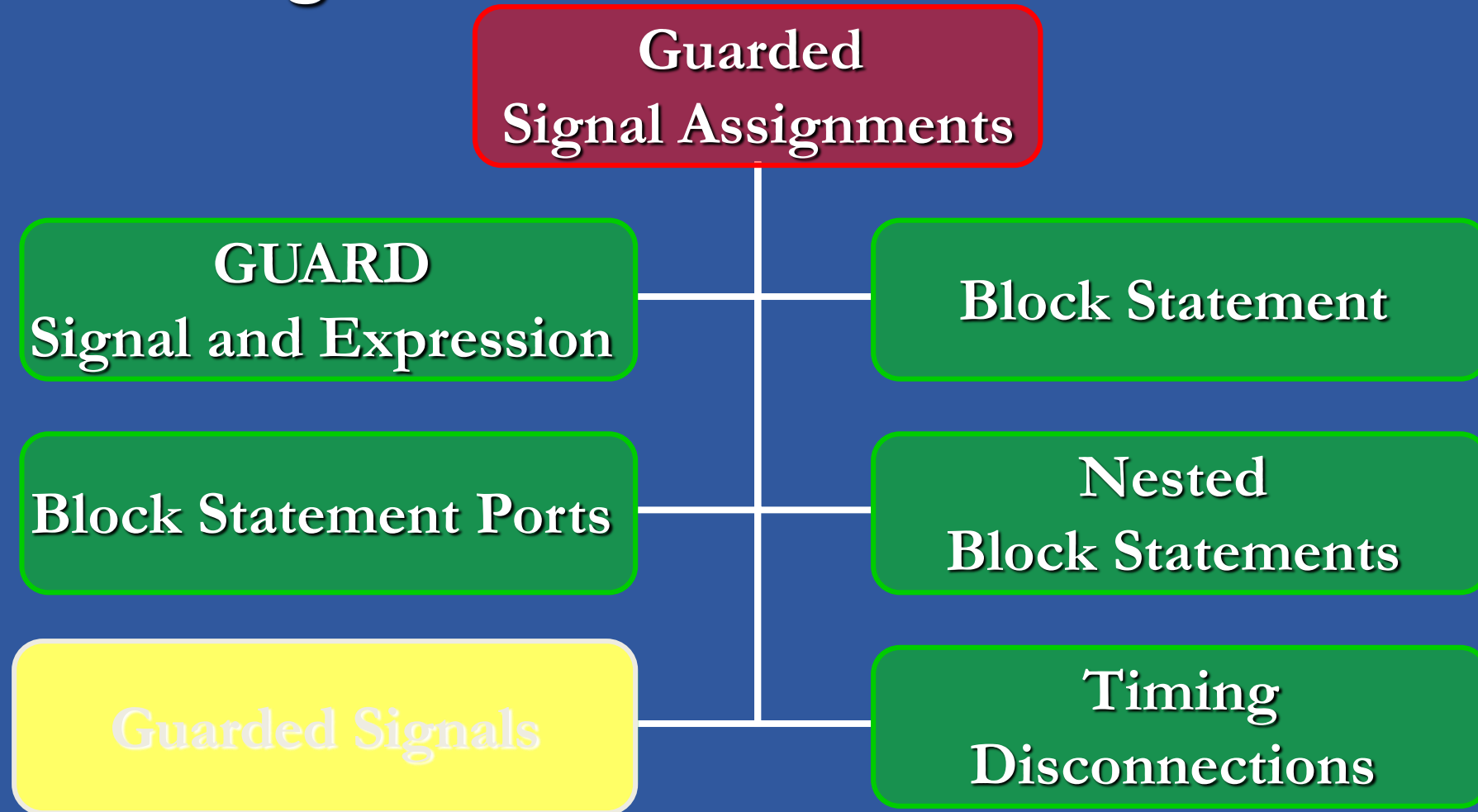

# Guarded Signals

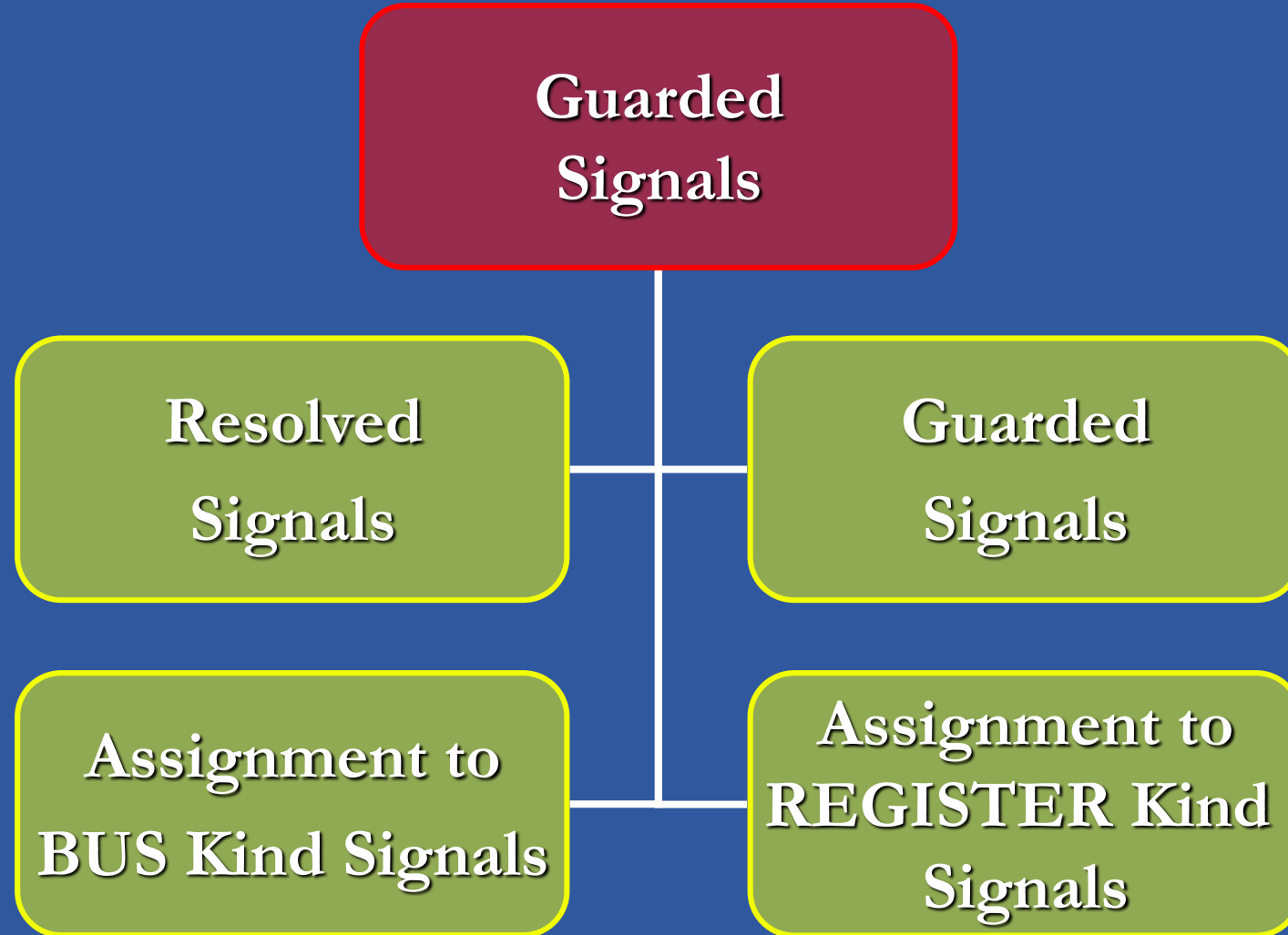


# Resolved Signals

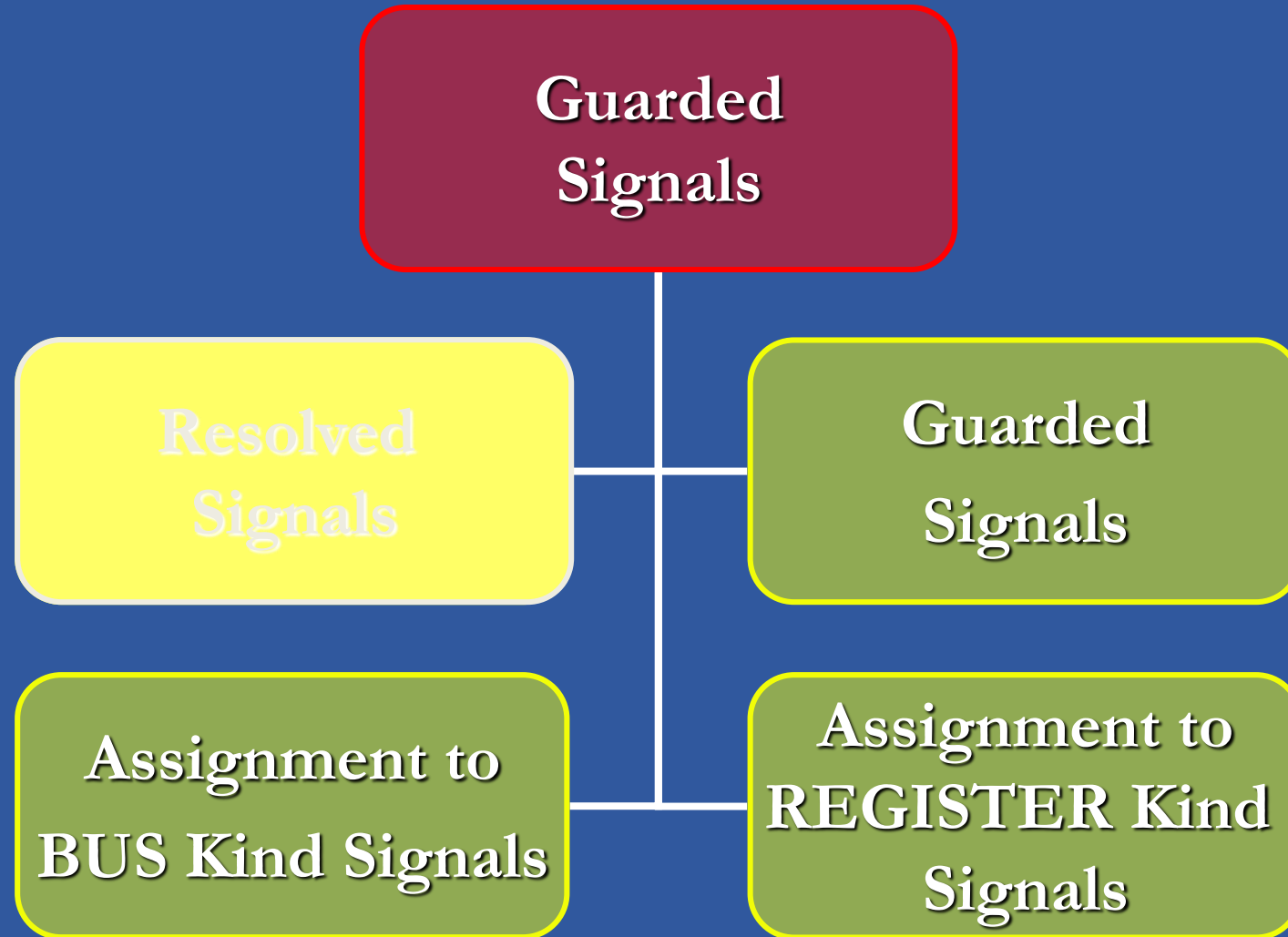

# Resolved Signals

- Resolved signals can have multiple concurrent drivers
- Associated with a resolved signal is a resolution function that resolves between multiple values assigned to a signal.
- VHDL predefined *std\_logic* resolved type
- Limiting the use of resolved signals to having only one concurrent driver.
- With a resolution function, there is a default resolved value:
  - Becomes the value of the resolved signal if the signal has no driver.
  - Defined by the resolution function and may be different from the default value of signal
  - The default resolved value for *std\_logic* type is 'Z'.

# Guarded Signals

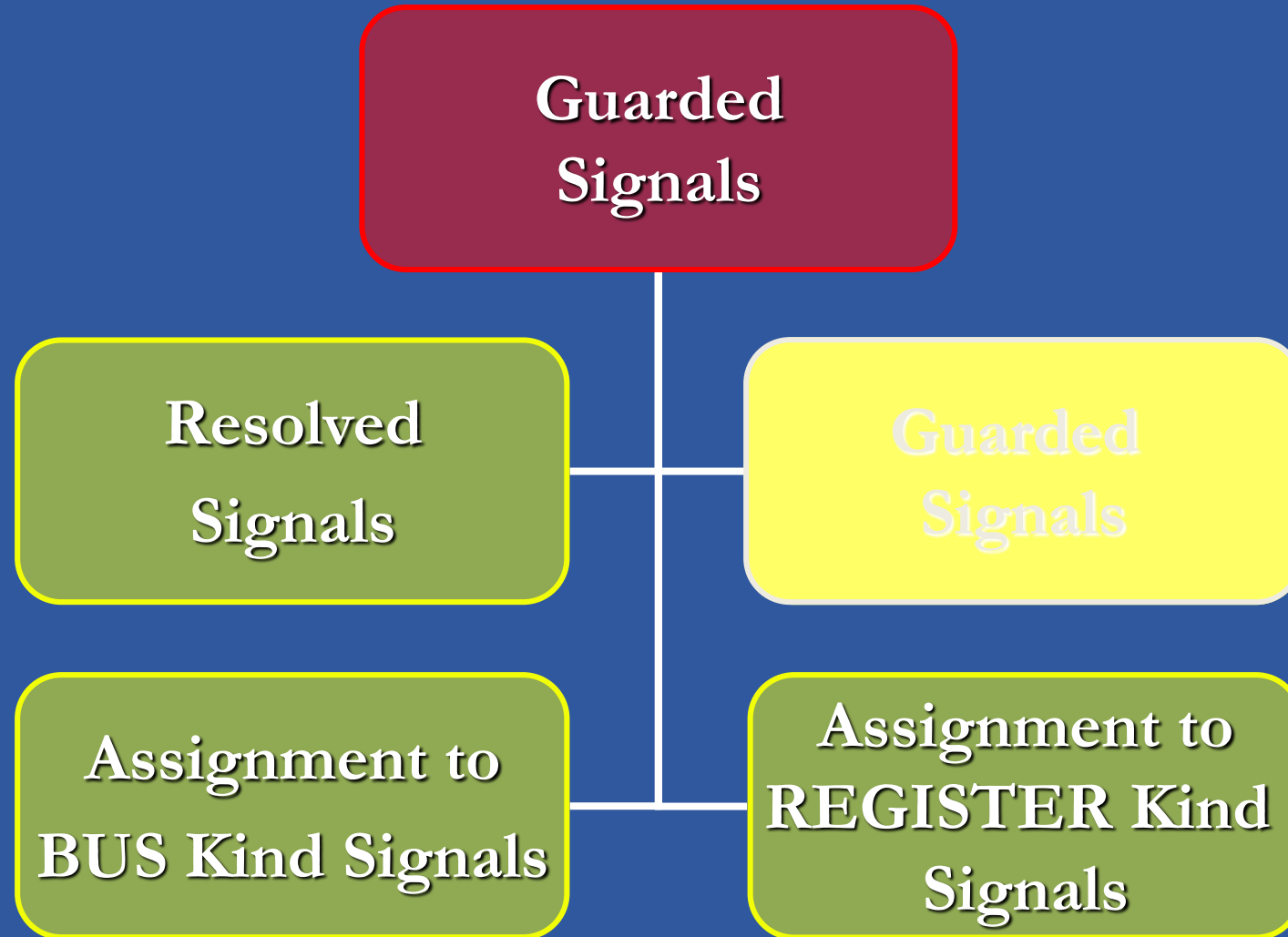




# Resolved Signals

- A resolved signal can be declared to have a kind.
- Kind specification follows the type mark of the resolved signal in its declaration.
- Kind of a signal can be
  - **BUS**
  - **REGISTER**
- If undriven or if a disconnection occurs:
  - A guarded signal of BUS kind receives its default resolved value
  - An undriven REGISTER kind guarded signal retains its old value (the value before disconnection).

# Assignment to BUS Kind Signals

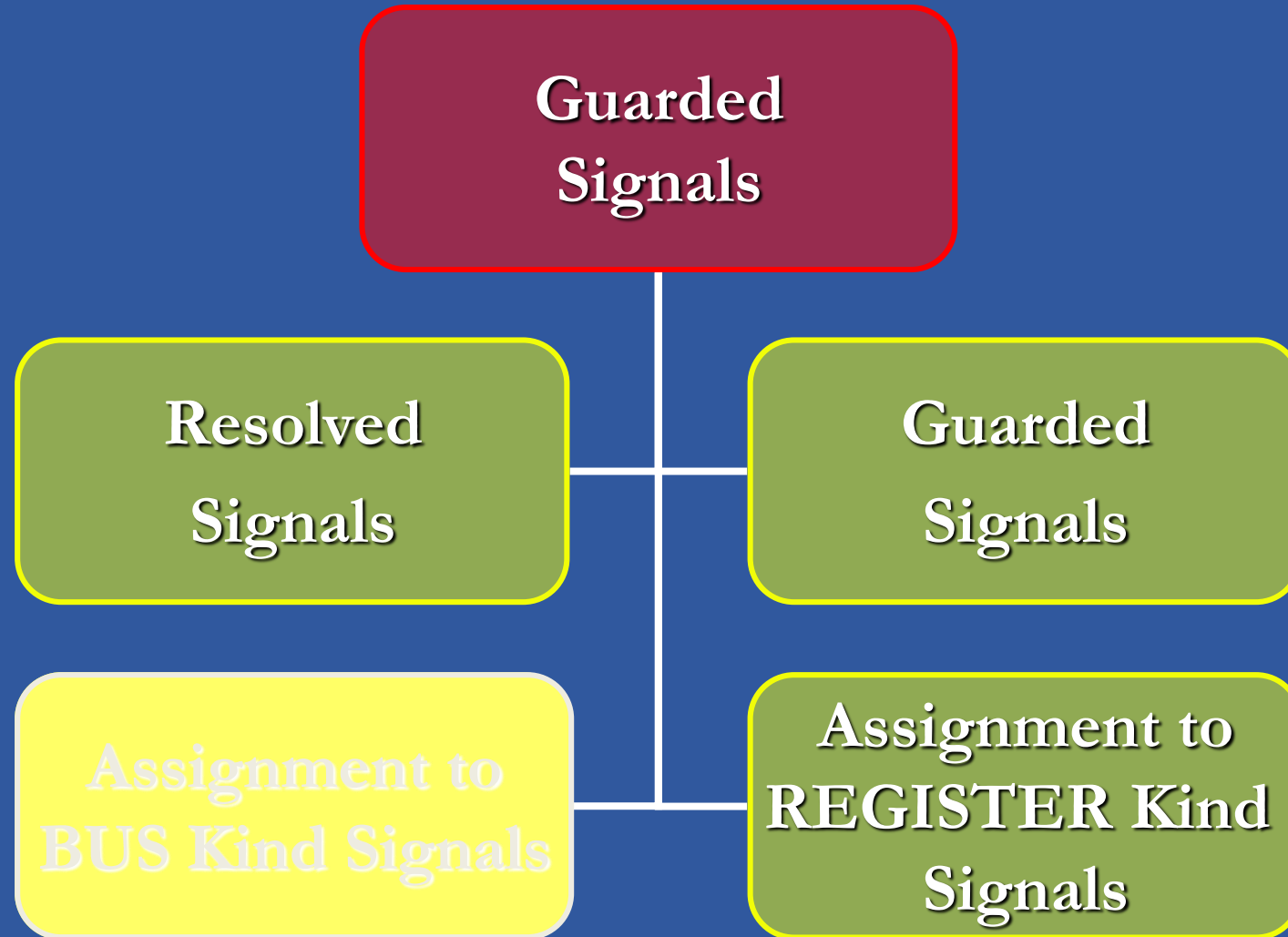


# Assignment to BUS Kind Signals

```
ENTITY multiplexer_en IS
    PORT (a, b, s, e : IN std_logic; w : OUT std_logic);
END ENTITY;
--
ARCHITECTURE blocking OF multiplexer_en IS
    SIGNAL t : std_logic BUS;
BEGIN
    tri: BLOCK (e='1') BEGIN
        t <= GUARDED (a AND NOT s) OR (b AND s);
        w <= t;
    END BLOCK tri;
END ARCHITECTURE blocking;
```


- BUS Kind Guarded Signal

# Assignment to BUS Kind Signals

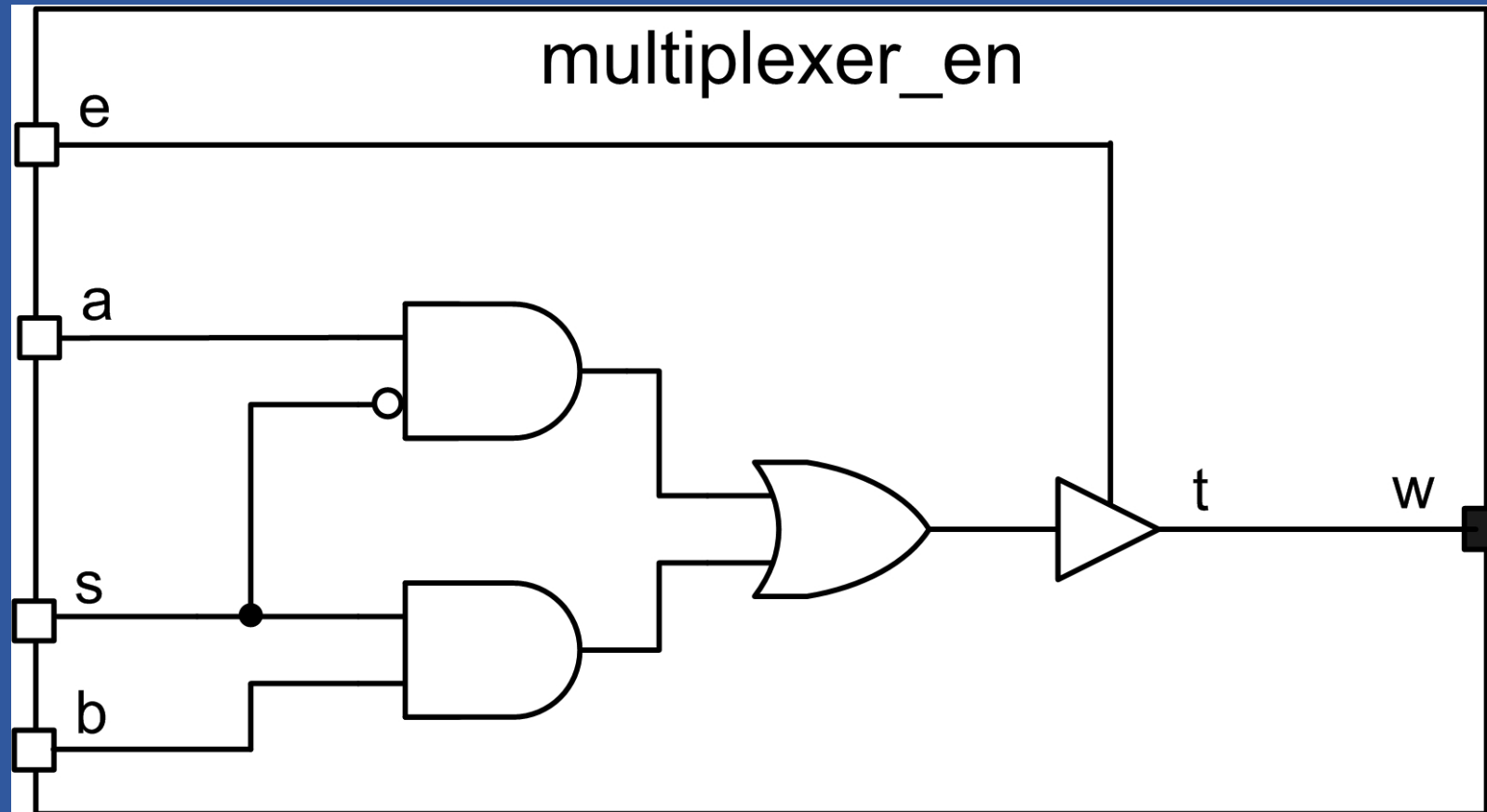

- Hardware Corresponding to *multiplexer\_en*

# Assignment to REGISTER Kind Signals

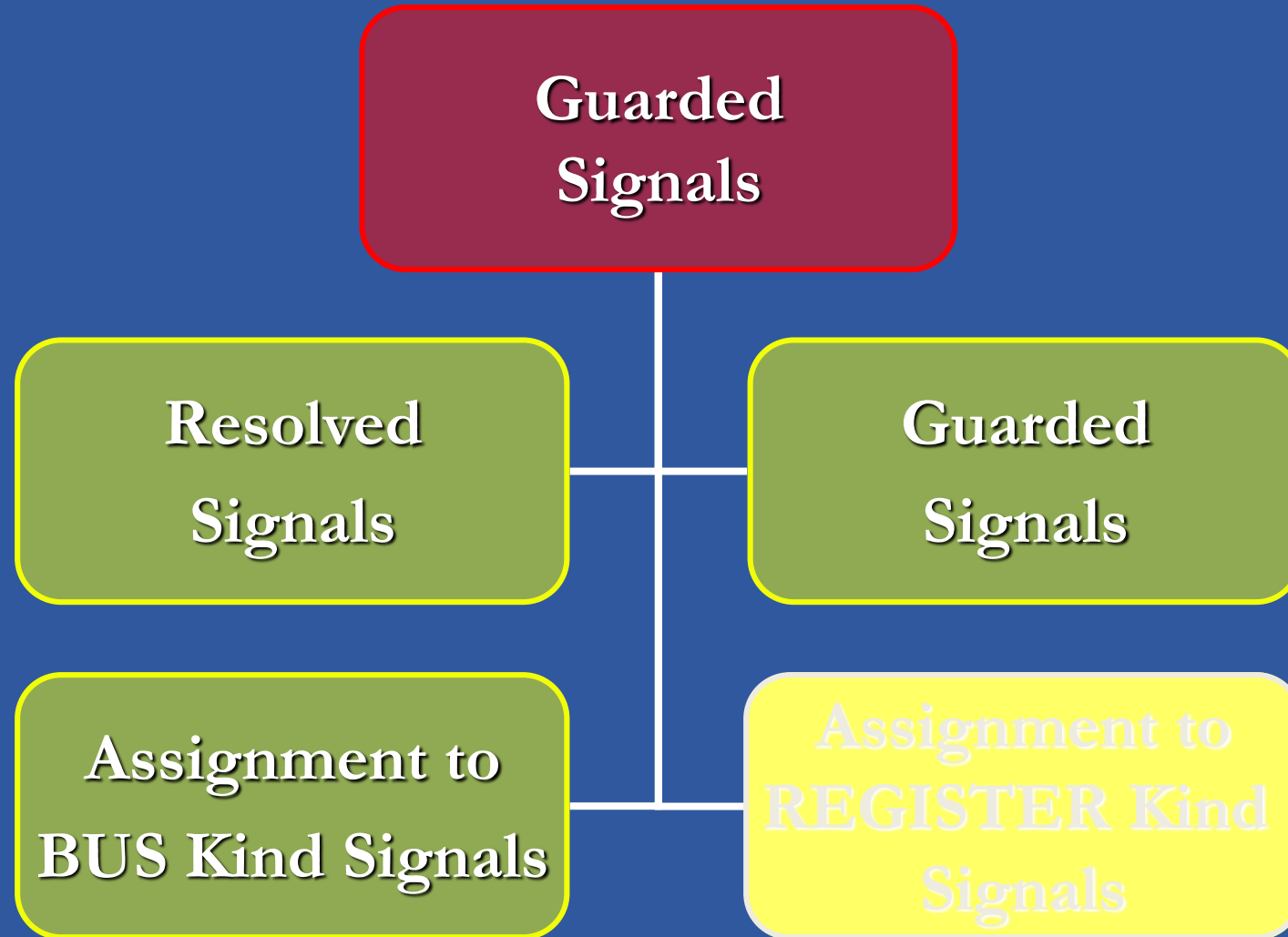


# Assignment to REGISTER Kind Signals

```
LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
ENTITY stdflop IS
    PORT (reset, din, clk, cen : IN std_logic:= '0';
          qout : OUT std_logic);
END ENTITY;
--
ARCHITECTURE blockport OF stdflop IS BEGIN
    reg: BLOCK (clk = '1' AND NOT clk'STABLE)
        PORT (r, d, c : IN std_logic; q : OUT std_logic);
        PORT MAP (reset, din, clk, qout);
        SIGNAL ff : std_logic REGISTER;
    BEGIN
        ff <= GUARDED '0' WHEN r = '1' ELSE d;
        q <= ff;
    END BLOCK reg;
END ARCHITECTURE blockport;
```

- REGISTER Kind Guarded Signal

# Timing Disconnections

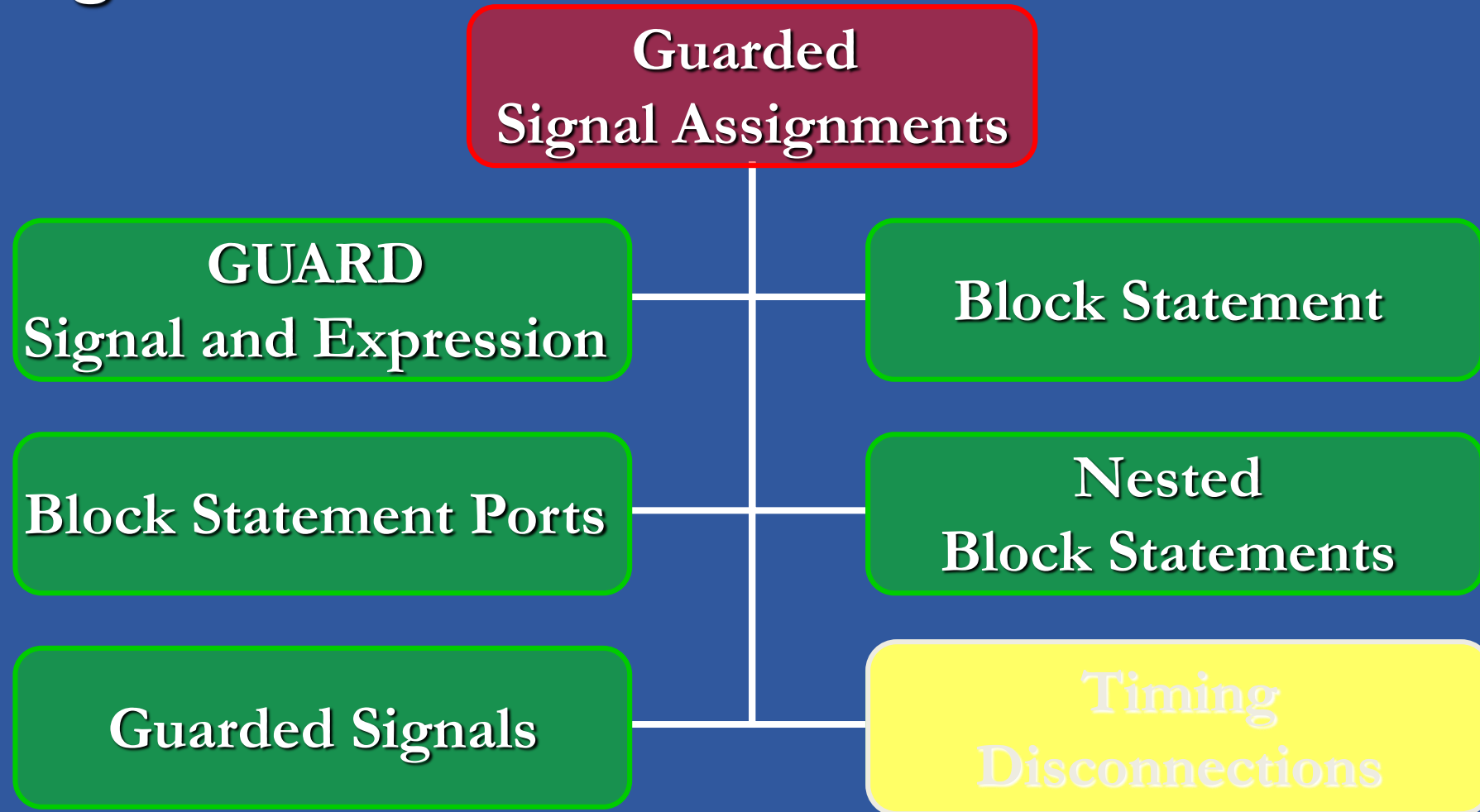

# Timing Disconnections

```
ARCHITECTURE timedisconnect OF multiplexer_en IS
    SIGNAL t : std_logic BUS;
    DISCONNECT t : std_logic AFTER 3.25 NS;
BEGIN
    tri: BLOCK (e='1') BEGIN
        t <= GUARDED (a AND NOT s) OR (b AND s);
        w <= t;
    END BLOCK tri;
END ARCHITECTURE timedisconnect;
```

- Multiplexer with Disconnect Time




# Timing Disconnections

```
ARCHITECTURE timed OF multiplexer_en_tester IS
    SIGNAL a, b, s, e, w1, w2 : std_logic;
BEGIN
    UUT1: ENTITY WORK.multiplexer_en (blocking)
        PORT MAP (a, b, s, e, w1);
    UUT2: ENTITY WORK.multiplexer_en (timedisconnect)
        PORT MAP (a, b, s, e, w2);
    a <= '0', '1' AFTER 20 NS, '0' AFTER 45 NS,
        '1' AFTER 71 NS;
    b <= '1', '0' AFTER 11 NS, '1' AFTER 37 NS,
        '0' AFTER 79 NS;
    s <= '0', '1' AFTER 29 NS, '0' AFTER 67 NS,
        '1' AFTER 97 NS;
    e <= '0', '1' AFTER 33 NS, '0' AFTER 83 NS,
        '1' AFTER 99 NS;
END ARCHITECTURE timed;
```


- Comparing Disconnection Timing

# Timing Disconnections

 

- **Comparing Disconnection Times**


# Timing Disconnections

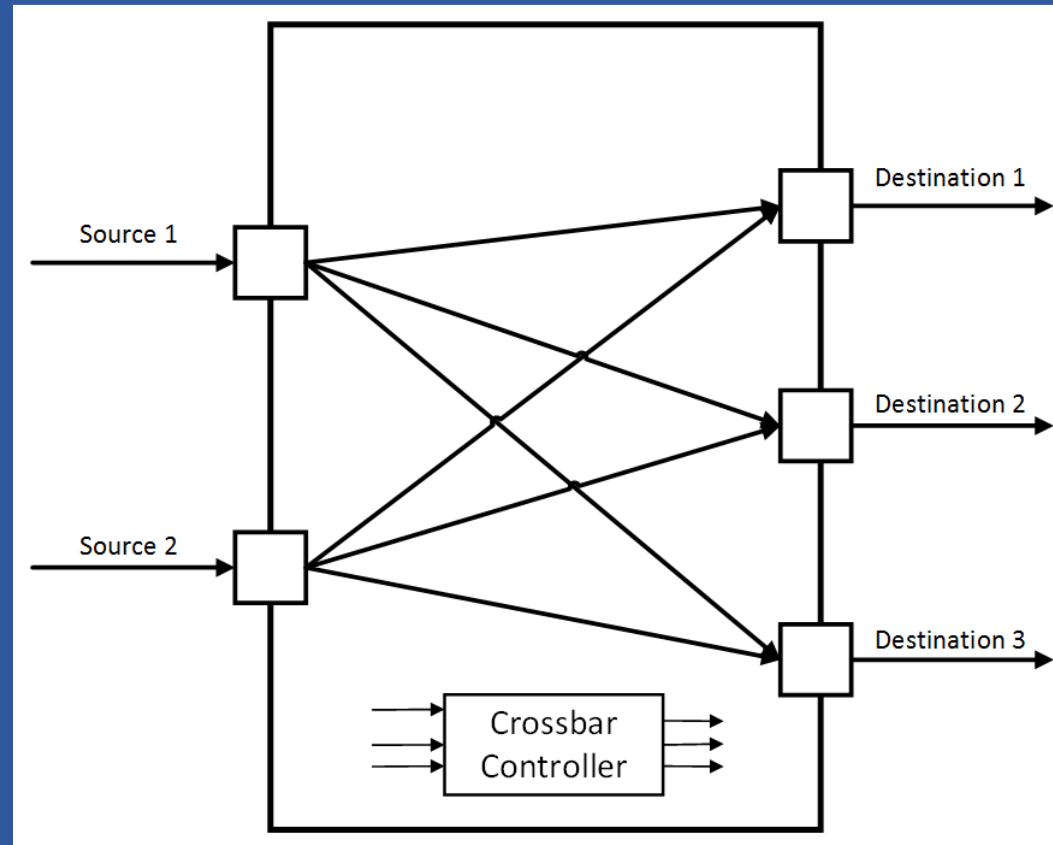

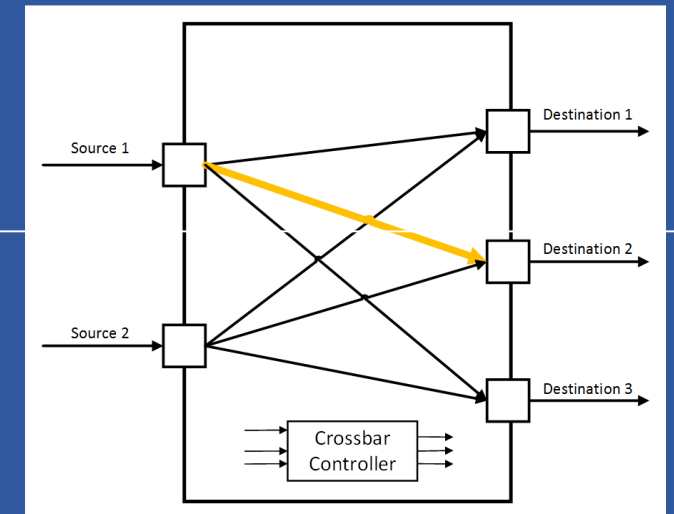
# Timing Disconnections

```
ARCHITECTURE timedisconnect OF crossbar IS
    SIGNAL s1d2: std_logic_vector(7 DOWNTO 0) BUS;
    DISCONNECT s1d2: std_logic_vector(7 DOWNTO 0) AFTER 3.25 NS;
    ...
BEGIN
    tri: BLOCK (cont_en='1') BEGIN
        s1d2 <= GUARDED (s1turn AND s1tod2);
        d2 <= s1d2;
    ...
    END BLOCK tri;
END ARCHITECTURE timedisconnect;
```

- A crossbar connection with Disconnect Time



# Bus Connection

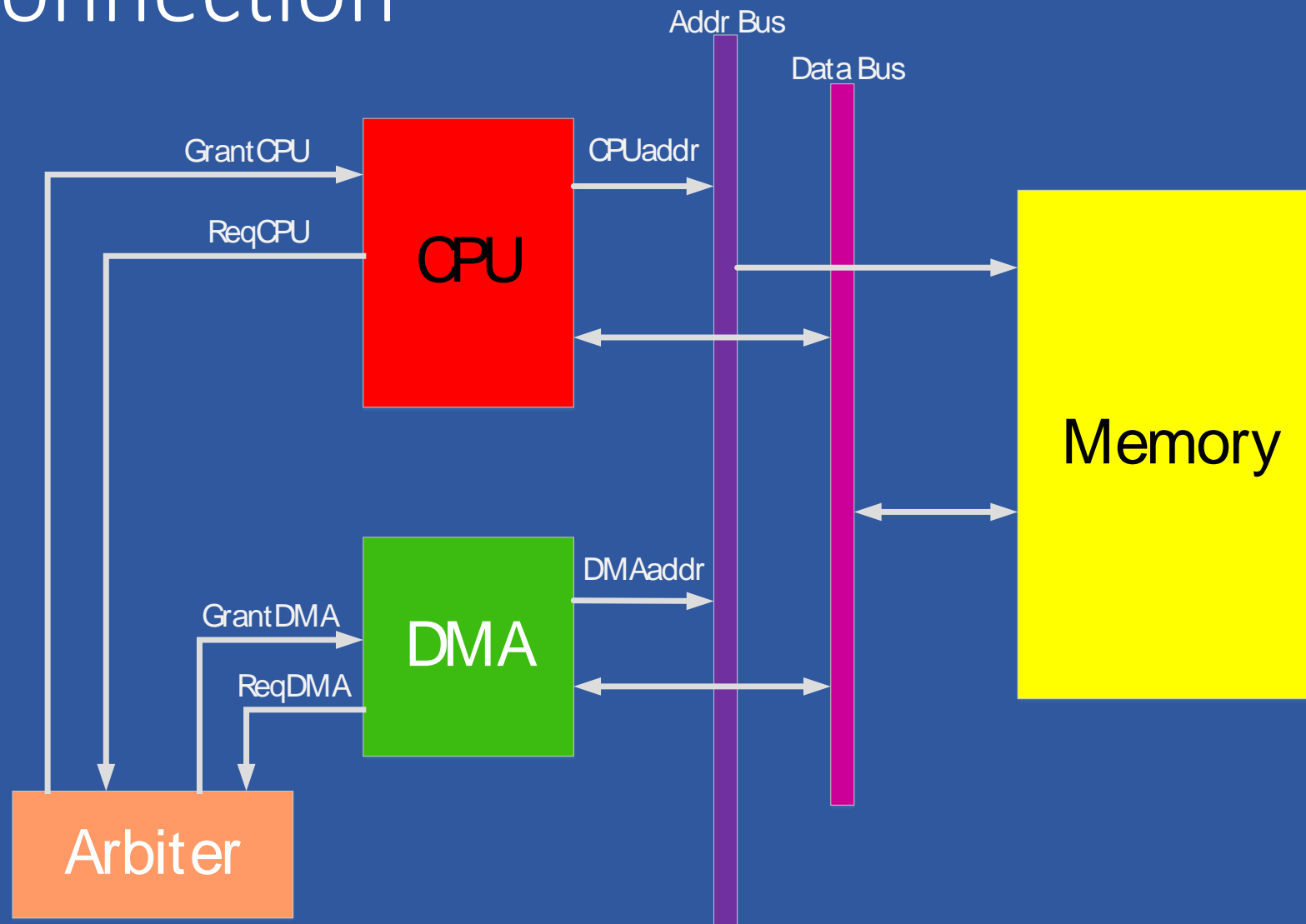

# Bus Connection

```
ARCHITECTURE Blocked OF DMA IS
BEGIN
    BLOCK (GrantDMA = '1') BEGIN
        addrBus <= GUARDED (DMAaddr);
    END BLOCK;

    PROCESS ( ... ) BEGIN
        ...
        WAIT FOR GrantDMA;
        ...
    END PROCESS;

END ARCHITECTURE Blocked;
```

# Bus Connection

```
ARCHITECTURE Blocked OF CPU IS
BEGIN
  addr: BLOCK (GrantCPU = '1')
  BEGIN
    addrBus <= GUARDED (CPUaddr);
  END BLOCK addr;

  ...

  data: BLOCK (GrantCPU = '1' AND W_Mem = '1')
  BEGIN
    dataBus <= GUARDED (CPUdata);
  END BLOCK data;

  ...
END ARCHITECTURE Blocked;
```

# Summary

- **The focus of this chapter was on**
  - **Concurrent bodies of VHDL**
  - **Signal assignments**
  - **Block statements**
  - **Guarded signals and guarded assignments**
- **The constructs discussed here enable description of hardware at a level higher than what was discussed in the previous chapter.**
- **For more behavioral descriptions VHDL offers sequential statements within concurrent bodies that will be discussed in the next chapter.**



# Acknowledgment

Slides developed by:

Homa Alemzadeh

First revision 2017 by:

Bahar Behazin

Second revision 2019 by:

Saba Yousefzadeh