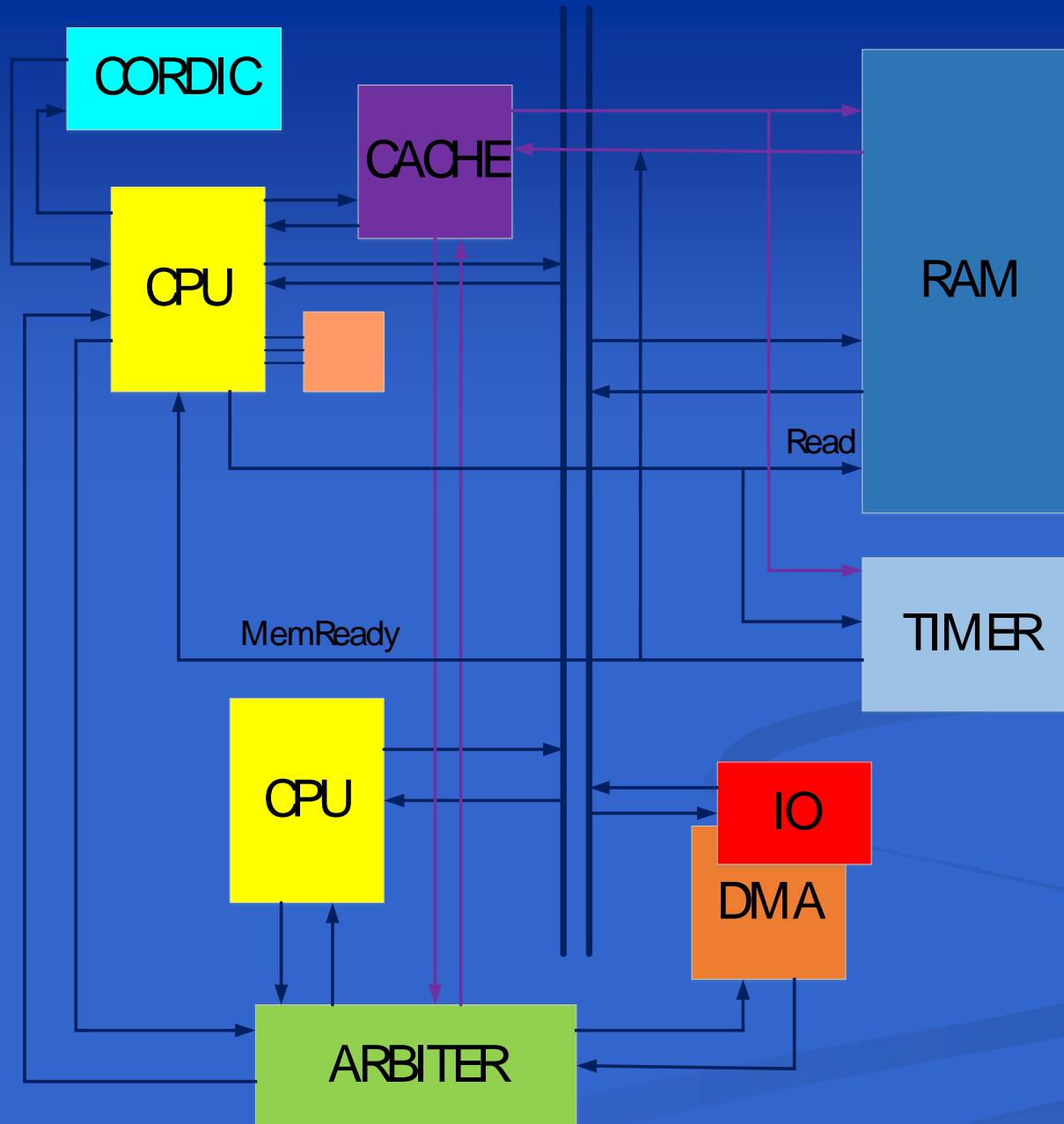


Chapter 8


Hardware Cores and Models

Hardware Cores and Models


- 8.1 Memory and Queue Structures
 - 8.2.1 Generic RAM Core
 - 8.2.2 Synthesizable Push-Pop Stack
 - 8.2.3 Synthesizable Circular FIFO
 - 8.2.4 Dynamic Access Type FIFO
- 8.2 Arithmetic Cores
- 8.3 Components with Separate Control and Data Parts
 - 8.4.1 Sequential Multiplier
 - 8.4.2 von Neumann Computer Model
- 8.4 Summary



Memory and Queue Structures

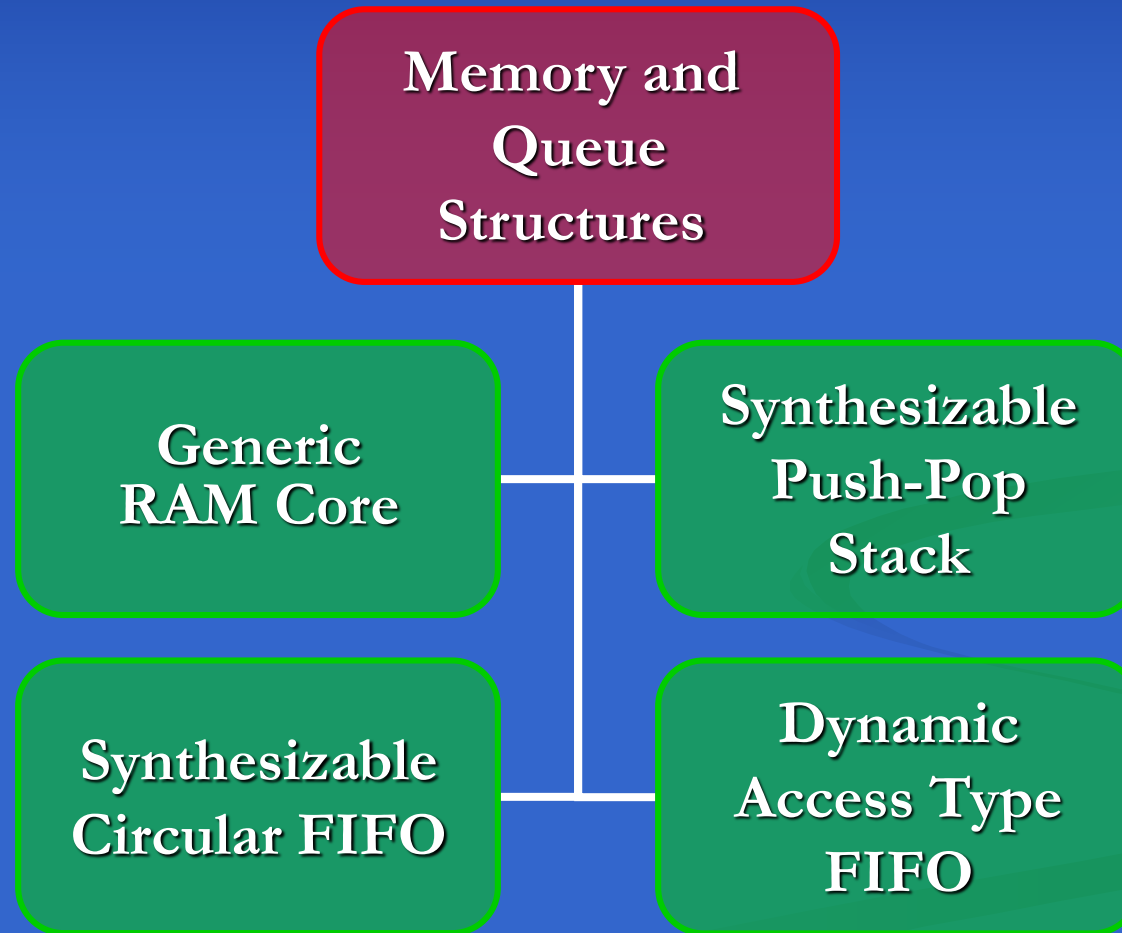

Generic RAM Core

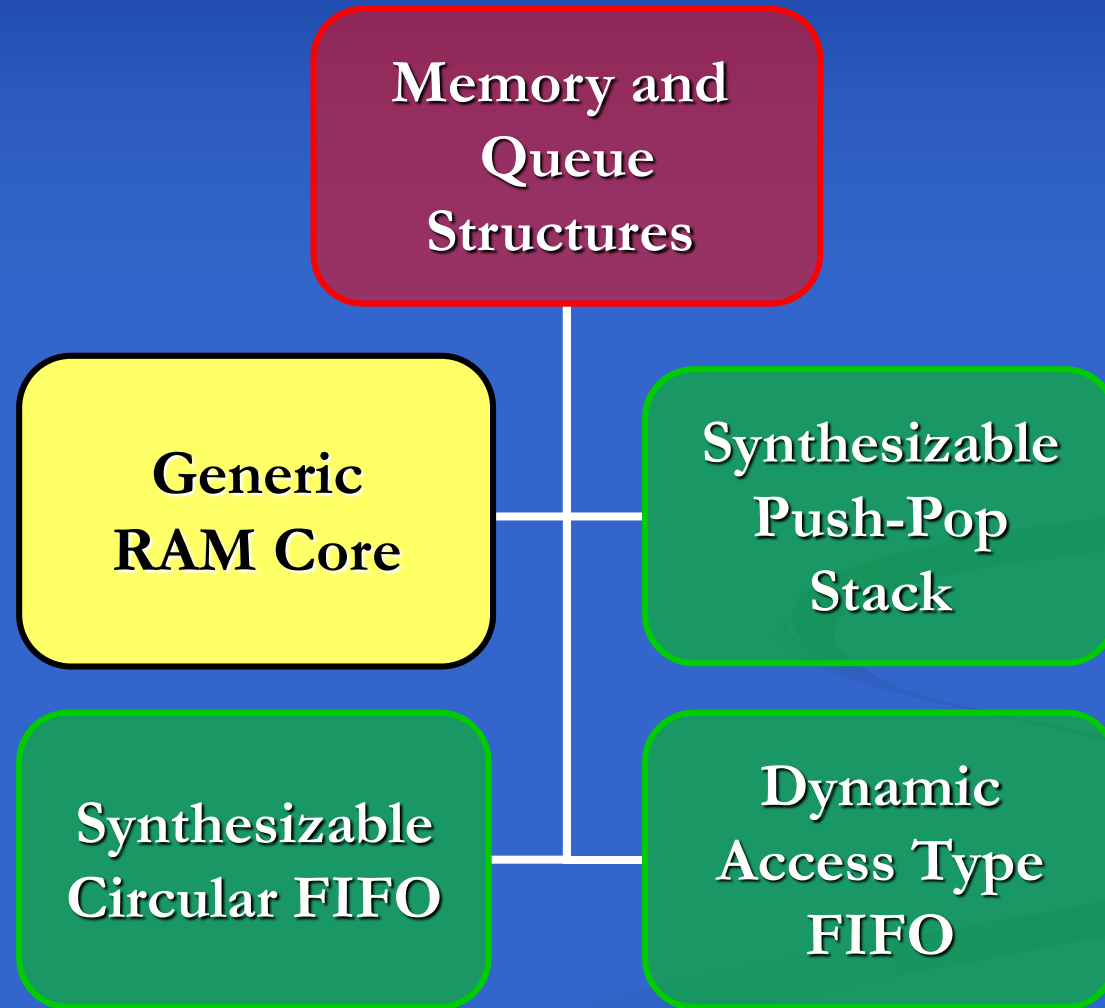

Generic RAM Core

```
PROCEDURE init_mem (VARIABLE memory: OUT mem;
                   CONSTANT datafile: STRING) IS
    FILE stddata : TEXT;
    VARIABLE l : LINE;
    VARIABLE data : std_logic_vector(memory'RANGE(2));
BEGIN
    FILE_OPEN (stddata, datafile, READ_MODE);
    FOR i IN memory'RANGE(1) LOOP
        READLINE (stddata, l); READ (l, data);
        FOR j IN memory'REVERSE_RANGE(2) LOOP
            memory (i,j) := data(j);
        END LOOP;
    END LOOP;
END PROCEDURE init_mem;
```

- TEXTIO Based Memory init and dump Procedure

Generic RAM Core

```
PROCEDURE dump_mem (VARIABLE memory: IN mem;  
                   CONSTANT datafile: STRING) IS  
    FILE stddata : TEXT;  
    VARIABLE stdvalue : std_logic;  
    VARIABLE l : LINE;  
BEGIN  
    FILE_OPEN (stddata, datafile, WRITE_MODE);  
    FOR i IN memory'RANGE(1) LOOP  
        FOR j IN memory'REVERSE_RANGE(2) LOOP  
            stdvalue := memory (i, j);  
            WRITE (l, stdvalue);  
        END LOOP;  
        WRITELINE (stddata, l);  
    END LOOP;  
END PROCEDURE dump_mem;
```

- TEXTIO Based Memory init and dump Procedure (Continued)

Generic RAM Core

```
USE IEEE.std_logic_TEXTIO.ALL;
ENTITY std_logic_ram IS
    PORT (address, datain : IN std_logic_vector;
          dataout : OUT std_logic_vector;
          cs, rwbar : IN std_logic; opr : IN BOOLEAN);
END ENTITY std_logic_ram;
--
ARCHITECTURE behavioral OF std_logic_ram IS
    TYPE mem IS ARRAY (NATURAL RANGE <>,
                       NATURAL RANGE <>) of std_logic;
BEGIN
    . . . . .
    . . . . .
END ARCHITECTURE;
```

- Std_logic Unconstrained Memory

Generic RAM Core

```
PROCESS
    CONSTANT memsize : INTEGER := 2**address'LENGTH;
    VARIABLE memory : mem (0 TO memsize-1,
                           datain'RANGE);

    BEGIN
        id: IF opr'EVENT THEN
            IF opr=TRUE THEN init_mem (memory, "memdata.dat");
            ELSE dump_mem (memory, "memdump.dat"); END IF;
        END IF;
        wr: IF cs = '1' THEN
            IF rwbar = '0' THEN -- Writing
                FOR i IN dataout'RANGE LOOP
                    memory(conv_integer(address),i):=datain (i);
                END LOOP;
            . . . . .
            . . . . .
        END IF;
    END PROCESS;
```

- Std_logic Unconstrained Memory (Continued)


Generic RAM Core

```
PROCESS
    CONSTANT memsize : INTEGER := 2**address'LENGTH;
    VARIABLE memory : mem (0 TO memsize-1,
                           datain'RANGE);

    BEGIN
        . . . . .
        ELSE -- Reading
            FOR i IN datain'RANGE LOOP
                dataout(i) <= memory(conv_integer(address), i);
            END LOOP;
        END IF;
    END IF;
    WAIT ON cs, rwbar, address, datain, opr;
END PROCESS;
```

- Std_logic Unconstrained Memory (Continued)

Synthesizable Push-Pop Stack

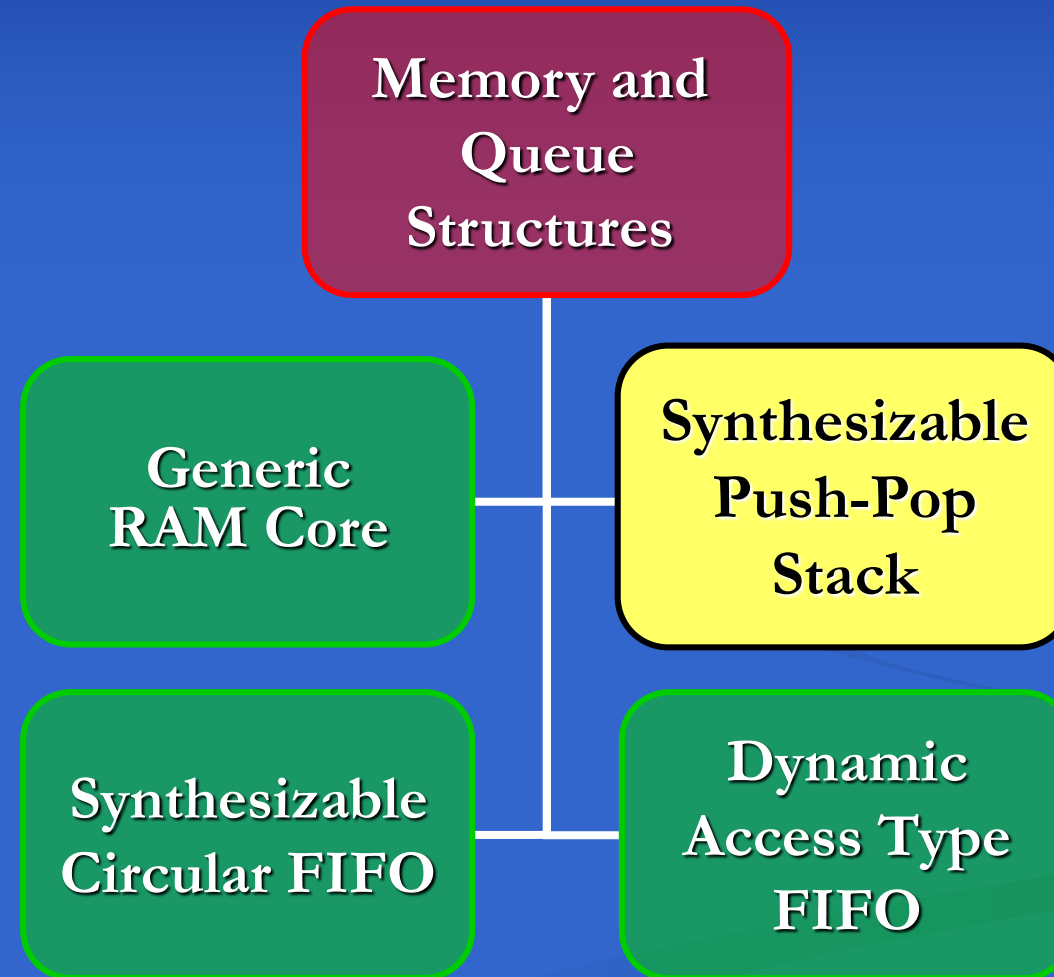

Synthesizable Push-Pop Stack

```
ENTITY stack IS
  GENERIC ( max: std_logic_vector := "101111" );
  PORT (STin : IN std_logic_vector;
        clk, push, pop : IN std_logic;
        opr : IN BOOLEAN;
        Sout : OUT std_logic_vector;
        empty, full : OUT std_logic);
END ENTITY stack;
--
```

- Stack Controller Outline

Synthesizable Push-Pop Stack

```
ARCHITECTURE behavioral OF stack IS
  SIGNAL ram_in, ram_out : std_logic_vector (STin'RANGE);
  SIGNAL ram_addr, p_ptr : std_logic_vector (max'RANGE)
                        := (OTHERS => '0');
  SIGNAL cs, rw_bar, full_temp : std_logic:= '0';
  SIGNAL empty_temp : std_logic:= '1';

BEGIN
  -- UPDATING PTR
  -- POP/PUSH
  -- INSTANTIATE MEMORY
  -- HANDLING EMPTY AND FULL
END ARCHITECTURE behavioral;
```

- Stack Controller Outline (Continued)

Synthesizable Push-Pop Stack

```
-- UPDATING PNTR
Update_pntr: PROCESS (clk)
BEGIN
    IF (clk = '1' AND clk'EVENT) THEN
        IF pop = '1' THEN
            IF empty_temp /= '1' THEN
                pntr <= pntr - 1;
            END IF;
        ELSIF push = '1' THEN
            IF full_temp /= '1' THEN
                pntr <= pntr + 1;
            END IF;
        END IF;
    END IF;
END PROCESS;
```

- Stack Pointer Update

Synthesizable Push-Pop Stack

```
-- POP/PUSH
pop_push: PROCESS (pop, push ,STin, ramout, pnttr)
BEGIN
    ramaddr <= (OTHERS => '0');
    cs <= '0';
    rwbar <= '1';
    ramin <= (OTHERS => '0');
    STout <= (STin'RANGE => '0');
    IF (pop = '1' AND empty_temp = '0') THEN
        ramaddr <= pnttr - 1;
        cs <= '1';
        rwbar <= '1';
        STout <= ramout;
        . . .
    END IF;
END;
```

- *Pop_push* Process

Synthesizable Push-Pop Stack

```
-- POP/PUSH
pop_push: PROCESS (pop, push ,STin, ramout, pnttr)
BEGIN
    . . . . .
    . . . . .
    ELSIF (push = '1' AND full_temp = '0') THEN
        ramaddr <= pnttr;
        cs <= '1';
        rwbar <= '0';
        ramin <= STin;
    END IF;
END PROCESS pop_push;
```

- *Pop_push* Process (Continued)

Synthesizable Push-Pop Stack


```
-- INSTANTIATE MEMORY
UU1: ENTITY WORK.std_logic_ram (behavioral)
PORT MAP (ramaddr, ramin, ramout, cs, rwbar, opr);

-- HANDLING EMPTY AND FULL
empty_temp <= '1' WHEN (pntr = (pntr'RANGE => '0')) ELSE '0';
full_temp <= '1' WHEN (pntr = max) ELSE '0';


empty <= empty_temp;
full <= full_temp;
```

- RAM Instantiation and *empty* and *full* Flags

Synthesizable Circular FIFO

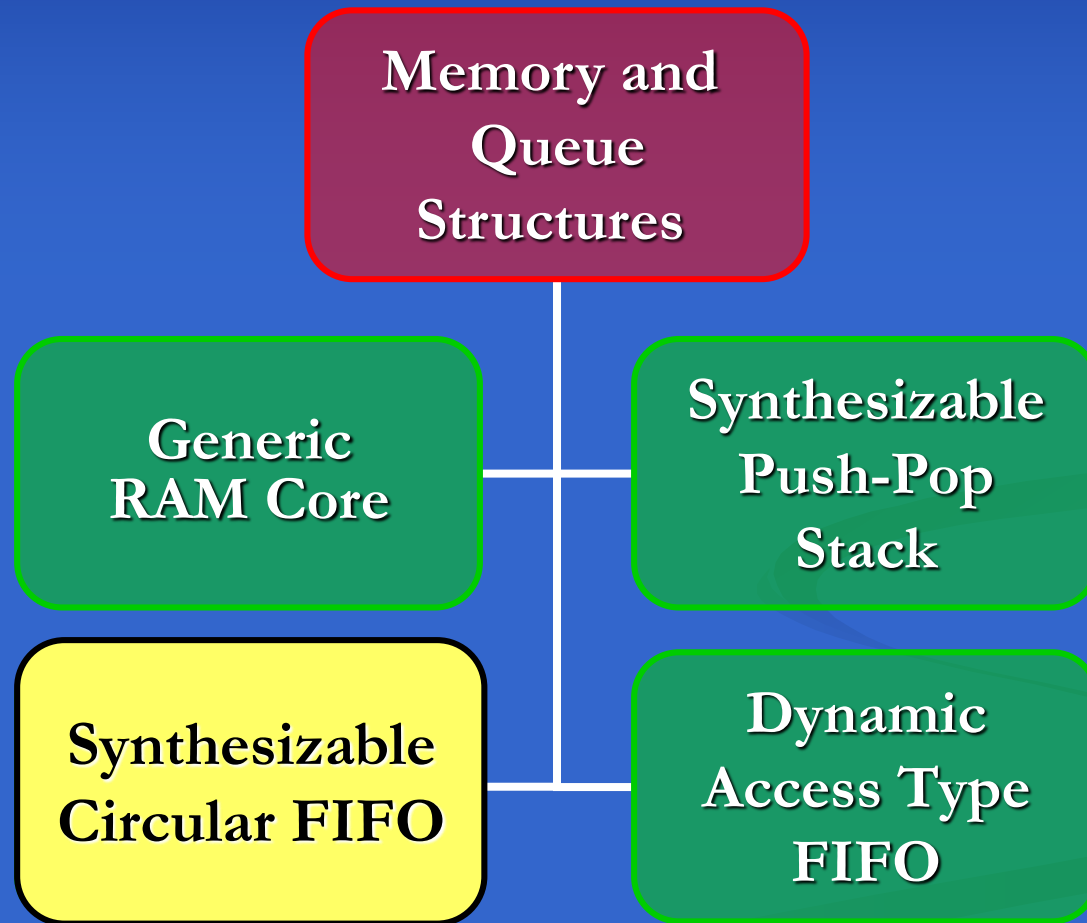

Synthesizable Circular FIFO

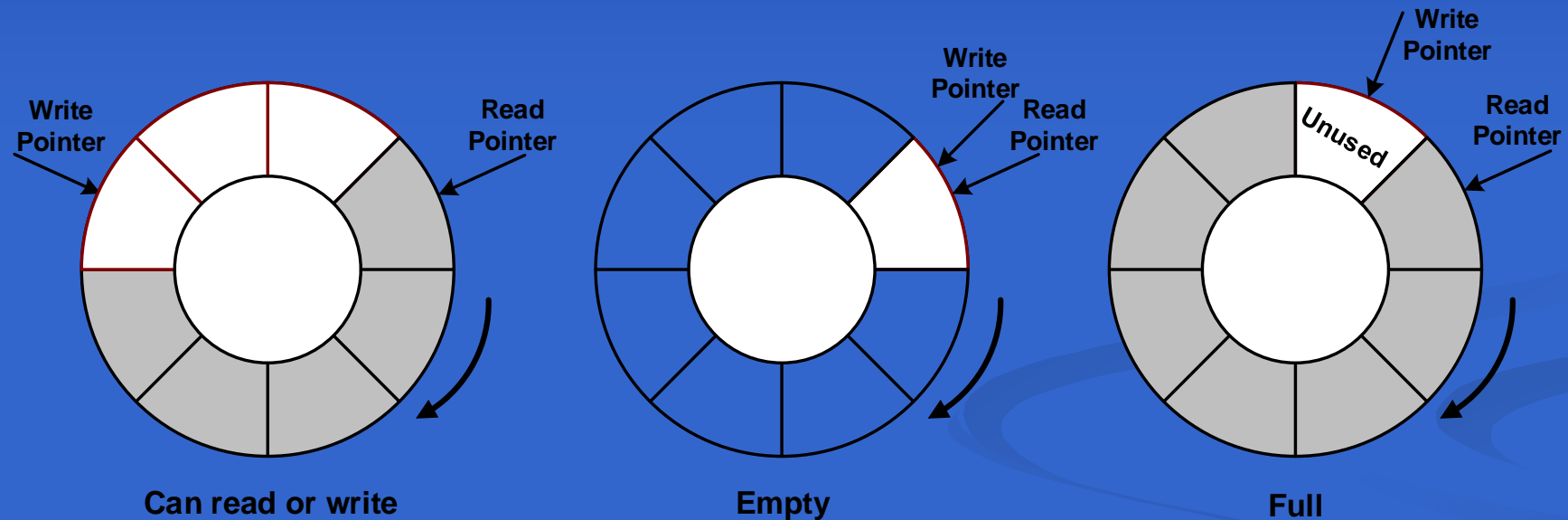

- Circular FIFO

Synthesizable Circular FIFO

```
LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
USE IEEE.std_logic_unsigned.ALL;
ENTITY fifo_unconst IS
    GENERIC (fifo_size : std_logic_vector := "1000");
    PORT (data_in : IN std_logic_vector;
          clk : IN std_logic;
          rst, rd, wr : IN std_logic;
          empty, full : OUT std_logic;
          data_out : OUT std_logic_vector);
END ENTITY ;
--
```

- FIFO VHDL Code Outline

Synthesizable Circular FIFO

```
ARCHITECTURE procedural OF fifo_unconst IS

    CONSTANT fsz : INTEGER := conv_integer (fifo_size);
    CONSTANT asz : INTEGER := fifo_size'LENGTH - 1;
    CONSTANT wsz : INTEGER := data_in'LENGTH; --word_size;
    TYPE memory IS ARRAY (NATURAL RANGE <>) OF std_logic_vector (wsz-1 DOWNTO 0);
    SIGNAL fifo_ram : memory (0 TO fsz-1);
    SIGNAL rd_ptr, wr_ptr:std_logic_vector(asz-1 DOWNTO 0) := (OTHERS => '0');
    SIGNAL full_temp, empty_temp : std_logic;
BEGIN

END ARCHITECTURE;
```


- FIFO VHDL Code Outline (Continued)

Synthesizable Circular FIFO

```
ARCHITECTURE procedural OF fifo_unconst IS
    . . . . .
    . . . . .
BEGIN
    -- WRITE
    -- READ
    -- POINTER
    empty_temp <= '1' WHEN ( rd_ptr=wr_ptr) ELSE '0';
    full_temp <= '1' WHEN ( rd_ptr=wr_ptr + 1) ELSE '0';
    empty <= empty_temp;
    full <= full_temp;
END ARCHITECTURE;
```


- FIFO VHDL Code Outline (Continued)

Synthesizable Circular FIFO

 


▪ FIFO Block Diagram


Synthesizable Circular FIFO

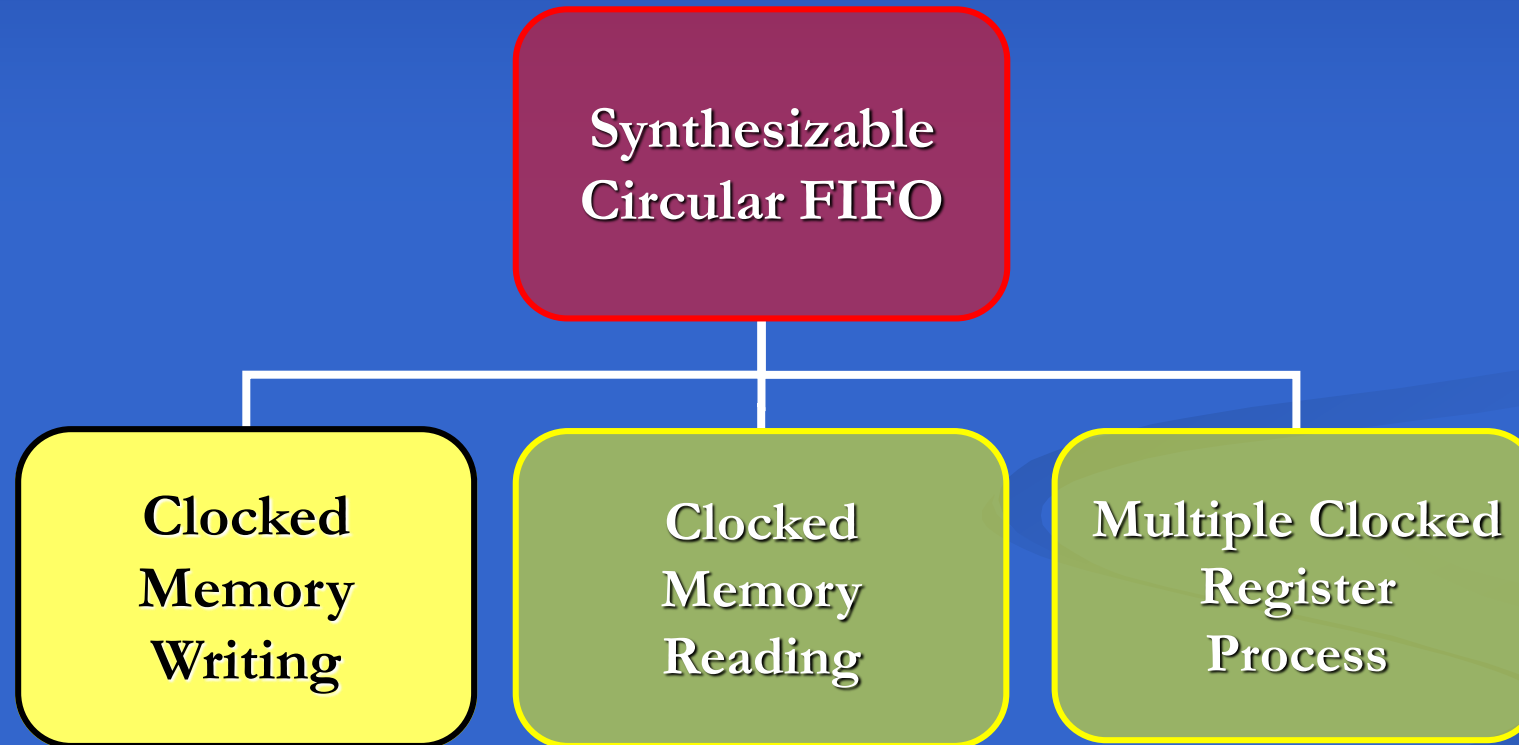

Clocked Memory Writing

 

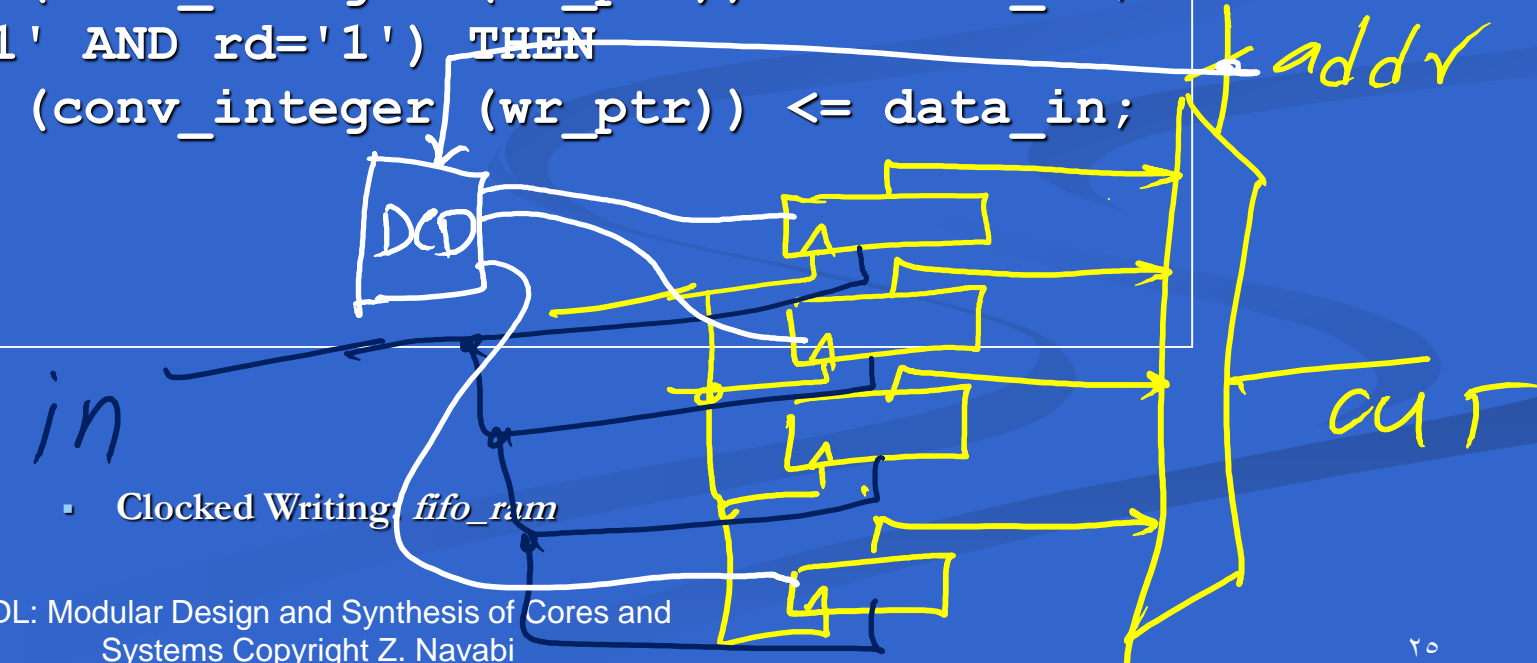
```
write : PROCESS (clk) BEGIN
  IF (clk='1' AND clk'EVENT) THEN
    IF (wr='1' AND full_temp='0') THEN
      fifo_ram (conv_integer (wr_ptr)) <= data_in;
    ELSIF (wr='1' AND rd='1') THEN
      fifo_ram (conv_integer (wr_ptr)) <= data_in;
    END IF;
  END IF;
END PROCESS;
```



▪ Clocked Writing *fifo_ram*

Clocked Memory Reading



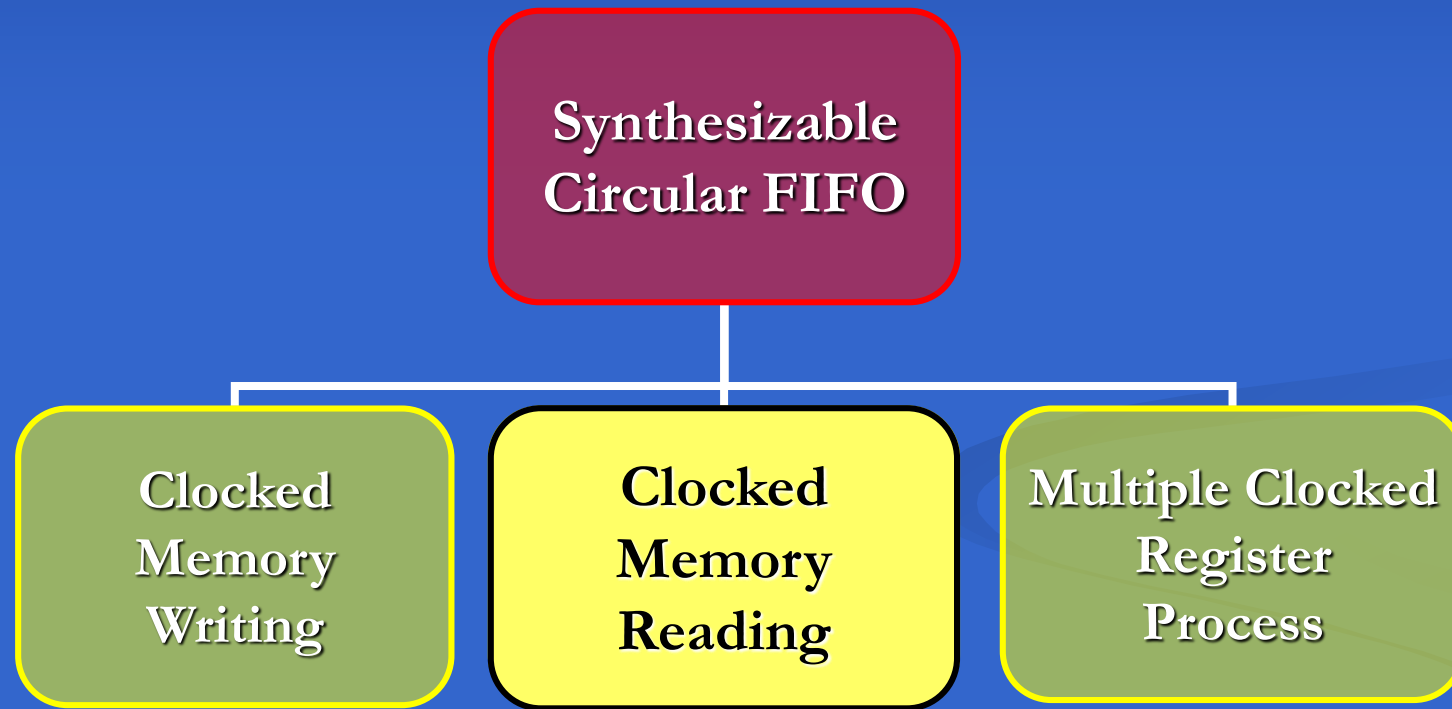


Clocked Memory Reading

```

read : PROCESS (clk) BEGIN
  IF (clk='1' AND clk'EVENT) THEN
    IF (rd='1' AND empty_temp='0') THEN
      data_out <= fifo_ram (conv_integer (rd_ptr));
    ELSIF (rd='1' AND wr='1' AND empty_temp='1') THEN
      data_out <= fifo_ram (conv_integer (rd_ptr));
    END IF;
  END IF;
END PROCESS;

```

   


$$(r.e) . r.w.e$$

$$(\bar{r}+e).r.w.e = r.w.e$$

- Clocked Reading: *fifo_ram*

Multiple Clocked Register Process

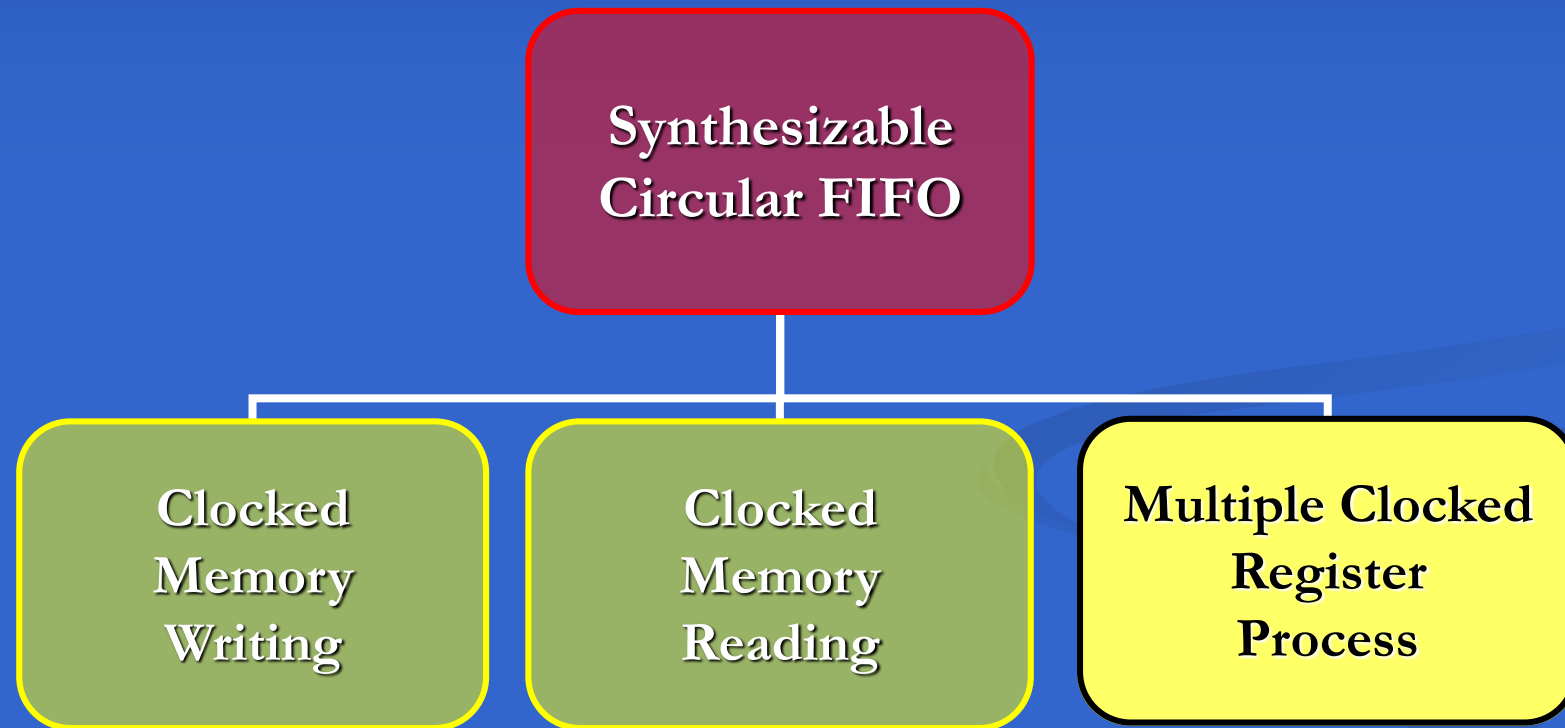

Multiple Clocked Register Process

```
pointer : PROCESS (clk) BEGIN
  IF (clk='1' AND clk'EVENT) THEN
    IF rst='1' THEN
      wr_ptr <= (OTHERS => '0');
      rd_ptr <= (OTHERS => '0');
    ELSE
      . . . . .
      . . . . .
      . . . . .
    END IF;
  END IF;
END PROCESS;
```


- Updating FIFO Pointers

Multiple Clocked Register Process

```
. . . . .
ELSE
  IF (wr='1' AND full_temp='0') OR (wr='1' AND rd='1') THEN
    wr_ptr <= wr_ptr+1;
  ELSE
    wr_ptr <= wr_ptr;
  END IF;
  IF (rd='1' AND empty_temp='0') OR (wr='1' AND rd='1') THEN
    rd_ptr <= rd_ptr+1;
  ELSE
    rd_ptr <= rd_ptr;
  END IF;
END IF;
```

- Updating FIFO Pointers (Continued)

Dynamic Access Type FIFO

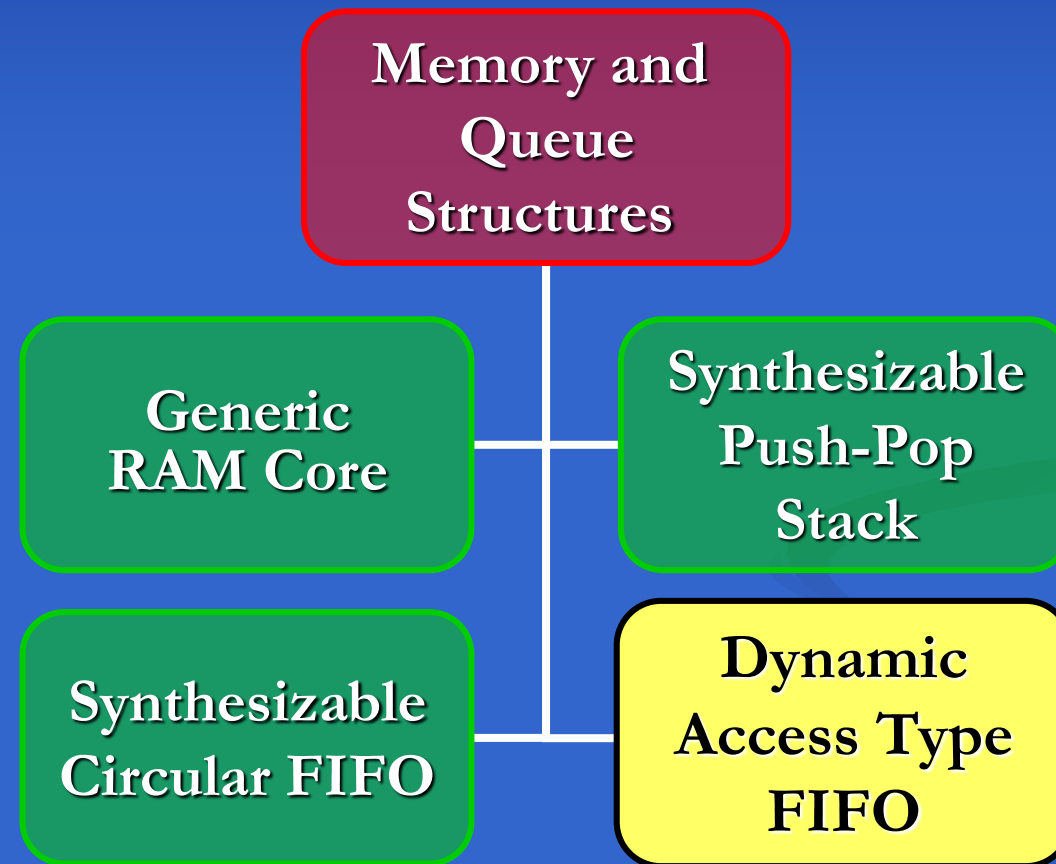

Dynamic FIFO Structure

```
TYPE fifo_element;  
TYPE pointer IS ACCESS fifo_element;  
TYPE fifo_element IS RECORD  
    data : std_logic_vector (7 DOWNT0 0);  
    link : pointer;  
END RECORD;  
SHARED VARIABLE head, tail : pointer :=  
NULL;
```

Dynamic FIFO Structure ▀


Different Hardware Levels

- Arithmetic Cores
 - Wrappers
 - Interfaces
 - CPUs
-
- All applications may not fit this categorization


Arithmetic Cores

- Completely independent from connection handling
- Can be used as embedded cores in embedded designs
 - Carry Lookahead Adder
 - Sequential Multiplier
 - Booth Multiplier
 - Sinh of x
 - FIR filter


Arithmetic Cores

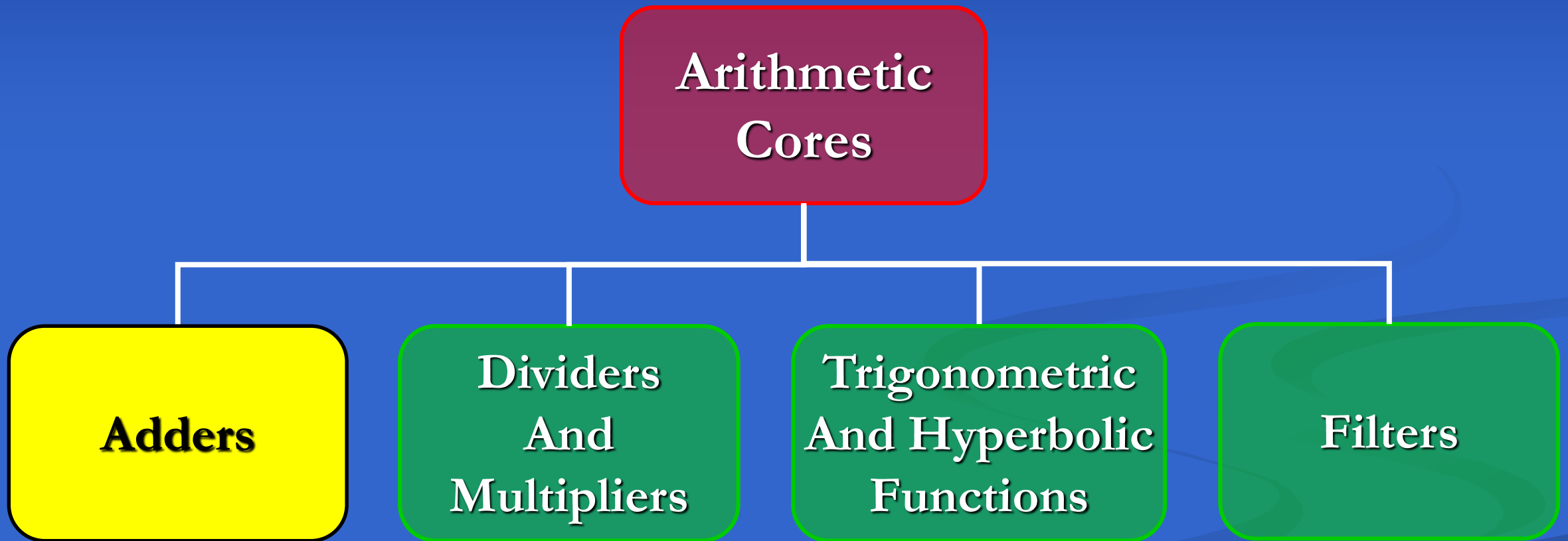

Adders

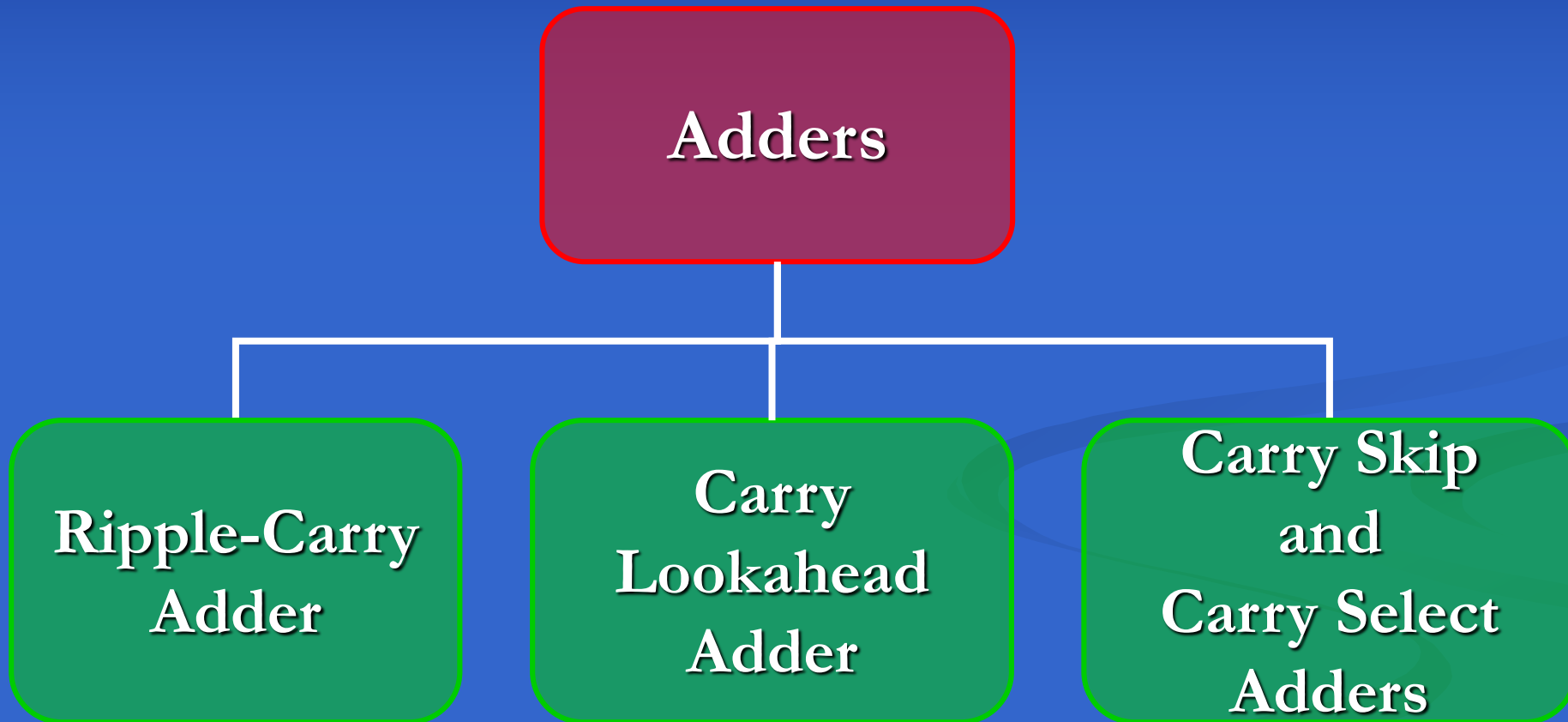


One-bit Full-Adder Circuit

 


$$sum_i = a_i \text{ xor } b_i \text{ xor } c_i$$
$$c_{i+1} = a_i b_i + b_i c_i + a_i c_i$$


Ripple-Carry Adder

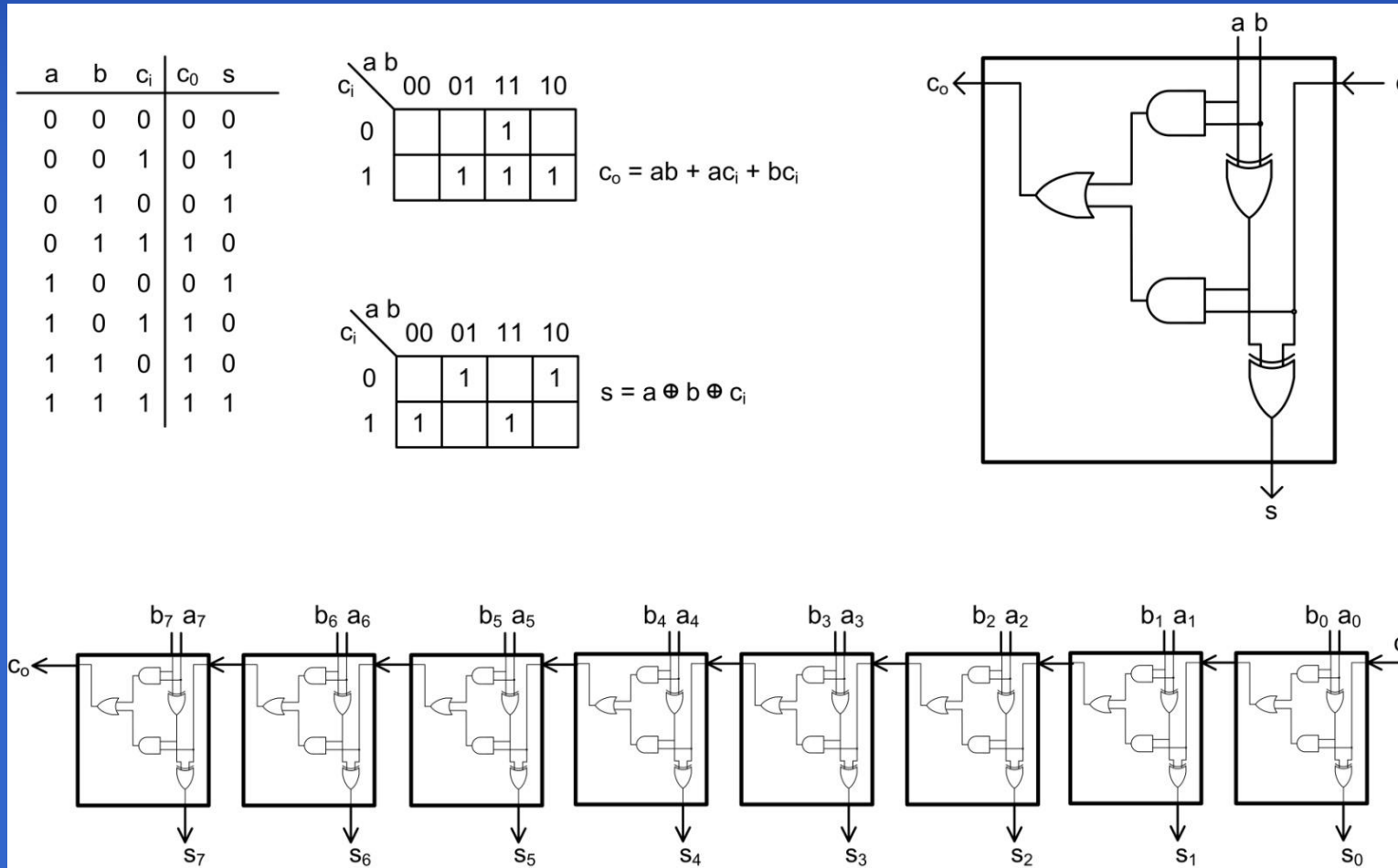

Carry Lookahead Adders

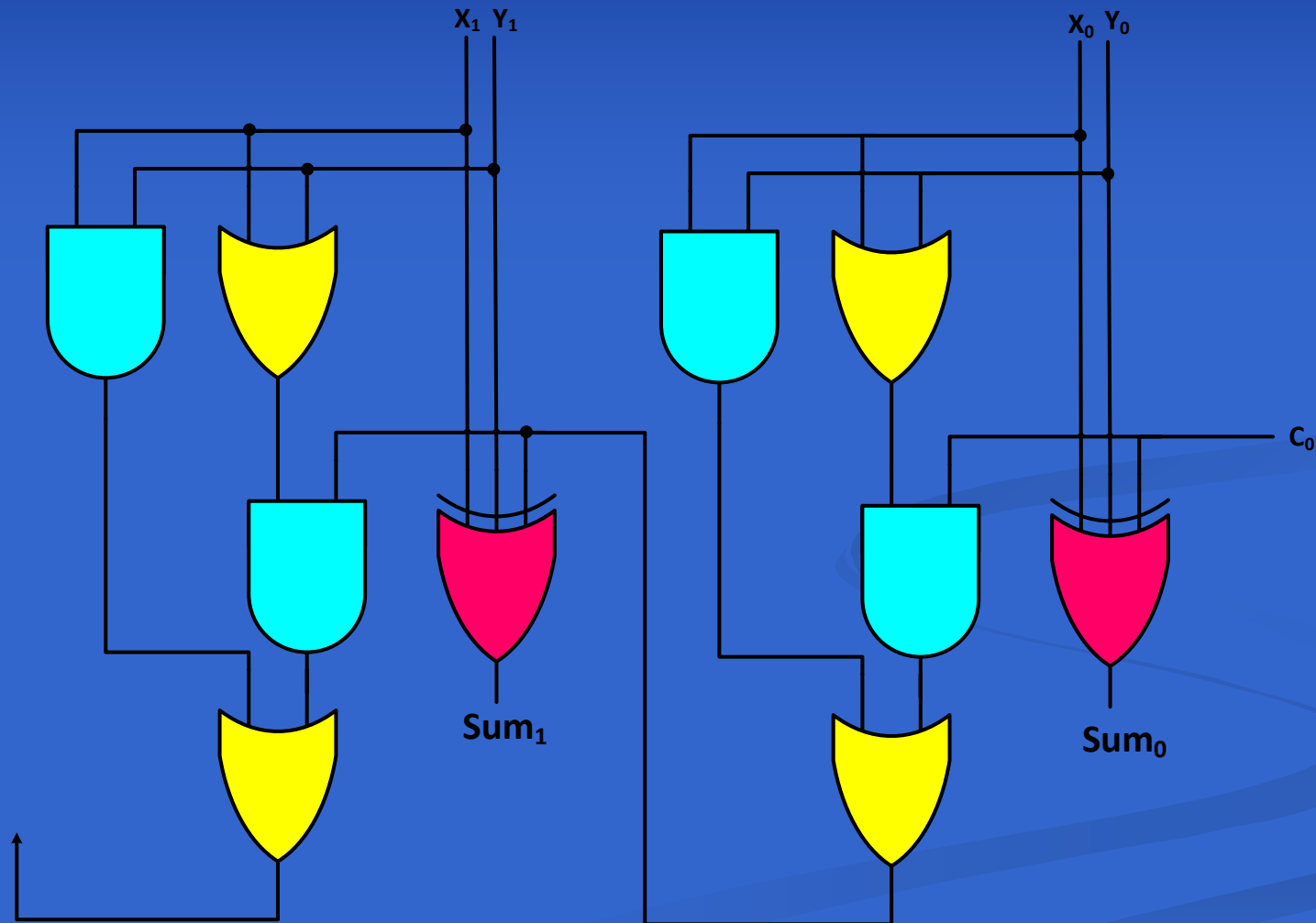


 Group Propagate (PG) and Group Generate (GG) for an 8-bit CLA




- Ripple carry between blocks
- Carry look ahead inside blocks

Carry-Select Adder

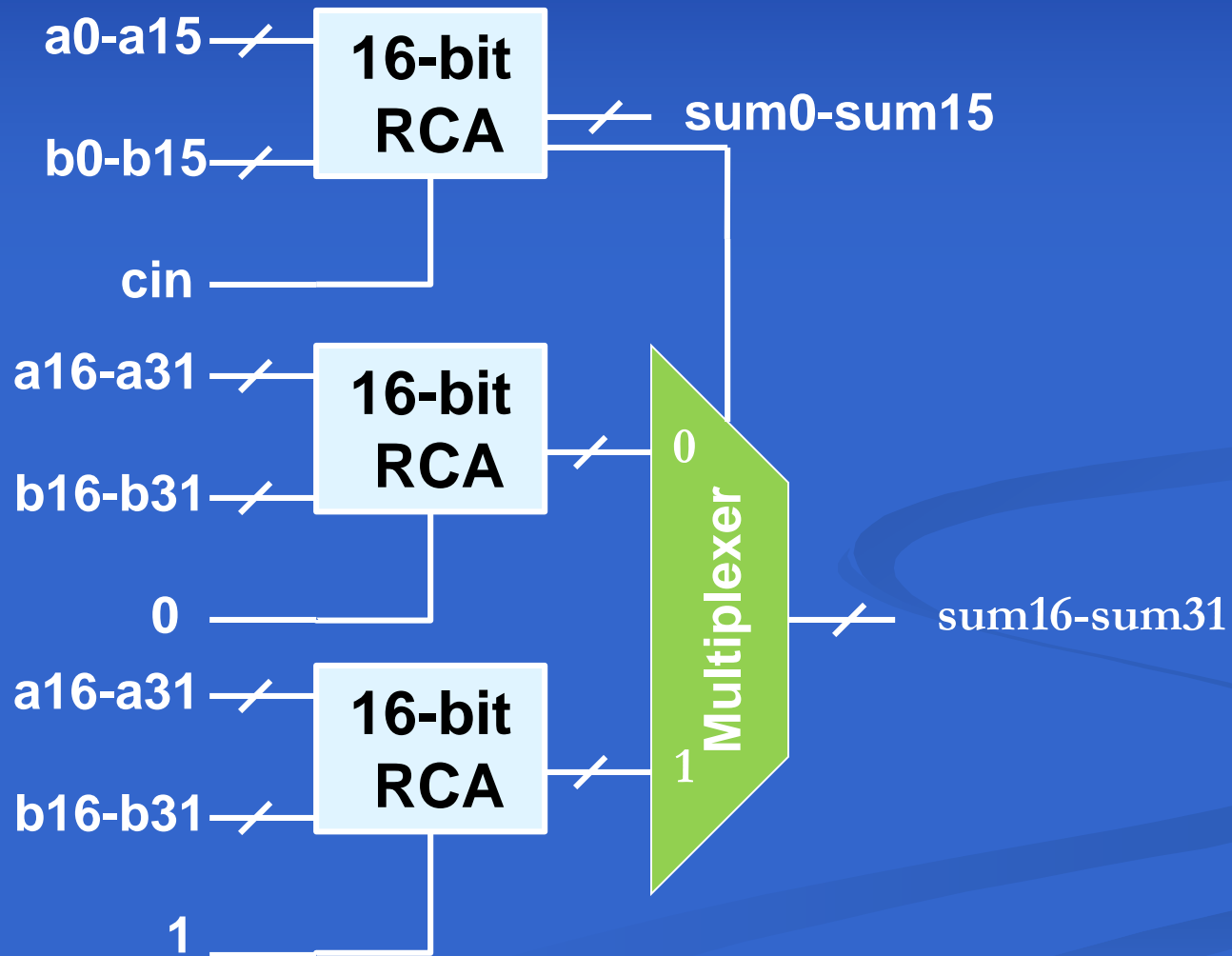


Arithmetic Cores

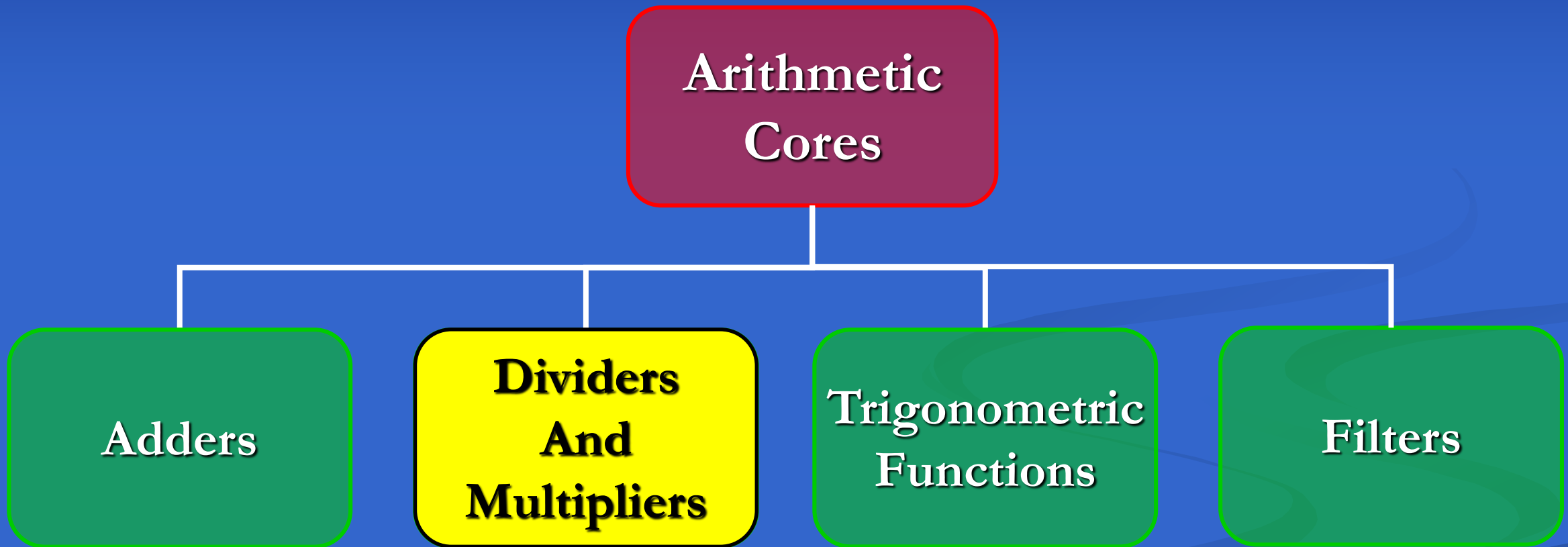


Multiplication

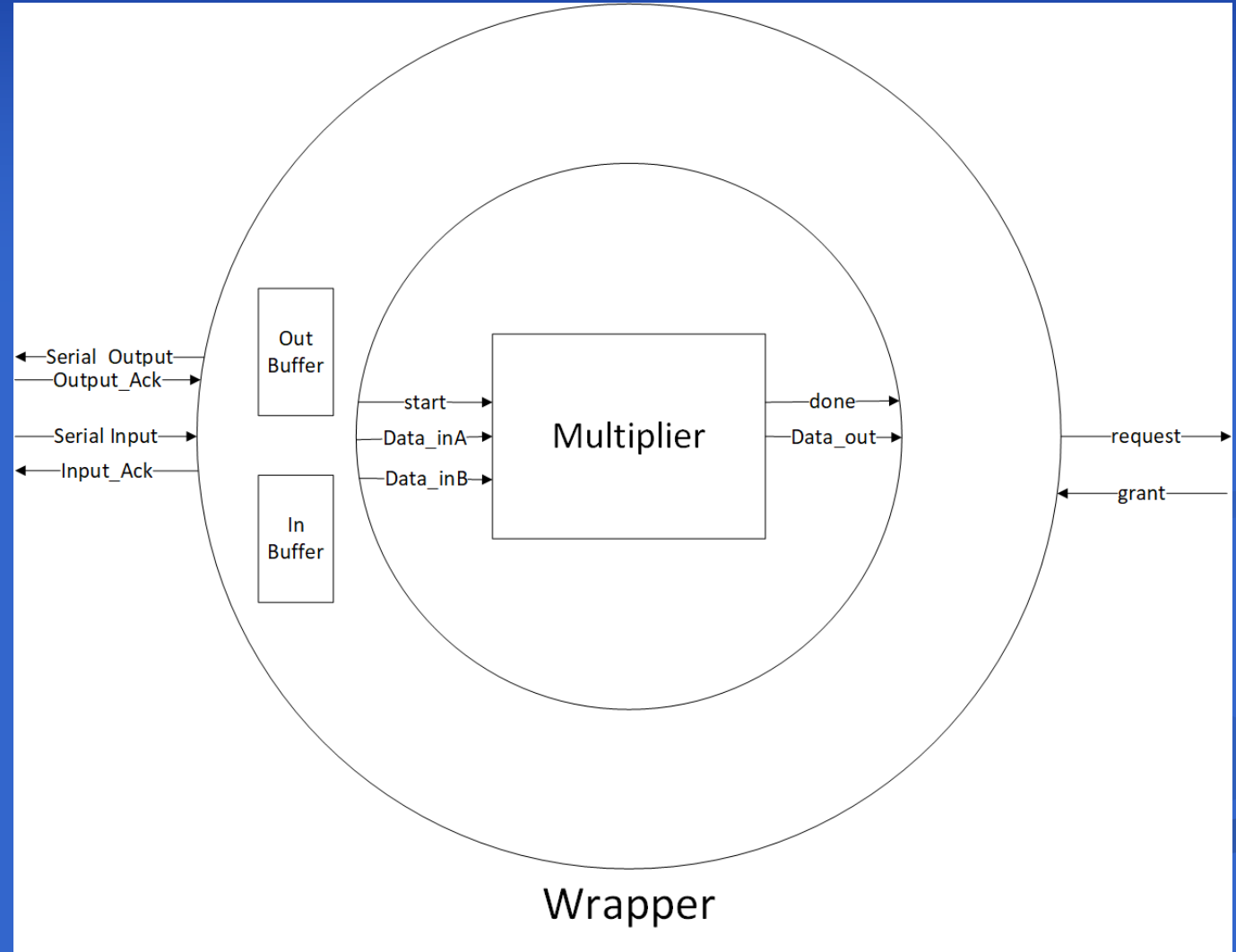- Sequential Multiplier
- Array Multiplier
- Booth Multiplier




Array Multiplier

 - Figure circuit multiplies its x_i and y_i inputs using the AND gate that is marked with a dot
- Adds this result with its input partial product p_i , using its carry input c_i .
- This cell generates a partial product p_o , a carry output c_o , and passes x_i and y_i inputs on to its outputs (x_o and y_o).




Array Multiplier

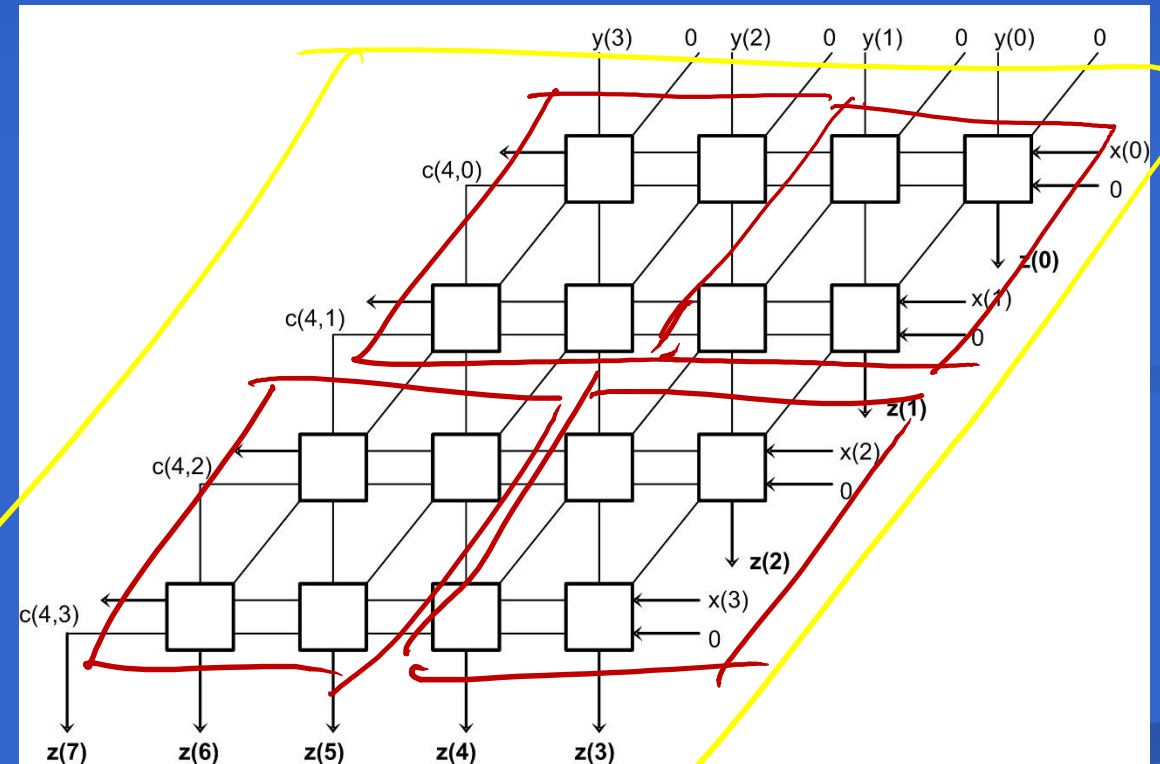- 4×4 array multiplier that uses 16 of the multiplier cells.
- A 32-bit multiplier requires 1024 such cells.




Shift-and-add Multiplication Process

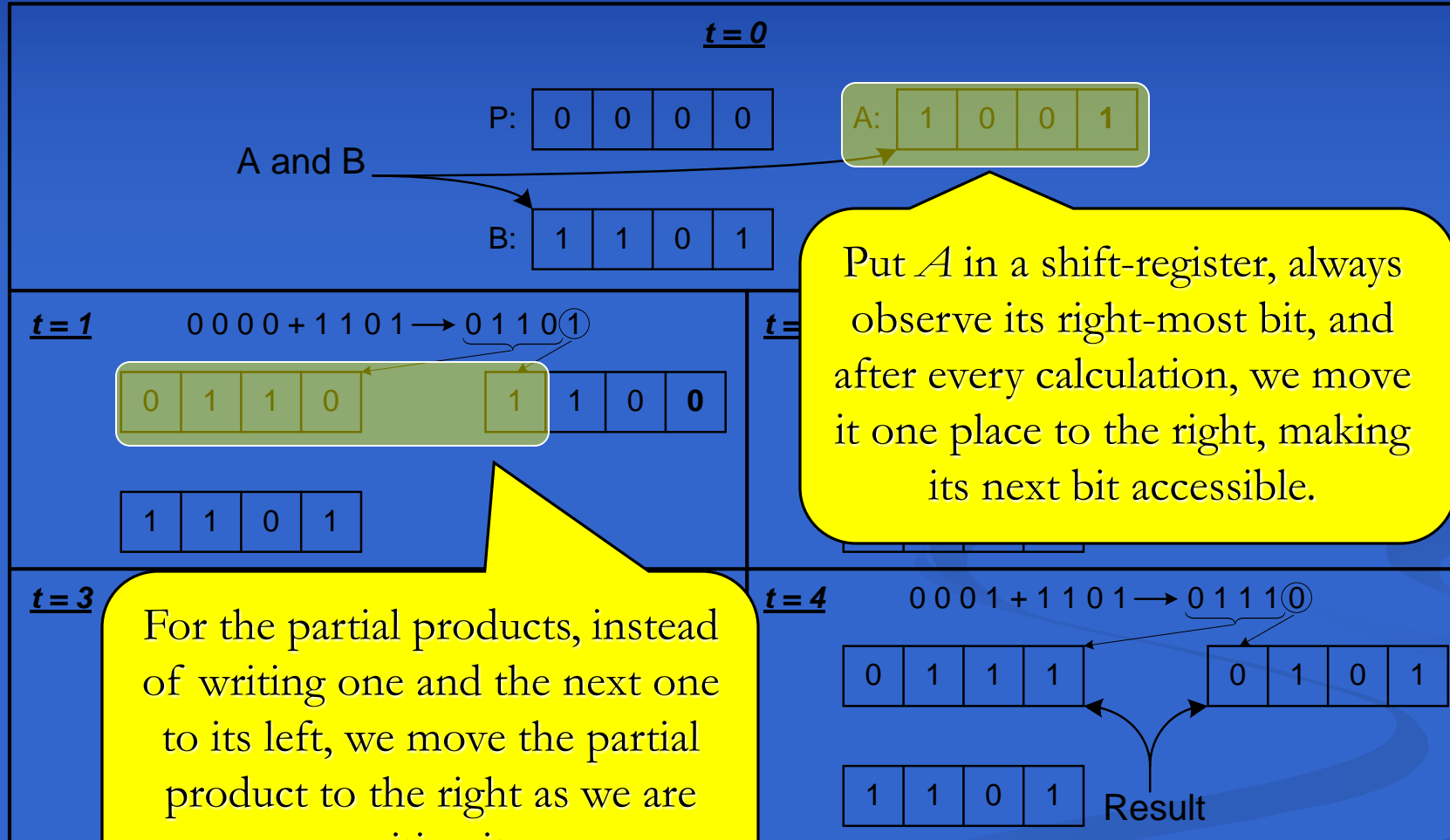


- Hardware Process

Shift-and-add Multiplication Process

 


- Hardware Oriented Multiplication Process (Continued)

Shift-and-add Multiplication Process

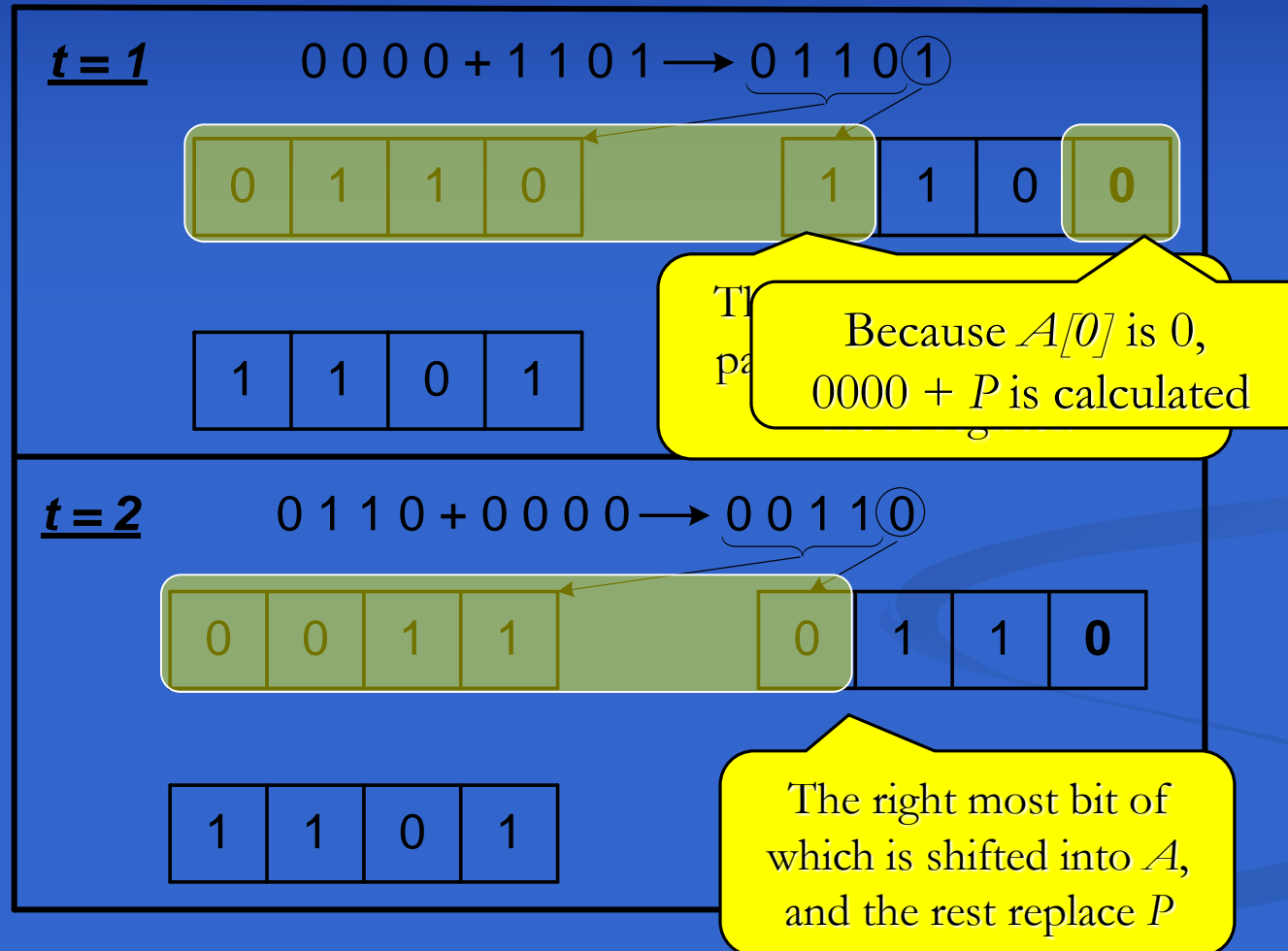

- Hardware Oriented Multiplication Process (Continued)


Shift-and-add Multiplication Process

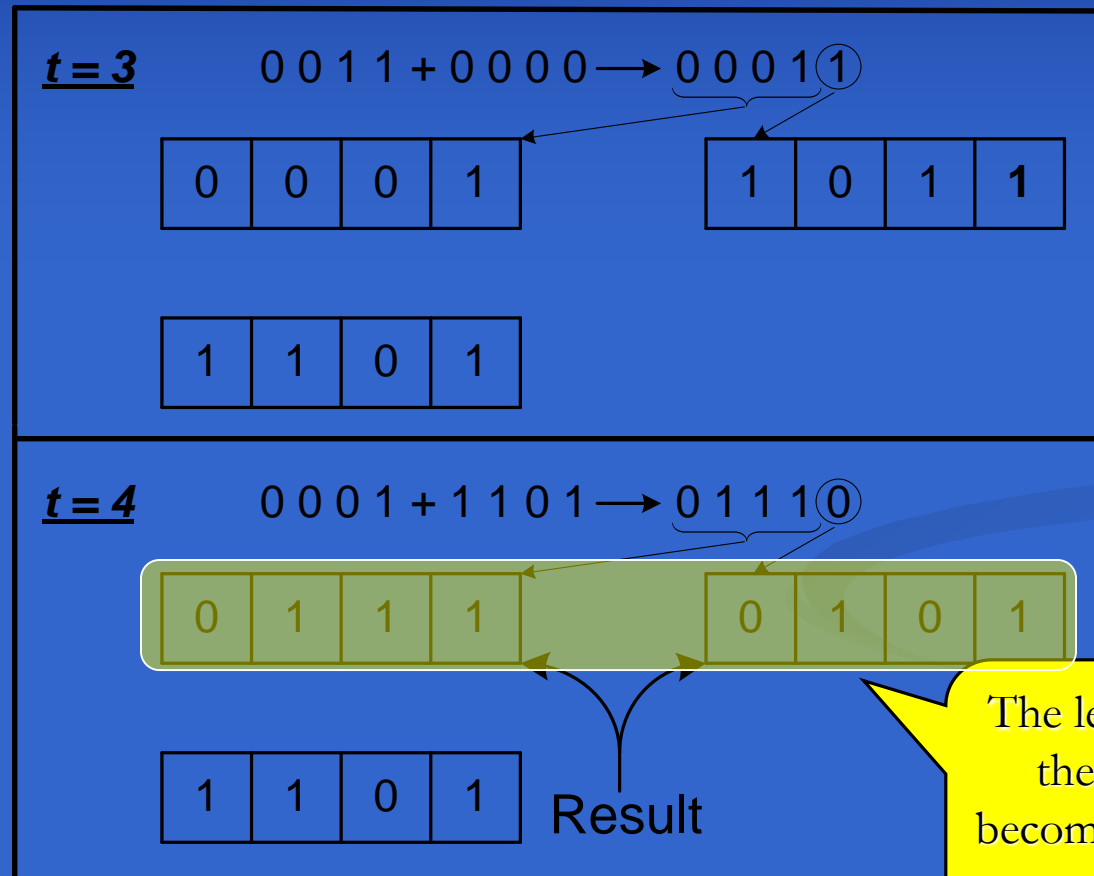


The least significant 4 bits of the multiplication result become available in A and the most-significant bits in P .

- Hardware Oriented Multiplication Process (Continued)

Sequential Multiplier Design

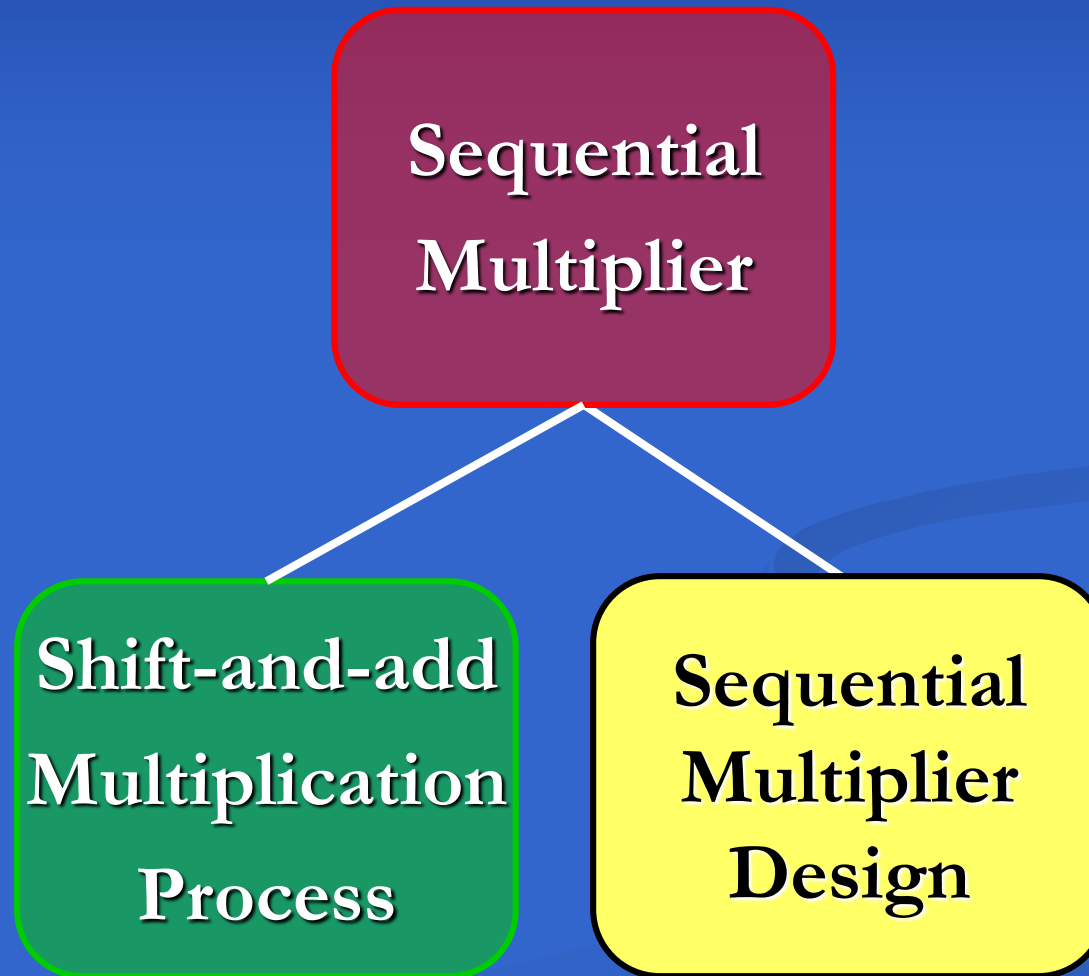


Sequential Multiplier

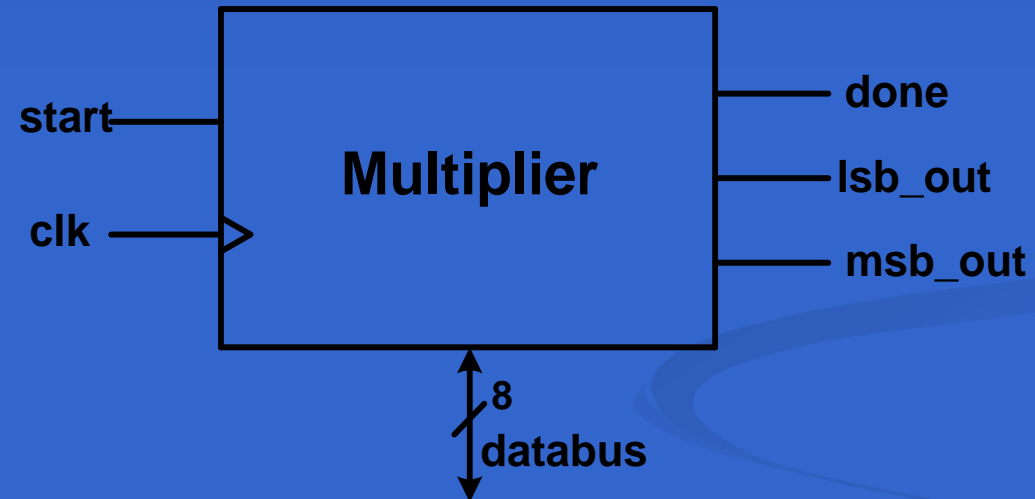


- Multiplier Block Diagram

Sequential Multiplier

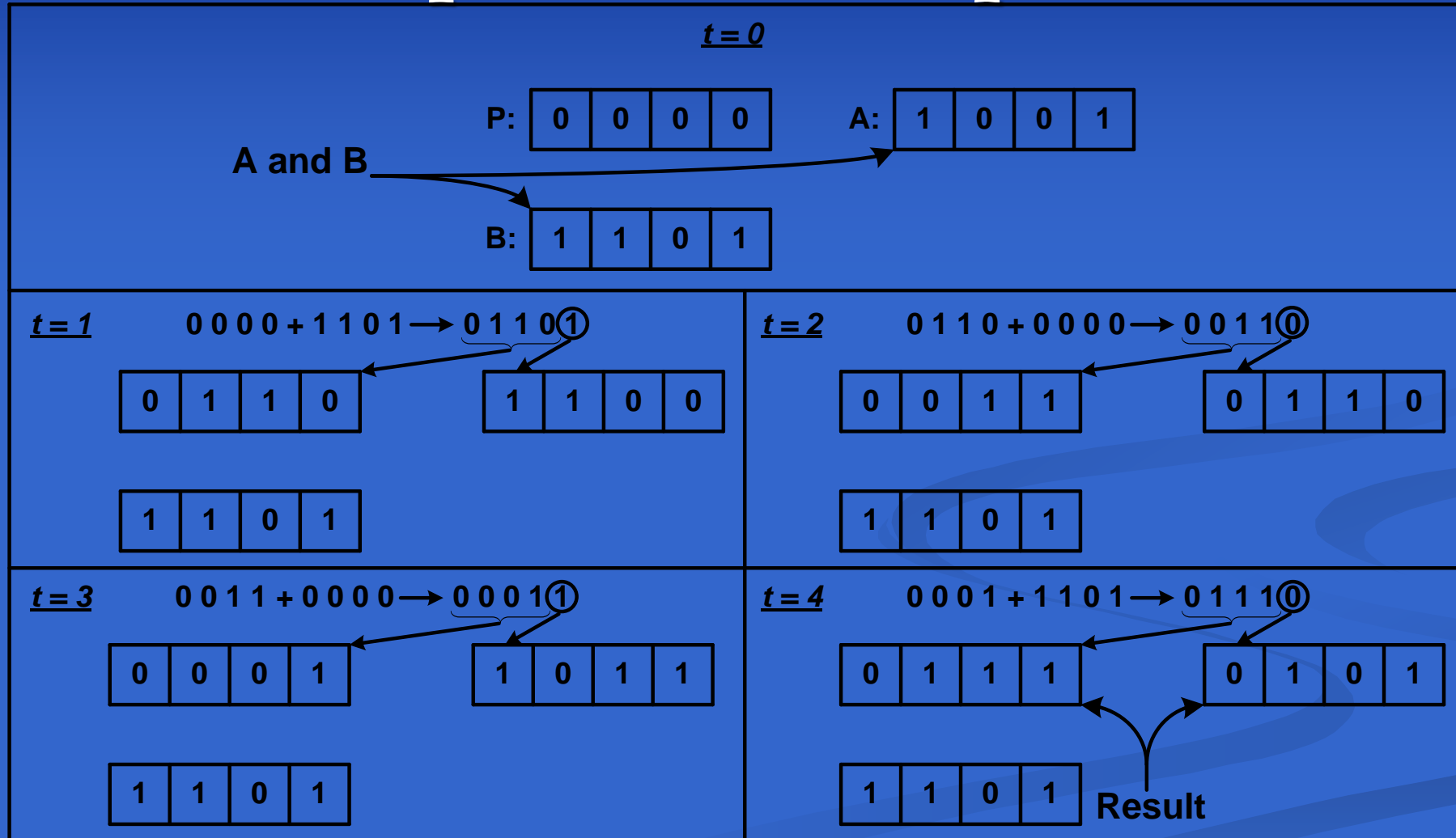


- Hardware Oriented Multiplication Process


Sequential Multiplier

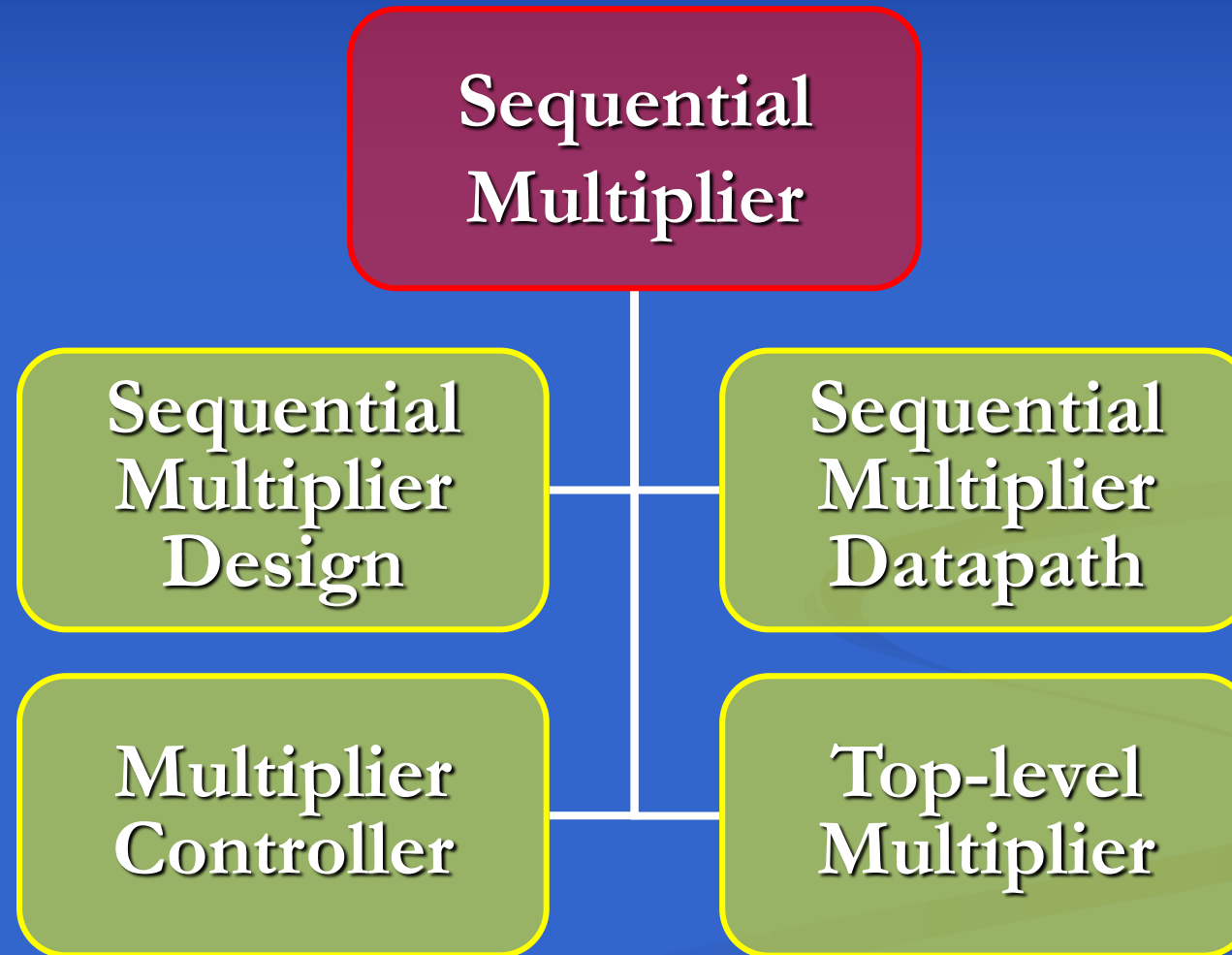

Sequential Multiplier Design

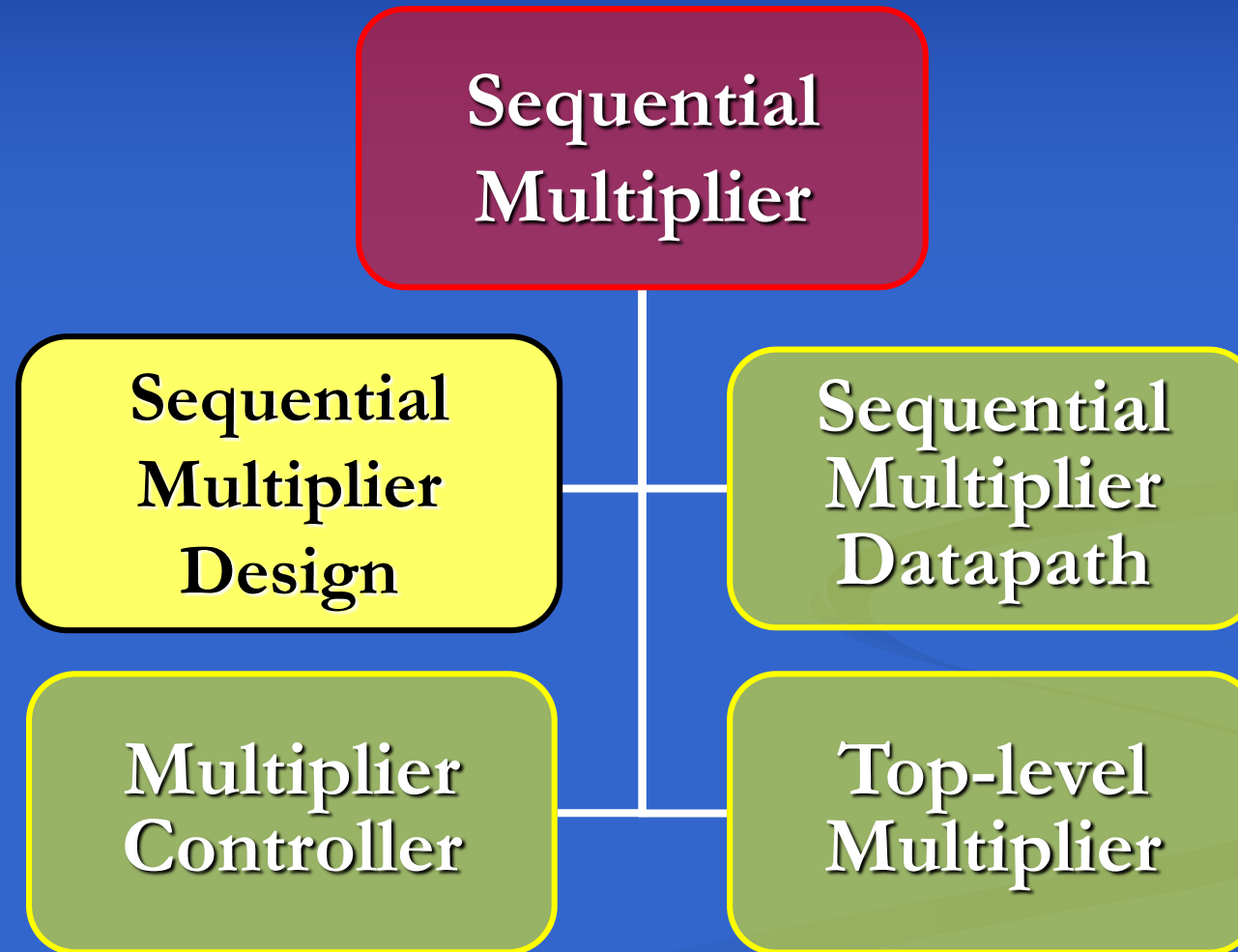


Sequential Multiplier Design

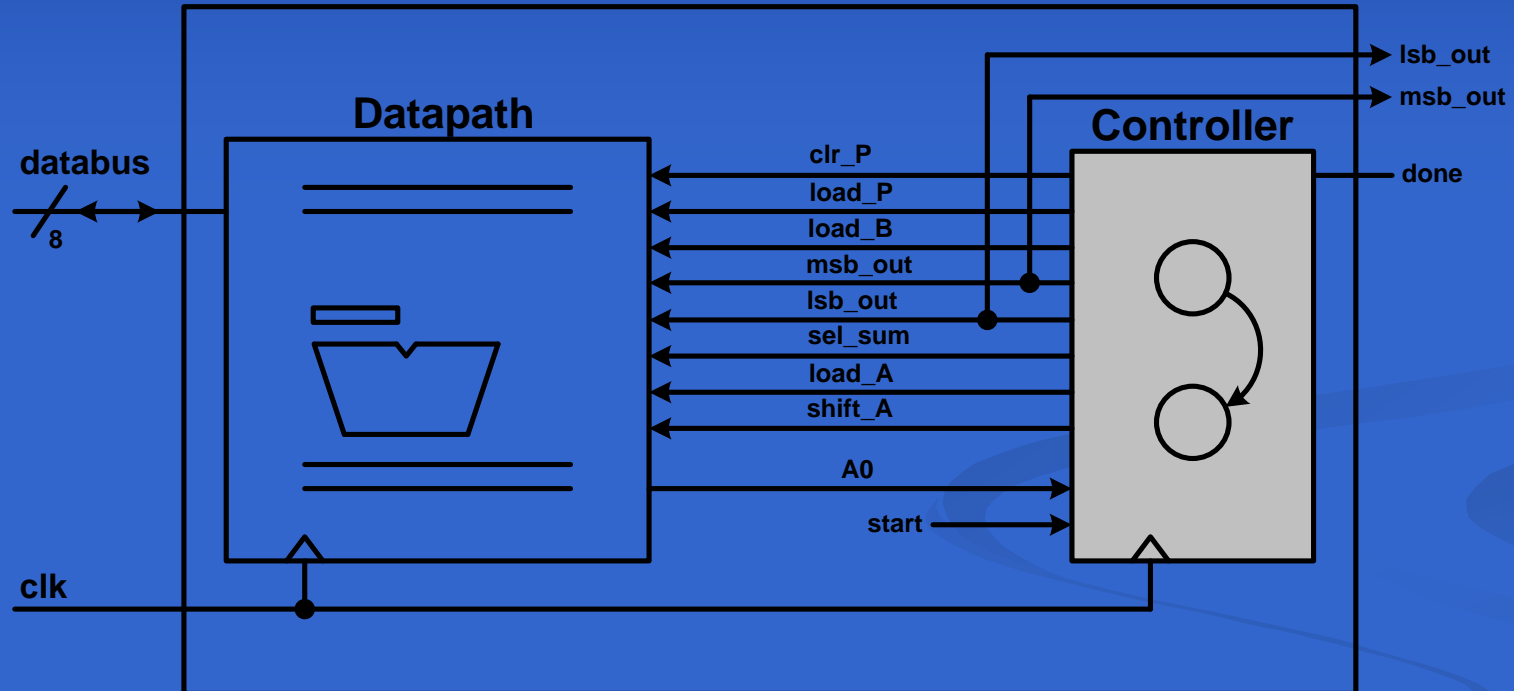


- Datapath and Controller

Sequential Multiplier Design

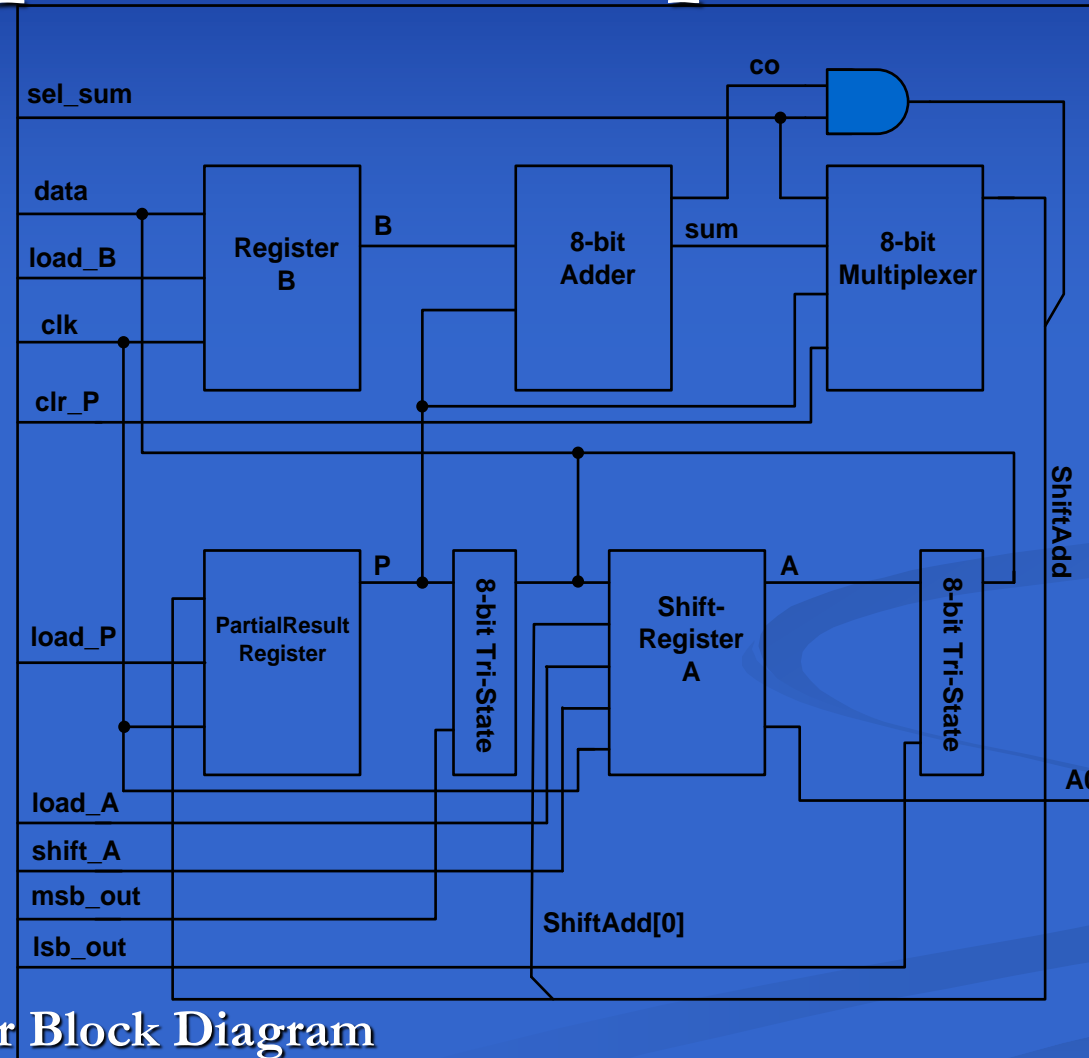

- Multiplier Block Diagram

Sequential Multiplier Datapath

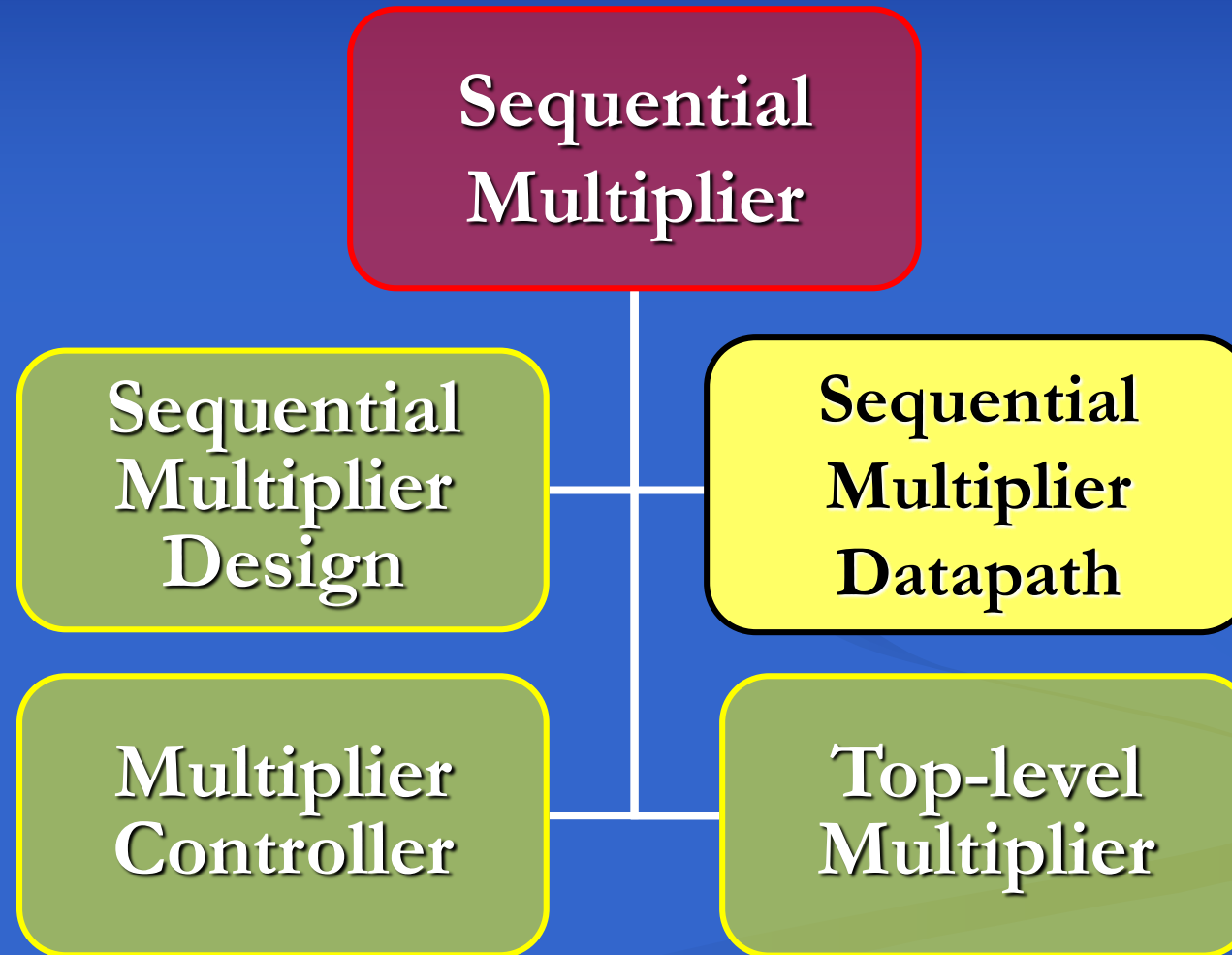

Sequential Multiplier Datapath

```
ENTITY datapath IS
  PORT (clk, clr_P, load_P, load_B : IN std_logic;
        msb_out, lsb_out, sel_sum : IN std_logic;
        load_A, shift_A : IN std_logic;
        data : INOUT std_logic_vector (7 DOWNTO 0);
        A0 : OUT std_logic);
END ENTITY;

--
ARCHITECTURE procedural OF datapath IS
  SIGNAL sum, ShiftAdd : std_logic_vector (7 DOWNTO 0);
  SIGNAL A, B, P : std_logic_vector (7 DOWNTO 0);
  SIGNAL co : std_logic;
  SIGNAL op : std_logic_vector (1 DOWNTO 0);
  SIGNAL result : std_logic_vector (8 DOWNTO 0);
  . . . . .
END ARCHITECTURE procedural;
```

- Shift-and-add Multiplier Datapath

Sequential Multiplier Datapath

```
PROCESS (clk) BEGIN
    IF (clk = '0' AND clk'EVENT) THEN
        IF (load_B = '1') THEN B <= data;
        END IF;
    END IF;
END PROCESS;
--
PROCESS (clk) BEGIN
    IF (clk = '0' AND clk'EVENT) THEN
        IF (load_P = '1') THEN
            P <= (co AND sel_sum) & ShiftAdd (7 DOWNTO 1);
        END IF;
    END IF;
END PROCESS;
--
```

- Shift-and-add Multiplier Datapath (Continued)

Sequential Multiplier Datapath

```
PROCESS (clk) BEGIN
  IF (clk = '0' AND clk'EVENT) THEN
    CASE op IS
      WHEN "01" => A <= ShiftAdd(0) &
                    A(7 DOWNTO 1);
      WHEN "10" => A <= data;
      WHEN OTHERS => A <= A;
    END CASE;
  END IF;
END PROCESS;
. . . . .
```

- Shift-and-add Multiplier Datapath (Continued)


Sequential Multiplier Datapath

```
. . . . .
result <= ('0' & P) + ('0' & B);
co <= result(8);
sum <= result(7 DOWNTO 0);

A0 <= A(0);
ShiftAdd <= (OTHERS => '0') WHEN clr_P = '1' ELSE
             P WHEN sel_sum = '0' ELSE sum;
data <= A WHEN lsb_out = '1' ELSE (OTHERS => 'Z');
data <= P WHEN msb_out = '1' ELSE (OTHERS => 'Z');
op <= load_A & shift_A;
END ARCHITECTURE procedural;
```

- Shift-and-add Multiplier Datapath (Continued)

Multiplier Controller

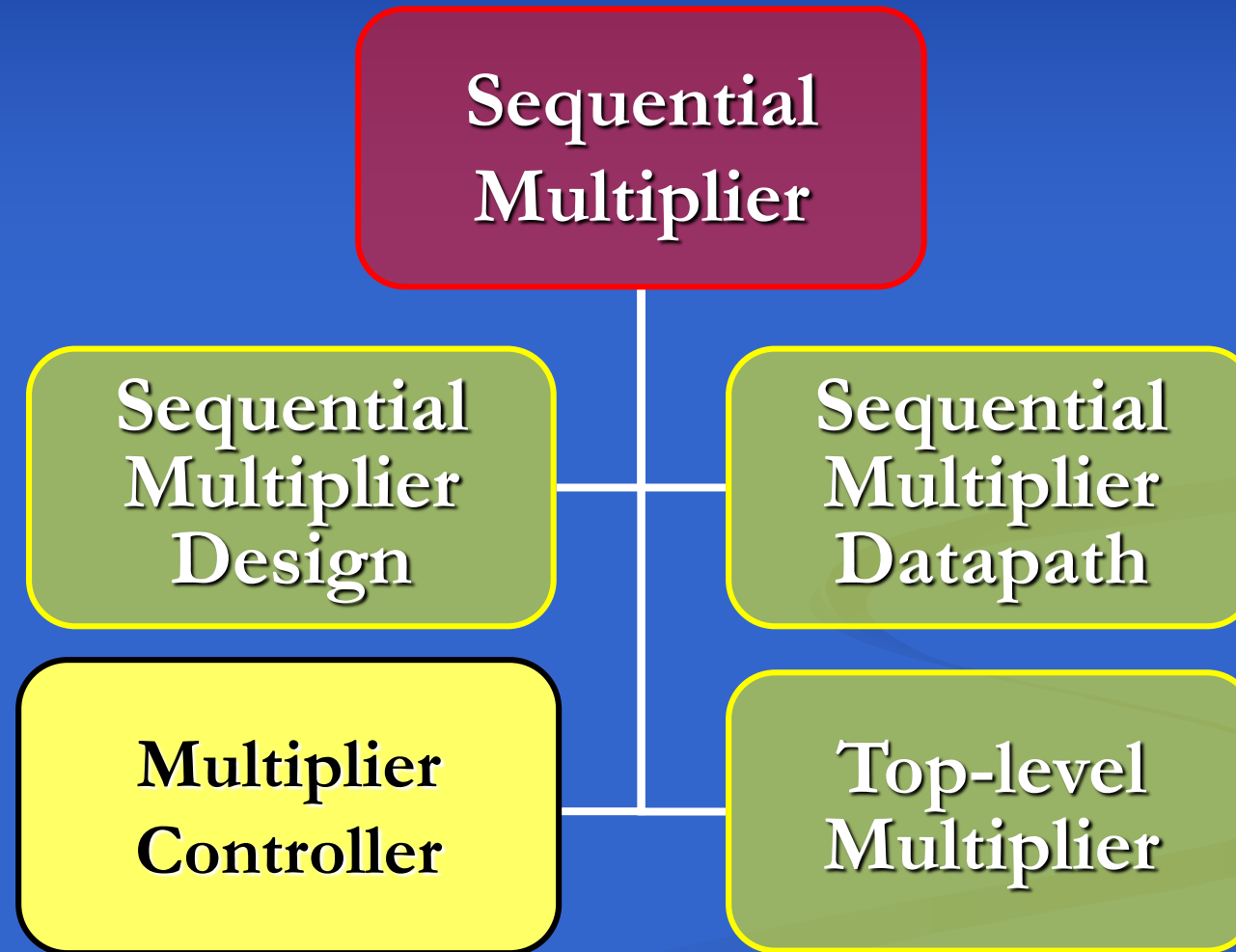

Multiplier Controller

```
LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
USE IEEE.std_logic_unsigned.ALL;
ENTITY controller IS
    PORT (clk, start, A0 : IN std_logic;
          clr_P, load_P, load_B : OUT std_logic;
          msb_out, lsb_out, sel_sum : OUT std_logic;
          load_A, Shift_A, done : OUT std_logic);
END ENTITY;
--
```

- Multiplier Controller

Multiplier Controller

```
ARCHITECTURE procedural OF controller IS
  TYPE state IS (idle, init,
                 m1, m2, m3, m4, m5, m6, m7, m8,
                 rs1t1, rs1t2);
  SIGNAL current : state;
BEGIN
  sequential: PROCESS (clk) BEGIN
    IF (clk = '0' AND clk'EVENT) THEN
      CASE current IS
        WHEN idle =>
          IF start = '0' THEN current <= idle;
          ELSE
            current <= init;
          END IF;
          . . . . .
        END PROCESS; --
```

- Multiplier Controller (Continued)

Multiplier Controller


```
sequential: PROCESS (clk) BEGIN
  IF (clk = '0' AND clk'EVENT) THEN
    CASE current IS
      . . . . .
      WHEN init =>
        current <= m1;
      WHEN m1 | m2 | m3 | m4 | m5 | m6 | m7 | m8
        =>
        current <= state'SUCC(current);
      WHEN rslt1 =>
        current <= rslt2;
      WHEN rslt2 =>
        current <= idle;
      WHEN OTHERS =>
        current <= idle;
    END CASE;
  END IF;
END PROCESS;
```



- Multiplier Controller

Multiplier Controller

```
sequential: PROCESS (clk) BEGIN
    . . . . .
END PROCESS; --
combinational: PROCESS (current, start, A0) BEGIN
    clr_P <= '0'; load_P <= '0';
    load_B <= '0';
    msb_out <= '0'; lsb_out <= '0';
    sel_sum <= '0'; load_A <= '0';
    Shift_A <= '0'; done <= '0';
    CASE current IS
        WHEN idle =>
            IF start = '0' THEN
                done <= '1';
            ELSE
                load_A <= '1';
                clr_P <= '1';
                load_P <= '1';
            END IF;
    END CASE;
END PROCESS;
```

 

Multiplier Controller

```
combinational: PROCESS (current, start, A0) BEGIN
  CASE current IS
    . . . . .
    WHEN init =>
      load_B <= '1';
    WHEN m1 | m2 | m3 | m4 | m5 | m6 | m7 | m8
      =>
      Shift_A <= '1';
      load_P <= '1';
      IF (A0 = '1') THEN
        sel_sum <= '1';
      END IF;
    WHEN rs1t1 =>
      lsb_out <= '1';
    WHEN rs1t2 =>
      msb_out <= '1';
```


- Multiplier Controller

Multiplier Controller

```
combinational: PROCESS (current, start, A0) BEGIN
  CASE current IS
    . . . . .
  WHEN rslt2 =>
    msb_out <= '1';
  WHEN OTHERS =>
    clr_P <= '0'; load_P <= '0';
    load_B <= '0'; msb_out <= '0';
    lsb_out <= '0'; sel_sum <= '0';
    load_A <= '0'; Shift_A <= '0';
    done <= '0';
  END CASE;
END PROCESS;
END ARCHITECTURE procedural;
```

- Multiplier Controller

Top-level Multiplier

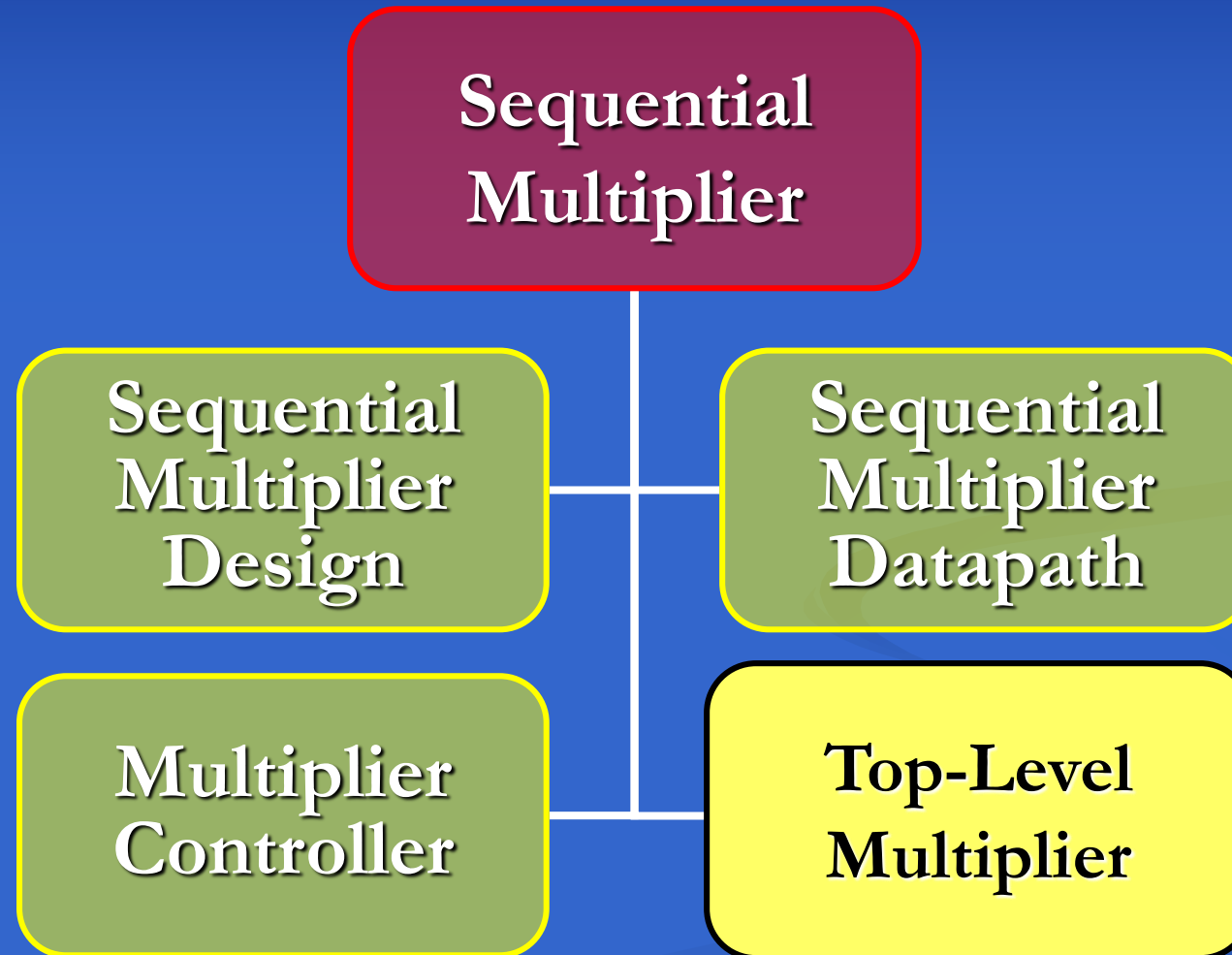

Top-level Multiplier

```
ENTITY Multiplier IS
  PORT (clk, start : IN std_logic;
        databus : INOUT std_logic_vector (7 DOWNTO 0);
        lsb_out, msb_out, done : OUT std_logic);
END ENTITY;
--
ARCHITECTURE structural OF Multiplier IS
  SIGNAL clr_P, load_P, load_B, msb_out_t, A0 : std_logic;
  SIGNAL lsb_out_t, sel_sum, load_A, Shift_A : std_logic;
BEGIN
  . . . . .
  . . . . .
END ARCHITECTURE structural;
```

- Top-level Multiplier Module

Top-level Multiplier

```
ARCHITECTURE structural OF Multiplier IS
BEGIN
    dpu : ENTITY WORK.datapath(procedural)
        PORT MAP (clk, clr_P, load_P, load_B,
                 msb_out_t, lsb_out_t, sel_sum,
                 load_A, Shift_A, databus, A0 );
    cu : ENTITY WORK.controller(procedural)
        PORT MAP (clk, start, A0, clr_P, load_P, load_B,
                 msb_out_t, lsb_out_t, sel_sum,
                 load_A, Shift_A, done );

    msb_out <= msb_out_t;
    lsb_out <= lsb_out_t;
END ARCHITECTURE structural;
```

- Top-level Multiplier Module (Continued)

Booth Multiplier

- Booth algorithm is for signed number multiplication.
- The algorithm is similar to the sequential multiplication shift-and-add algorithm, except that two bits, instead of only one bit, will be considered for making shift, add, and subtract decisions.
- An extra bit (initially 0) is added to the right of A, and decisions for adding B to the partial product ($P+B$) and shifting, subtracting B from the partial product ($P-B$) and shifting, or just shifting the partial product will be based on the right-most two bits of the extended A.

Booth Multiplier- Example

A×B

B=01101101

A=10110110

A is a negative number.


A: 101101100 : +0 × 2⁰ = 000
 101101100 : -1 × 2¹ = -002
 101101100 : -0 × 2² = 000
 101101100 : +1 × 2³ = +008
 101101100 : -1 × 2⁴ = -016
 101101100 : -0 × 2⁵ = 000
 101101100 : +1 × 2⁶ = +064
 101101100 : -1 × 2⁷ = -128

-074

A×B= (B× +000) + (B× -002) + (B× -000) + (B× +008) +
 (B×-016) + (B× -000) + (B× +064) + (B× -128)


B: 1101
 A: 1011 ← = 8 + 2 + 1
 8
 4
 2
 1
 = 11

Booth Multiplier

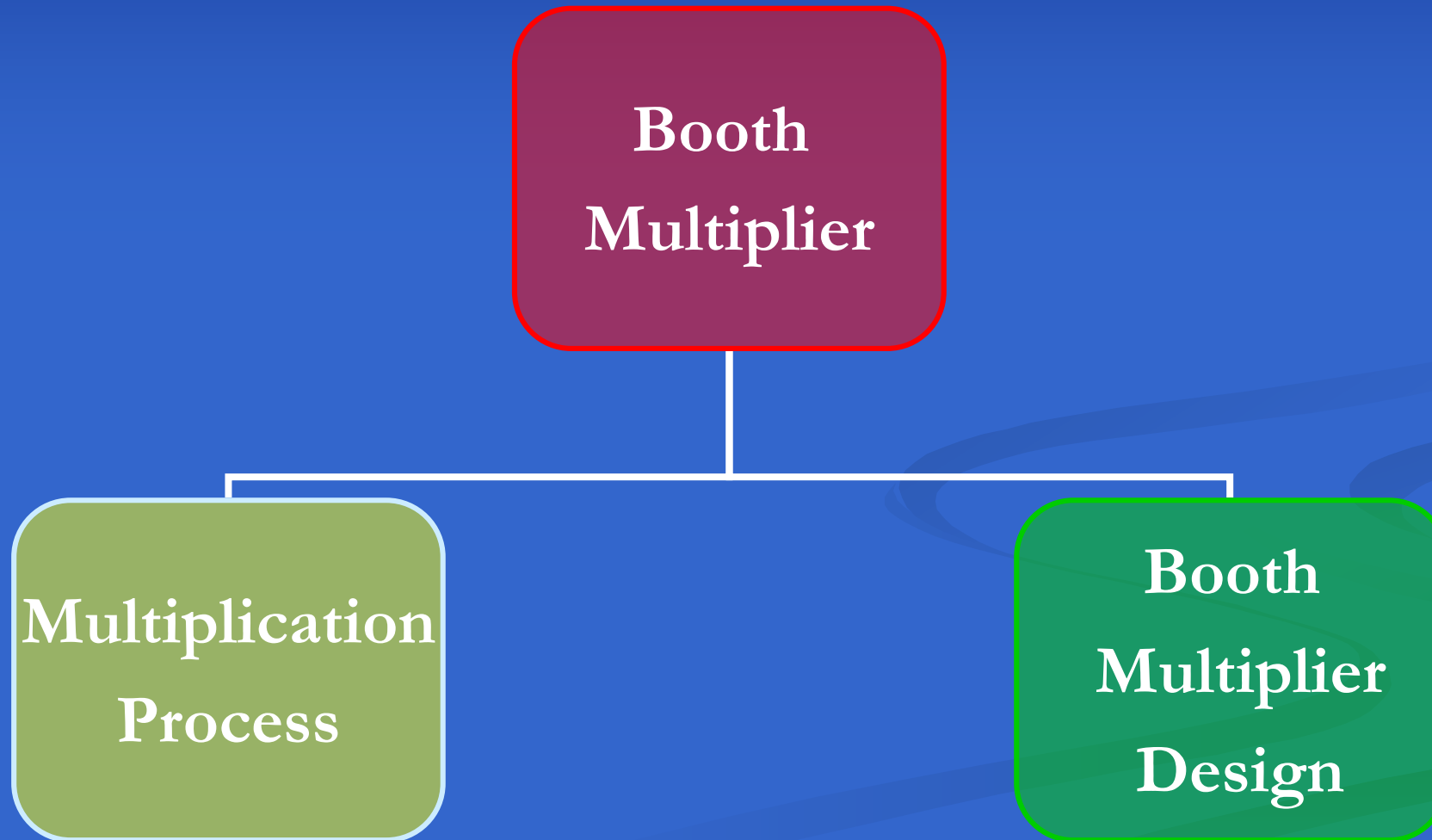


Multiplication Process

- Initialization:
 - Two registers Mcand containing first operand and P containing the result
Mcand is 32-bit and P is 65-bit register
 - Mcand = A, P = {32'b0, B, 1'b0}
- **step1:** Check the two lowest bits of P
 - 11 or 00: go to step 3.
 - 01 or 10: go to step 2
- **step2:**
 - LSBs of P: 01 => Mcand is added to the most 32 bits of P.
 - LSBs of P: 10 => Mcand is subtracted from the most 32 bits of P.
- **step3:** Shift P one place to the right
- End of Multiplication: P[64:1] contains the result.

 

Multiplication Process

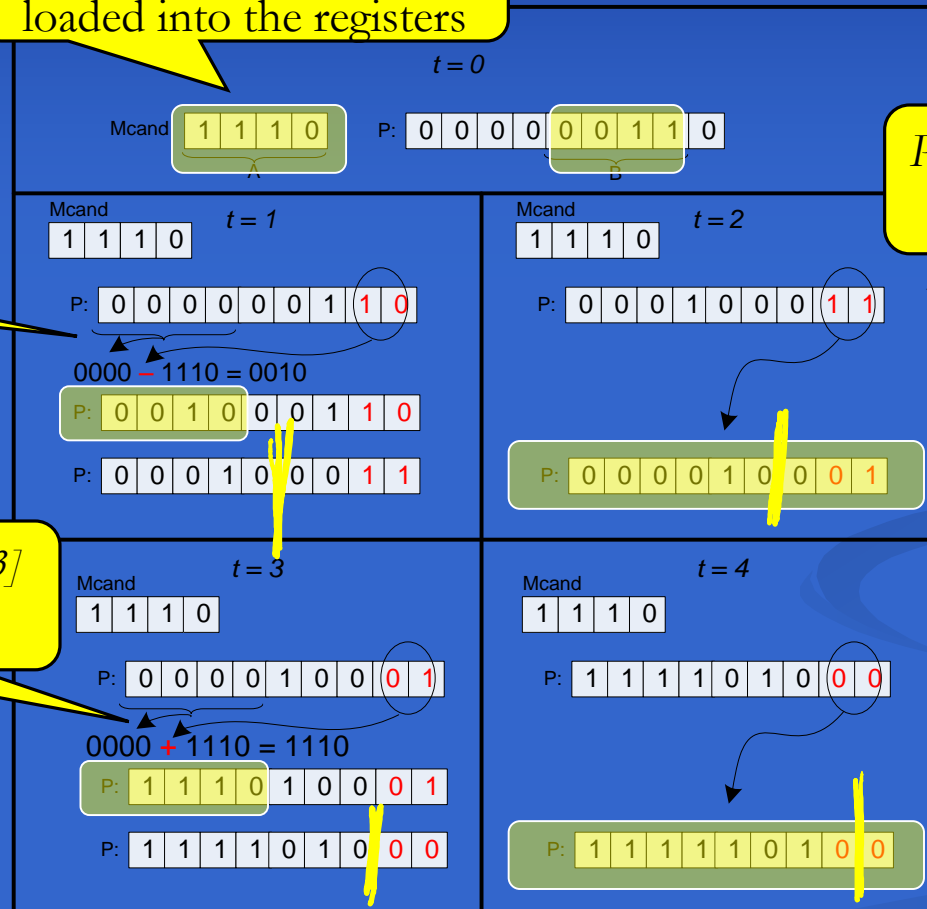Inputs A and B are loaded into the registers




$Mcand$ is subtracted from $P[64:33]$ because $P[1:0]$ is 10.

$P[1:0]$ is 11 and 00, P is shifted to right.

$Mcand$ is added to $P[64:33]$ because $P[1:0]$ is 01.

- Hardware Oriented Multiplication Process (continued)
 VHDL: Modular Design and Synthesis of Cores and Systems Copyright Z. Navabi

Multiplication Process

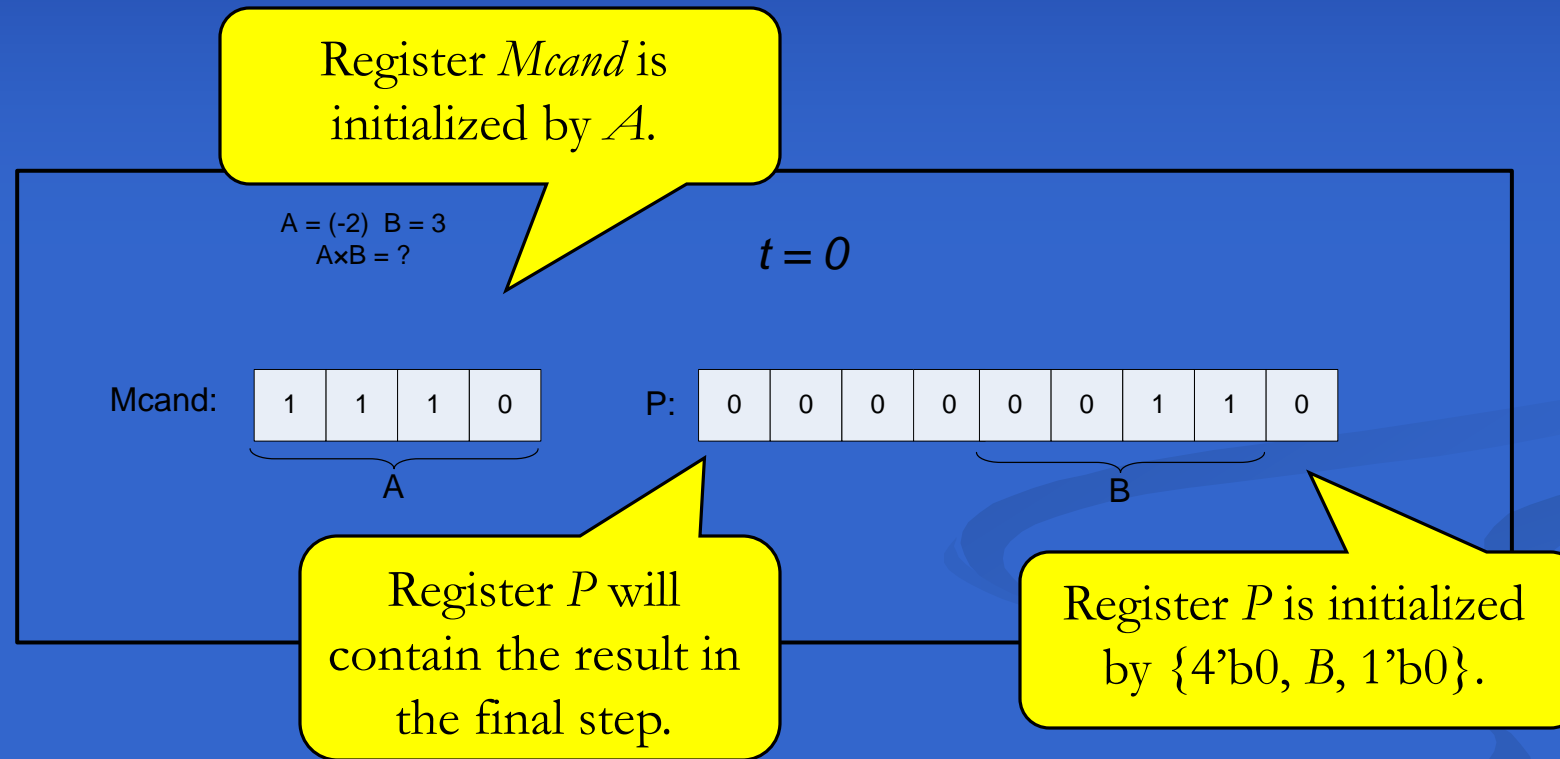

- Hardware Oriented Multiplication Process (Continued)

Multiplication Process

$t = 1$

Mcand



1	1	1	0
---	---	---	---

First, we check the two LSBs of P .



$0000 - 1110 = 0010$

  Second, because $P[1:0]$ is 10, we subtract M_{cand} from higher part of P .



Third, we shift P one place to right.

- Hardware Oriented Multiplication Process (Continued)



Multiplication Process

$t=2$

First, we check the two LSBs of P .

Mcand

1	1	1	0
---	---	---	---

  

Second, because $P[1:0]$ is 11, we only need to shift P to right.

- Hardware Oriented Multiplication Process (Continued)


Multiplication Process

$t = 3$

First, we check the two LSBs of P .

Mcand



1	1	1	0
---	---	---	---

 

Second, because $P[1:0]$ is 01, we add $Mcand$ to upper 32 bits of P .

The MSB is one due to performing signed shift on P

$0000 + 1110 = 1110$

  

Third, we shift P one place to right.

- Hardware Oriented Multiplication Process (Cont...)


Multiplication Process

$t = 4$

First, we check the two LSBs of P .

Second, because $P[1:0]$ is 00, we only need to shift P to right.

 
The MSB is one due to performing signed shift on P




The final result is now on the $P[64:1]$.

Hardware Oriented Multiplication Process


Booth Multiplier

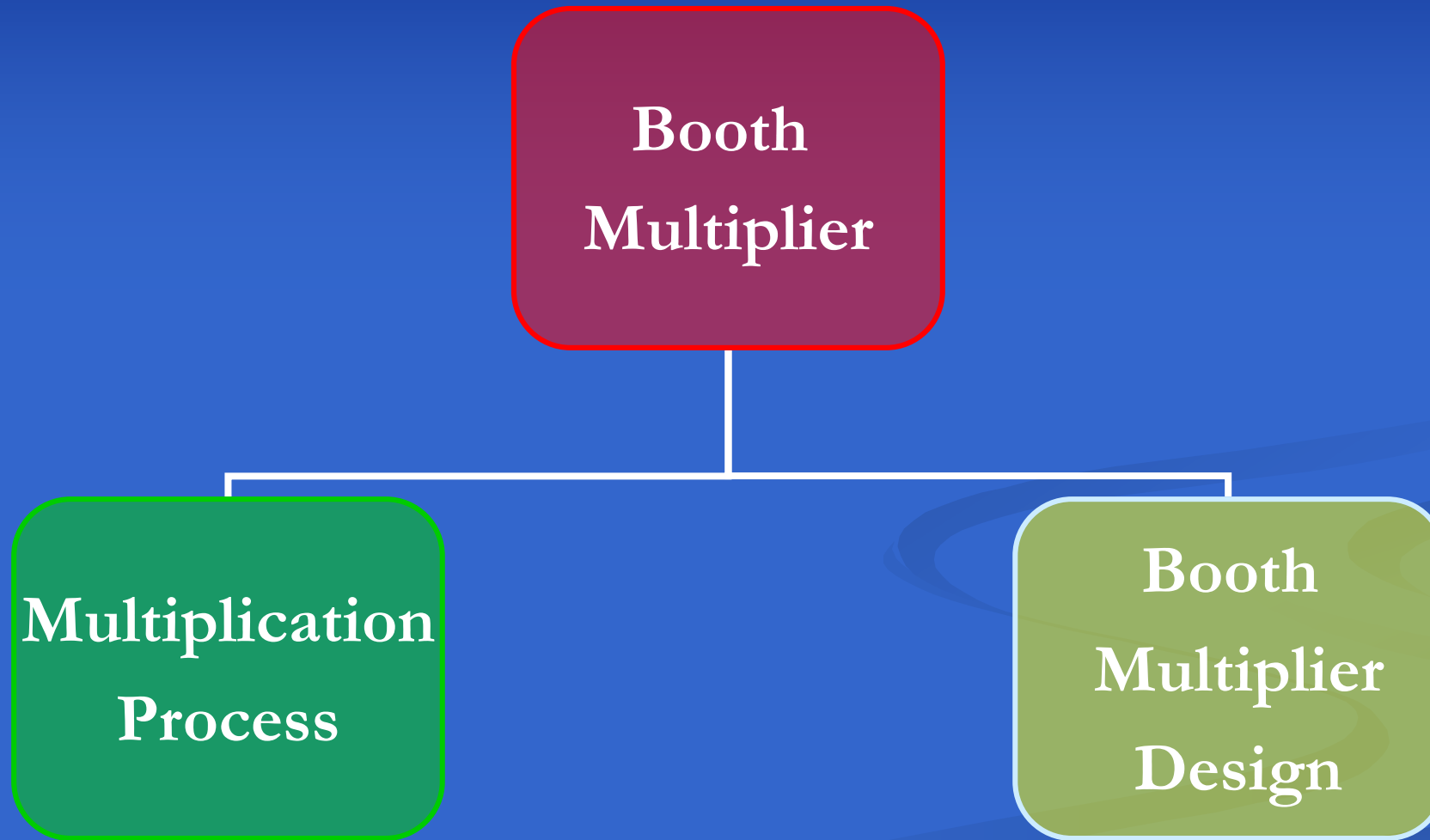

Booth Multiplier Design

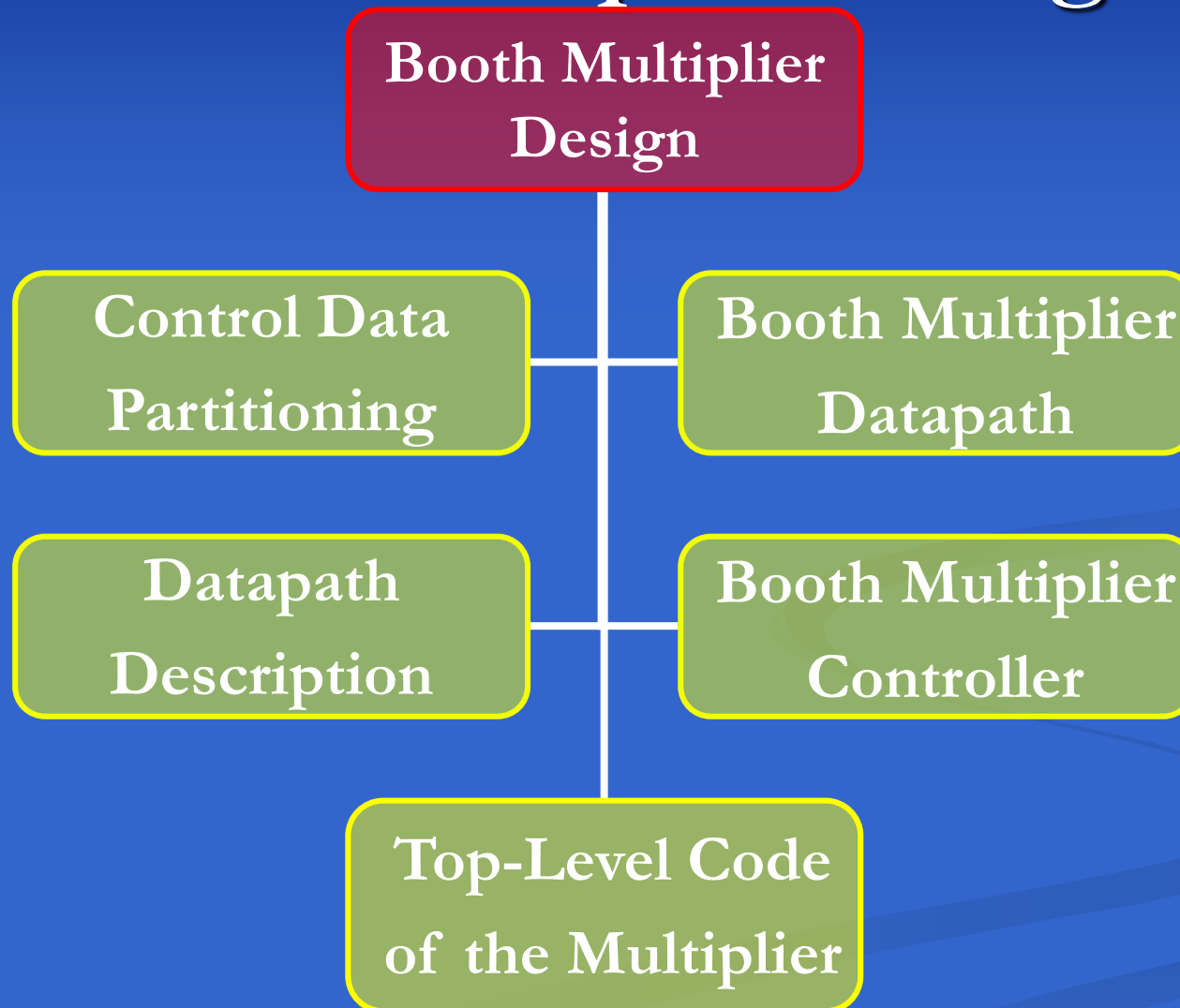

Booth Multiplier Design

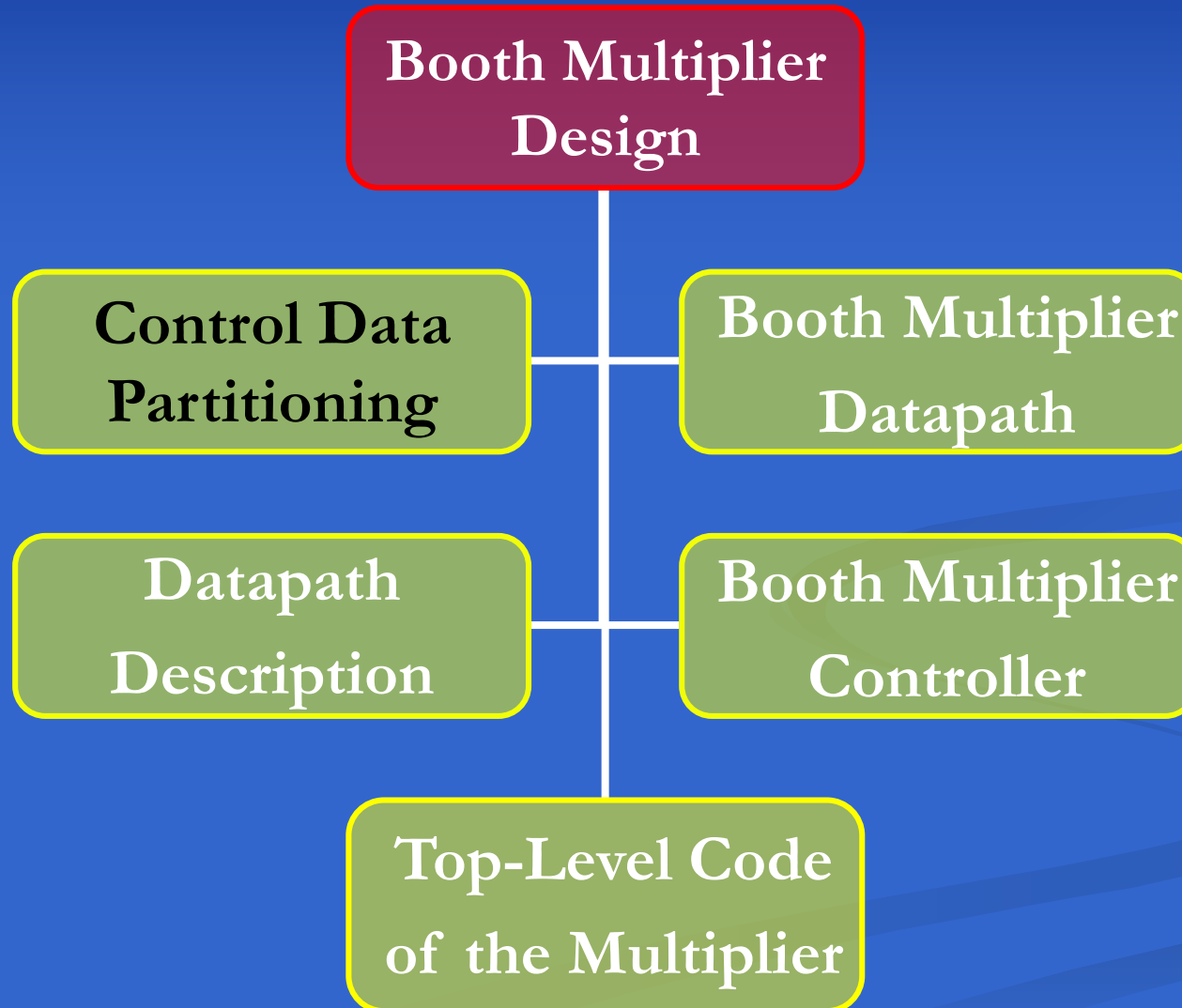

Control Data Partitioning


Data part consists of registers, logic units, and their interconnecting buses.

In each new state, several control signals are issued, and the components of the datapath start reacting to these signals.

Triggered with the same clock signal


The controller is a state machine that issues control signals for control of what gets clocked into the data registers.

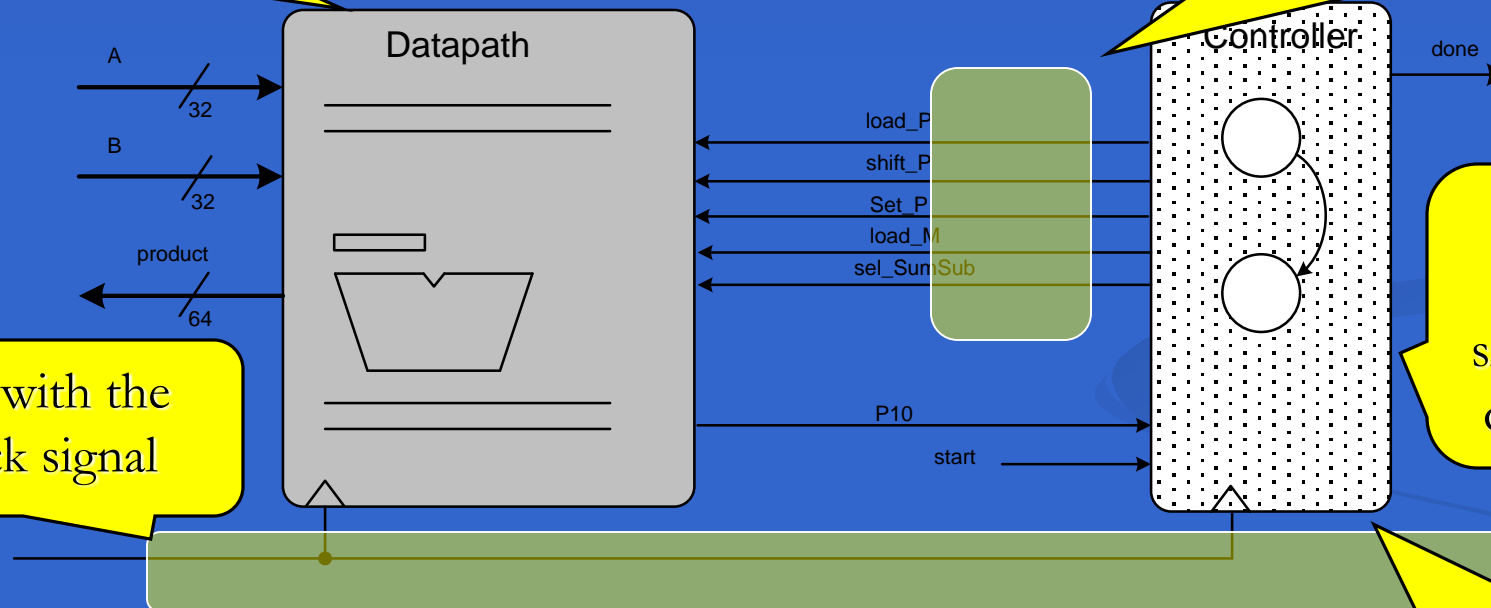On the rising edge of the system clock, the controller goes into a new state.




▪ Datapath and Controller

Booth Multiplier Design

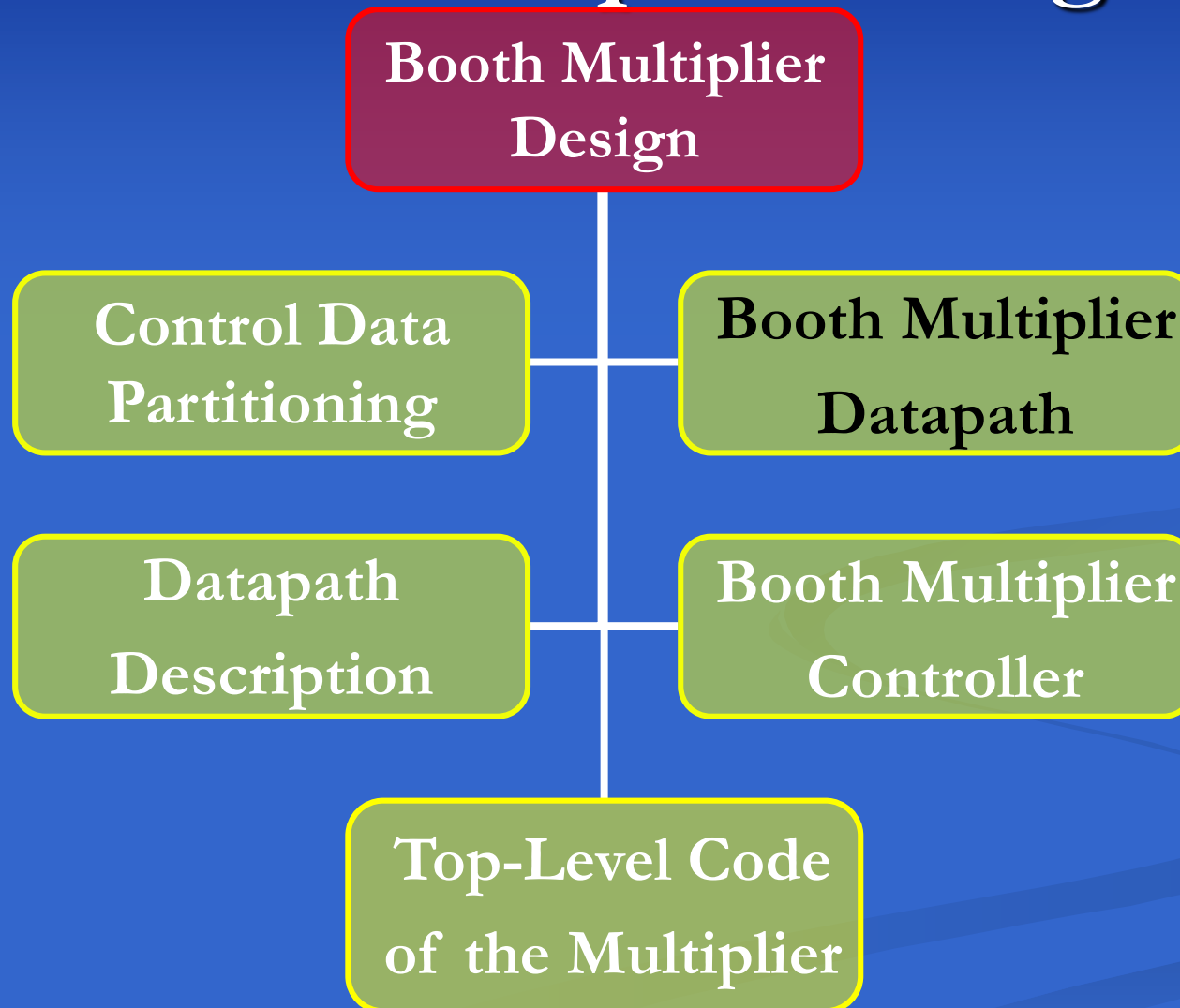


Multiplier Data

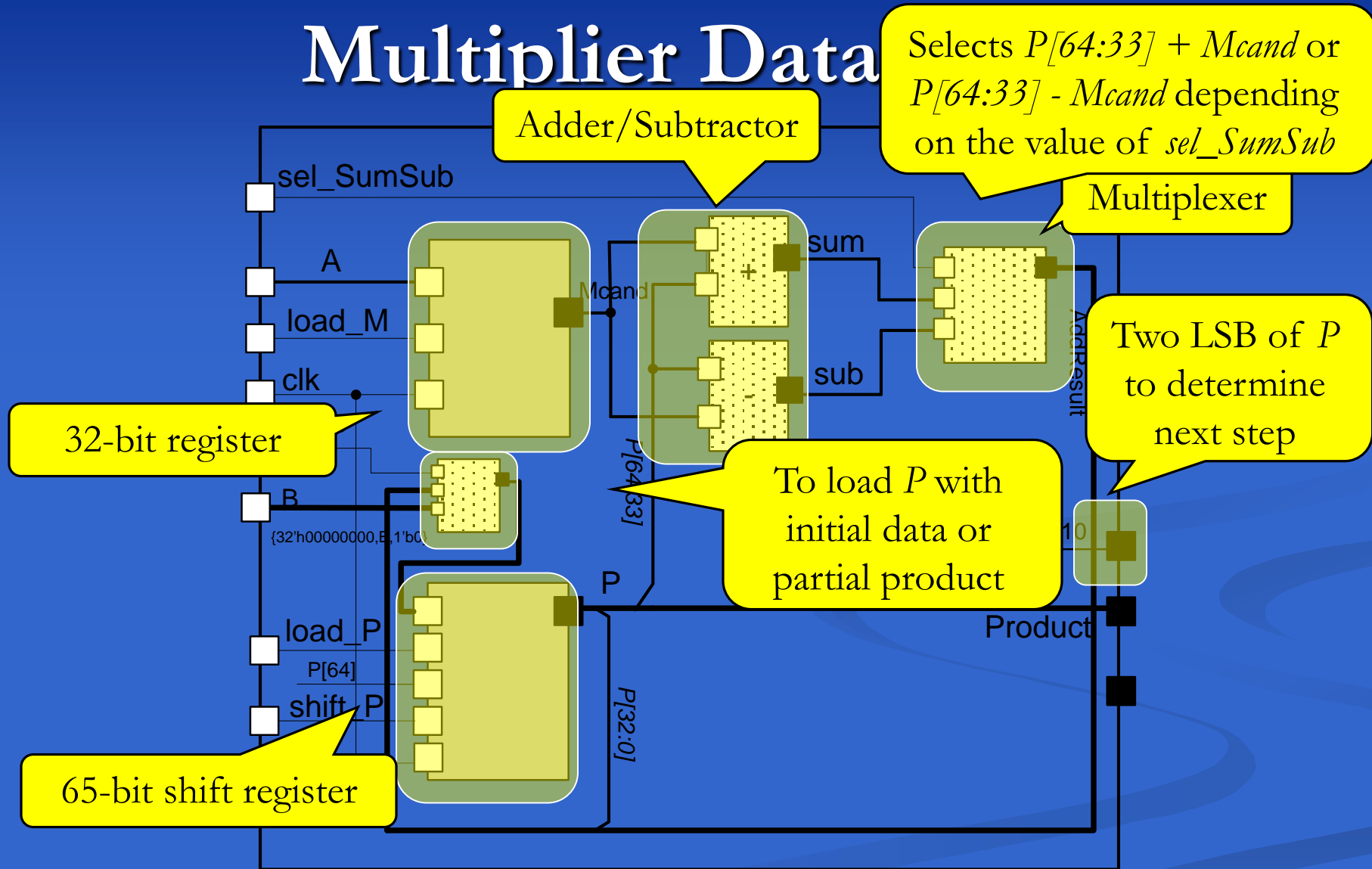

■ Multiplier Block Diagram

Booth Multiplier Design

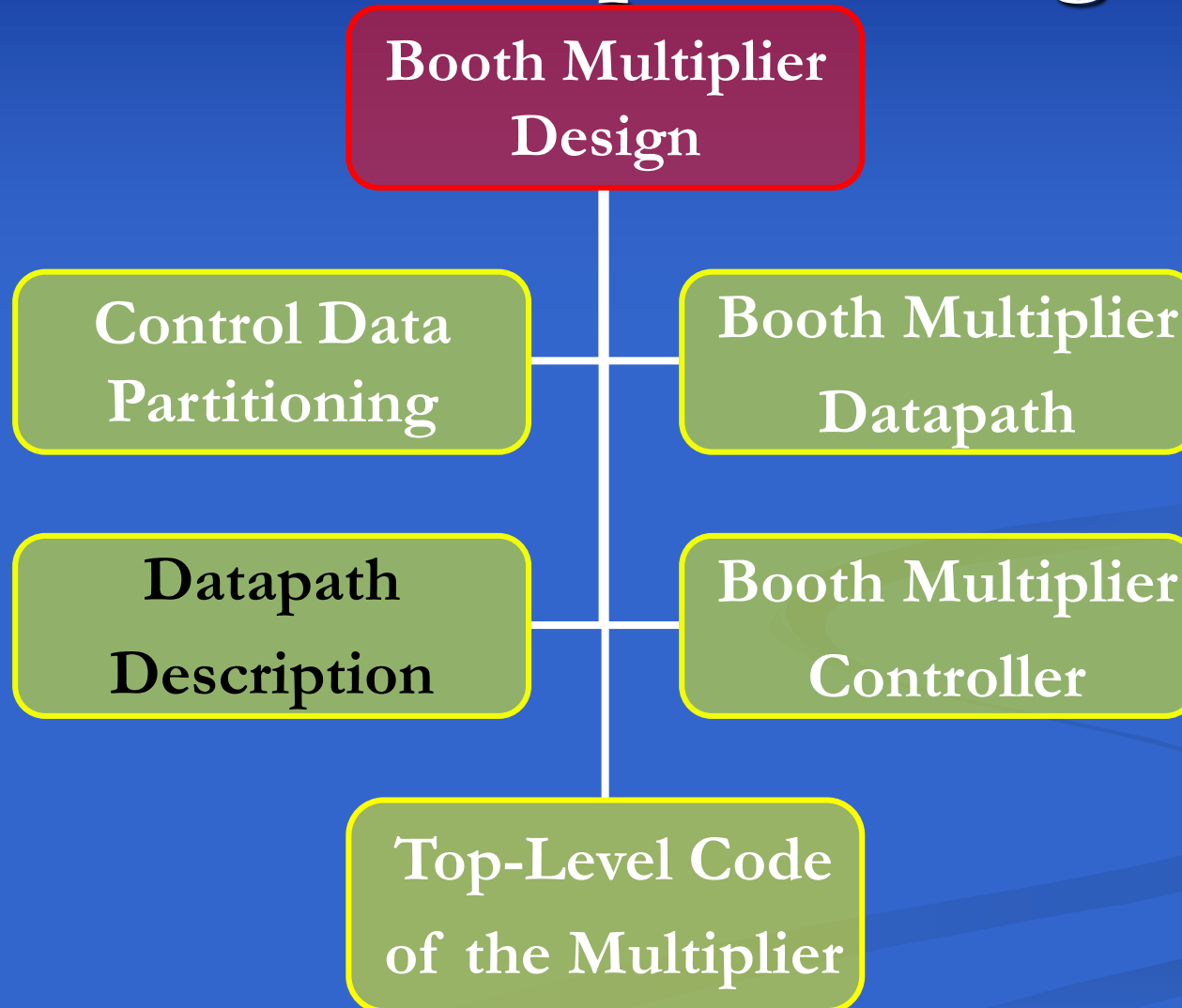

Datapath Description

```
ENTITY datapath is
    PORT( clk, Set_P, load_M, load_P,
          shift_P, preset, sel_SumSub : IN std_logic;
          A, B : IN std_logic_vector (31 downto 0);
          Product : OUT std_logic_vector (63 downto 0);
          P10 : OUT std_logic_vector (1 downto 0));
END ENTITY;

ARCHITECTURE procedural OF datapath IS

    SIGNAL sum, sub, AddResult, Mcand : std_logic_vector ( 31 downto 0);
    SIGNAL data, P : std_logic_vector (64 downto 0);
    SIGNAL ls : std_logic_vector (1 downto 0);

BEGIN
```

- Datapath Code

Datapath Description

Represents
32-bit register
Mcand for
keeping input
A

```
PROCESS (clk) BEGIN
    IF (clk = '0' AND clk'EVENT) THEN
        IF (load_M = '1') THEN Mcand <= A;
        END IF;
    END IF;
END PROCESS;

PROCESS (clk) BEGIN
    IF (clk = '0' AND clk'EVENT) THEN
        CASE (ls) IS
            WHEN "01" => P <= P(64) & P(64 DOWNTO 1);
            WHEN "10" => P <= data;
            WHEN OTHERS => P <= P;
        END CASE;
    END IF;
END PROCESS;

.....
```

Implements the
65-bit shift-register for keeping
the result and partial products

- Datapath Code (continued)

Two LSB of P going to controller to determine the next step

Datapath Description

```
P10 <= P(1 downto 0);  
sum <= P(64 downto 33) + Mcand;  
sub <= P(64 downto 33) - Mcand;
```

The *Mcand* is added or subtracted to/from upper 32 bits of P

```
AddResult <= sum WHEN sel_SumSub = '1' ELSE sub;
```

sel_SumSub selects *sum* or *sub* to store in the P

```
data <= ("00000000000000000000000000000000") & B & '0') WHEN Set_P = '1'  
      ELSE (AddResult & P(32 downto 0)) ;
```

Initial data or intermediate data going to P based on *Set_P*

```
Product <= P(64 downto 1);
```


```
ls <= load_P & shift_P;
```

```
END ARCHITECTURE procedural;
```

The final result will be placed on the *Product*

- Datapath Code (continued)

Booth Multiplier Design

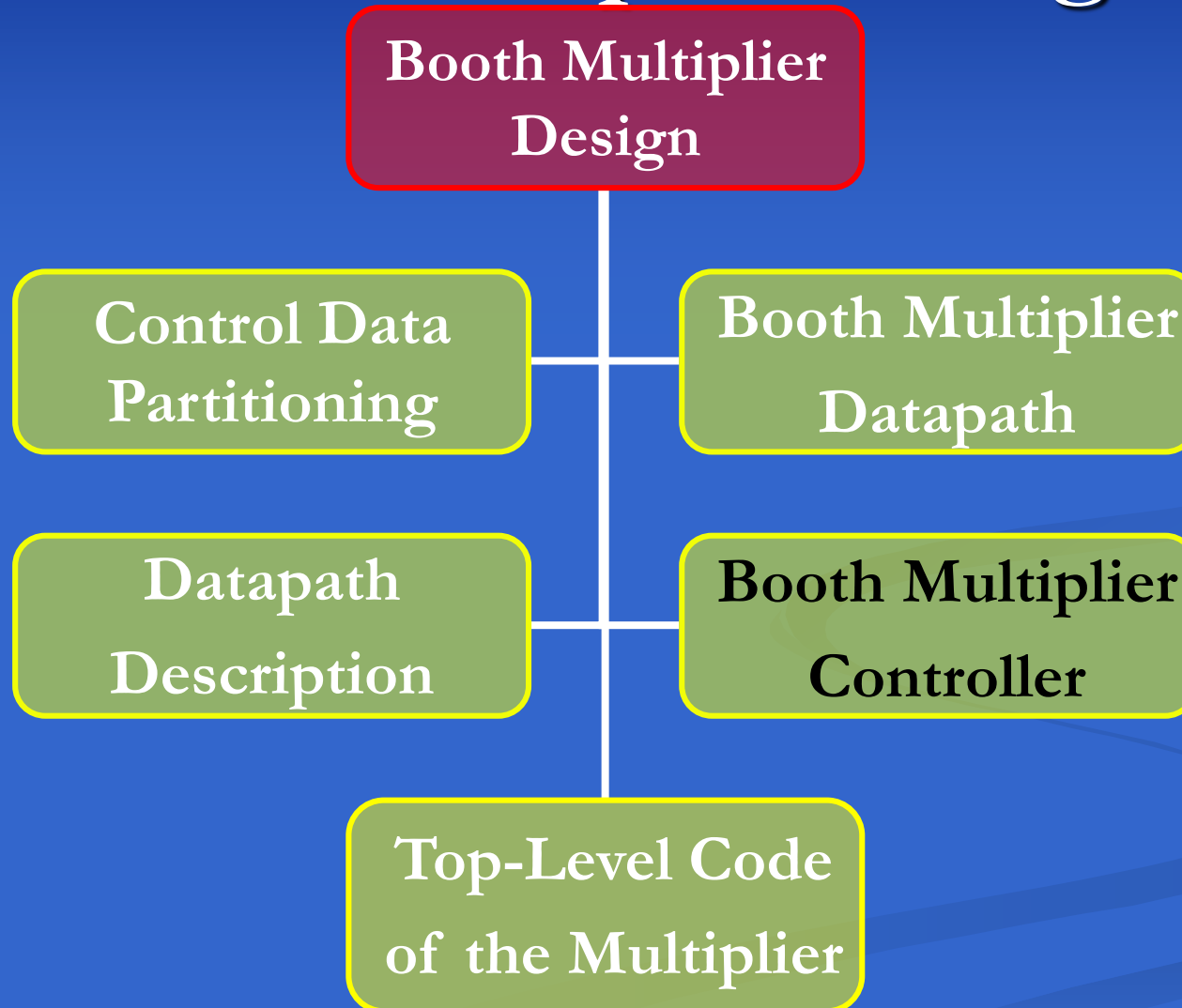

Multiplier Controller

States of Multiplier

idle

Multiplier waits for *start* while loading M and P

Check_2bits

Checking 2 LSB of P to specify the next step

Sum_Sub

Multiplier adds or subtracts M and to/from $P[64:33]$ based on $P10$

Shift

Multiplier shifts P one place to right

- Multiplier Control States

Multiplier Controller

```
ENTITY controller IS PORT (clk, start : IN std_logic;
                           P10 : IN std_logic_vector (1 downto 0);
                           Set_P, load_M, load_P : OUT std_logic;
                           shift_P, sel_SumSub, done : OUT std_logic);
END ENTITY;

ARCHITECTURE procedural OF controller IS
    TYPE state IS (idle, Check_2bits, Sum_Sub, Shift);
    SIGNAL current, nextState : state;
    SIGNAL CntValue : std_logic_vector (5 downto 0);
    SIGNAL preset, cntEn, cntZero : std_logic;
BEGIN
    .....
```

States of multiplier

- Controller Code

Multiplier Controller


```
PROCESS (clk) BEGIN
  IF (clk = '0' AND clk'EVENT) THEN
    IF (preset = '1') THEN
      CntValue <= "100000";
    ELSE
      IF (cntEn = '1') THEN
        CntValue <= CntValue - 1;
      ELSE
        CntValue <= CntValue;
      END IF;
    END IF;
  END IF;
END PROCESS;
```

```
cntZero <= '1' WHEN (CntValue = "000000") ELSE '0';
```

- Controller Code

Implements the 6-bit down counter for counting number of steps

Indicates that if all steps are done

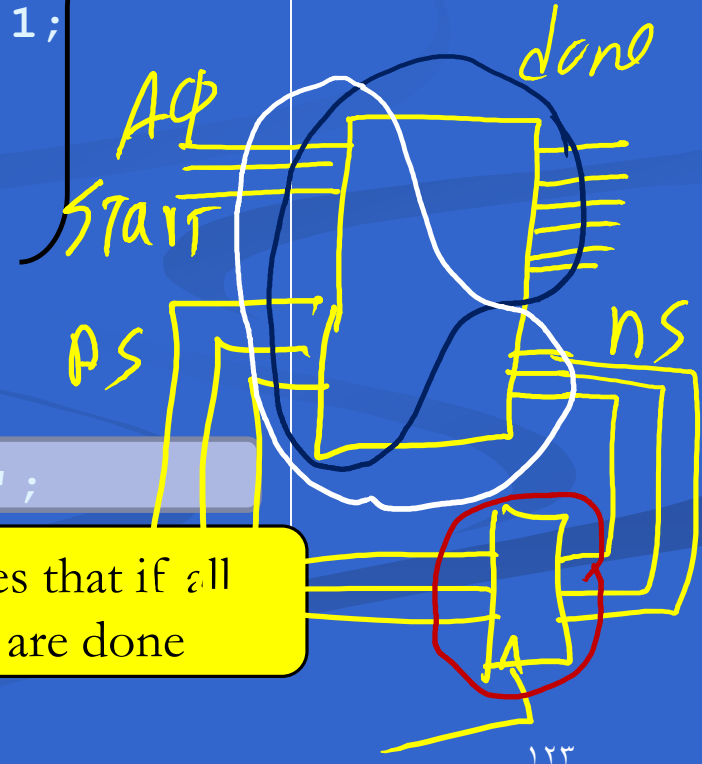

Multiplier Controller

Process block to issue control signals and make state transitions

```
PROCESS (current, start, P10) BEGIN
  Set_P <= '0';      load_M <= '0';      load_P <= '0';
  shift_P <= '0';   sel_SumSub <='0'; cntEn <= '0';
  done <= '0';      preset <= '0';
  CASE ( current ) IS
    WHEN idle =>
      IF (start = '0') THEN
        done <= '1';
      ELSE
        Set_P <= '1'; load_P <= '1';
        load_M <= '1'; preset <= '1';
      END IF;
    WHEN Sum_Sub =>
      IF (P10 = "01") THEN
        load_P <= '1'; sel_SumSub <= '1';
      ELSIF (P10 = "10") THEN
        load_P <= '1';
      END IF;
  END CASE;
END PROCESS;
```

All control signal outputs are set to their inactive values.

To initialize *P* register

To load *Mcand*

To preset the counter to 32

If *P10* is 01, *sel_SumSub* is one, indicating that *Mcand* should be added to upper bits of *P*

If *P10* is 10, *sel_SumSub* remains zero, indicating that *Mcand* should be subtracted from upper bits of *P*

Controller Code (continued)

Multiplier Controller

```
WHEN Shift =>  
    cntEn <= '1';  
    shift_P <= '1';  
WHEN OTHERS =>  
    Set_P <= '0';    load_M <= '0';    load_P <= '0';  
    shift_P <= '0';    sel_SumSub <= '0'; cntEn <= '0';  
    done <= '0';    preset <= '0';  
END CASE;  
END PROCESS;
```

P will be shifted to the right and counter will count down, showing that one step is done.

- Controller Code (continued)

Multiplier Controller

```
PROCESS (current, start, P10, cntZero) BEGIN
  CASE ( current ) IS
    WHEN idle =>
      IF (start = '0') THEN
        nextState <= idle;
      ELSE
        nextState <= Check_2bits;
      END IF;
    WHEN Check_2bits =>
      IF (cntZero = '0') THEN
        IF (P10 = "00" or P10 = "11") THEN
          nextState <= Shift;
        ELSIf (P10 = "10" or P10 = "01") THEN
          nextState <= Sum_Sub;
        END IF;
      ELSE
        nextState <= idle;
      END IF;
  END CASE;
END PROCESS;
```

Another always block for state transition

If $P10$ is 11 or 00, P should only be shifted, otherwise, $Mcand$ should be added or subtracted to/from it before shifting operation.

To check the number of multiplication steps

- Controller Code

Multiplier Controller

```
    WHEN Sum_Sub =>
        nextState <= Shift;
    WHEN Shift =>
        nextState <= Check_2bits;
    END CASE;


END PROCESS;

PROCESS (clk) BEGIN
    IF( clk = '1' and clk'event ) THEN
        current <= nextState;
    END IF;
END PROCESS;

END ARCHITECTURE procedural;
```

- Controller Code

Booth Multiplier Design

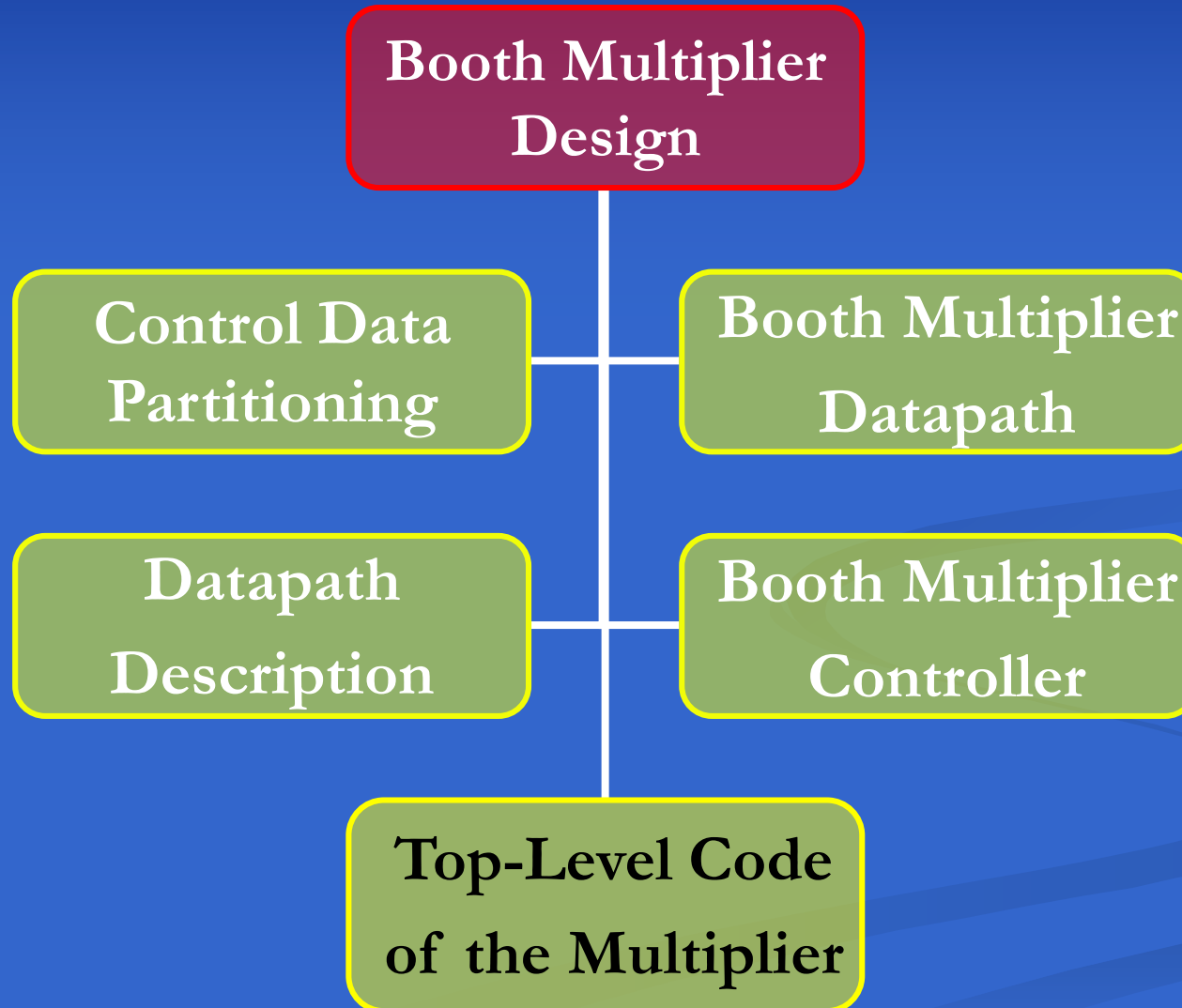

Booth Multiplier

VHDL Implementation

```
ENTITY booth_mult IS
    PORT (mc, mp : IN std_logic_vector (7 downto 0);
          clk, start : IN std_logic;
          prod : OUT std_logic_vector (15 downto 0);
          busy : OUT boolean);
END ENTITY booth_mult;
ARCHITECTURE behavioral OF booth_mult IS
    SIGNAL A, M : std_logic_vector (mc'RANGE);
    SIGNAL Q : std_logic_vector (mc'LENGTH DOWNT0 0);
    SIGNAL sum, dif : std_logic_vector (mc'RANGE);
    SUBTYPE cnt IS INTEGER RANGE 0 TO mc'LENGTH;
    SIGNAL count : cnt := 0;
BEGIN
    . . . . .
END ARCHITECTURE behavioral;
```

- Booth Algorithm VHDL Code

Booth Multiplier VHDL Implementation

```
BEGIN
  sum <= A + M;
  dif <= A - M;
  prod <= A & Q (mc'LENGTH DOWNTO 1);
  busy <= (count < mc'LENGTH);
  Counter: PROCESS (clk) BEGIN
    IF (clk = '1' AND clk'EVENT) THEN
      IF (start = '1') THEN count <= 0;
      ELSIF (count < mc'LENGTH) THEN count<= count + 1;
      END IF;
    END IF;
  END PROCESS;
  . . . . .
END ARCHITECTURE behavioral;
```

- Booth Algorithm VHDL Code (Continued)

Booth Multiplier VHDL Implementation

```
RegClocking: PROCESS (clk) BEGIN
  IF (clk = '1' AND clk'EVENT) THEN
    IF (start = '1') THEN
      A <= (OTHERS => '0');
      M <= mc;
      Q <= mp & '0';
    ELSIF (count < mc'LENGTH) THEN
      . . . . .
      . . . . .
    END IF;
  END IF;
END PROCESS;
```

- Booth Algorithm VHDL Code (Continued)

Booth Multiplier VHDL Implementation

```
. . . . .
ELSIF (count < mc'LENGTH) THEN
  CASE Q(1 DOWNT0 0) IS
    WHEN "01" =>                --ADD AND SHIFT
      Q <= sum(0) & Q(Q'LEFT DOWNT0 1);
      A <= sum(sum'LEFT) &
          sum(sum'LEFT DOWNT0 1);
    WHEN "10" =>                --SUBTRACT AND SHIFT
      Q <= dif(0) & Q(Q'LEFT DOWNT0 1);
      A <= dif(dif'LEFT) &
          dif(dif'LEFT DOWNT0 1);
    WHEN OTHERS =>             --SHIFT ONLY
      Q <= A(0) & Q(Q'LEFT DOWNT0 1);
      A <= A(A'LEFT) & A(A'LEFT DOWNT0 1);
  END CASE;
END IF;
END IF;
END PROCESS;
```


Handshaking

- Completely independent from data handling
- Wrappers and Interfacing Utilities help to implement handshaking
- Simple handshaking
- Register file
- Data 32-bit block

Types of handshaking


- Handshaking between two systems
- Handshaking for accessing a shared bus
- Memory handshaking
- DMA mode or burst mode

Why Handshaking


- Two systems want to communicate data and they don't necessarily have the same timing
- The systems have to send some signals before the actual data is transmitted
- Handshaking implementation is a part of the control of the system

Between Two Systems Handshaking


 
- Each system has its own clocking
- They have to have certain signals to talk



Fully Responsive Handshaking


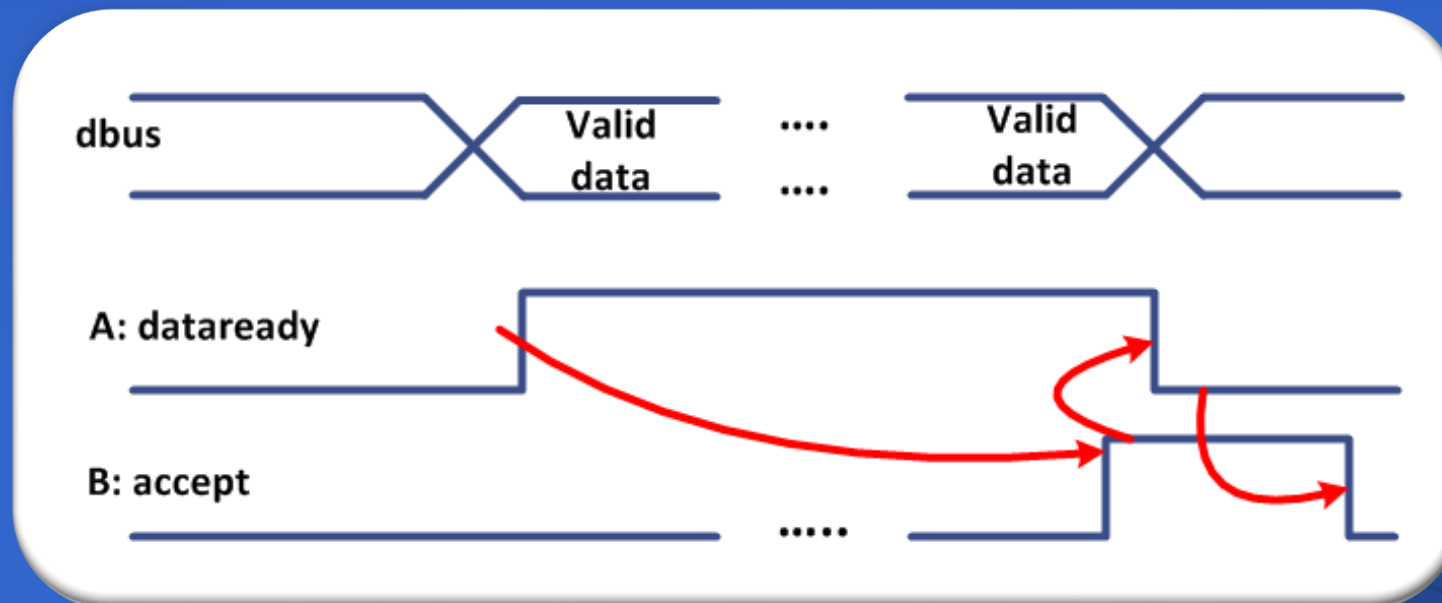


Fully Responsive Handshaking

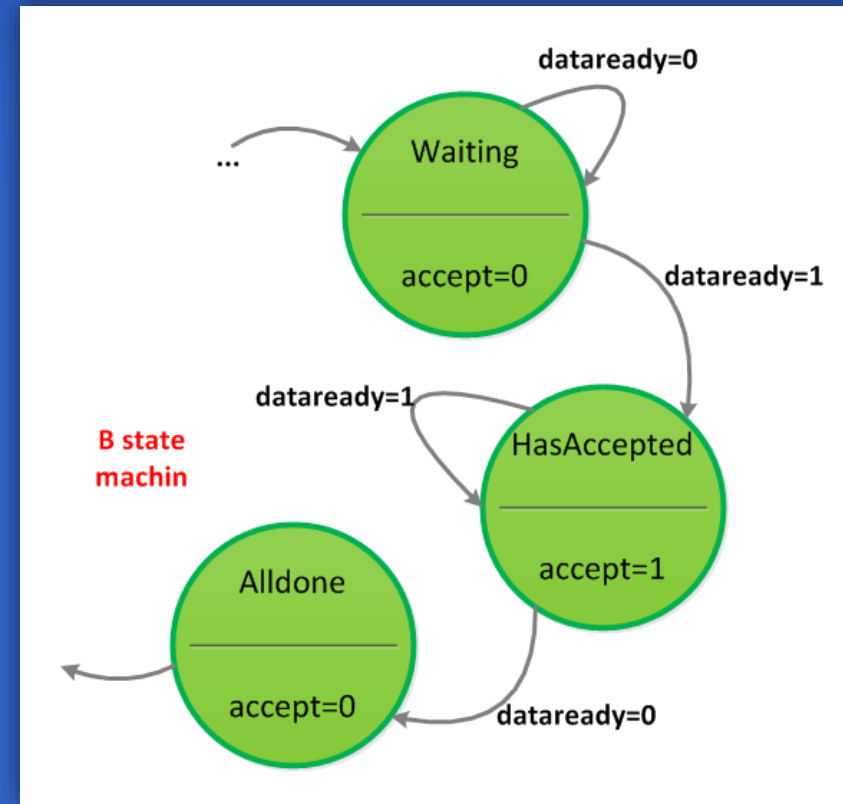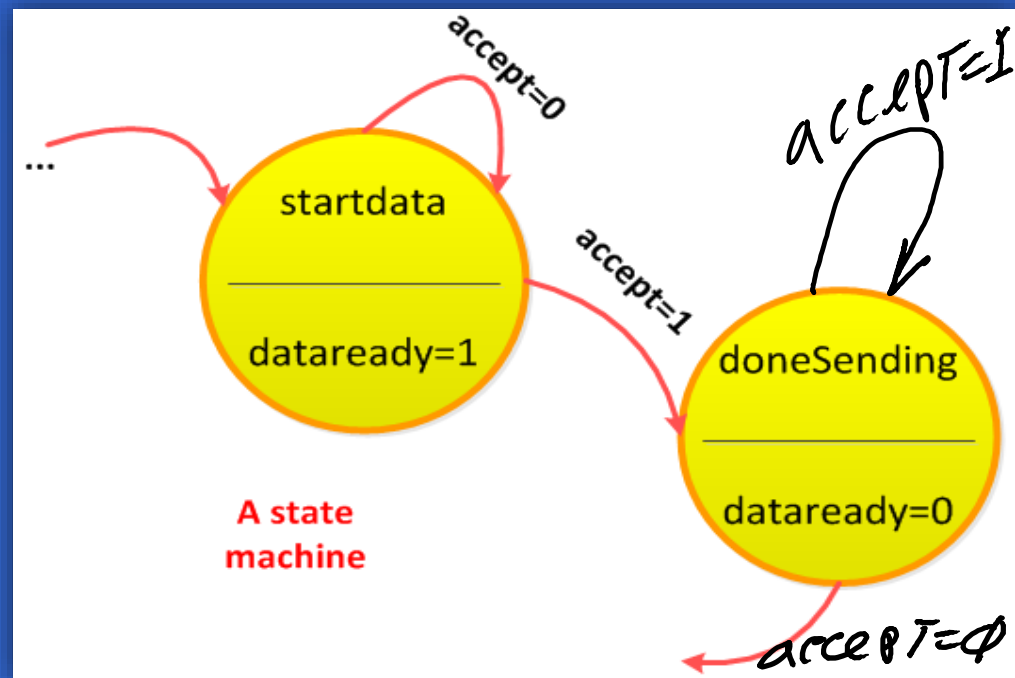

Handshaking for Accessing a Shared Bus

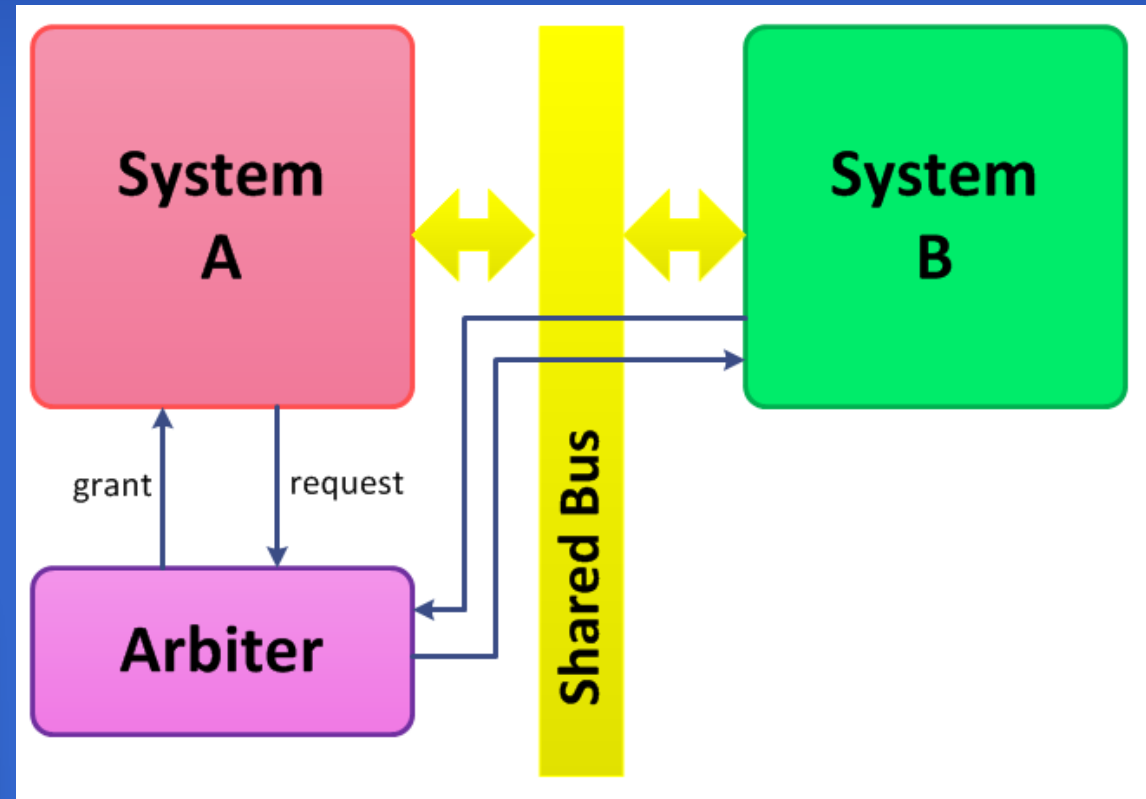
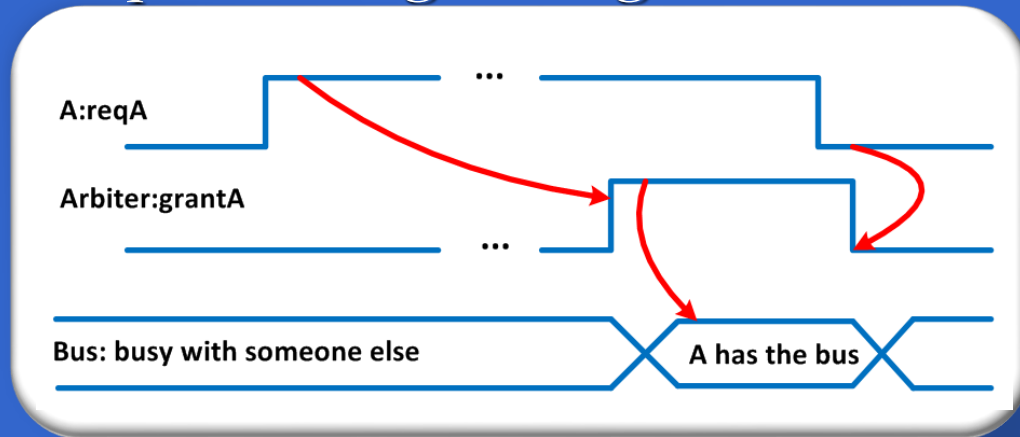
- Using an arbiter to assure that none of the systems will simultaneously access the shared bus
- Each system has to have its own request and grant signals






Two Level Handshaking

- Assume that system A wants to send some data to B through a shared bus
- At first A should talk to the arbiter and catches the bus by issuing a request
- Once it puts the data on bus it informs system B by issuing ready
- After data is picked up by B, A removes its request

Two level handshaking

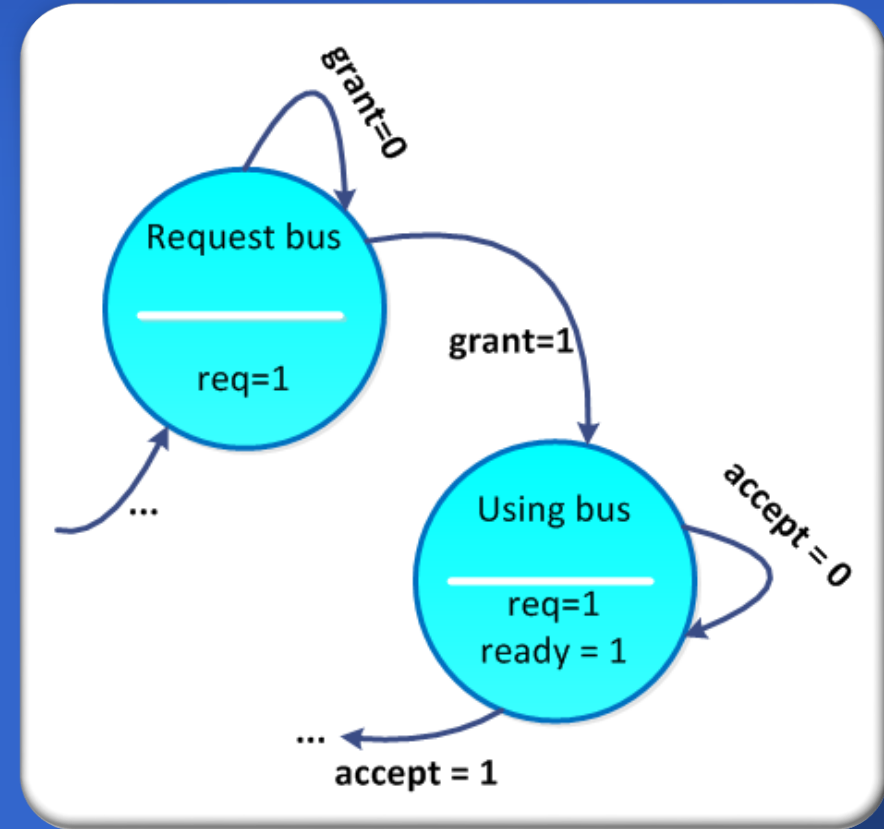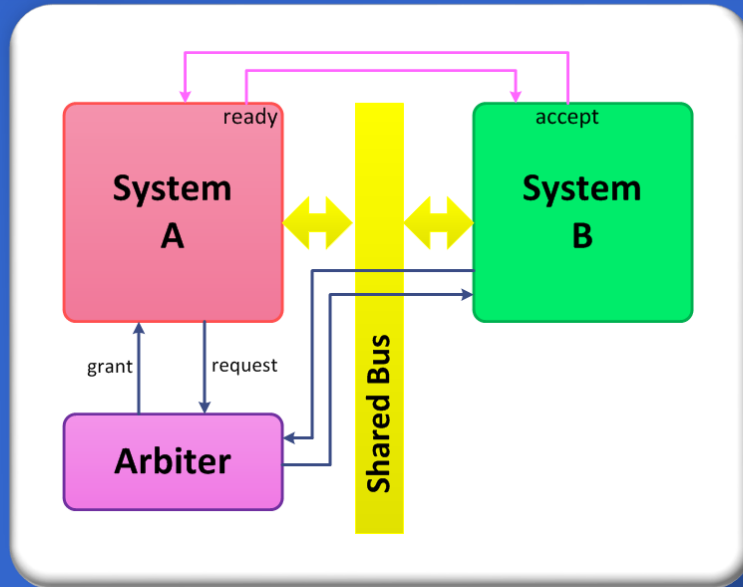

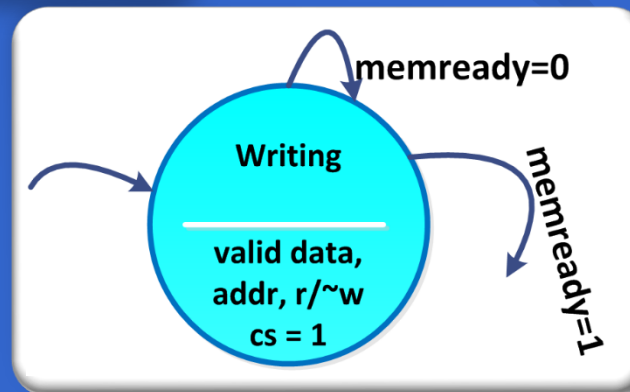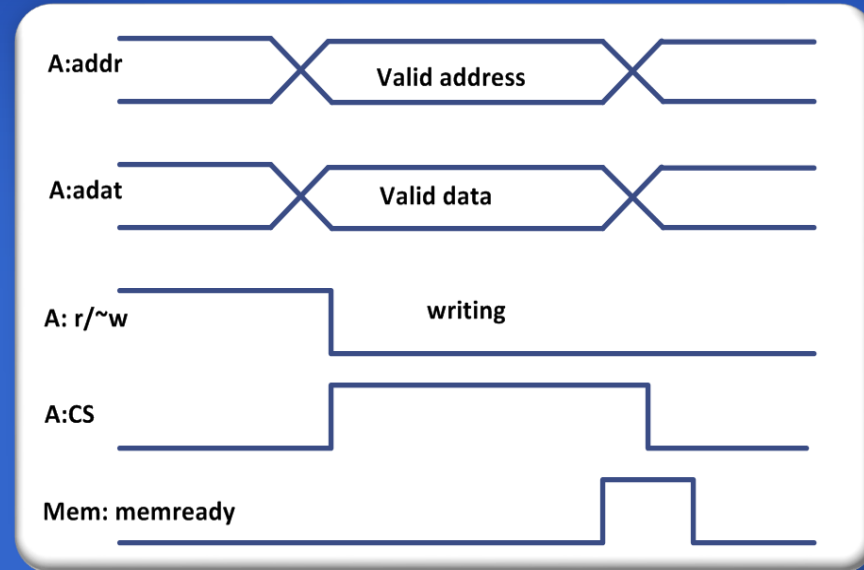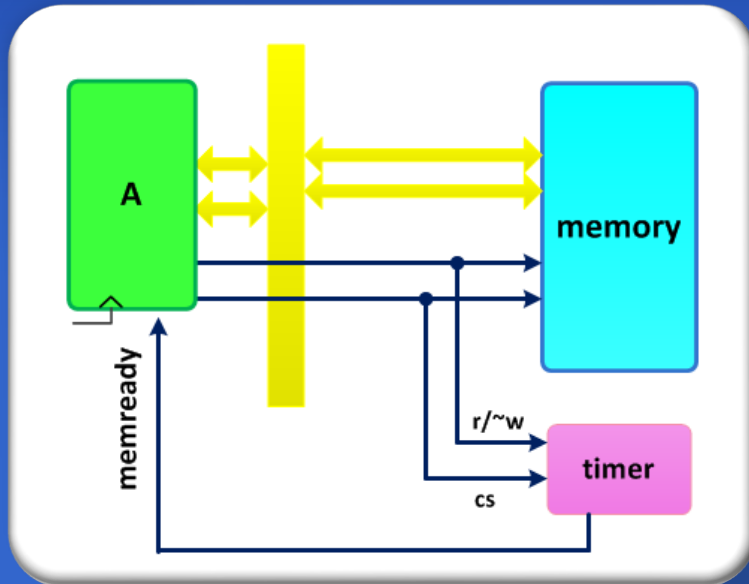Handshaking Type Three: memory handshaking




Combining Type Two and Three of Handshaking



- We can combine type two and three of handshaking
- At first A should deal with arbiter and gets the permission of using the bus
- Then it should send signals to the memory and waits for memready

Handshaking Type Four: DMA Mode Or Burst Mode

 
- Burst writing or DMA writing or block writing




Memory Interface: Design Example

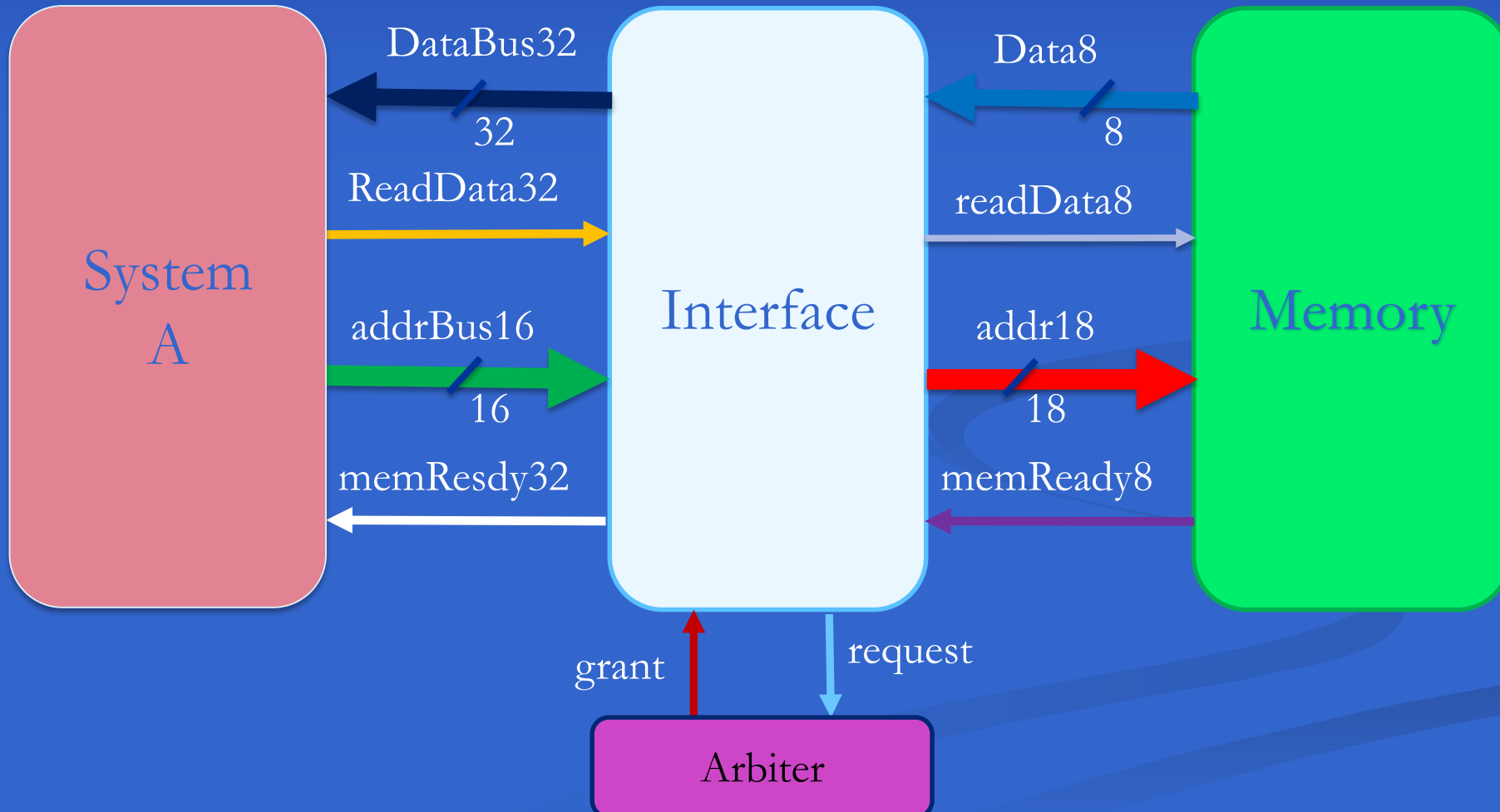 

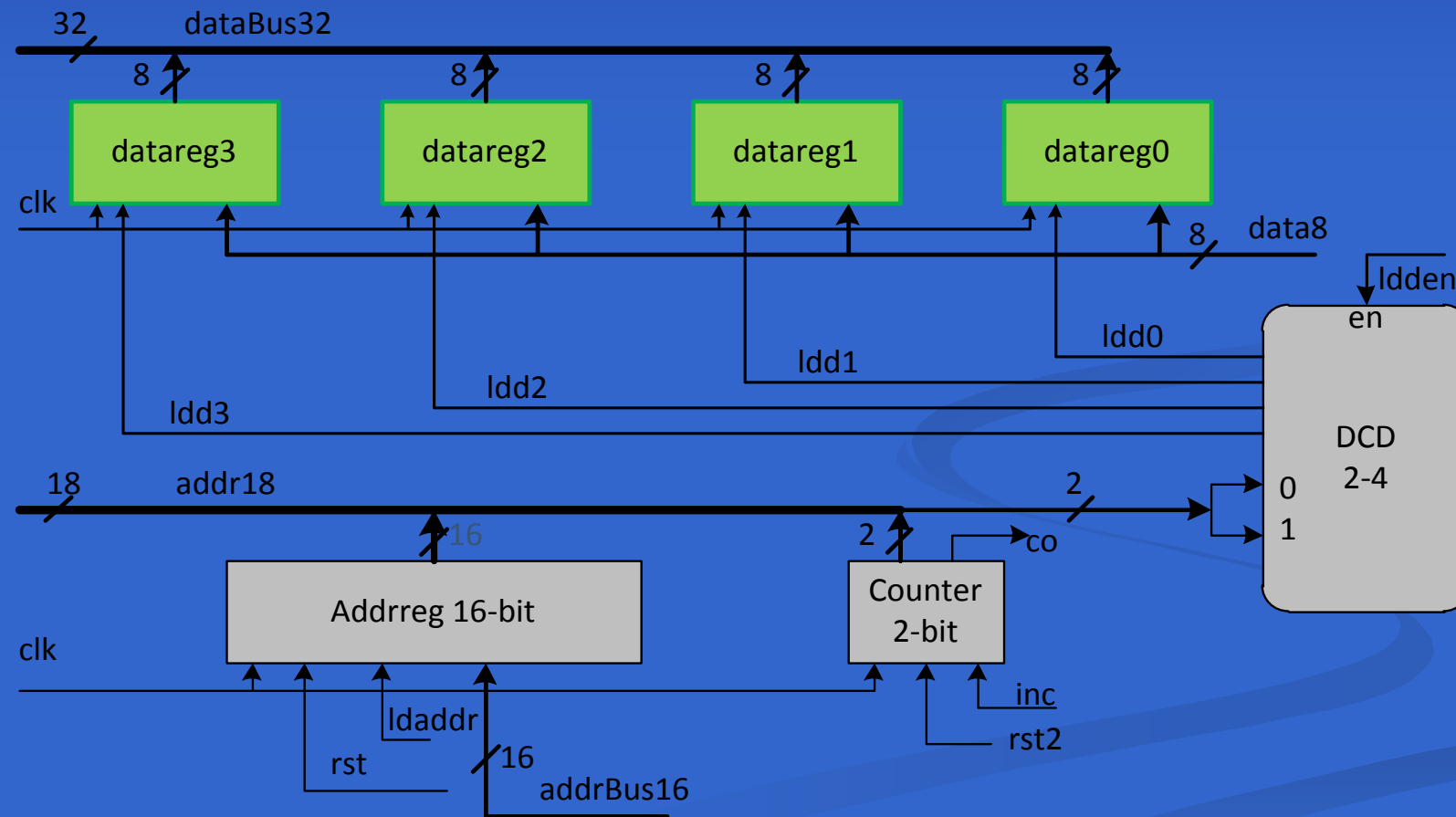
Memory Interface: Datapath & Controller Partitioning




Memory Interface: State Machine

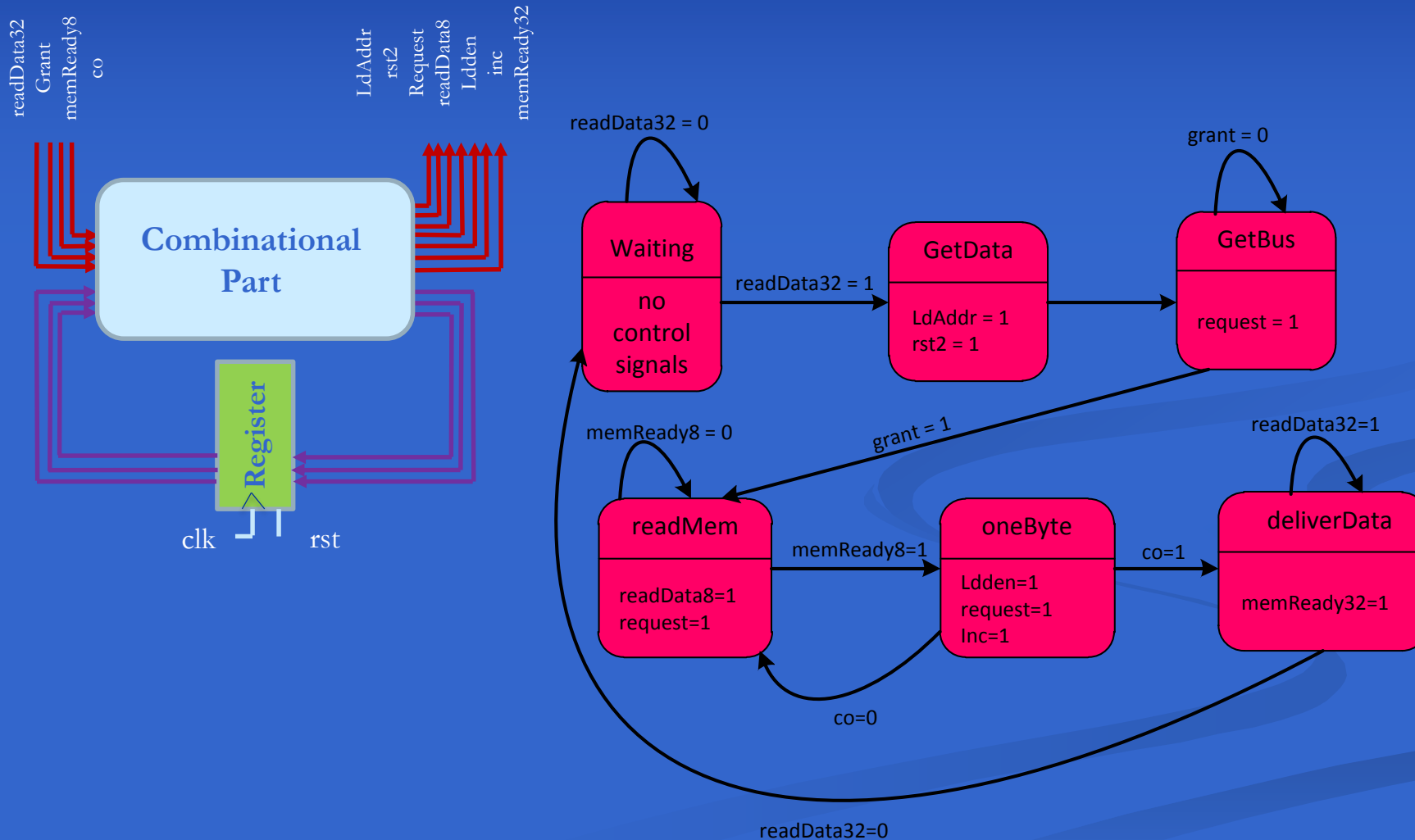


Exponential Module

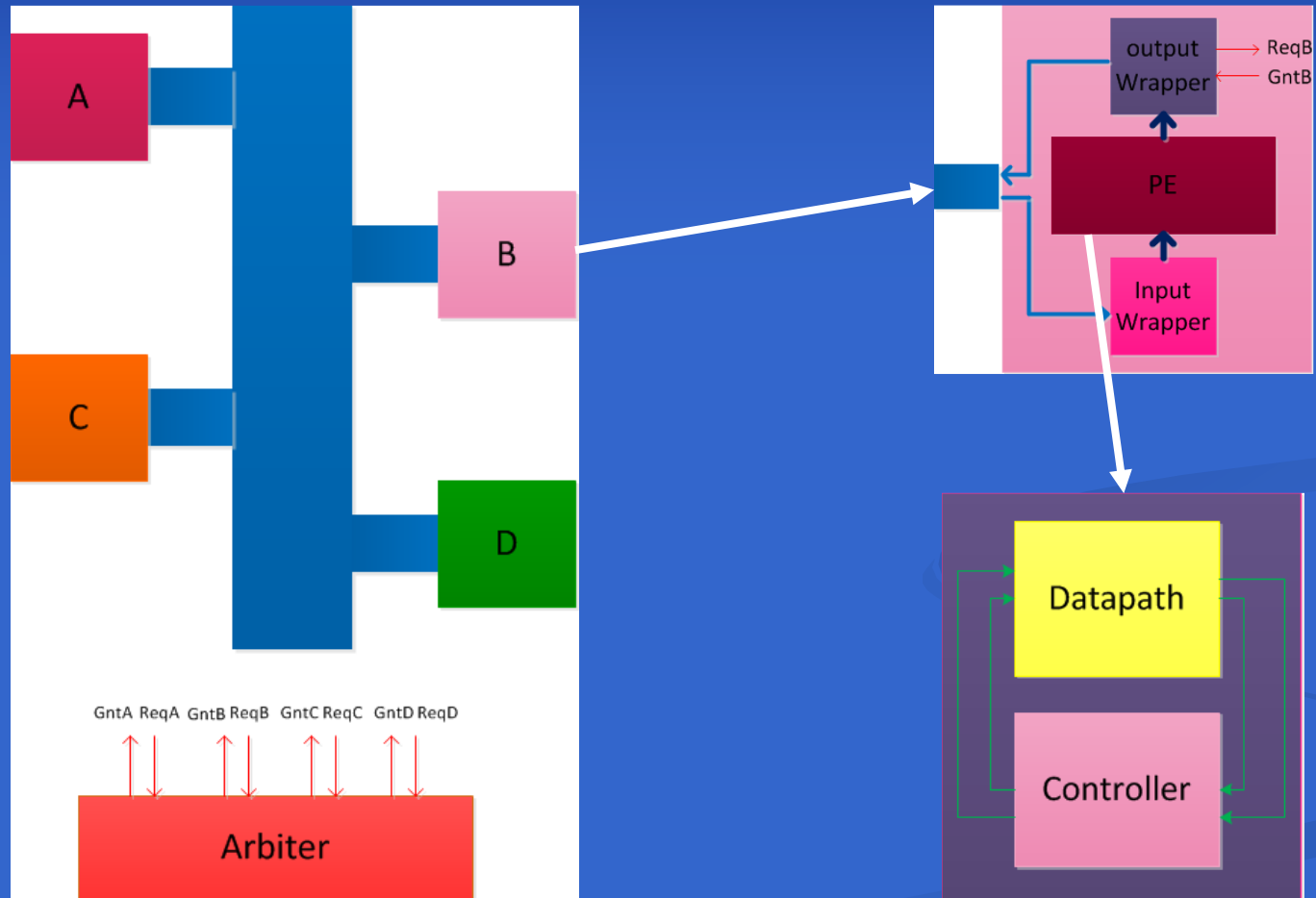

Exponential Module

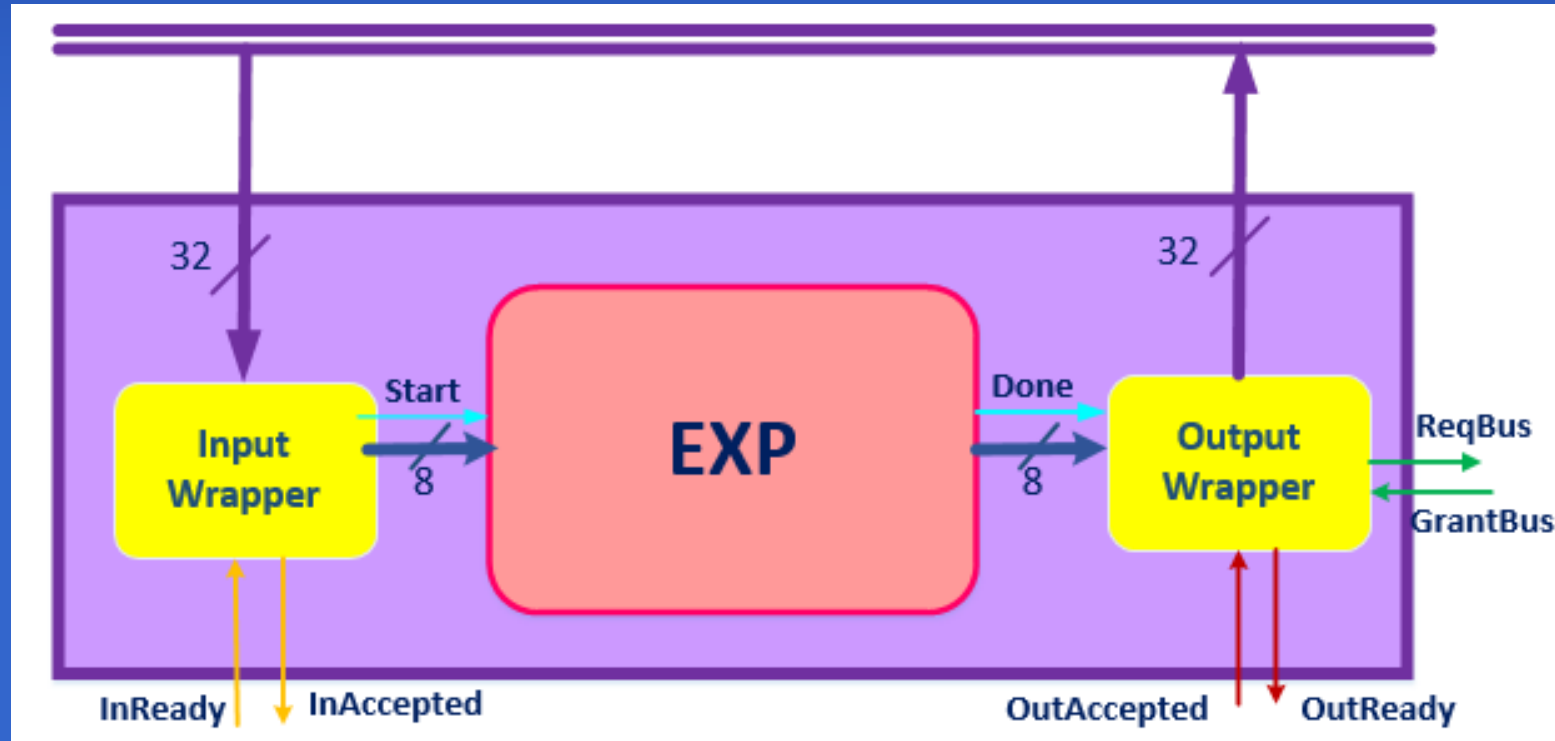

Exponentiation Module

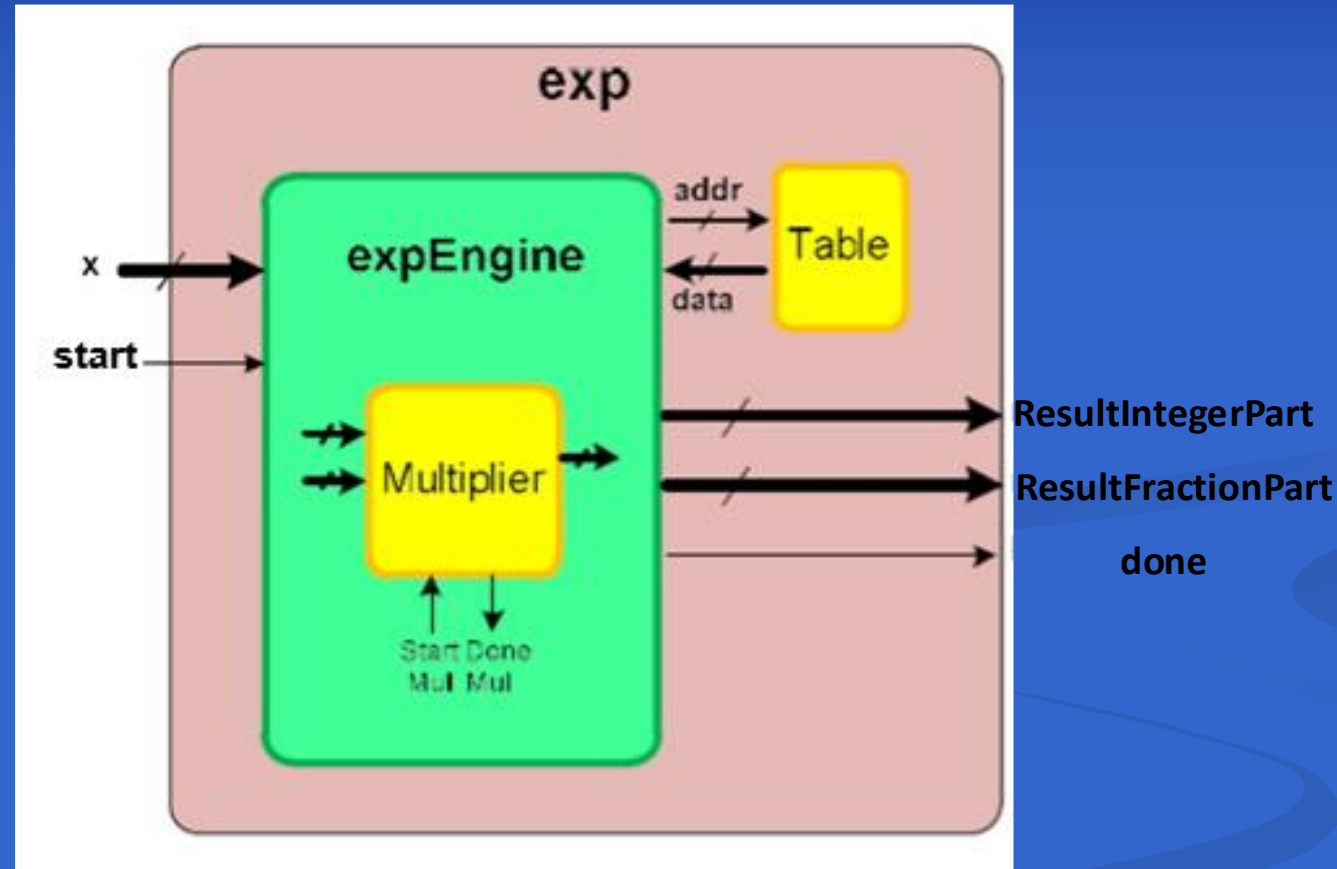


Exponential Function Algorithm

$$e^x = \sum_{k=0}^{\infty} \frac{x^k}{k!}$$


```
e = 1;  
a = 1;  
for( i = 1; i < n; i++ ) {  
    a = a * x * ( 1 / i );  
    e = e + a;  
}
```

Datapath / Controller

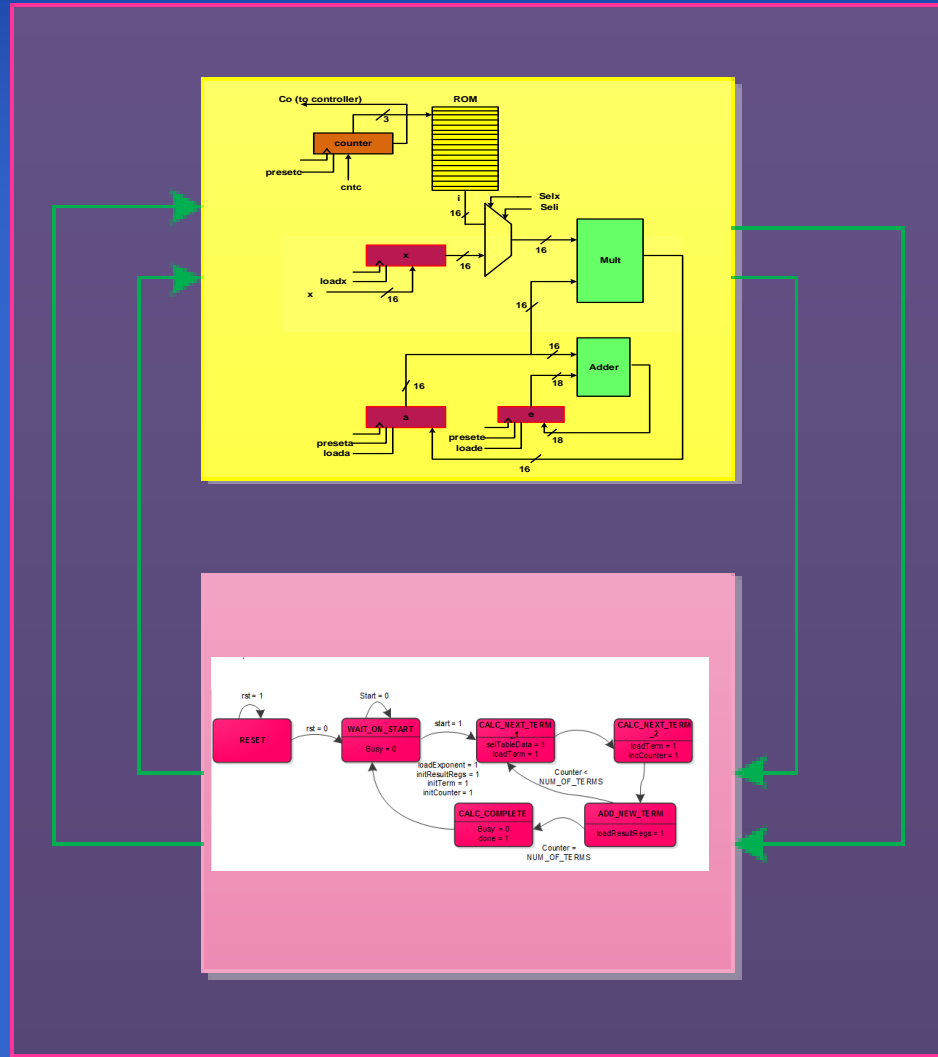


VHDL: Modular Design and Synthesis of Cores and Systems Copyright Z. Navabi

Datapath

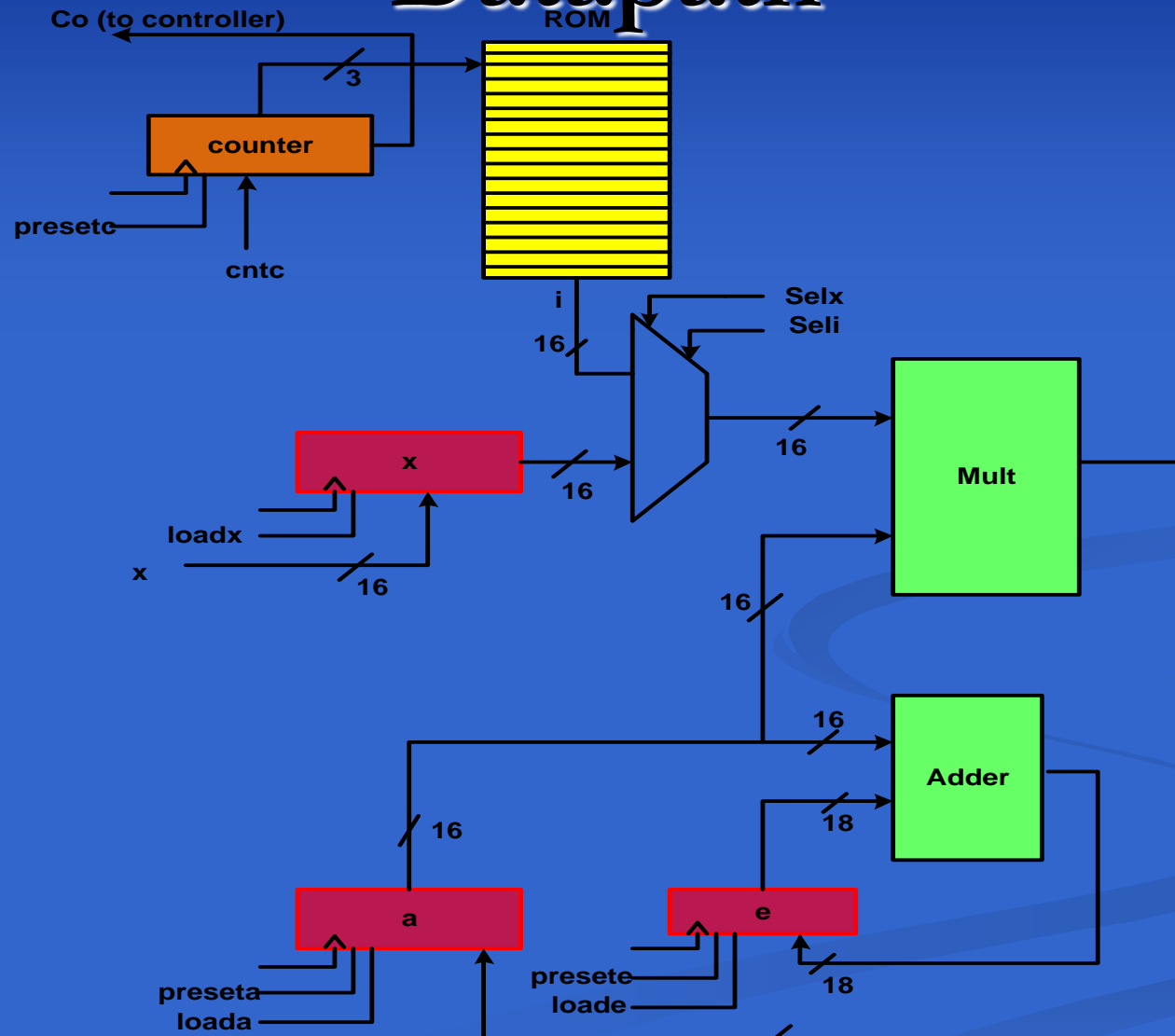


VHDL: Modular Design and Synthesis of Cores and Systems Copyright Z. Navabi

Controller

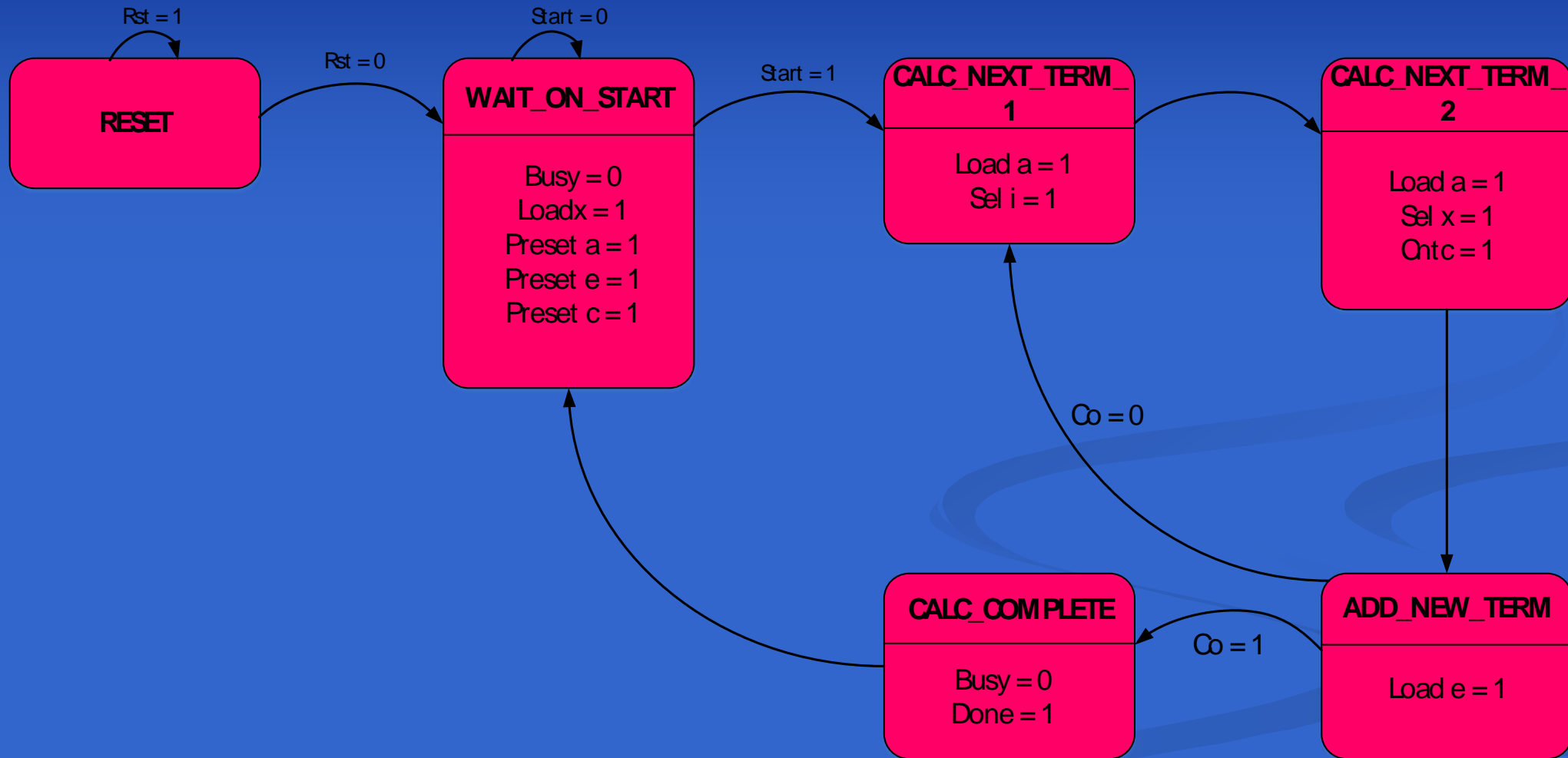


Input Wrapper:

Datapath & Controller Partitioning


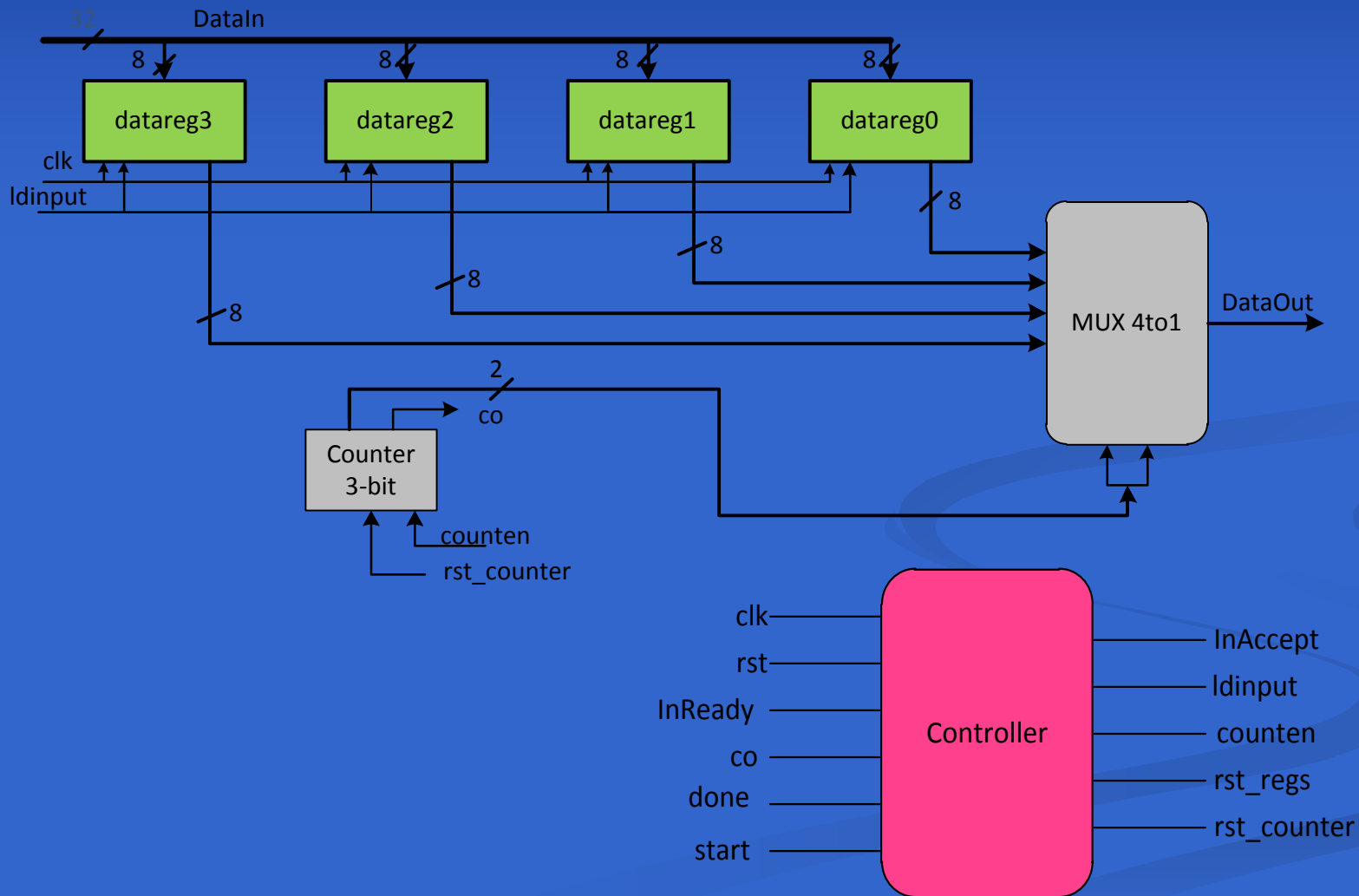


Input Wrapper: State Machine

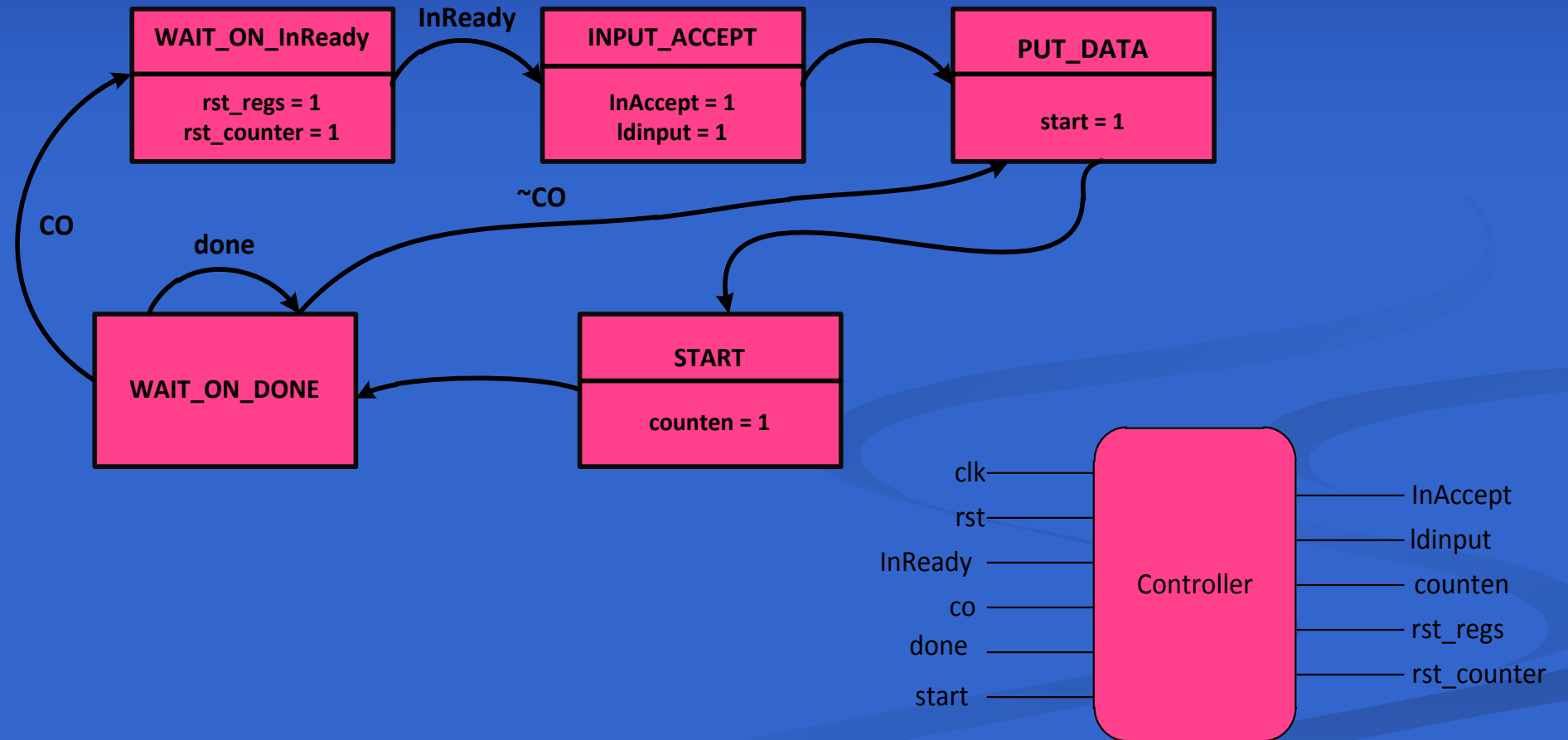


Output Wrapper:


Datapath & Controller Partitioning

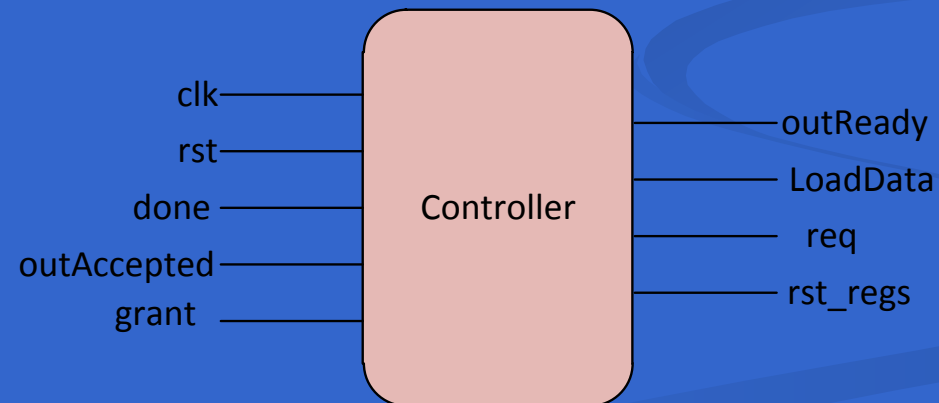 

Output Wrapper: State Machine

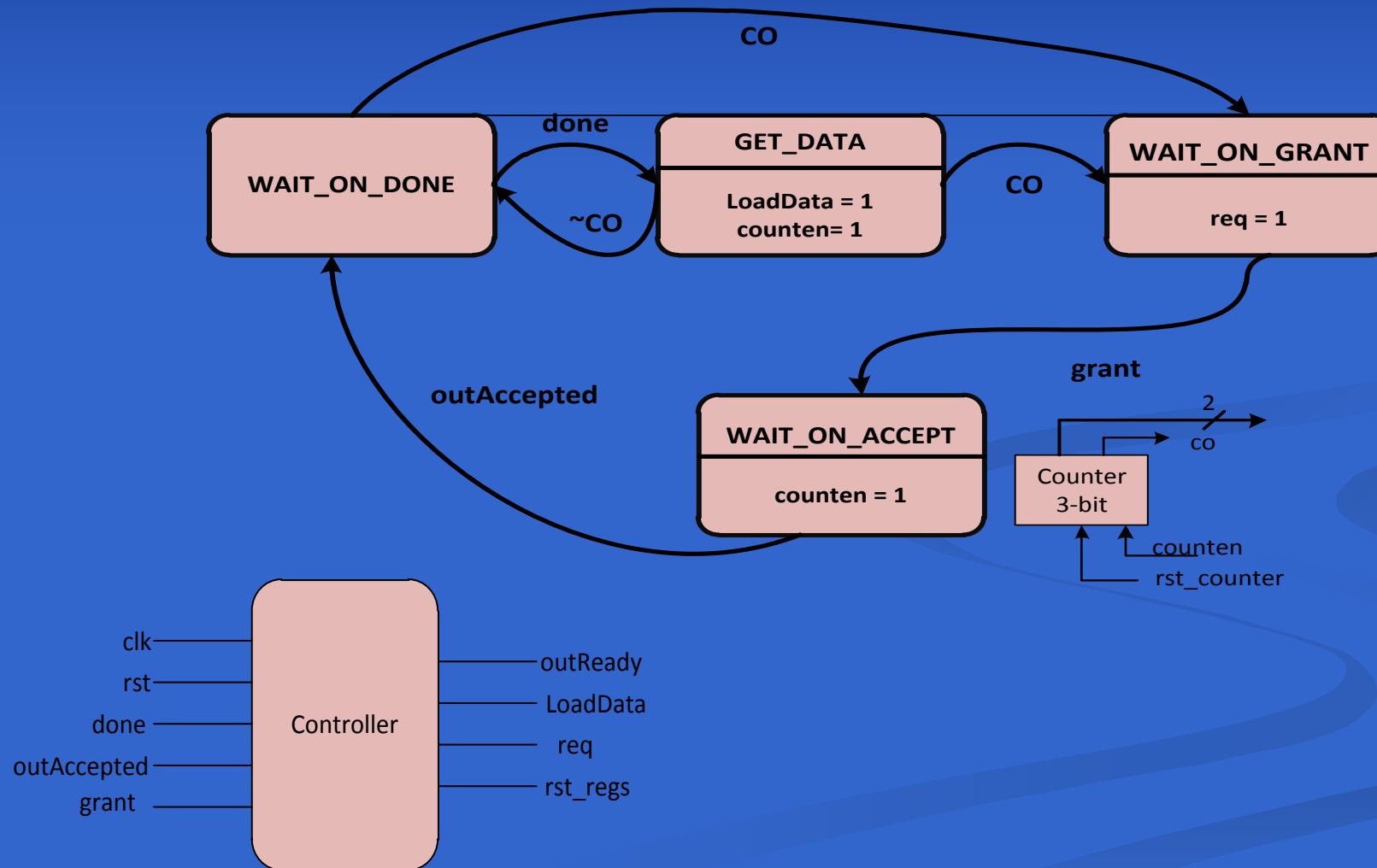


Complete System

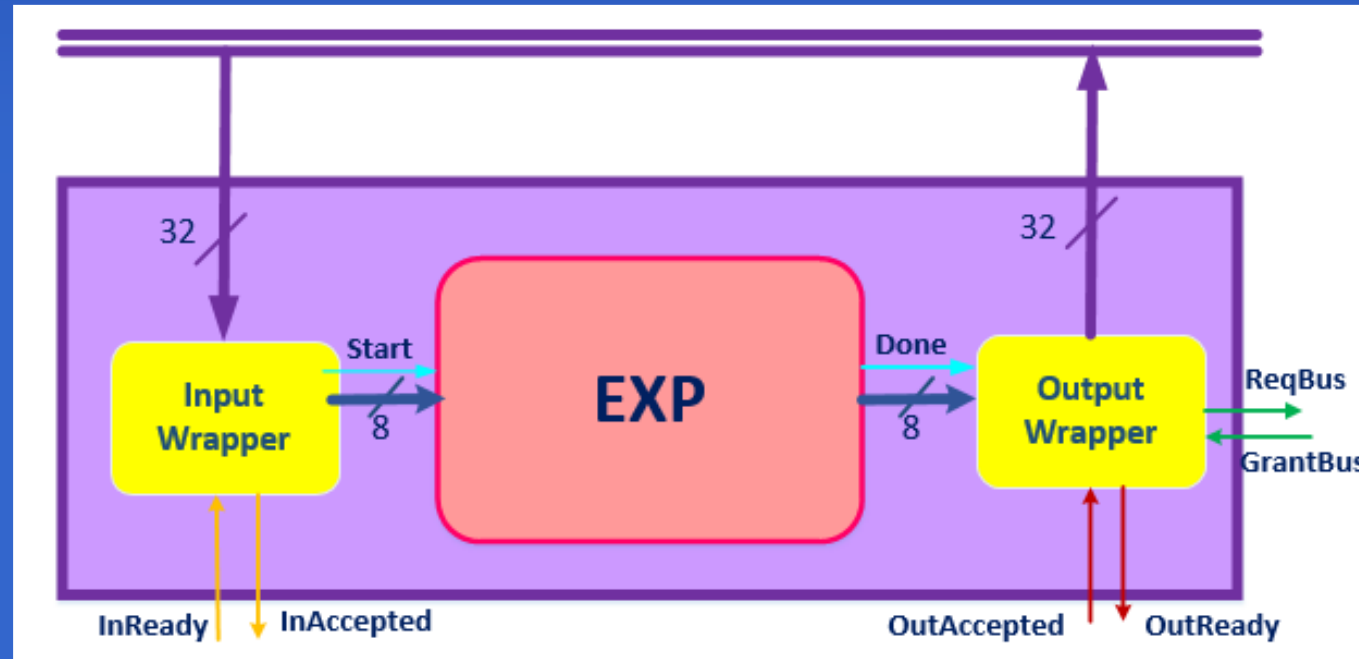

CORDIC

- The CORDIC algorithm is an iterative technique based on the rotation of a vector which allows many transcendental and trigonometric functions to be calculated
- It is achieved using only shifts, additions/subtractions and table look-ups which map well into hardware

CORDIC

 

$$\begin{aligned}x' &= x \cos \phi - y \sin \phi \\y' &= y \cos \phi + x \sin \phi\end{aligned}$$


$$\begin{aligned}x' &= \cos \phi \cdot [x - y \tan \phi] \\y' &= \cos \phi \cdot [y + x \tan \phi]\end{aligned}$$

$$\begin{aligned}x_{i+1} &= K_i [x_i - y_i \cdot d_i \cdot 2^{-i}] \\y_{i+1} &= K_i [y_i + x_i \cdot d_i \cdot 2^{-i}]\end{aligned}$$


CORDIC Advantages

- Number of gates required in hardware implementation on an FPGA, are minimum and hardware complexity is greatly reduced
- Cost of a CORDIC hardware implementation is less as only shift registers, adders and look-up table (ROM) are required
- Delay involved during processing is comparable to that of a division or square-rooting operation
- No multiplication and only addition, subtraction and bit-shifting operation



CORDIC Architecture

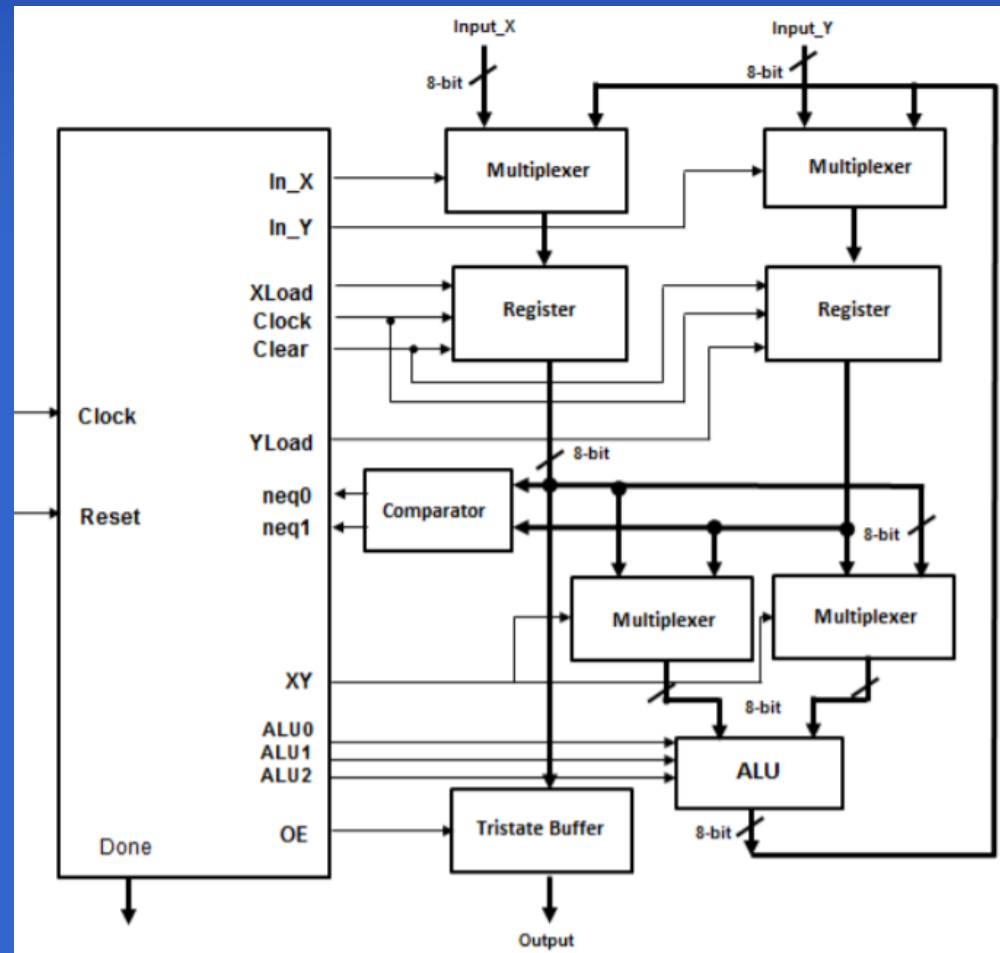

General Datapath

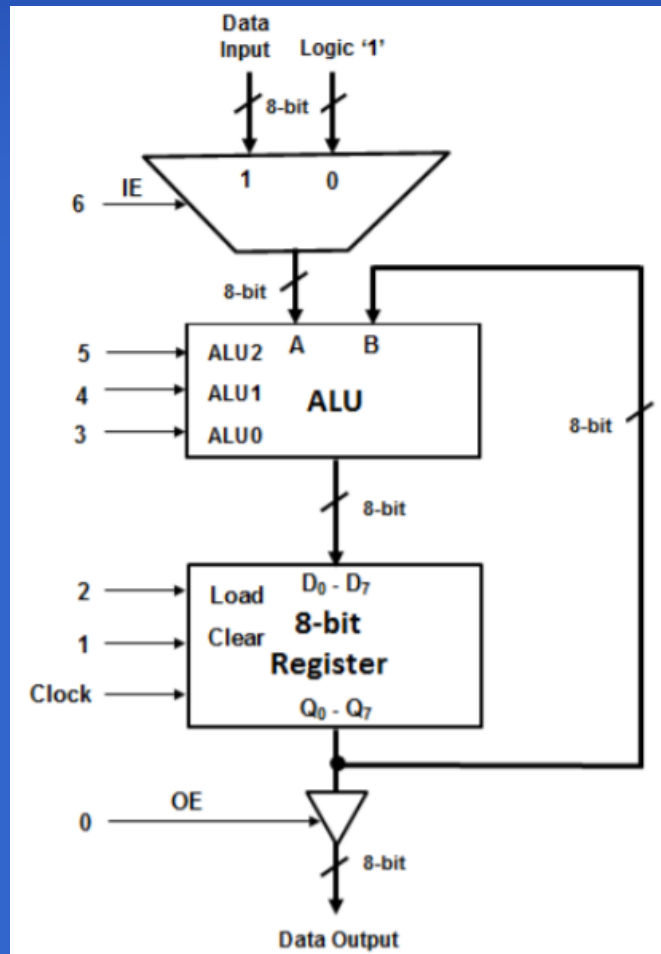

Controller

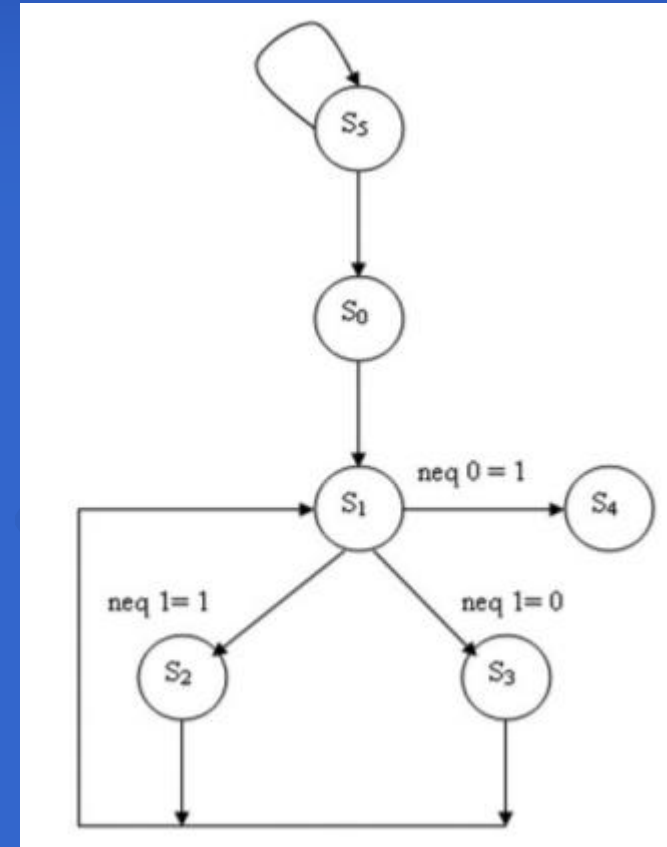 

- Accelerator right
- Left
- Extended instructions
- Near memory
- filter FIR from register file (rf in the wrapper)

The other category is interfaces or wrappers

- Wrappers
- Data sizing form ICEEP notes, that includes hand-shaking and arbitration
- A wrapper only for handshaking, another for data sizing only for burst connections, and the other for rf handling for extended insts rf can be the rf of the processor mapped to this rf


Interfacing hardware

- LRU, very different from other structures
- DMA, using arbitration handles the memory reads and writes
- Not arithmetic hardwares


CPUs

- Von Neumann architectures
- They have instructions, a processor with 4 instructions, it only accesses the memory, instruction fetch
- Next step is the Somayeh processor which is a processor that does the arithmetic work like sine, cosine, it only loads the program and has a pc to fetch the instruction
- Program counter or the sequencer
- SAYEH Processor


von Neumann Computer Model

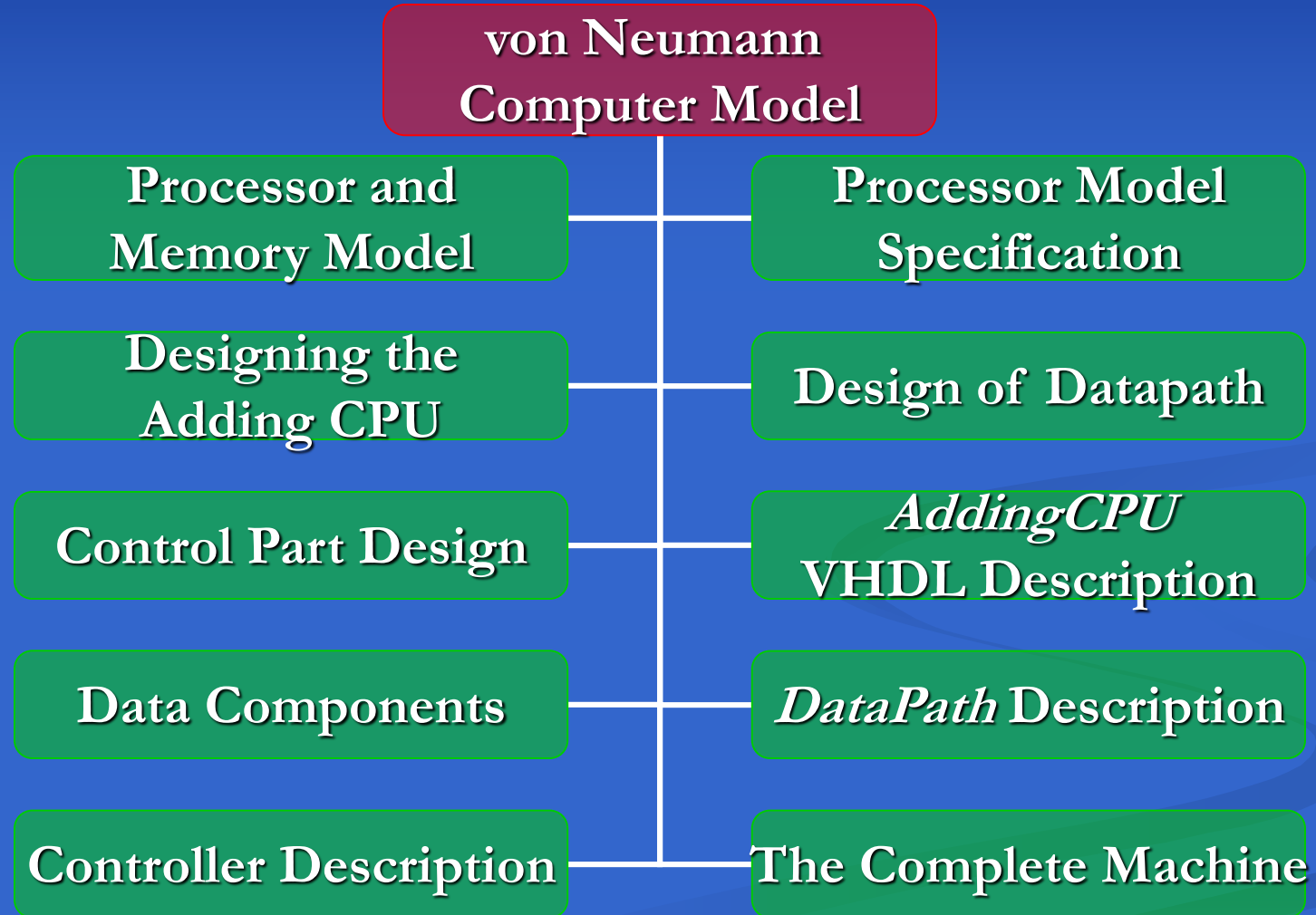

Processor and Memory Model

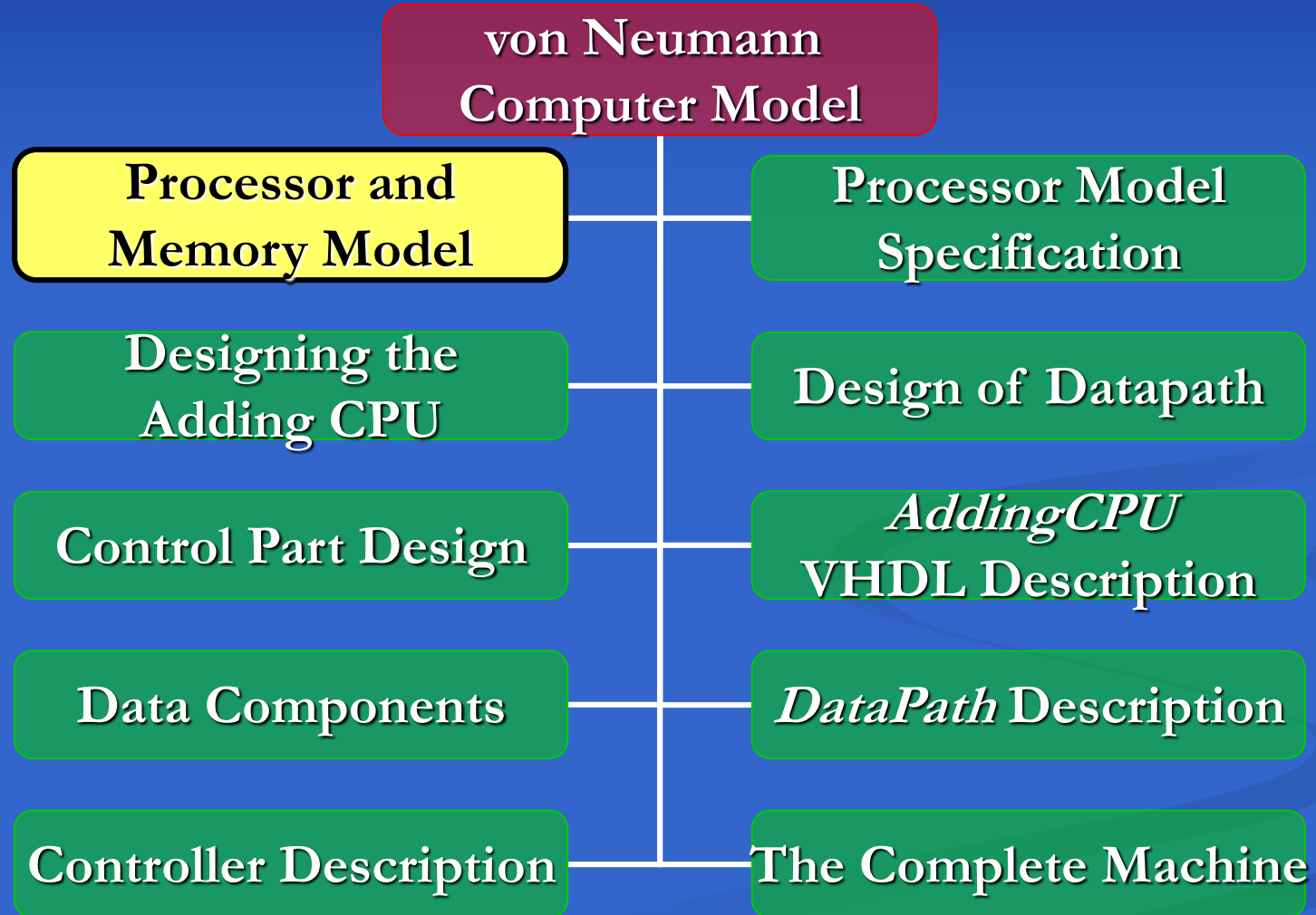


Processor and Memory Model

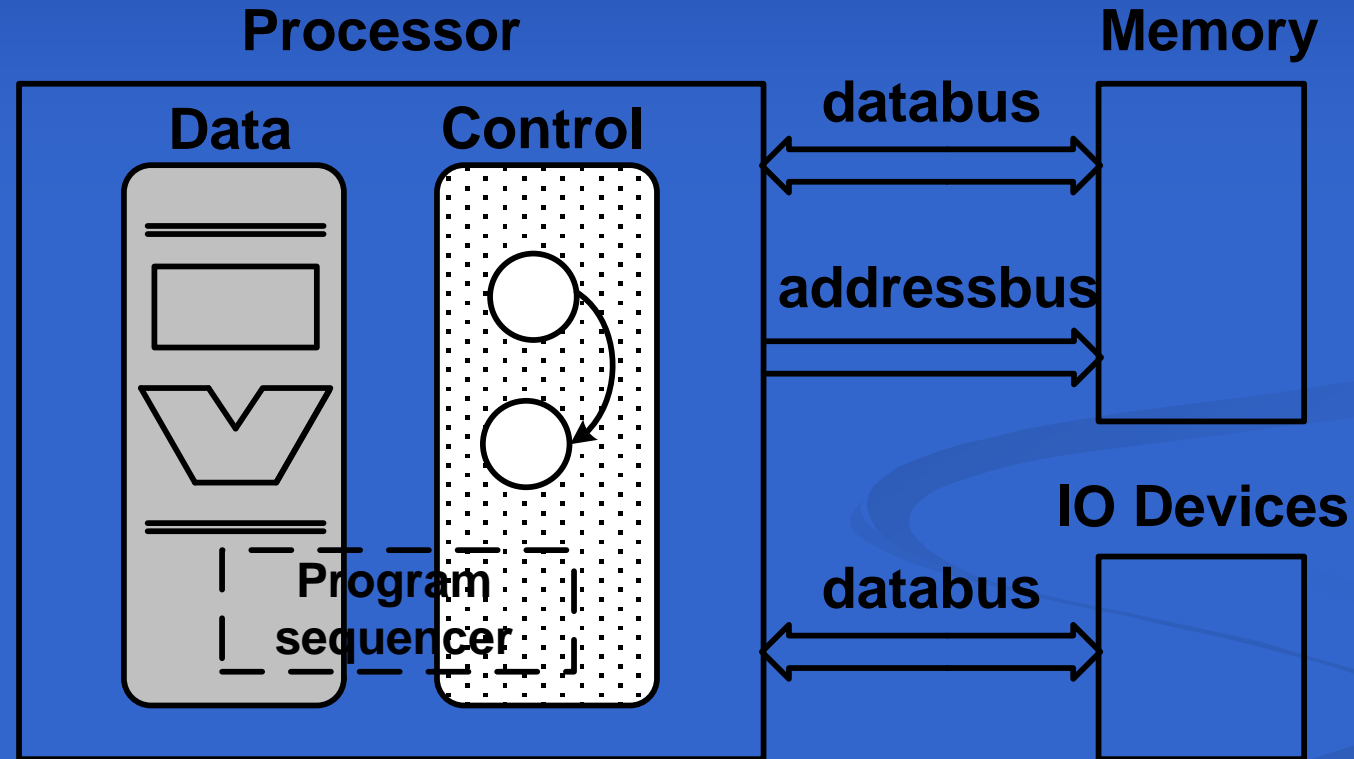


- von Neumann Process Model

Processor Model Specification

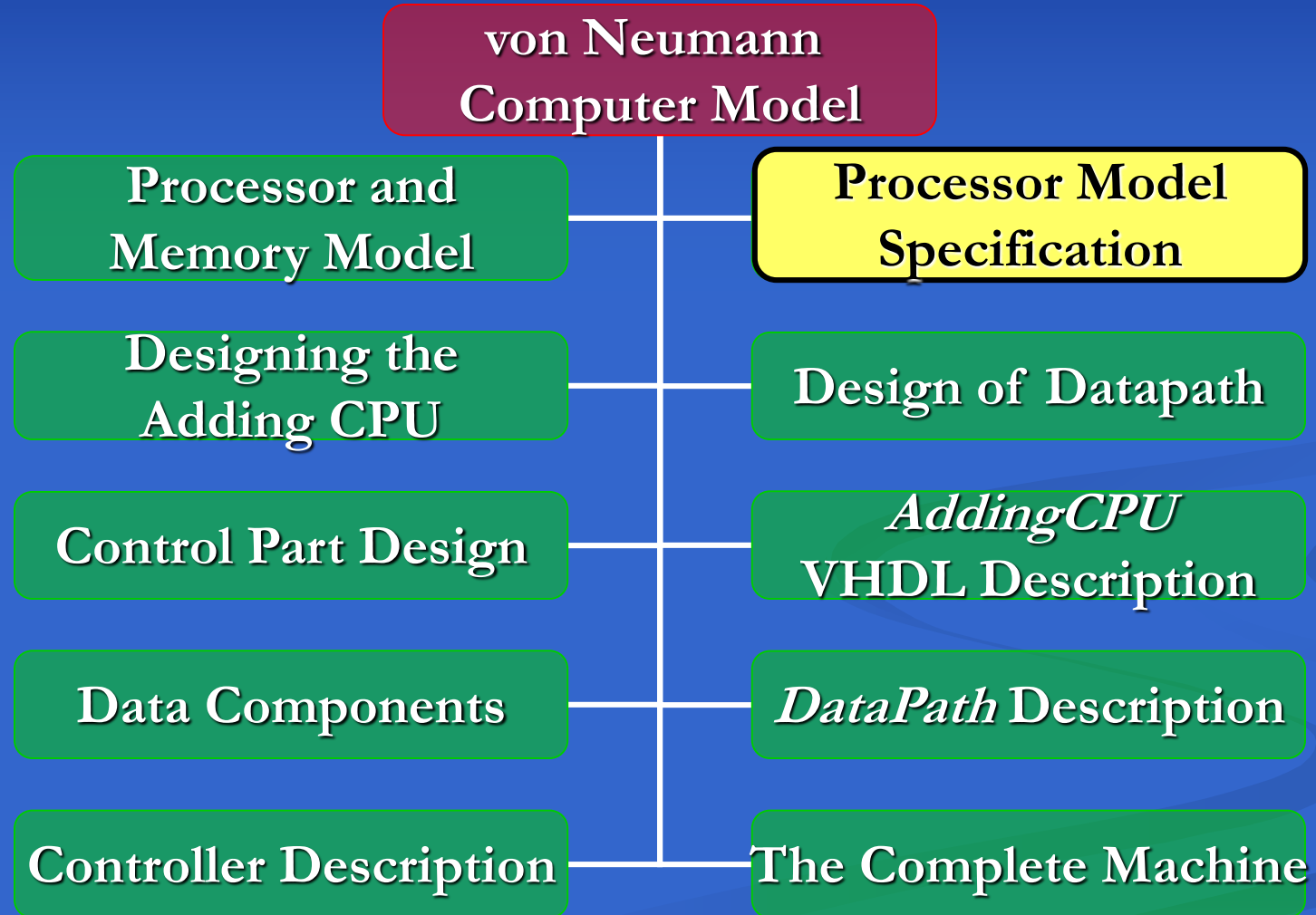

Processor Model Specification

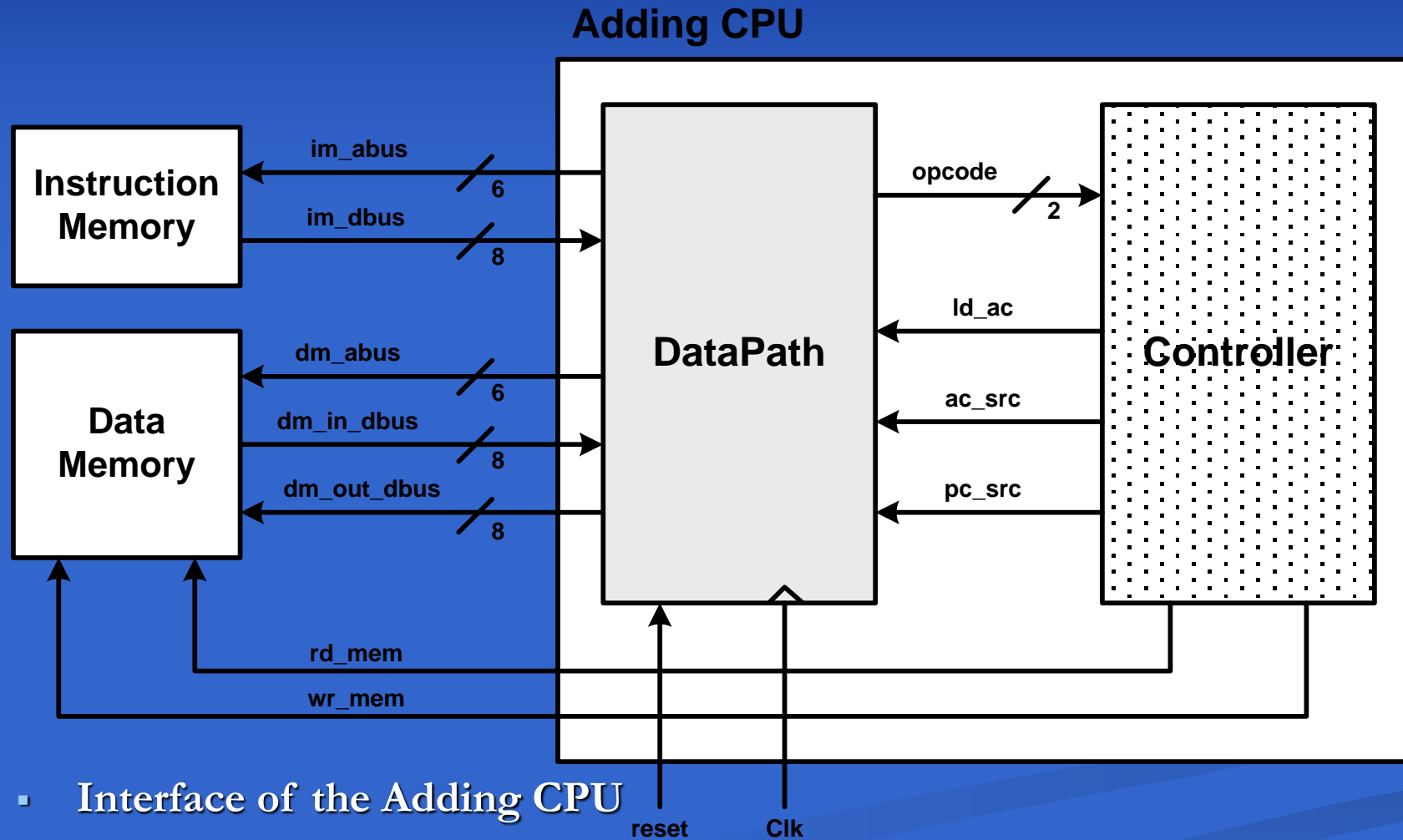

Processor Model Specification

Memory-Transfer & Control-Flow Instruction Format:




Arithmetic Instruction Format:




- Instruction Format


Designing the Adding CPU

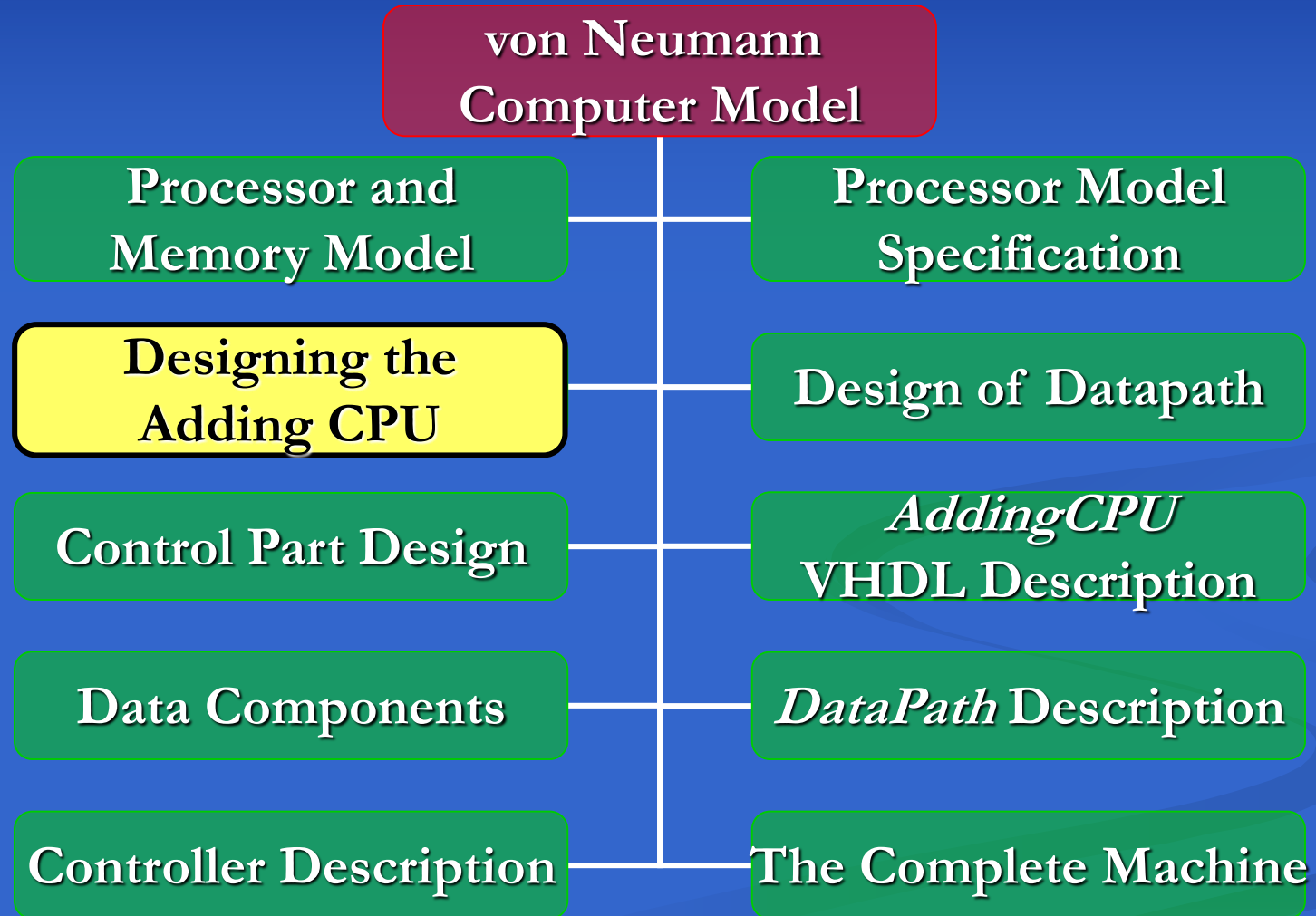

Design of Datapath

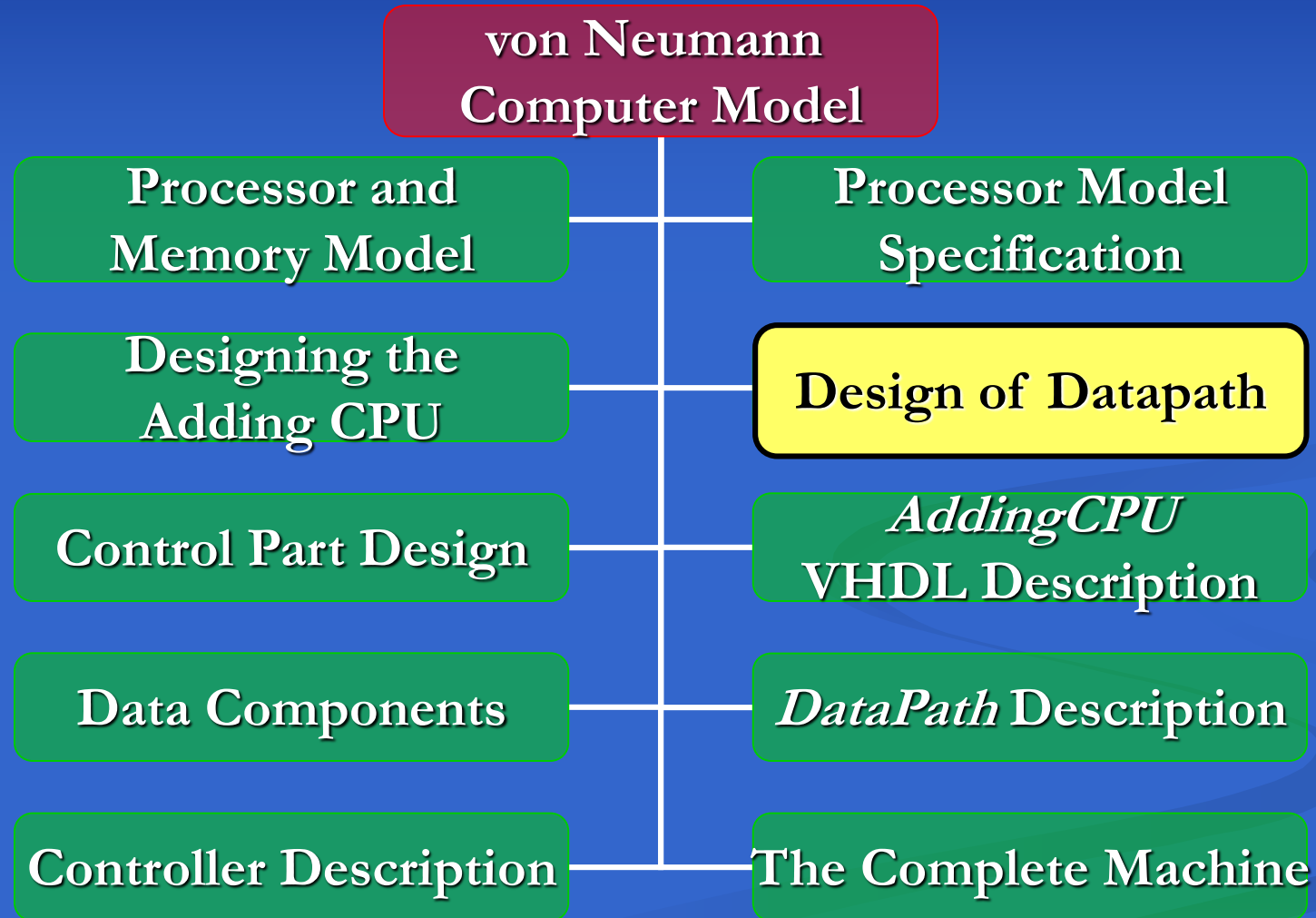


Design of Datapath

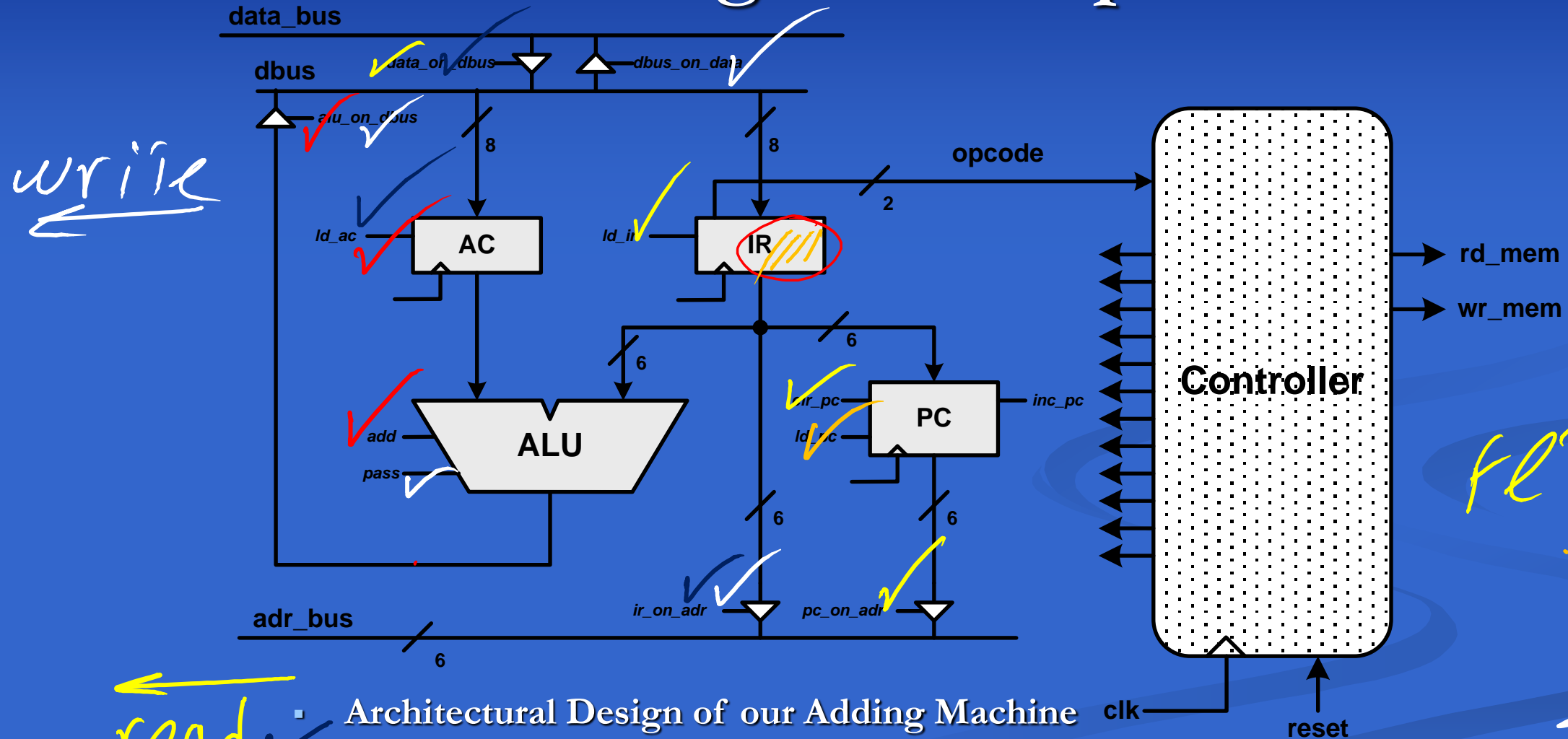


Architectural Design of our Adding Machine

FETCH
Jump
Ld A
STA
Add

Control Part Design

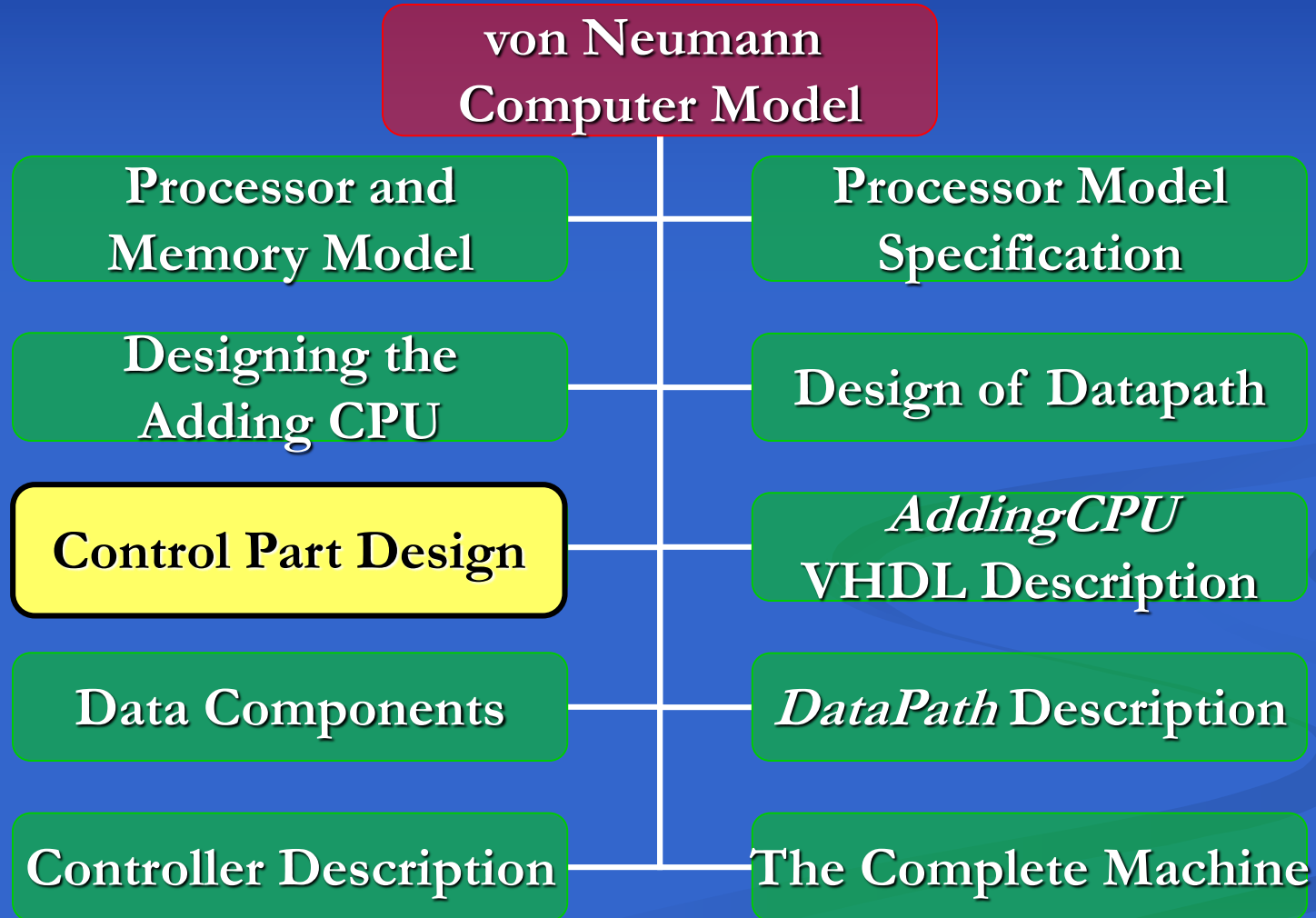


Control Part Design

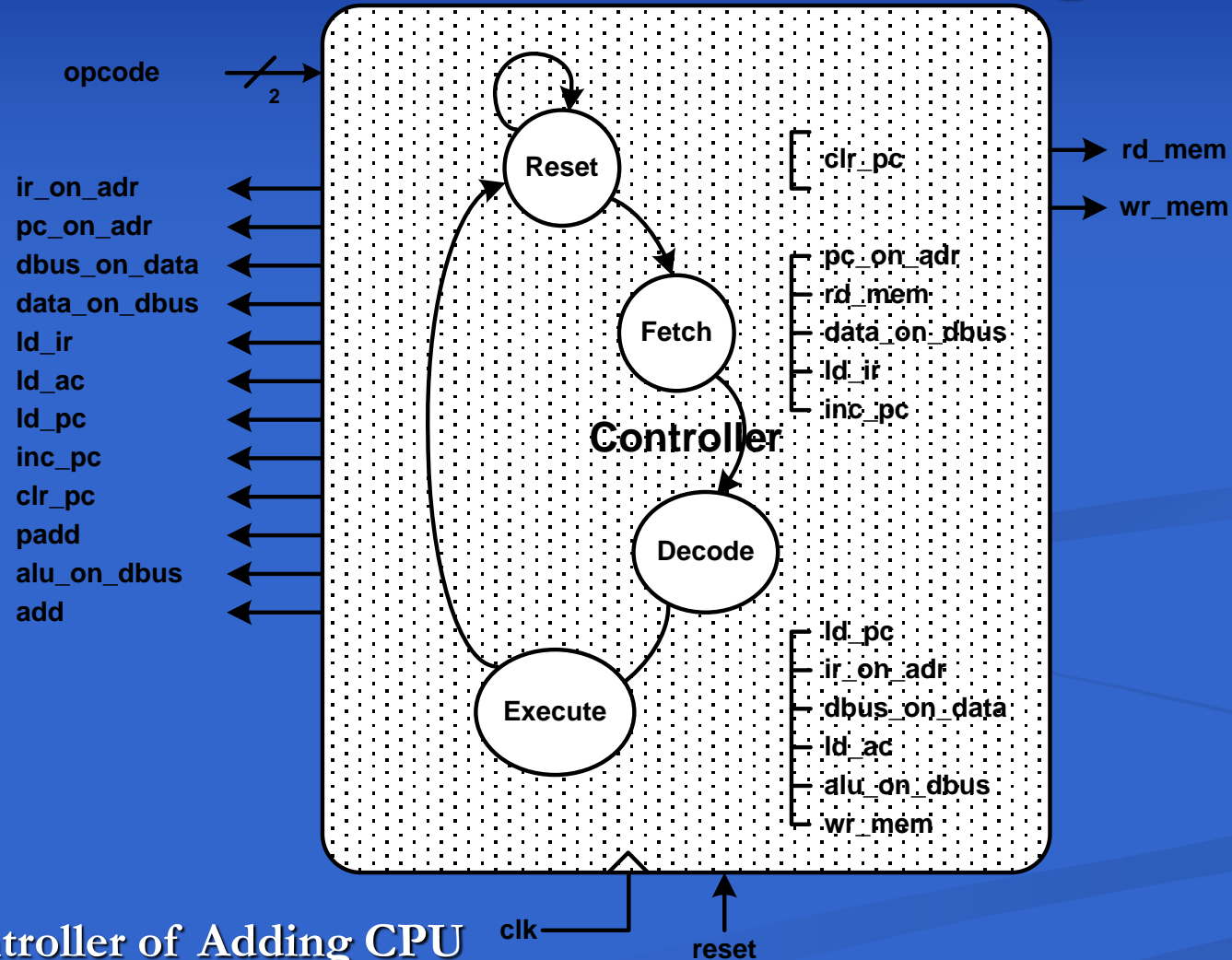


- **Controller of Adding CPU**

Adding CPU VHDL Description

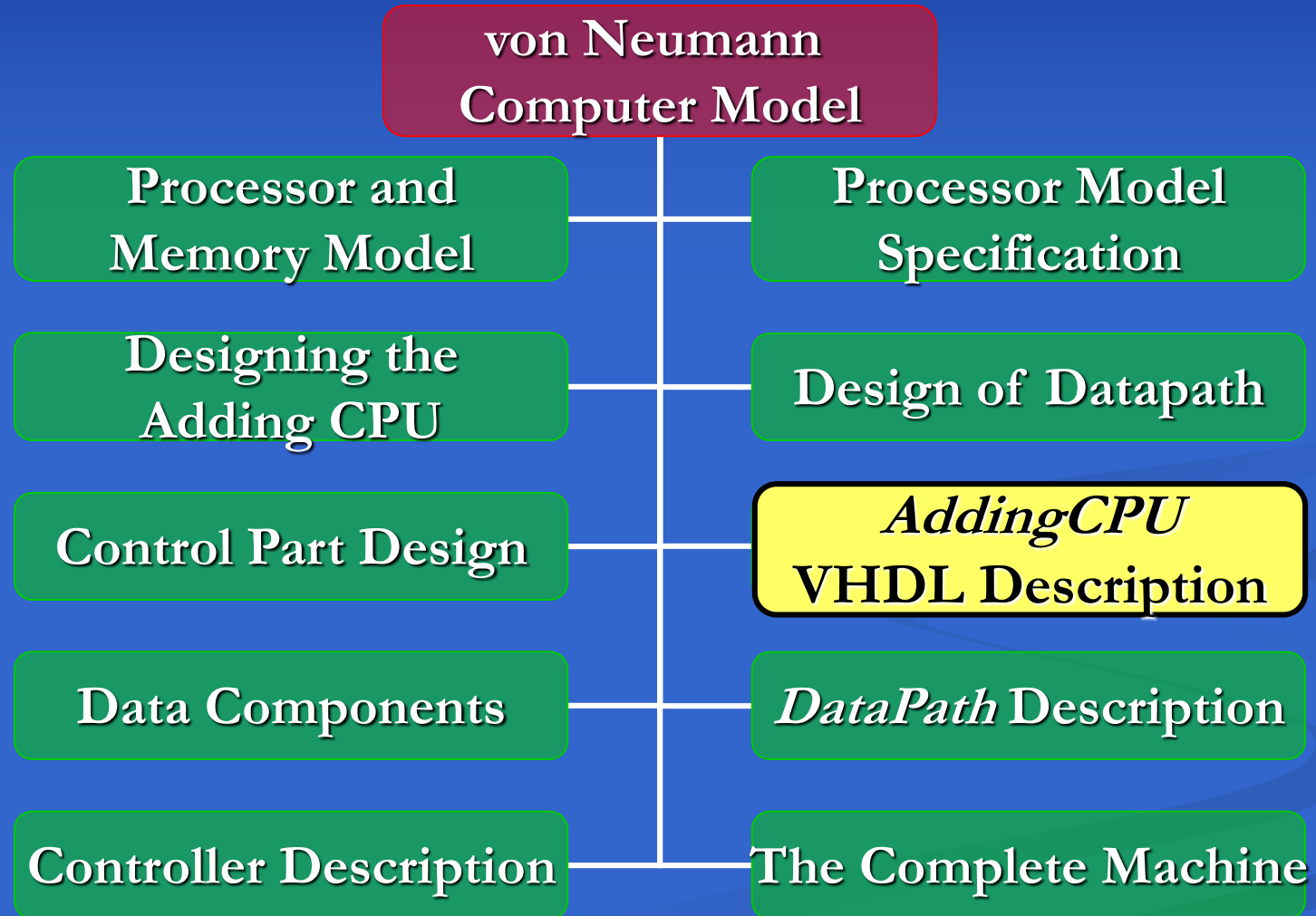

Data Components

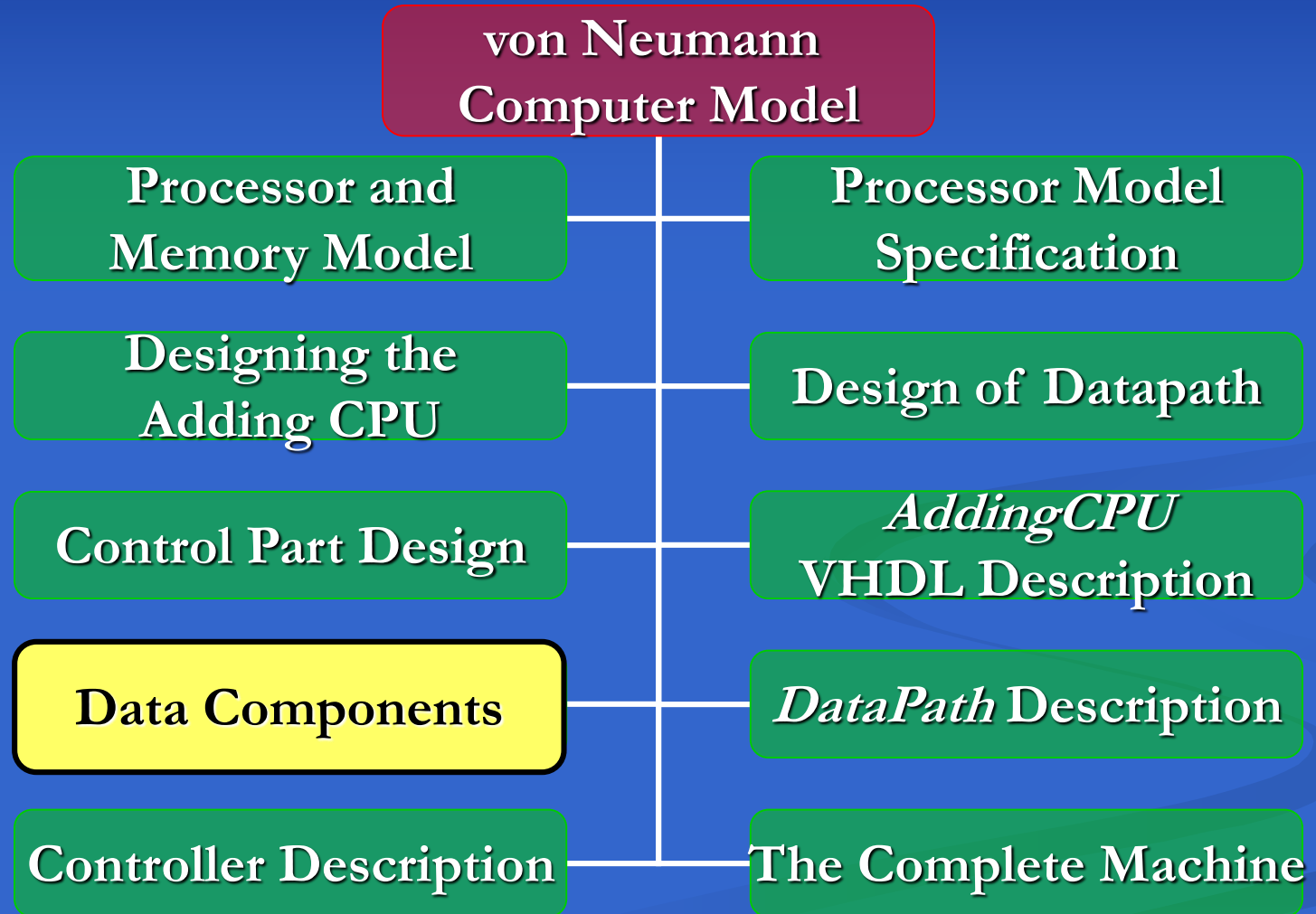

Data Components

```
ENTITY AC IS
    PORT (data_in : IN std_logic_vector(7 DOWNTO 0);
          load, clk : IN std_logic;
          data_out : OUT std_logic_vector(7 DOWNTO 0));
END ENTITY ;
--
ARCHITECTURE procedural OF AC IS BEGIN
    PROCESS (clk) BEGIN
        IF clk = '1' AND clk'EVENT THEN
            IF load = '1' THEN
                data_out <= data_in;
            END IF;
        END IF;
    END PROCESS;
END ARCHITECTURE;
```

- Datapath Components of the Adding Machine

Data Components

```
ENTITY IR IS
    PORT (data_in : IN std_logic_vector(7 DOWNTO 0);
          load, clk : IN std_logic;
          data_out : OUT std_logic_vector(7 DOWNTO 0));
END ENTITY ;
--
ARCHITECTURE procedural OF IR IS BEGIN
    PROCESS (clk) BEGIN
        IF clk = '1' AND clk'EVENT THEN
            IF load = '1' THEN data_out <= data_in; END IF;
        END IF;
    END PROCESS;
END ARCHITECTURE;
```

- Datapath Components of the Adding Machine (Continued)

Data Components


```
ENTITY PC IS
    PORT (data_in : IN std_logic_vector(5 DOWNTO 0);
          load, inc, clr, clk : IN std_logic;
          data_out : OUT std_logic_vector(5 DOWNTO 0));
END ENTITY ;
ARCHITECTURE procedural OF PC IS
    SIGNAL pc : std_logic_vector(5 DOWNTO 0);
BEGIN
    PROCESS (clk) BEGIN
        IF clk = '1' AND clk'EVENT THEN
            IF clr = '1' THEN pc <= (OTHERS => '0');
            ELSIF load = '1' THEN pc <= data_in;
            ELSIF inc = '1' THEN pc <= pc + 1; END IF;
        END IF;
    END PROCESS;
    data_out <= pc;
END ARCHITECTURE;
```

Data Components

```
ENTITY ALU IS
  PORT (a, b : IN std_logic_vector(7 DOWNTO 0);
        pass, add : IN std_logic;
        alu_out : OUT std_logic_vector(7 DOWNTO 0));
END ENTITY ;
ARCHITECTURE functional OF ALU IS
  SIGNAL alu_res : std_logic_vector(7 DOWNTO 0);
BEGIN
  PROCESS (a, b, pass, add) BEGIN
    IF pass = '1' THEN alu_res <= a;
    ELSIF add = '1' THEN alu_res <= a + b;
    ELSE alu_res <= (OTHERS => '0');
    END IF;
  END PROCESS;
  alu_out <= alu_res;
END ARCHITECTURE;
```

- Datapath Components of the Adding Machine (Continued)

DataPath Description

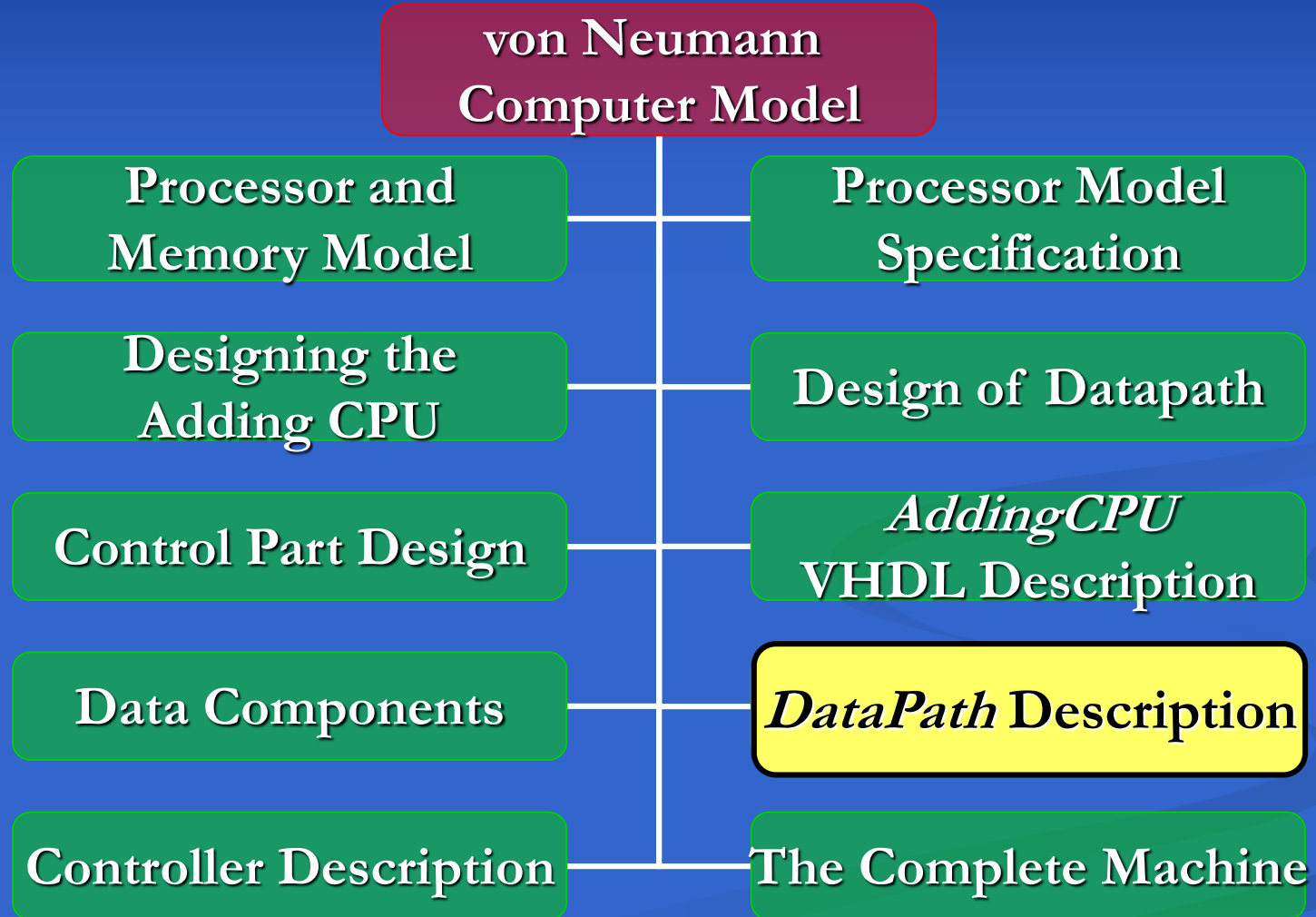

DataPath Description

```
ENTITY datapath IS
    PORT (ir_on_adr, pc_on_adr, dbus_on_data : IN std_logic;
          data_on_dbus, ld_ir, ld_ac, ld_pc : IN std_logic;
          inc_pc, clr_pc,
              pass, add, alu_on_dbus, clk : IN std_logic;
          adr_bus : OUT std_logic_vector(5 DOWNTO 0);
          op_code : OUT std_logic_vector(1 DOWNTO 0);
          data_bus : INOUT std_logic_vector(7 DOWNTO 0));
END ENTITY ;
ARCHITECTURE structural OF datapath IS
    SIGNAL dbus, ir_out, a_side :
        std_logic_vector(7 DOWNTO 0);
    SIGNAL alu_out, b_side : std_logic_vector(7 DOWNTO 0);
    SIGNAL pc_out : std_logic_vector(5 DOWNTO 0);
    . . . . .
END ARCHITECTURE;
```

- Adding CPU Datapath Description

DataPath Description

```
ARCHITECTURE structural OF datapath IS
BEGIN
  IR : ENTITY WORK.IR(procedural)
      PORT MAP (dbus, ld_ir, clk, ir_out);
  PC : ENTITY WORK.PC(procedural)
      PORT MAP (ir_out(5 DOWNT0 0), ld_pc, inc_pc,
              clr_pc, clk, pc_out);
  AC : ENTITY WORK.AC(procedural)
      PORT MAP (dbus, ld_ac, clk, a_side);
  ALU : ENTITY WORK.ALU(functional)
      PORT MAP (a_side, b_side, pass, add, alu_out );

  b_side <= '0' & '0' & ir_out(5 DOWNT0 0);
  . . . . .
END ARCHITECTURE;
```


- Adding CPU Datapath Description (Continued)

DataPath Description

```
ARCHITECTURE structural OF datapath IS
BEGIN
    . . . . .
    adr_bus <= ir_out(5 DOWNT0 0) WHEN ir_on_adr = '1'
            ELSE (OTHERS => 'Z');
    adr_bus <= pc_out WHEN pc_on_adr = '1' ELSE
            (OTHERS => 'Z');
    dbus <= alu_out WHEN alu_on_dbus = '1' ELSE
            (OTHERS => 'Z');
    data_bus <= dbus WHEN dbus_on_data = '1' ELSE
            (OTHERS => 'Z');
    dbus <= data_bus WHEN data_on_dbus = '1' ELSE
            (OTHERS => 'Z');
    op_code <= ir_out(7 DOWNT0 6);
END ARCHITECTURE;
```

- Adding CPU Datapath Description (Continued)

Controller Description

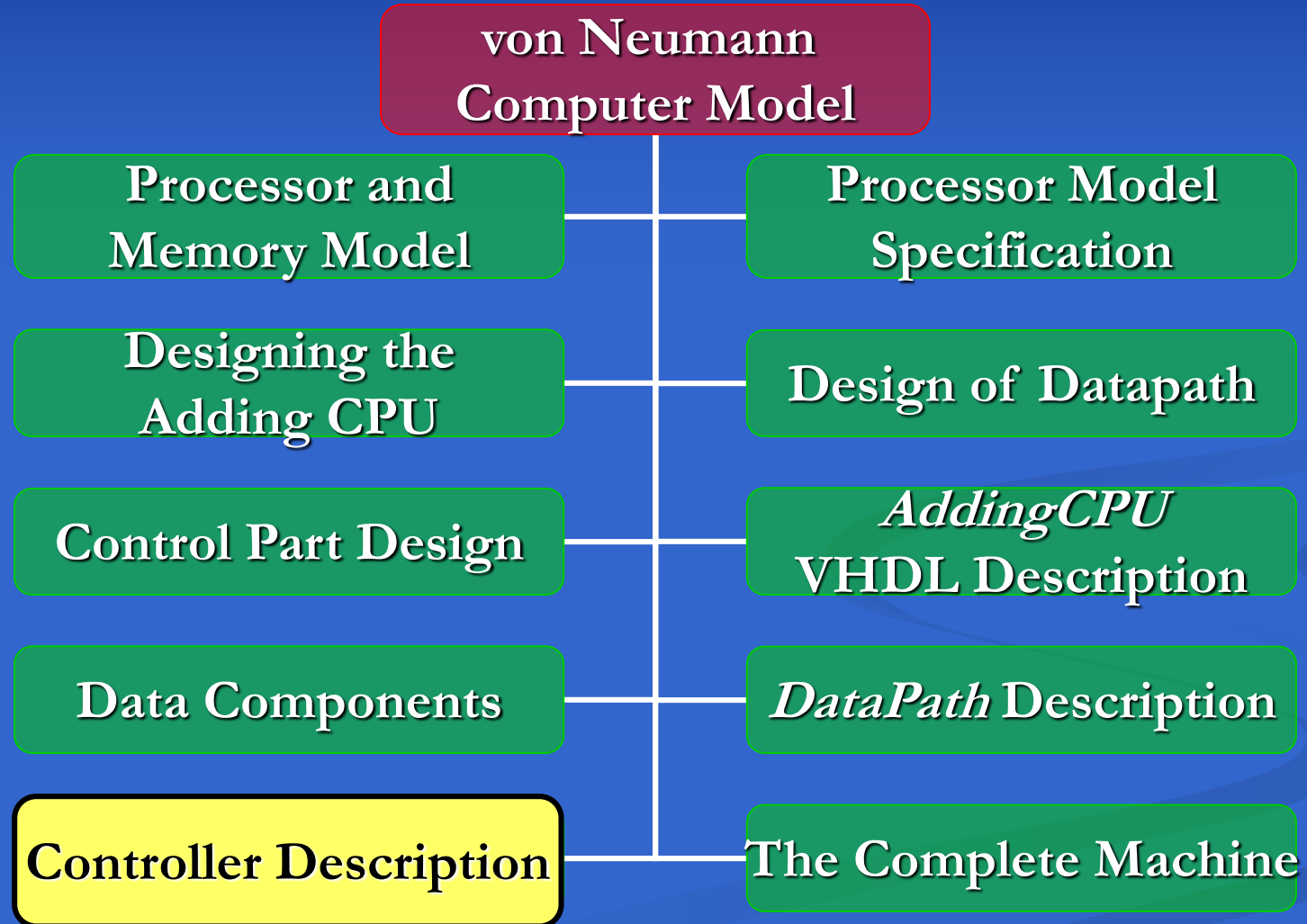

Controller Description

```
ENTITY controller IS
  PORT (rst, clk : IN std_logic;
        op_code : IN std_logic_vector(1 DOWNTO 0);
        rd_mem, wr_mem : OUT std_logic;
        ir_on_adr, pc_on_adr : OUT std_logic;
        dbus_on_data, data_on_dbus, ld_ir : OUT std_logic;
        ld_ac, ld_pc, inc_pc, clr_pc, pass : OUT std_logic;
        add, alu_on_dbus : OUT std_logic);
END ENTITY ;
--
ARCHITECTURE procedural OF controller IS
  TYPE state IS (Reset, Fetch, Decode, Execute);
  SIGNAL present_state, next_state : state;
BEGIN
  . . . . .
END ARCHITECTURE ;
```

- Controller VHDL Code

Controller Description

```
ARCHITECTURE procedural OF controller IS
BEGIN
  PROCESS (clk)--Sequential
  BEGIN
    IF clk = '1' AND clk'EVENT THEN
      IF rst = '1' THEN
        present_state <= Reset;
      ELSE
        present_state <= next_state;
      END IF;
    END IF;
  END PROCESS;
  --
  . . . . .
END ARCHITECTURE;
```

- Controller VHDL Code (Continued)

Controller Description

```
PROCESS (present_state, rst) --Combinational
BEGIN
    rd_mem <= '0'; wr_mem <= '0'; ir_on_adr <= '0';
    pc_on_adr <= '0'; dbus_on_data <= '0';
    data_on_dbus <= '0'; ld_ir <= '0'; pass <= '0';
    ld_ac <= '0'; ld_pc <= '0'; inc_pc <= '0';
    clr_pc <= '0'; add <= '0'; alu_on_dbus <= '0';
    CASE present_state IS
        WHEN Reset =>
            IF rst = '1' THEN
                next_state <= Reset;
            ELSE
                next_state <= Fetch;
            END IF;
            clr_pc <= '1';
            . . . . .
```

- Controller VHDL Code (Continued)

Controller Description

```
PROCESS (present_state, rst, op_code) --Combinational
BEGIN
    . . . . .
    WHEN Fetch =>
        next_state <= Decode;
        pc_on_adr <= '1';
        rd_mem <= '1';
        data_on_dbus <= '1';
        ld_ir <= '1';
        inc_pc <= '1';
    WHEN Decode =>
        next_state <= Execute;
    . . . . .
END PROCESS;
. . . . .
```

- Controller VHDL Code (Continued)

Controller Description

```
.....  
WHEN Execute =>  
  next_state <= Fetch;  
  CASE op_code IS  
    WHEN "00" =>  
      ir_on_adr <= '1'; rd_mem <= '1';  
      data_on_dbus <= '1'; ld_ac <= '1';  
    WHEN "01" =>  
      dbus_on_data <= '1'; alu_on_dbus <= '1';  
      pass <= '1'; wr_mem <= '1';  
      ir_on_adr <= '1';  
    WHEN "10" =>  
      ld_pc <= '1';  
    WHEN "11" =>  
      add <= '1'; alu_on_dbus <= '1';  
      ld_ac <= '1';
```


- Controller VHDL Code

Controller Description

```
. . . . .  
WHEN OTHERS =>  
    rd_mem <= '0'; pc_on_adr <= '0';  
    pass <= '0';  
    ir_on_adr <= '0'; wr_mem <= '0';  
    ld_ac <= '0';  
    dbus_on_data <= '0'; data_on_dbus <= '0';  
    ld_ir <= '0'; alu_on_dbus <= '0';  
    add <= '0';  
    inc_pc <= '0'; clr_pc <= '0';  
    ld_pc <= '0';  
    END CASE;  
    WHEN OTHERS => next_state <= Reset;  
    END CASE;  
END PROCESS;  
END ARCHITECTURE;
```

- Controller VHDL Code

The Complete Machine

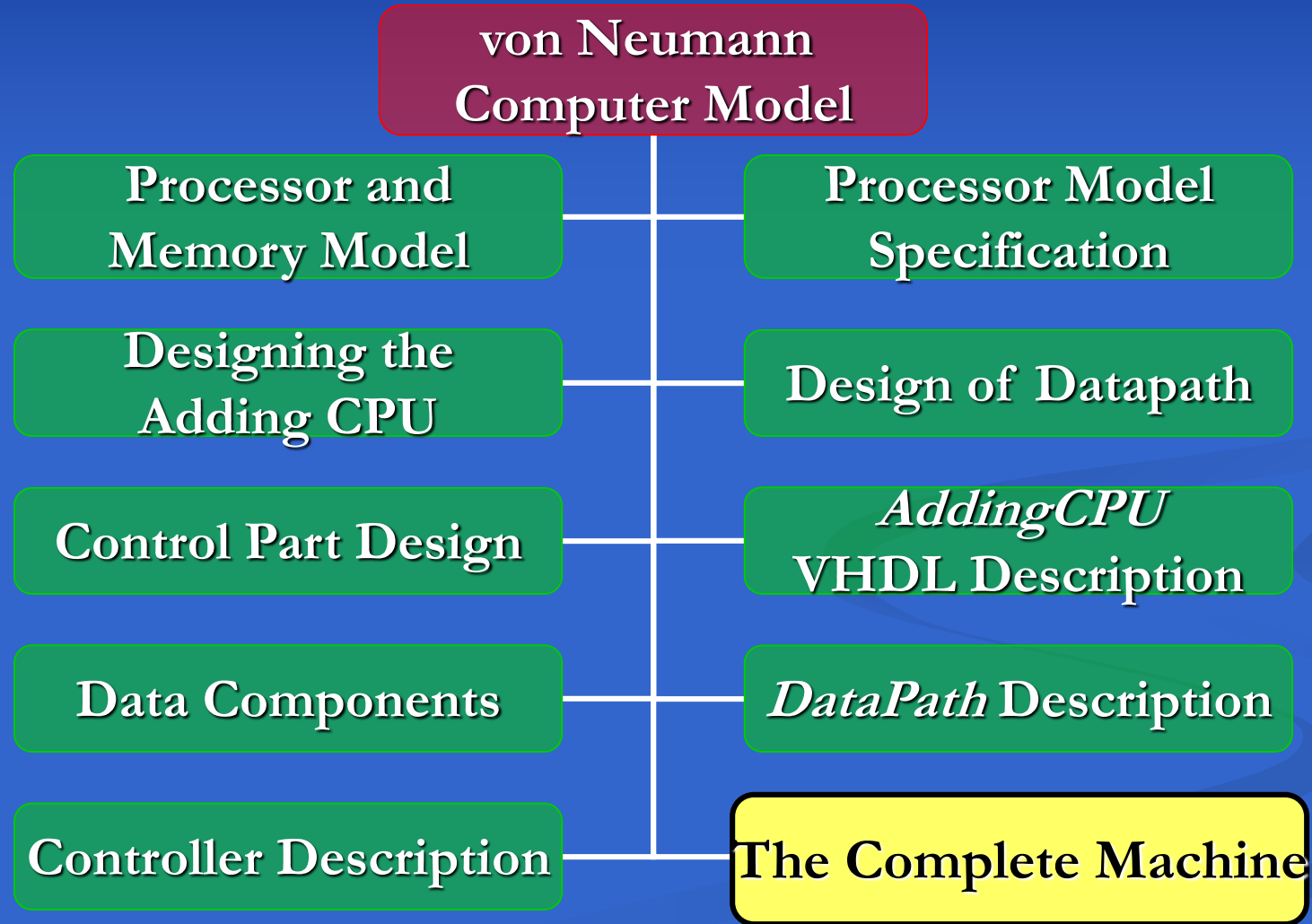

The Complete Machine

```
ENTITY addingCPU IS
  PORT (reset, clk : IN std_logic;
        adr_bus : OUT std_logic_vector(5 DOWNT0 0);
        rd_mem, wr_mem : OUT std_logic;
        data_bus : INOUT std_logic_vector(7 DOWNT0 0));
END ENTITY ;
--
ARCHITECTURE structural OF addingCPU IS
  SIGNAL ir_on_adr, pc_on_adr, dbus_on_data : std_logic;
  SIGNAL data_on_dbus, ld_ir, ld_ac, ld_pc : std_logic;
  SIGNAL inc_pc, clr_pc : std_logic;
  SIGNAL pass, add, alu_on_dbus : std_logic;
  SIGNAL op_code : std_logic_vector(1 DOWNT0 0);
BEGIN
  . . . . .
END ARCHITECTURE;
```

- AddingCPU Top-level Description

The Complete Machine

```
ARCHITECTURE structural OF addingCPU IS
BEGIN
  CU: ENTITY WORK.Controller
    PORT MAP (reset, clk, op_code, rd_mem,
              wr_mem, ir_on_adr, pc_on_adr,
              dbus_on_data, data_on_dbus,
              ld_ir, ld_ac, ld_pc, inc_pc,
              clr_pc, pass, add, alu_on_dbus );
  DP: ENTITY WORK.DataPath
    PORT MAP (ir_on_adr, pc_on_adr, dbus_on_data,
              data_on_dbus, ld_ir, ld_ac, ld_pc,
              inc_pc, clr_pc, pass, add,
              alu_on_dbus, clk, adr_bus, op_code,
              data_bus );
END ARCHITECTURE;
```

- AddingCPU Top-level Description (Continued)

Summary

- This chapter presented VHDL code and descriptions for several hardware components.
- Emphasized on synthesizable cores
- Considered situations that a core model was to be for evaluation purposes only
- We discussed:
 - Individual stand-alone component descriptions
 - Design partitioning
 - Putting sub-components of a system together for formation of complete systems.

Acknowledgment

Slides developed by:

Homa Alemzadeh

Edited December 2017, by:

Bahar Behazin

Last edited April 2019, by:

Saba Yousefzadeh